

Registered by Australia Post
publication No. NBP 0240


Australia's Top Selling Electronics Magazine

Electronics Australia

AUGUST 1987

Aust* \$3.50


NZ \$4.95 ^{Incl} GST

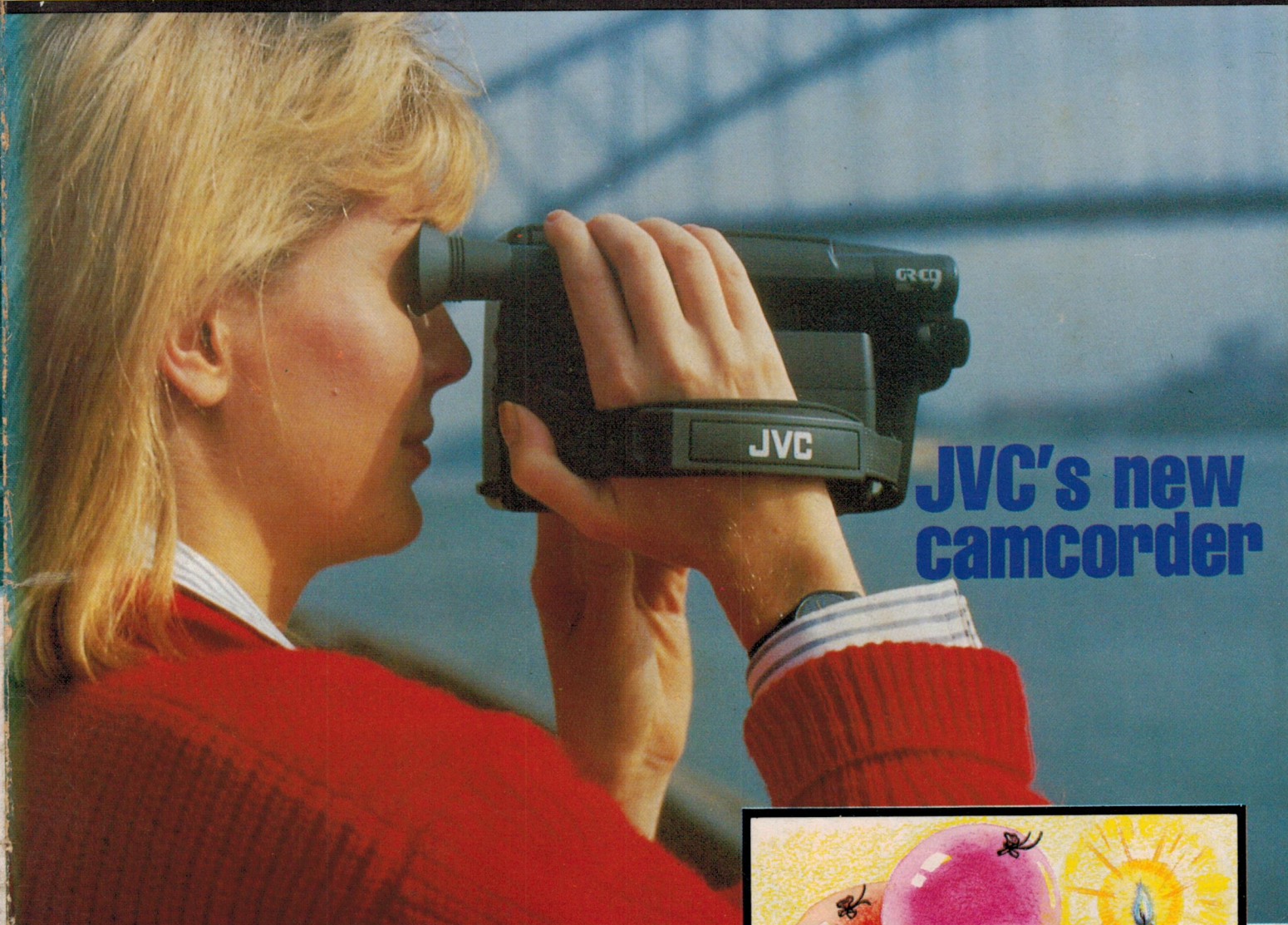

**JVC's new
camcorder**

- **DAT's the future
of audio tape recording**
- **Computer strobe flash**
- **Low cost video movies**

SPECIAL BIRTHDAY ISSUE!

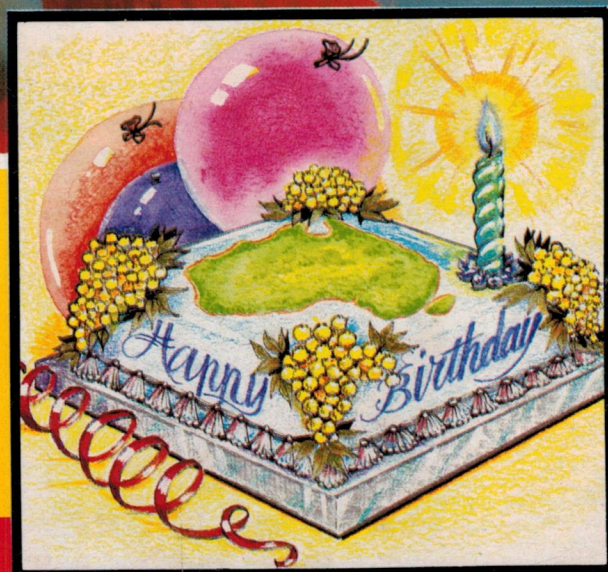

Design in TI's new

The new IBM® Token-Ring Network promises to become the industry standard. And if you are wondering about the best and quickest way to tie your product into this new 4-Mb/sec LAN, here's your solution: **The TMS380 chip set from Texas Instruments.**

TI's TMS380 is the *only* commercial chip set tested — and system-verified — by IBM. It's *the* silicon standard for this new high-speed office-system LAN.

And for a sure, fast entry into this exciting new market, you can begin with TI's TMS380 Design-in Accelerator Kit.

Q. What kinds of products can communicate through the new LAN?

A. With the TMS380 chip set, almost any.

TI's new TMS380 chip set was developed jointly with IBM. Its general-purpose system interface allows many kinds of equipment from various manufacturers to communicate through the IBM Token-Ring Network. And since this is an open network, any product in which you use the TMS380 can communicate with any other, when common languages are used.

Q. Is expensive cabling required?

A. No.

Your customers have the option of using telephone twisted pair or shielded twisted pair. And the point-to-point topology of the token ring makes it ideal for fiber optics, since the taps that are necessary with bus topologies are not required.


Q. Where does TI's TMS380 chip set fit in?

A. It's the heart of your LAN adapter card or subsystem.


The TMS380 chip set is a complete solution for the physical interface and media-access control. Its integrated LAN-adapter architecture provides for efficient, transparent handling of the IEEE 802.5 protocols. TI's TMS380 in your product will give your customers freedom to choose the cabling system that best suits their needs. And the flexibility to interface with any of the popular logical-link-control and higher-layer protocols.

◀ **Everything you need** to begin designing your own IBM Token-Ring Network LAN adapter is included in your TI *Design-in Accelerator Kit*: Three TMS380 chip sets, comprehensive literature, and debug software.

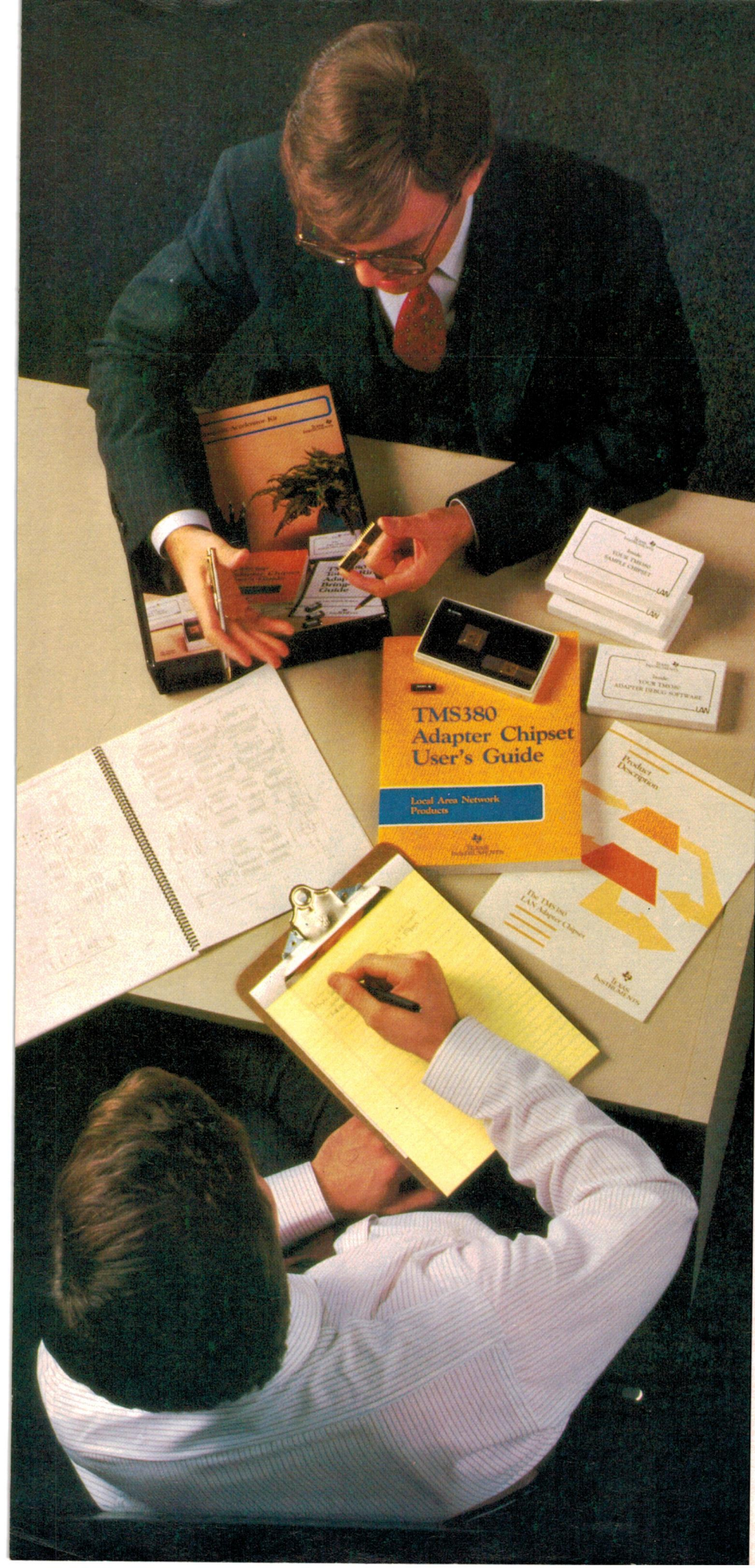*Registered trademark of International Business Machines Corp.



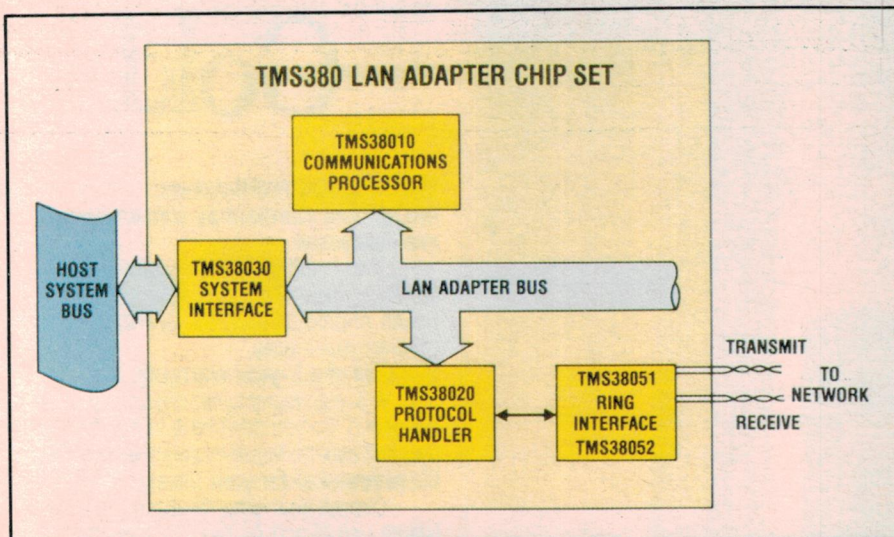IBM compatibility with token-ring-LAN chip set.



Five TMS380 chips form the heart of your LAN adapter. The TMS38030 automatically manages the interface between system memory and the adapter. The TMS38010 processes and buffers data. The TMS38020 contains RAS and LAN-management software and handles data in accordance with IEEE 802.5 protocols. And the TMS38051 and TMS38052 monitor cabling integrity, control network insertion, and perform clocking and signal conditioning.

Q. What about network management?

A. Every service your system needs is built in.

TI's new TMS380 chip set includes "self-healing" features that ensure the reliability, availability, and serviceability (RAS) of the network. And only the TMS380 chip set has them.

Among these special features are fault isolation of cable-system failures, error reporting, self-test diagnostics, and LAN-management services. So you're relieved of the risk, time, and expense of developing custom hardware and software for these essential functions.

Q. Can it grow with my needs and my customers'?

A. Yes.

On-chip RAS and LAN-management software make TI's TMS380 chip set completely compatible with the IBM Token-Ring LAN and give it a stable foundation to meet the need for future network expansion. As higher performance standards develop, the TMS380 chip set will accommodate them.

Q. What's this about an Accelerator Kit?

A. It's your head start to IBM token-ring compatibility.

TI's Design-in Accelerator Kit will give you a head start on designing IBM Token-

Ring Network compatibility into your products. It includes three chip sets, the TMS380 User's Guide, and the Token Ring Adapter Bring-Up Guide with debug software.

TEXAS INSTRUMENTS

Creating useful products and services for you.

TEXAS INSTRUMENTS FIELD SALES OFFICES

Melbourne: (03) 267-4677

Sydney: (02) 887-1122

TEXAS INSTRUMENTS DISTRIBUTORS

ADELAIDE:

EC & E: (08) 232-0001

VSI: (08) 267-4848

BRISBANE:

Rifa: (07) 832-3700

VSI: (07) 52-5022

MELBOURNE:

Rifa: (03) 480-1211

VSI: (03) 543-6445

PERTH:

VSI: (09) 328-8499

SYDNEY:

Rifa: (02) 858-5966

VSI: (02) 439-8622

To: Texas Instruments Australia
6 Talavera Rd.,
North Ryde 2113

- ☐ Please rush me a TMS380 Data Package.
☐ Place my name on the TMS380 Mail List.

Company

Name


Address

..... Suburb State

Postcode Ph: ()

Good as Gold

FLUKE
1,000,000

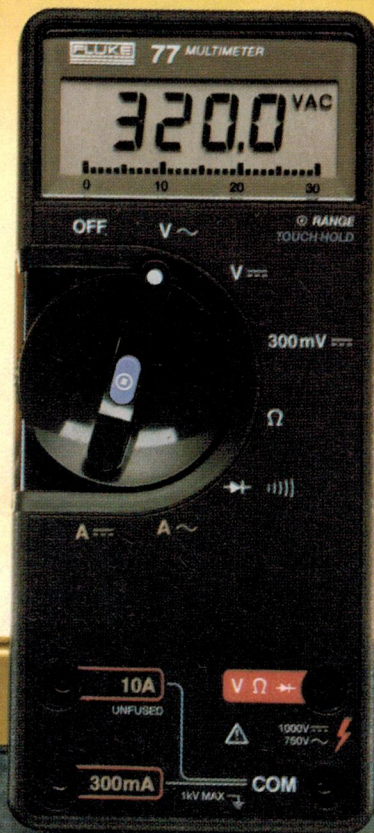

The 70 Series Multimeters: the shining standard by which others are measured.

These multimeters are produced through advanced technology that assures you a wealth of product features. Giving you solid value for your money.

Security of a 3-year warranty.

A 3-year warranty reduces your cost of ownership. So you don't have to pay the price over and over for lesser-quality multimeters.


More features for your money.

Choose from either the basic 73 or the feature-rich 75 and 77. You'll find the features you need at the price you can afford. Touch Hold™ for capturing and holding readings. Audible tones to signal you for continuity. Autoranging for simple operation. And a sleep mode for extending battery life up to 2000 hours.

Unsurpassed quality.

Like other Fluke products these multimeters offer you uncompromised quality at competitive prices. Visit your electronics representative today and get your hands on a 70 Series Multimeter. You'll see that brilliant performance is within your reach.

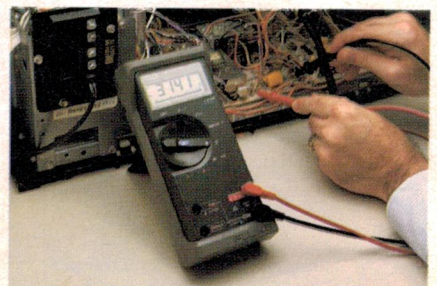FROM THE WORLD LEADER
IN DIGITAL MULTIMETERS.



FLUKE 73, 75, 77

0.7%, 0.5%, and 0.3% basic dc accuracy	3-year warranty
Analog/digital display	Audible continuity (75 & 77)
Volts, ohms, 10A, diode test	Range hold (75 & 77)
Autorange	Multipurpose holster (77)
2000+ hour battery life	Touch Hold function (77)

Talk to your local Elmesco distributor about Fluke —

- A.C.T. John Pope Electrical (062) 80 6576 • J Blackwood & Sons (062) 80 5235 • George Brown (062) 80 4355
- N.S.W. Ames Agency 699 4524 • J Blackwood & Sons • George Brown 519 5855 Newcastle 69 6399 • Bryan Catt Industries 526 2222 • D.G.E. Systems (049) 69 1625
- Petro-Ject 550 1388 • David Reid 267 1385 • W. F. Dixon (049) 61 5628 • Macelec (042) 29 1455 • Ebson 707 2111 • Selectoparts 708 3244 • Geoff Wood 427 1676
- Novacastran Electronic Supply (049) 62 1358
- N. TERRITORY J Blackwood & Son (089) 84 4255, 52 1788 • Thew & McCann (089) 84 4999
- QUEENSLAND Auslec (07) 8541661 • Petro-Ject (075) 91 4199 • St Lucia Electronics 52 7466 • Cliff Electronics 341 4655 • L. E. Boughen 369 1277
- Fred Hoe & Sons 277 4311 • The Electronic Shop (075) 32 3632 • Thompson Instruments (Cairns) (070) 51 2404
- S. AUSTRALIA Protronics 212 3111 • Trio Electrix 212 6235 • Industrial Pyrometers 352 3688 • J Blackwood & Son 46 0391 • Petro-Ject 363 1353
- TASMANIA George Harvey (003) 31 6533 (002) 34 2233
- VICTORIA Radio Parts 329 7888 • George Brown Electronics Group 878 8111 • G B Telespares 328 4301 • A.W.M. Electrical Wholesalers • Petro-Ject 419 9377
- J Blackwood & Sons 542 4321 • R.K.B. Agency 29 7336 • Sirs Sales (052) 78 1251 • Mektronics Co 690 4593 • Truscott Electronics 723 3094
- W. AUSTRALIA Atkins Carlyle 481 1233 • Dobbie Instruments 276 8888 • Protronics 362 1044

FLUKE®

Electronics Australia

Volume 49, No.8


August 1987

AUSTRALIA'S LARGEST SELLING ELECTRONICS MAGAZINE — ESTABLISHED IN 1922

65 this month!

It's our 65th birthday this month! Read about the early days of the magazine in our feature starting on page 24...

Strobe flash adapter

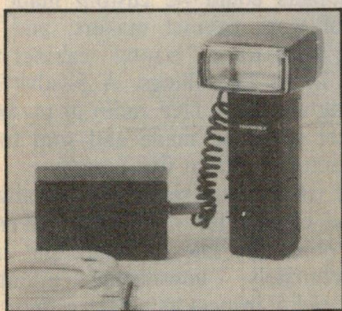

Need to stop moving objects? You can with a low cost electronic flash, using this strobe adapter. It hooks up to your Apple or Microbee. See page 82.

Digital audio tapes

Heard about the new DAT recorders that let you make home audio recordings with CD quality? The good news starts on page 10.

ON THE COVER

JVC's new GR-C9EA is claimed to be the smallest VHS-system video camcorder yet produced. It features a CCD pickup array and records on compact cassettes that play back in a standard VHS recorder, via an adapter — see page 6.

Features

- 14 X-WING HELICOPTERS *They're coming, and they're fast!*
- 24 A DREAM THAT LASTED 65 YEARS *Birthday feature story*
- 44 FUNWAY VIDEO *First the books and kits, now a movie!*
- 72 HOME MOVIES ON THE (VERY) CHEAP *Using old video gear*
- 92 COMPACT NEW 10MHZ SCOPE RUNS FROM BATTERIES *OK 1010*
- 118 LOCAL AREA NETWORKS — 3 *Ring functions and hardware*
- 125 WIN A LAN DEVELOPMENT SYSTEM *\$10,000 prize from TI*

Entertainment Electronics

- 6 WHAT'S NEW IN ENTERTAINMENT ELECTRONICS *Video, audio*
- 10 DAT'S THE FUTURE OF AUDIO TAPE RECORDING *And it's good!*
- 48 COMPACT DISC REVIEWS *Haydn, Brahms, Grieg & Mozart*
- 88 PIGGYBACK FM BROADCASTING REACHES AUSTRALIA

Projects and Technical

- 40 THE SERVICEMAN *A journey into unfamiliar territory*
- 46 CIRCUIT & DESIGN IDEAS *Measuring complex impedance*
- 59 LOW COST WIRELESS GUITAR LINK *No more messy cables!*
- 62 SOLID STATE UPDATE *New chip for RS-232C interfaces*
- 64 A REALLY BIG LED DISPLAY MODULE *Digits 153mm high...*
- 68 A 4-DIGIT COMBINATION LOCK *Uses a single pushbutton*
- 82 COMPUTER CONTROLLED ELECTRONIC STROBE *Low cost!*
- 106 UNDERSTANDING COLOUR TV — 7 *The complete receiver*

News and Comment

- 4 LETTERS TO THE EDITOR *More on vintage radio, etc*
- 5 EDITORIAL *Our 65th birthday issue!*
- 18 FORUM *Gilding the lily: Is it worthwhile?*
- 34 NEWS HIGHLIGHTS *Monitoring health in Antarctica*
- 94 NEW PRODUCTS *More of them than ever!*
- 126 INFORMATION CENTRE *Answers to readers' queries*

Departments

- | | |
|-------------------------|-----------------------|
| 50 BOOK REVIEWS | 128 MARKETPLACE |
| 114 EA CROSSWORD PUZZLE | 130 COMING NEXT MONTH |
| 114 50 AND 25 YEARS AGO | 128 NOTES AND ERRATA |

MANAGING EDITOR

Jamieson Rowe, B.A., B.Sc.,
SMIREE

EDITORIAL STAFF

Rob Evans, CET (RMIT)
Henk Mulder, HTS EE
Carmel Triulcio

GRAPHIC DESIGNER

Brian Jones

ART PRODUCTION

Alana Horak

PRODUCTION

Kylie Prats

SECRETARIAL

Naomi Lenthen

ADVERTISING PRODUCTION

Brett Baker

Vikki Patching (Vic)

ADVERTISING MANAGER

Selwyn Sayers

PUBLISHER

Michael Hannan

HEAD OFFICE,**EDITORIAL & ADVERTISING**

180 Bourke Road, Alexandria, NSW 2015
P.O. Box 227, Waterloo 2017.

Phone: (02) 693 6666

Fax number: (02) 693 2842 Telex: AA74488

NSW Representative: Mark Lewis

INTERSTATE ADVERTISING OFFICES

Melbourne: 221a Bay Street, Port Melbourne, Vic. 3207.

Phone: (03) 646 3111

Representative: John Oliver

Brisbane: 26 Chermide Street, Newstead, Qld 4006.

Phone: (07) 854 1119

Representative: Bernie Summers

Adelaide: John Fairfax & Sons Ltd,

101 Weymouth Street, Adelaide, SA 5000.

Phone: (08) 212 1212

Representative: Mike Mullin

Perth: John Fairfax & Sons Ltd,

454 Murray Street, Perth WA 6000.

Phone: (09) 481 3171

Representative: Estelle de san Miguel

New Zealand: 3rd Floor, Communications House, 12 Heather Street, Parnell, Auckland, New Zealand.

Phone: (09) 39 6096. Telex: NZ 63122

SPORTBY

Representative: John Easton



ELECTRONICS AUSTRALIA is published monthly by The Federal Publishing Company Pty Limited.


Typeset and printed by Hannanprint, 140 Bourke Road, Alexandria, NSW for The Federal Publishing Company Pty Ltd.

Distributed by Newsagents Direct Distribution Pty Ltd, 17 Doody Street, Alexandria NSW 2015

Registered by Australia Post — publication No. NBP 0240

ISSN 0313-0150

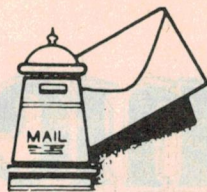*Recommended and maximum Australian retail price only.



Letters to the editor

A bouquet

Congratulations on your return to the magazine! I'm sure that with you back in the driving seat, EA has a bright future.

I've enjoyed the time we worked together, both when you were still at EA the first time and then when you came to Dick Smith Electronics. You made an important contribution there as well, and we had a lot of fun. But I know your real love has always been writing and editing, and they're the things you do best. So it's great to see you and EA back together again — an ideal combination.

I expect to see some exciting things in EA soon, so get cracking. What about a few good stories on what Australians are doing in electronics, for a start. We have a lot to be proud of!

Anyhow, all the best for the future.

Dick Smith,

Australian Geographic,
Terrey Hills, NSW.

Comment: Thanks for the bouquet, Dick. You've done pretty well at publishing yourself, among other things! We've already got some stories on Aussie developments in the pipeline, too . . .

Vintage radios

Your articles by John Hill on vintage radios contain views with which I fully agree, bringing back memories of the good old days of the early 1930's when mains powered radios were taking over from the battery driven variety.

As an electrical apprentice at that time, and a subscriber to *Wireless Weekly*, I became a manufacturer in a very minor way (no licence, naturally!) for a limited circle of friends.

My interest lay in TRF receivers of better than average tonal quality, as against the hiss and background noise of the superheterodyne. Preferred circuits were for receivers of 5 to 8 valves, including rectifier, with two or three stages of RF tuning, which gave reasonable selectivity of the few broadcasting stations in operation at that time. Some of the models built incorporated push pull output and dual 8 or 10 inch speakers.

The quality of output was, as John

Hill states, quite impressive, especially if the speakers were mounted in large cabinets. Rola was a popular choice of speaker. Jensen was another. Also impressive were the prices of components at that time. Mains transformers for push pull 5 watt output were rated at 150 watts, the HT secondary centre tapped winding giving 385 volts each side at 150mA. These transformers, made in Australia under the name "Radiokes" cost seven shillings and sixpence (75 cents). RCA valves could be purchased from the distributor at retail less 40, less 10, and a further 5% for cash. This brought the cost of a 280 rectifier to 28c.

Cabinets could be custom made by out of work cabinet makers, and the going price for a "mantel" cabinet was from 15 to 25 shillings. A 5-valve (including rectifier) TRF radio in plywood cabinet could be made and sold for a satisfactory profit at five pounds.

We (there were several of us) always waited eagerly for the *Wireless Weekly* to give us the latest circuits and tips. Unfortunately, unwelcome attention from radio inspectors who, rather unreasonably, we thought, required us to produce licences to manufacture, spelt the demise of our small circle of radio builders. Countless models of commercial makes were available from Europe, Australia and local sources.

There are still valve radios in operation — cowsheds are a favourite location — but real antiques, such as the German Loewe (a single large valve containing multiple stages) would be hard to come by now. Reconditioning of oldtimers as suggested by John Hill is certainly a hobby to be considered seriously, being relatively inexpensive and satisfying.

Ian Page,

Mangawhai, New Zealand.

Proclamation of "Declared Articles"

By order published in the Government Gazette No.60 of 27 March 1987, Electric Fence Energiser, Bayonet Cap Lampholder and Edison Screw Lampholder were proclaimed as declared articles effective from 1 July 1987. The ear-

lier definition of Normal Bayonet Lampholder was also revoked.

Electric fence energisers and Edison screw lampholders which are within the declaring definition, will require certificates of approval from 1 July 1987.

Existing certificates of approval for bayonet cap lampholders (B14) and Edison screw lampholders will be cancelled from 1 July 1987, and it will be necessary for these certificates to be returned. Applications for replacement certificates of approval must therefore be initiated without delay.

The prescribed fee for applications for bayonet cap lampholder and Edison screw lampholder is \$55.00. For electric fence energisers the application fee is \$142.00.

Where guidance is required on whether a particular article falls within the scope of the definitions, advice may be obtained from the Energy Authority's Equipment Approvals Section.

N.C. Watson,
Energy Authority of NSW,
Sydney, NSW.

Vintage radios: sets & parts available

I have available an Airzone chassis circa 1935, including, handbook, a Ferguson Radio (1.4V valve type) circa 1947, and some sundry parts available "give away" to an interested party. My phone number (home) is (02) 451 9894.

Any assistance to avoid taking those items to the tip would be welcome.

Peter Grout,
Forestville, NSW.


Components for restoring vintage radios

Although I'm not into electronics (purely a hifi listener) I thought John Hill or your readers would be interested in the following information. I've recently received a catalogue from England put out by:

The Vintage Wireless Company, of
Tudor House, Cosham Street,
Mangotsfield, Bristol BS17 3EN,
England.

This catalogue has 166 pages and is full of the items which would seem impossible to obtain. There are 10 pages of new and boxed valves, several thousand in fact, from type A20B at 4 pounds to 829522. They keep just about everything: books, condensers, chokes, crystals, needles, gramophone parts,

continued on page 126

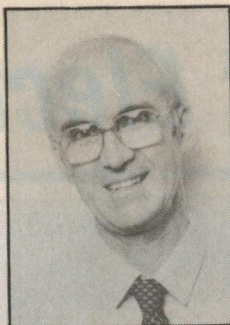

Editorial Viewpoint

Our 65th birthday issue!

This is a very special issue for us, because it marks the achievement of no less than 65 years of continuous publication.

August 1922 saw the first issue of *Wireless Weekly*, Australia's first magazine for enthusiasts working in the newly-discovered field of "wireless". It obviously met a need among both amateurs and the soon-to-emerge professionals, because it immediately took off and flourished along with the industry itself.

Over the years, as that industry changed and broadened in its scope, the magazine also adapted to those changes. In April 1939 it changed its name to *Radio & Hobbies*, to reflect the broader range of interests. At the same time it changed from a weekly into a monthly, to give more opportunity to deal with technical matters in more depth.

Since then, the magazine has changed its name twice more, each time to reflect the ever-broadening nature of its subject area. In the late 1950s, when television broadcasting began, it became *Radio, Television and Hobbies* (such a mouthful that everyone called it "R,TV & H" for short). Then in April 1965, it was changed to the present name, intended to convey what is still our ongoing aim: to project a uniquely Australian image in the exciting field of electronics, in all of its areas of application.

We're especially proud that this birthday issue carries a feature article on the early days of the magazine, written by my old boss Neville Williams. Our former Editor-in-Chief, Neville is the person with the longest-ever association with the magazine, and therefore ideally suited to write such a story. You'll find it makes fascinating reading — I certainly did!


Needless to say, although the magazine may have turned 65, we have no intention of retiring. Quite the contrary: we now have our sights set firmly on the ton (tonne?).

Electronics is a fascinating activity, whether you're working in it for your living or pursuing it as a hobby. It now pervades so many areas of human activity, and progresses at such a rate, that we're never going to be short of interesting news, feature articles and try-it-yourself projects to bring to you each month in EA.

So stick with us, as we continue our tradition of bringing you the best of electronics in Australia.

Jim Rowe

What's New In Entertainment Electronics

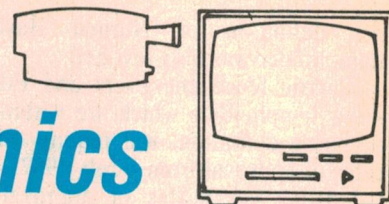

New compact VHS mini camcorder



JVC has released what it claims is the smallest VHS camera recorder in the world.

Called GR-C9EA, the new mini VHS video movie illustrates just how advanced video technology has become. Upholding two fundamental policies — format perfection and compatibility — JVC has pursued a rigorous set of objectives for every camera recorder produced since the first relatively basic VCR. These include reduction of weight and size, further enhancement of picture quality, superior reliability, and utilisation of the latest video technology throughout.

The new GR-C9EA record-only model, which was released in Australia in June, achieves all these objectives, according to JVC.

The GR-C9EA's record-setting com-

New TDK audio tape

TDK has released a new line-up of audio tapes, featuring improvements in formulation through to packaging.

TDK's range now offers a total of eight audio tapes — two metal, three High Position or Type II, and three Normal Position or Type I tapes.

Outstanding in the new TDK range is type SF (Super Fidelity), a new High Position Type II tape designed to offer similar performance to the very famous SA tape (Super Avilyn). SA is famous for its acceptance by most leading cassette deck manufacturers, as the alignment tape for their cassette decks in the High or Type II position.

"The new SF audio tape is designed to very similar specifications as the



TV-VCR combination from TEAC

Teac engineers have produced what could be the ultimate second TV set for the family.


The Teac Televideo is Australia's very first portable 34cm colour TV with its own inbuilt VHS video cassette recorder. In other words, a complete home video entertainment system made portable.

This new Teac unit is scarcely bigger than a conventional 34cm portable TV set. It weighs just 16.4kg and can be easily picked up — even by children — and moved from room to room, whether the bedroom or the family room. It has built-in antenna and merely needs to be plugged in to a

power outlet. Naturally, for optimum tuning capability it is preferable to connect the unit to a video/TV cable in the room where it is being used.

Despite its compact size, Teac Televideo has many of the features of individual TV's and videos. For example, it has a 12-function cordless remote control, full timer recording, one-touch record, still frame with special noise cancel facility, picture search and automatic rewind. It also offers 4-hour recording/playback capability.

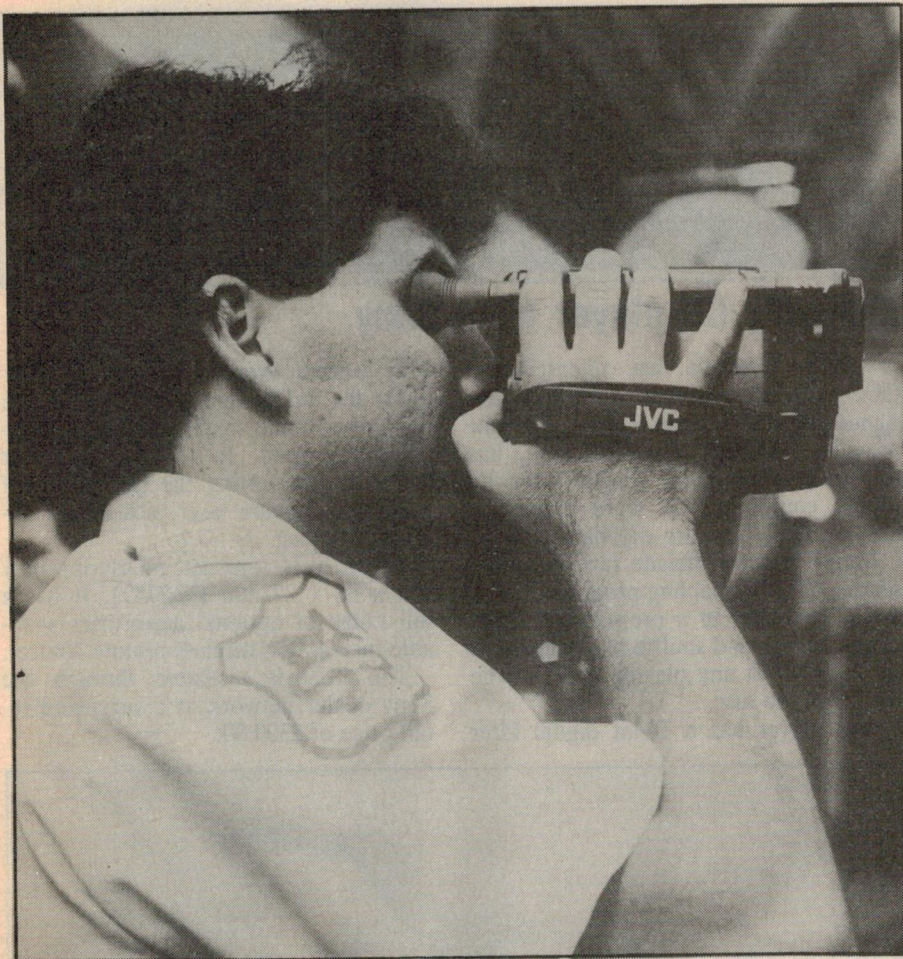The recommended retail price is \$1299 with a 12 month warranty or \$1399 with a 5 year warranty.



pactness and ultra-light weight (760 grams) were attained through a number of technological advancements and has resulted in further improved performance.

According to the managing director of Hagemeyer (Australasia), Mr Edwin Koemans, "The introduction of the GR-C9EA has been in response to market

demands for an easy-to-use camcorder which does not compromise consumer needs when it comes to the two major priorities in portable equipment — size and weight."

As the world's smallest and lightest VHS camera, the GR-C9EA is ideal for amateurs and professionals alike. Mr Koemans claims that even children will

find it easy to use. It offers up to one hour of recording on its mini VHS cassette, with playback on any VHS deck using an adaptor cassette.

Unlike other mini camcorders that sacrifice features for small size, the new GR-C9EA record-only model has all the functions expected from top-line camcorders. It's the first video camera to reduce weight and size by shaping the battery so that it can double as the camera's hand-grip.


Other features includes a new zero frame editing feature, employing micro-computer control which ensures noise-free transition between paused recordings, HQ (High Quality) system circuitry and auto white balancing which responds automatically to changes in light source, producing balanced results both indoors and out.

Delivering pictures that offer high



resolution even for rapidly moving subjects, the GR-VC9EA employs a new and very much improved high-performance CCD (Charge Coupled Device) that is fast, highly resistant to shock and vibrations, and less susceptible to image burn-in than conventional camera tubes.

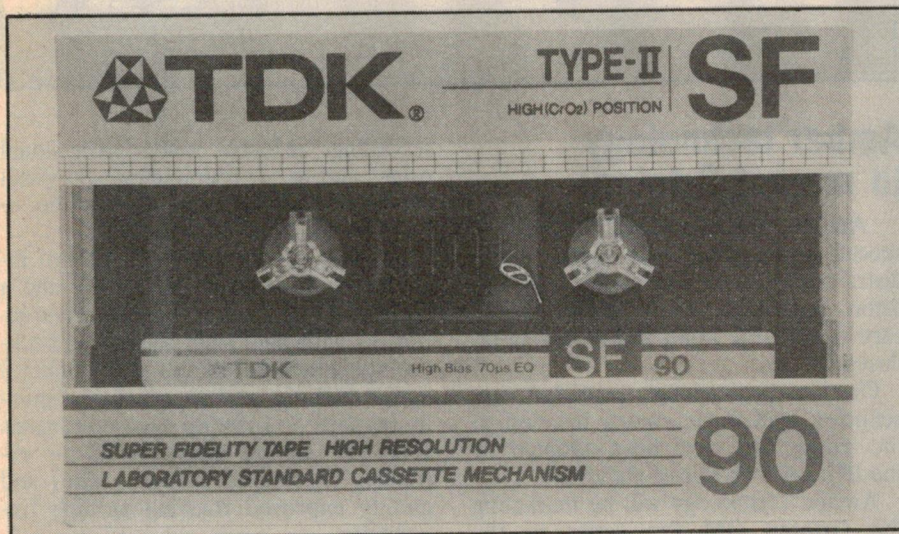Recommended retail price in Australia is \$2099.




previous SA, but with an economy price" said Mr Kihara, General Manager of TDK (Australia). SF is an extremely quiet tape, with bias noise a very low -61dB.

SF is well suited to most recording applications, particularly to classical and material with a wider dynamic range. The extended high frequency range to beyond 16kHz enables the higher order harmonics to be reproduced faithfully.


TDK has gone to considerable effort to improve the cassette housing of SF, housed in a new Laboratory Standard cassette mechanism. Recent research in cassette housing developments has shown that transport systems and housing are just as important as the magnetic material itself.

A NEW APPROACH TO DISTRIBUTED LOUDSPEAKER SYSTEMS

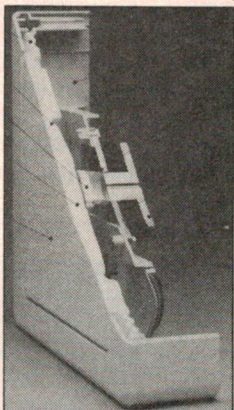The
Odyl
Group
Presents
the B.E.S. 180
deg dispersion
ceiling speakers



Less
than
8cm
deep!!

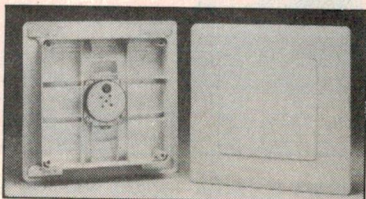


The amazing performance of these speaker panels can be enjoyed at a fraction of the cost of speaker systems currently available. They can be used indoors and outdoors for example, the AZTEC Stadium, Hollywood Bowl, Las Vegas Hilton, major US department stores etc. We offer a complete technical support package and engineering assistance.

ODYL GROUP LTD
112 JAMES ST
TEMPLESTOWE, VIC 3106
PHONE (03) 846 3022

N.S.W. OFFICE
63 KENT ST
SYDNEY, N.S.W. 2000
PHONE (02) 262 1304

Please forward details of
B.E.S. ceiling systems

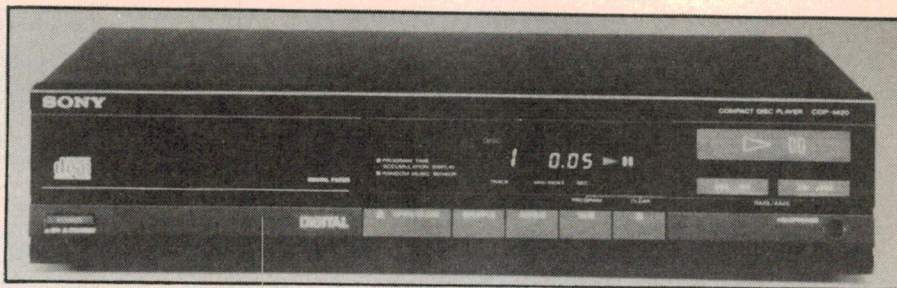Name
Address
Postcode
Phone
My project is, indoor, outdoor,
please describe.



Economy CD player from Sony

Sony Australia has released the CDP-M20, an economy CD player designed for the first time user. The unit provides features that research has shown are the most sought after by today's consumer, yet were previously only available in more expensive units.


Major features include random music search (RMS), enabling programming of up to 16 tracks in a pre-selected order of preference and shuffle play which lets the user select any playing order of the tracks on the disc.

The player has a 16-bit digital filter

with 2-times over sampling, which reduces the digital signal's influence upon the analog audio signal resulting in crystal clear sound. It also has unilinear converter preventing the generation of jitter and 3-beam laser pick-up for superior tracking.

The M20 is compact, measuring only 355 x 80 x 272mm (W/H/D). It has a full range of optional accessories available including a wireless remote control.

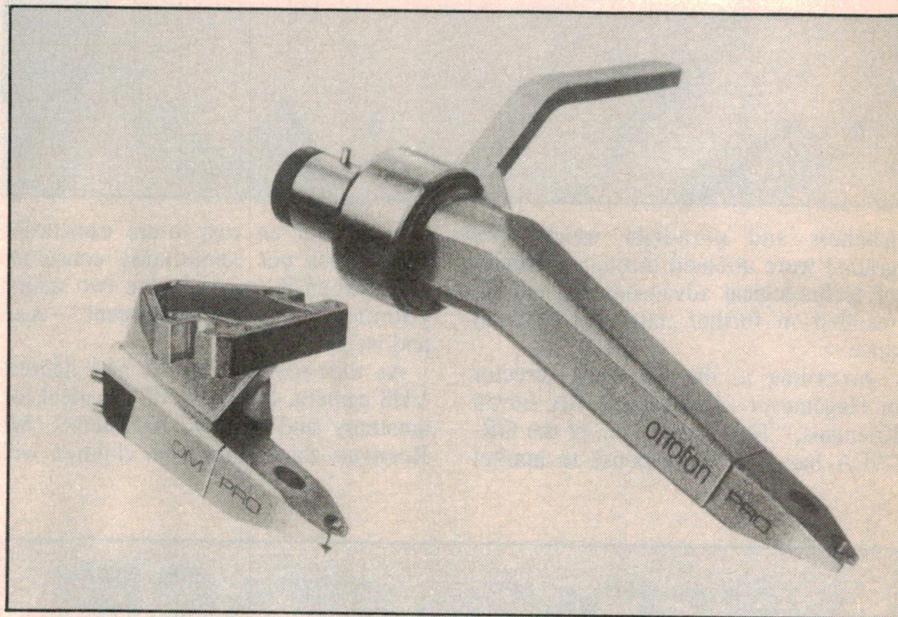The M20 is available through the Sony dealer network at a suggested retail price of \$399.00.



Amber technology to market Ortofon

Amber Technology has concluded a special arrangement with Scan Audio, distributors for the Denmark-based Ortofon, to market Ortofon's professional cartridges to the radio and recording industries.

Ortofon professional cartridges are acknowledged to be among the best in the world, and have been adopted by the BBC as a broadcast standard.

Amber Technology will be marketing the Ortofon OM Pro series to the



recording industry and professional users, and as an introductory offer will supply two units for the price of one, to the first one hundred purchasers.

Features of the Ortofon OM Pro include a full playback cue facility and a luminous tip, a more robust construction to withstand such rigours as back-cueing (practised by all disc jockeys) and scratching, and superb sound quality because of a low tip mass that means very low surface noise (with an extremely high signal to noise ratio) and greatly improved tracking at high frequencies.


ELECTRONICS

EXCITING JOBS WITH A FUTURE

1987

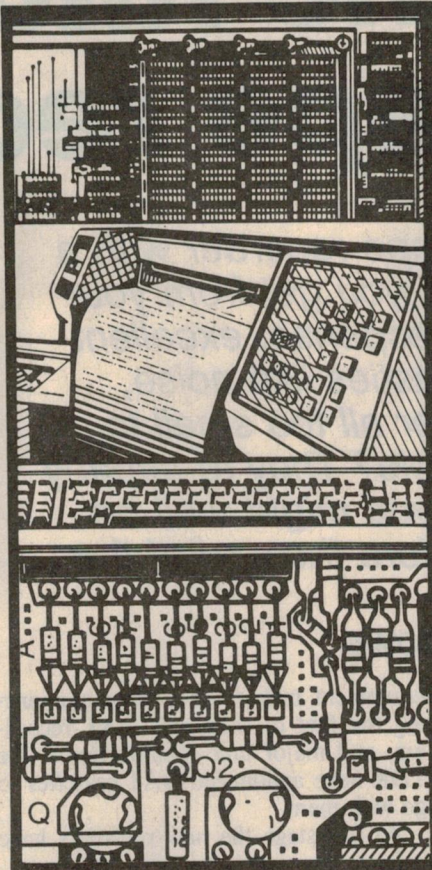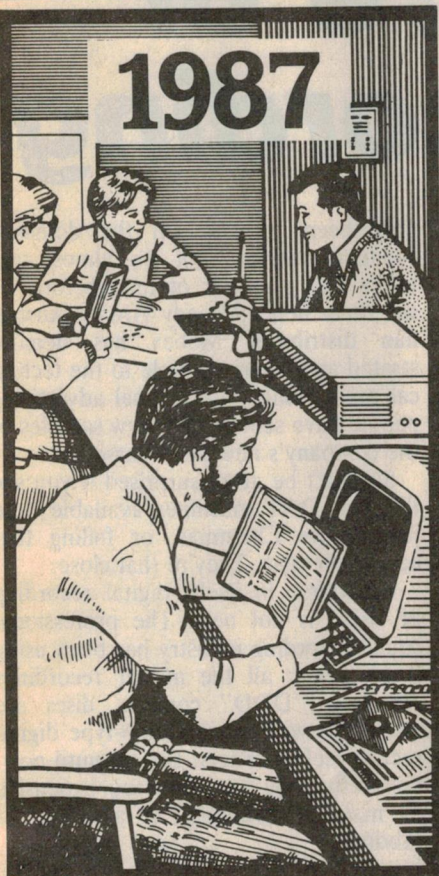

1990

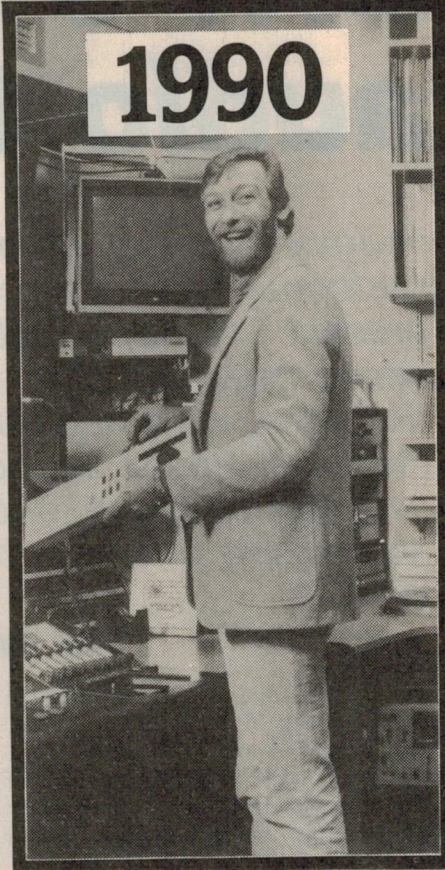

GET YOUR TRAINING NOW AND BE PREPARED FOR THE FUTURE


If you're interested in electronics, a Stott's Home Study Course can make it even more interesting. It could lead to an exciting career in the fast growing field of electronics.

You can start with Stott's Introduction to Electronics which gives you an understanding of the basic principles, then choose from Stott's range of electronics courses. Radio and Television Servicing, Radio Receivers, Colour Television, Introduction to Micro Computers, Digital

Electronics for Technicians & Servicemen or Industrial Electronics.

Stott's electronics courses offer plenty of practical work and 'hands on' experience through custom designed kits. You'll be skilfully guided by experienced, professional instructors, with individual attention and advice. You study at home, at your own pace.

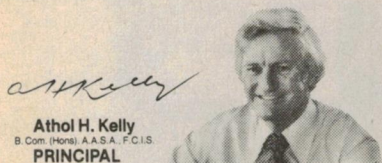Make your move towards a brighter future. But do it now. Send the coupon today.



Athol H. Kelly
B Com (Hons) A.A.S.A. F.C.I.S.
PRINCIPAL

"Stott's Correspondence College is Australian in origin and ownership, with a tradition of nearly 80 years fine educational service to men and women throughout Australia."

Stotts

CORRESPONDENCE COLLEGE
The name to trust in correspondence education

Melbourne, 140 Flinders Street, 3000. Tel: 654 6211
Sydney, 363 George Street, 2000. Tel: 29 2445
Brisbane, 65 Mary Street, 4000. Tel: 221 3972
Adelaide, 226 Pulteney Street, 5000. Tel: 223 3700
W. Perth, 25 Richardson Street, 6005. Tel: 322 5481
Hobart, 150 Collins Street, 7000. Tel: 34 2399
New Zealand, Box 30-990, Lower Hutt. Tel: 67 6592

WITH STOTT'S YOU CAN START ANY COURSE ANY TIME
OF THE YEAR AND PROGRESS AT YOUR OWN PACE.

PLEASE SEND ME FREE, AND WITHOUT OBLIGATION,
FULL DETAILS OF THE FOLLOWING COURSE:

(PLEASE PRINT)

MR. MRS. MISS

(AGE)

ADDRESS

POSTCODE

Stott's undertake that no sales counsellor will visit you.

ALA/ST6194/EA787

**The next revolution
in consumer electronics:**

DAT's the future of audio tape recording

Imagine a home audio tape recorder with a performance as good as you get from your present CD player: flat response, excellent stereo separation and nasties like noise, distortion, wow and flutter all too small to measure. Sound incredible? They're already available in Japan, and you might well be able to buy one here before the end of the year.

by JIM ROWE

Just as you thought you had adjusted to the wonders of compact discs (CDs), there's a new revolution looming on the consumer electronics horizon: digital audio tape, or DAT. Over the last few months, the major Japanese audio


equipment makers have been announcing the first of their new DAT recorders, and major tape manufacturers like TDK have announced DAT cassettes to go with them.

At this stage the new recorders have


only been released on the domestic Japanese market, but it's almost certainly just a matter of time before we see them here. Already Aiwa's Australian distributor Mobex has demonstrated an advance sample to the technical press, while TDK's local advertising people have sent out preview samples of the company's new DAT cassettes.

So don't be at all surprised if you see the first DAT machines available here just before Christmas, or failing that early next year. They're that close.

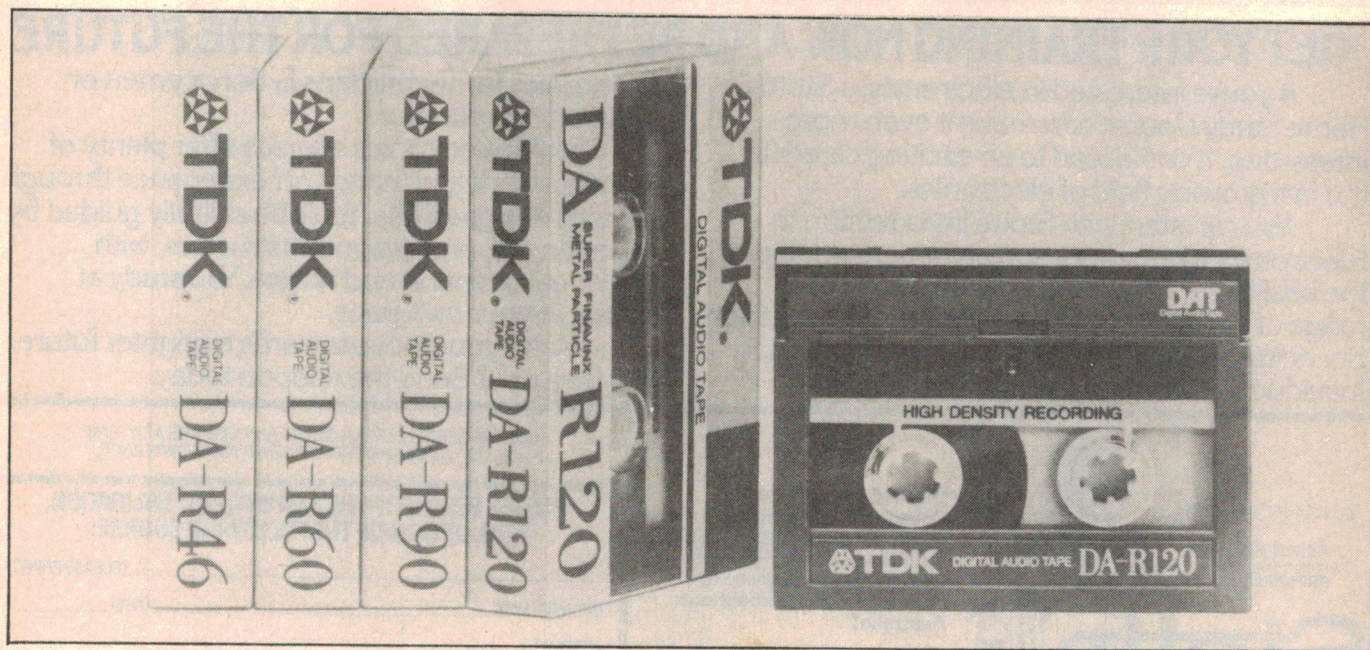Of course in itself, digital recording of audio is not new. The professional sound recording industry has been using it for years; all the master recordings for your "DDD" compact discs are made this way, using studio-type digital reel to reel recorders. But up until now, the technology has been too expensive to make it available as a consumer product.



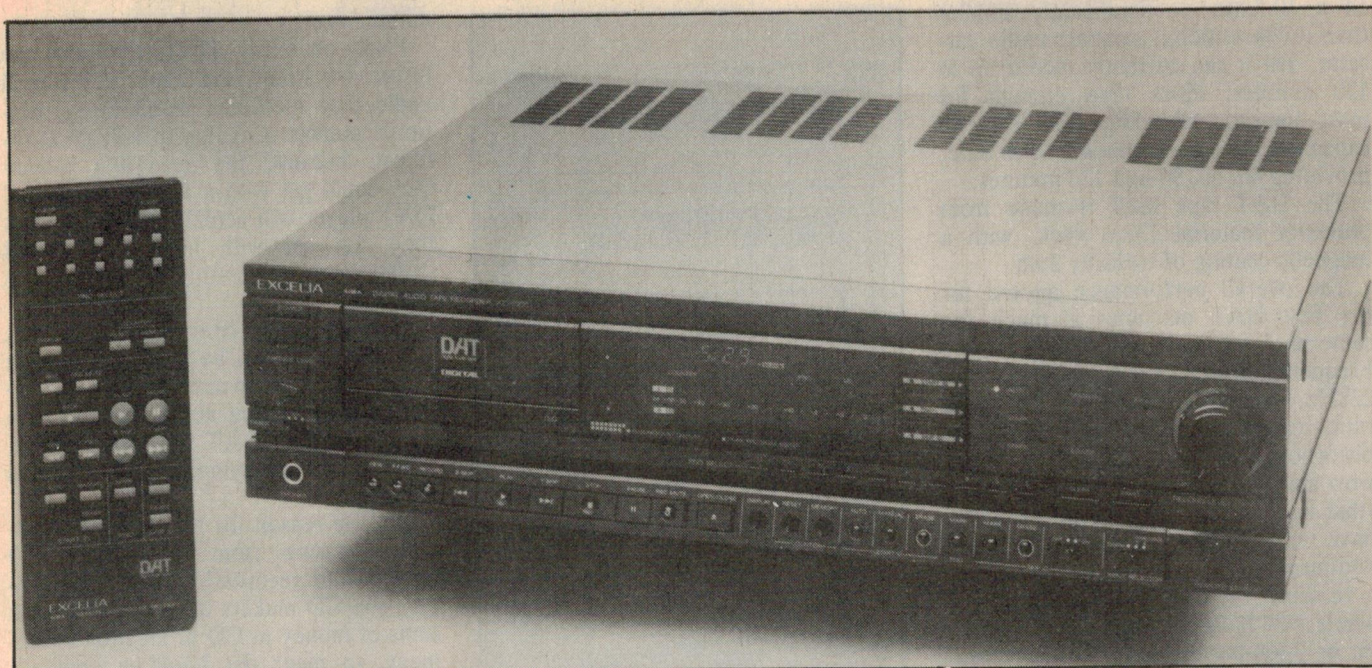At present, cassettes are available in four different playing times: 46, 60, 90 and 120 minutes. The prices currently range from about \$A12 to \$A20 each.



The Aiwa "Excelia" XD-001 DAT recorder, first to be released on the market in Japan, in March. Aiwa flew one out to Australia for a few days recently, for a series of demonstrations. As well as offering full CD-quality recording, it also provides an impressive range of operating functions: high speed track selection and skipping, random play programming and so on.

It was basically the tremendous success of CDs worldwide that started the Japanese audio equipment makers working on DAT in earnest. The CD boom showed that music lovers were eager for the vastly improved performance possible with digital recording: much lower noise and distortion levels, and virtually no wow and flutter at all. They also appreciated the greater operating convenience — no pickup arm to fiddle with (or drop!), the ability to find track selections automatically, and so on.

The manufacturers realised that as soon as people became used to this standard of reproduction and convenience, they were likely to want the same things from their home tape recorders. They certainly weren't likely to be willing to buy conventional analog recorders for much longer, so the market for these was obviously going to nosedive. The sooner the industry would be able to offer attractively priced DAT machines to take their place, the better.

In mid 1985, an industry conference was presented with the results of two investigations by working groups into possible DAT recording standards. One, called S-DAT, involved the use of a conventional stationary recording head system; the other, called R-DAT, employed a rotary head system very similar to that used in video recorders.

The conference chose the R-DAT system for immediate development of consumer DAT equipment, because it

was based on existing technology and therefore closer to the marketing stage. Some 81 different recording hardware, media and software companies attended the conference, including 21 firms from outside Japan, such as Philips. Virtually all the major Japanese firms were represented, including Sony, National (Matsushita), Toshiba, JVC, Aiwa (as subsidiary of Sony), TDK and so on.

Apparently the S-DAT system hasn't been dropped altogether, but may be developed for semi-professional use.


So the machines that have been released in Japan this year are R-DAT machines, and these are the type you're likely to see here later this year.

One of the reasons why DAT technology has been developed fairly quickly is that it has been able to make use of various other recent develop-

ments: the digital audio processing chips and techniques developed for CDs, plus the precision rotary-head recording techniques and high performance metal particle recording tapes developed for the latest 8mm video recorders.

In fact there are a lot of similarities between DAT technology and 8mm video technology. Both use much the same kind of tape, in a compact cassette — although in the case of DAT the tape is only 3.81mm wide. And both use a helical-scan rotary head system, to achieve a suitably high head-to-tape scanning speed. In the case of DAT, the linear head-to-tape scanning speed is about 40 metres per second, although the tape moves at only 8.15mm/sec (the head drum rotates at approximately 2000rpm).

The DAT cassette measures only 73 x

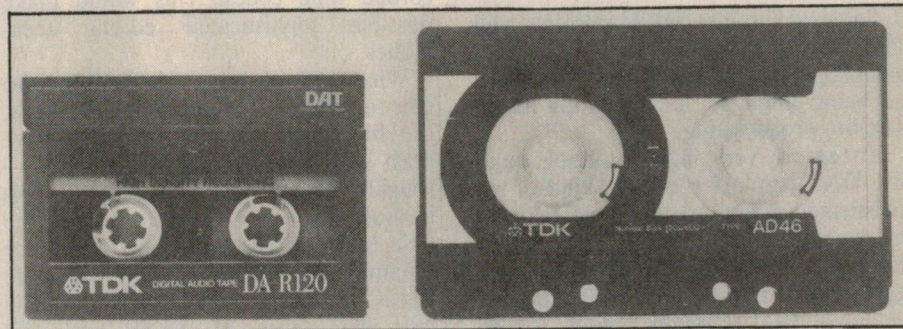

Comparison of one of the new DAT cassettes against a conventional compact audio cassette. They are even more compact, as you can see. TDK's DAT tape uses a 2µm metal-particle formulation, on a polyester base only 13µm thick. The tape is 3.81mm wide and moves at 8.15mm per second.

54 x 10.5mm — significantly smaller than a conventional compact audio cassette. Yet it can currently record up to 120 minutes, more than enough for most domestic recording. Four cassette capacities have been announced to date, providing 46, 60, 90 and 120 minutes.

The DAT tape itself is made from polyester material 13µm thick, with a magnetic coating of typically 2µm.

The overall performance quoted for the first DAT machines is much the same as for CD, if not slightly better. Frequency response is typically 2Hz — 22kHz, within 0.5dB; signal to noise ratio better than 92dB; total harmonic distortion less than .005% at 1kHz; wow and flutter below measurable limits (that is, less than .001%). All machines have two channels, for stereo recording and playback.

In short, the advent of DAT means a whole new ballgame in terms of domestic or "non-professional" audio recording. Virtually anyone with a DAT machine will have the potential to make recordings of a quality which up until now, could only be made using the most expensive studio equipment.


For the technical reader, DAT uses 16-bit linear sampling at a rate of 48kHz. This has been deliberately chosen to be different from, and incompatible with, the 44.1kHz sampling rate used by CDs — to prevent direct digital dubbing of CDs.

Many of the DAT recorders will also replay tapes recorded at the 44.1kHz sampling rate, however, allowing the possibility of pre-recorded DAT tapes produced from CD master recordings. However at present the world's recording software companies do not appear too keen on producing such tapes, because they have invested a lot of capital in expensive CD production plant.

Despite this, Japanese firms like Sony have already developed systems for duplicating pre-recorded DAT cassettes (see picture).

Some of the new DAT machines will also record and play back at a third sampling rate, 32kHz. This is described as being intended for use with future satellite broadcasting.

To ensure very high recording quality, DAT employs the same kind of sophisticated digital error correction techniques as CD. The Sony DTC-1000ES machine uses "feed forward super strategy" error correction, based on double encoded Reed-Solomon coding. It also uses four times over-sampling frequency digital filtering, and the same kind of dual D/A (and A/D) conversion used in the higher quality CD players.

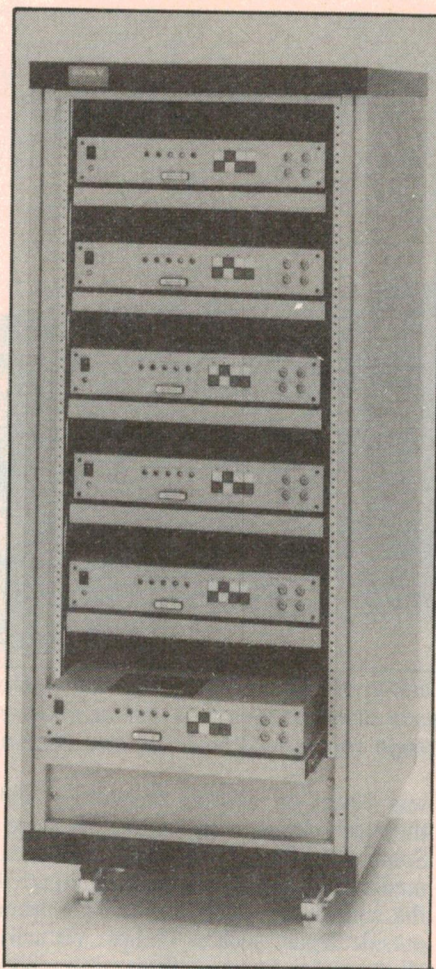

Looking ahead, Sony has produced this DAT software duplication system — for when the world's software publishers finally acknowledge the inevitability of DAT, and agree to play ball.

On the operating side, the new DAT players offer the same kind of random track selection, high speed searching (about 200 times normal speed) and function display facilities as modern CD players. Some of them also provide for random replay programming, using recorded time codes. This would make possible sophisticated editing techniques.

What kind of money do you have to pay to get all of these wonders? Well, the first units released in Japan have been selling for around 200,000 yen — roughly the equivalent of \$A2000. This is much the same as the price of the first home VCRs, allowing a bit for inflation. It's almost certain that the prices of DAT machines will gradually fall, like those of VCRs and CD players.

The cost of DAT cassettes currently ranges from about \$A12 for the 46-minute size to around \$A20 for the 120-

minute size.

Fairly obviously, DAT represents the future for home and semi-professional audio tape recording. Even the professional market is eyeing it with great interest, because the recording quality they could get with a \$2000 "domestic" DAT player will actually be better than they can get with most professional studio recorders costing up to 10 times as much.

The only query over DAT at present is just when it will be marketed outside Japan. Needless to say the Japanese industry is champing at the bit, because they sense that DAT will be a winner. They're not delaying export business willingly.

No, the reason for the delay is essentially pressure from the world's CD makers and recorded software publishers. The CD makers have invested huge sums of money in CD production equipment, to meet the booming demand. Needless to say, they'd like to get a little return on their investments before DAT could (possibly) affect CD sales.


The software publishers are also worried about people using DAT recorders to copy recordings from CDs, off air and even from conventional LPs. Although the DAT makers have given their machines a different sampling rate from CDs, to prevent direct digital copying, and have built in all sorts of circuitry to detect copy-protection codes (which are easy to build into digital recordings), the software people still aren't happy. At present they have imposed a virtual boycott on DAT, and it is apparently this kind of pressure which is largely responsible for the delays in marketing DAT outside Japan.

It seems to me that just as LPs and conventional audio cassettes have shared the audio recording market for years, CD and DAT will be able to do likewise. In fact I believe if anything, DAT is likely to give CDs a boost — by helping to raise everyone's standards and expectations concerning audio recording quality.

Like LPs and audio cassettes, CD and DAT have complementary roles. One is ideal for publishing pre-recorded music, on a virtually permanent medium, and for listening to that music with a maximum of convenience. The other is going to be excellent for making your own recordings, with the same kind of performance.

Frankly, I can't wait until we get our first DAT recorder for evaluation and review, so I can try one out and tell you all about them from first-hand experience!

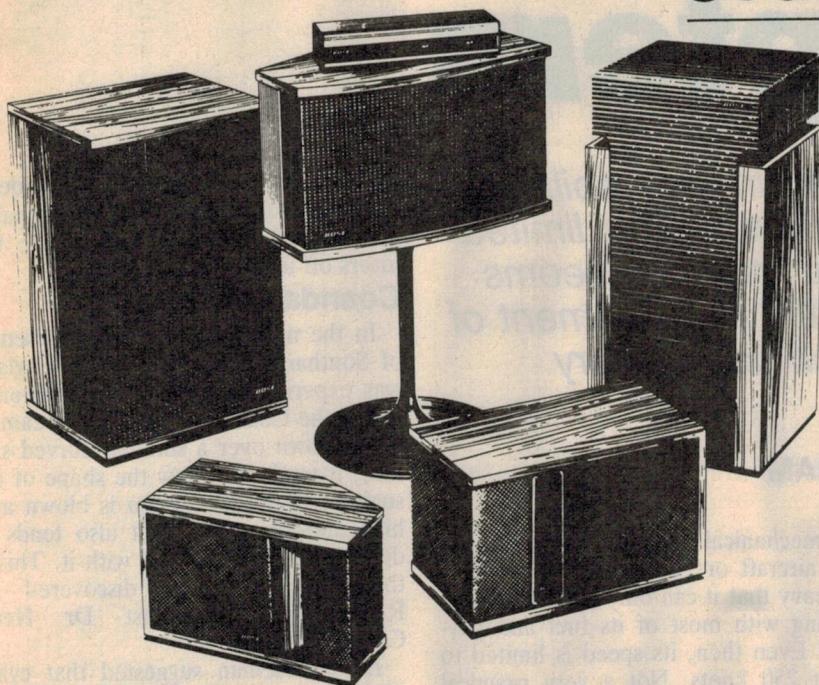Compact discs and spacious sound from Bose®



You've seen all the claims about compact discs, now it's time to put them to the test. Go into your local Bose dealer and listen to a compact disc played through a Bose Direct/Reflecting® Speaker System. Only Bose speakers produce a combination of reflected and direct sound, similar to what you hear at a live concert. They create an imaginary concert stage which recreates the spacious, lifelike performance captured by these new compact discs. So go into your local Bose dealer, and judge for yourself. Reading may be believing, but listening is proof.

BOSE®
Better sound through research.

Bose Australia Inc.


11 Muriel Ave., Rydalmere N.S.W. 2116 Tel: (02) 684 1022

AN ELECTRONICS AUSTRALIA PUBLICATION

NZ \$5.95 AUSTRALIA* \$4.95

OP AMPS Explained

by BRYAN MAHER

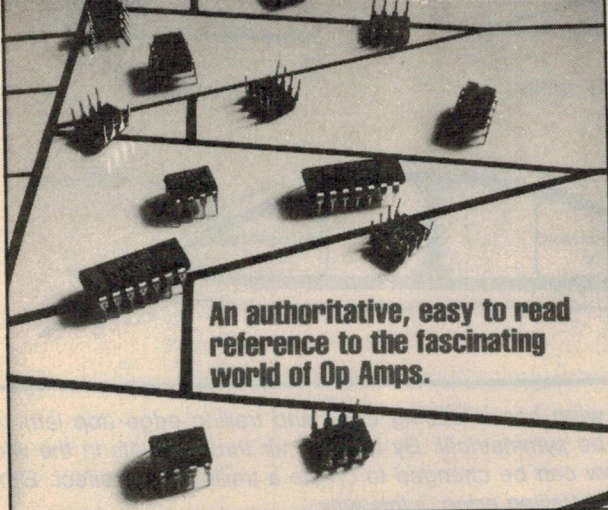

An authoritative, easy to read reference to the fascinating world of Op Amps.

Look inside almost any piece of modern electronic equipment (even things that are normally "digital") and you're likely to find op amps amplifying, filtering, shaping, clipping, detecting level changes or otherwise processing signals.

Without op amps, we'd still be in the electronic dark ages. And without sound basic understanding of the way they work and the way they're used, you probably won't get very far in today's world of electronics.

This book can be your guide and reference. It is authoritative, but at the same time very accessible and easy to read. The author has really boiled down the concepts of op-amp operation to make them understandable.

Recommended to all interested in linear electronics, operational amplifiers and their applications whether at hobby level or as a serious University or College student.

Send your order to:

Freepost No.4

**Federal Publishing Book Sales,
PO Box 227,**

Waterloo NSW 2017

(no stamp required if posted within Australia)

Price: \$4.50 plus \$1.00 p&p

X-wing helicopters

Helicopters are unsurpassed in their ability to hover, but their forward flight speed is limited to about 200km/h. Now that limitation seems likely to be overcome with the development of the X-wing helicopter, which uses a very unconventional rotor.

by IAN GRAHAM

Ever since Igor Sikorsky flew the prototype of his first helicopter in 1940, plane-makers have striven to build the helicopter's vertical take-off and hover performance into a fixed wing aeroplane.

One solution is to deflect a jet engine's exhaust downwards (called vectored thrust). Using this, an aircraft like the Harrier can be made to hover, but at a very high price in terms of fuel consumption. Helicopter designers approached the problem from the opposite direction. They attempted to increase the helicopter's comparatively low cruising speed by adding wings and extra engines.

Both approaches have met with limited success. Fixed wing VTOL (Vertical Take-Off and Landing) aircraft produce about a pound of lift per horsepower, while consuming about 40% of the aircraft's weight in fuel per hour. By contrast, a helicopter generates up to 12 pounds of lift per horsepower (about 7kg per kilowatt), while consuming only 2% of its weight in fuel per hour.

Although the helicopter is much more efficient at hovering, it can't approach the cruising speeds of fixed wing aircraft. A helicopter's forward speed is limited to about 200 knots, or perhaps as much as 350 knots with added wings and extra engines. To compete with fixed wing aircraft, helicopters have to increase their cruising speed to around 500 knots.

Why not simply build a rotor system onto a conventional fixed wing plane? It's been done, but the extra hydraulics

and mechanical hardware make this hybrid aircraft or "compound helicopter" so heavy that it can only operate by dispensing with most of its fuel and payload! Even then, its speed is limited to about 250 knots. Not a very practical solution.

A revolutionary new breed of aircraft is taking shape now in wind tunnels and on computer screens. The new breed will be capable of combining the fuel-efficient hovering performance of a helicopter with the high cruising speeds of a fixed wing plane, without having to leave its fuel and payload behind. Advances in computers, new materials and

air flow control science have made it possible to design rotor blades capable of doing things that would tear the rotors off any normal helicopter.

Coanda effect

In the mid-1960s, Dr Ian Cheeseman of Southampton University in England was experimenting with a phenomenon called the Coanda Effect. If a stream of air is blown over a smooth, curved surface, it tends to follow the shape of the surface. If the air stream is blown at a high enough pressure, it also tends to drag the surrounding air with it. This is the Coanda Effect, discovered by Romanian-born scientist Dr Henri Coanda in 1910.

Dr Cheeseman suggested that cylindrical rotors fitted to fixed wing aircraft could use the Coanda effect to generate lift for take-off and landing. The rotors would then be stopped during forward flight. The rotors now under development have evolved from cylinders into broad, wing-like structures.

Indeed, the broad, flat appearance of the vehicle's four rotors gives this propulsion system its popular name, X-wing.


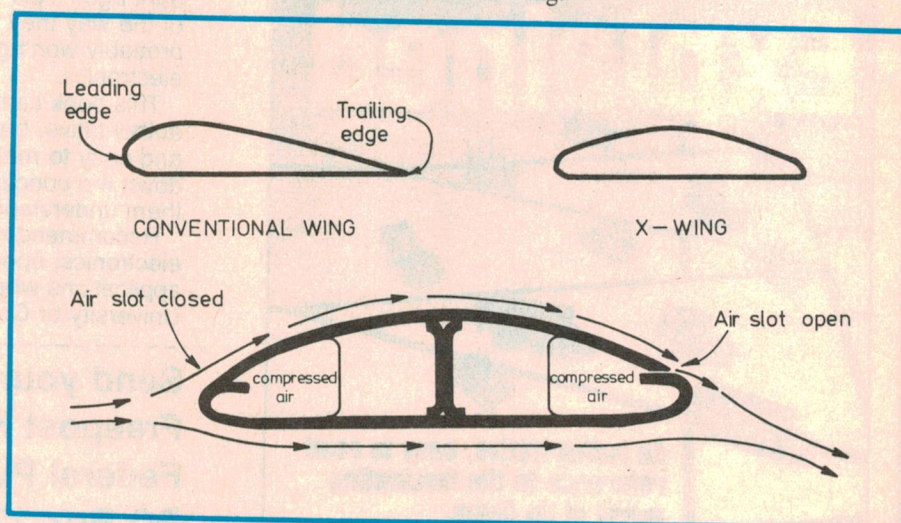


Fig.1: A normal aircraft wing has a leading edge and trailing edge (top left). An X-wing (top right) must be symmetrical. By blowing air through slots in the wing edge (above), the air flow can be changed to create a trailing edge effect. Either edge can be turned into a trailing edge in this way.

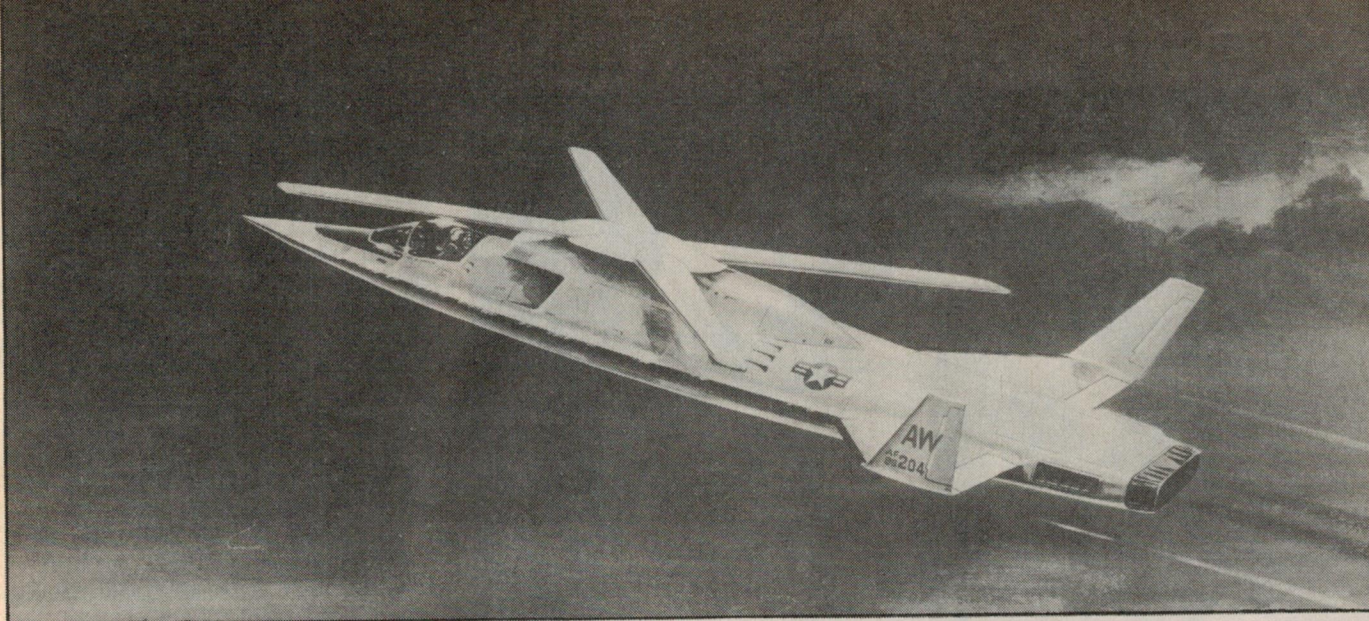

An artist's impression of a future X-wing jet aircraft, shown here in forward flight with stationary rotor/wings.

An X-wing aircraft takes off vertically like a conventional helicopter, by spinning its rotors. But in forward flight the rotors stop spinning and behave like two pairs of wings — one pair swept forward and the other swept back. It takes between 15 and 30 seconds to brake the rotors from take-off speed to a dead stop. Loss of lift during this time makes the aircraft very unstable and it might roll over in the air, but for something that goes by the horrendous name of "circulation control aerodynamics" allied to a powerful on-board computer system.

Two-way wings

Conventional aircraft always fly in the same direction (i.e., forward), and so their wings are shaped asymmetrically with a leading edge and a trailing edge. At take-off and landing some aircraft can produce more lift by extending flaps from the trailing edges of the wings.

X-wing aircraft can't do this, because as the rotors slow down, the trailing edge of a rotor blade on one half of a revolution becomes the leading edge on the other half. And when the rotors stop, a blade edge could be either a leading edge or a trailing edge, depending on where it stops. X-wing rotors must therefore be able to generate lift even when the airflow across them reverses.

Conventional, hydraulically operated flaps on both blade edges simply couldn't be extended and withdrawn quickly enough as each blade edge switched from leading edge to trailing edge. Even if they could, the resulting vibration would probably tear the aircraft apart.

This is where the Coanda effect

comes into play. By forcing air out of slots in the edges of an X-wing rotor blade, the air-flow around the rotor can be made to behave exactly as if the symmetrical blade was actually a normal wing with leading and trailing edges. If the edge of the blade has air blown through it, it becomes a trailing edge and when the air supply is switched off, it becomes a leading edge again.

A bewilderingly complicated system of 48 valves in the central hub switches a high-pressure air supply from one edge of each blade to the other edge. This is done rapidly enough to achieve the desired effect and solve the problems of instability and loss of lift as the four rotor/wings slow down and stop.

A normal helicopter controls its pitch and roll by tilting its rotor blades or the whole rotor hub. Fixed wing aircraft control pitch and roll by means of moveable control surfaces on the wings. X-wing aircraft can't do either of these,


because each X-wing must be rigidly connected to the central hub due to the complicated nature of the high pressure air supply to the rotors.

Helicopter rotor blades, which are so flexible that they droop down when stationary on the ground, become stiffer when they spin — in the same way as a floppy string with a weight on the end becomes rigid when the weight is whirled round. But when an X-wing aircraft stops its rotors in the air to convert to forward flight, these strengthening "spinning forces" disappear.


In addition, unlike the wings of a normal fixed wing aircraft, two of the X-wing aircraft's rotor/wings are swept forward. To resist the forces that tend to bend the wing tips up or down, X-wings have to be made even stiffer than normal aeroplane wings.

Rock and roll

X-wing aircraft can control pitch and

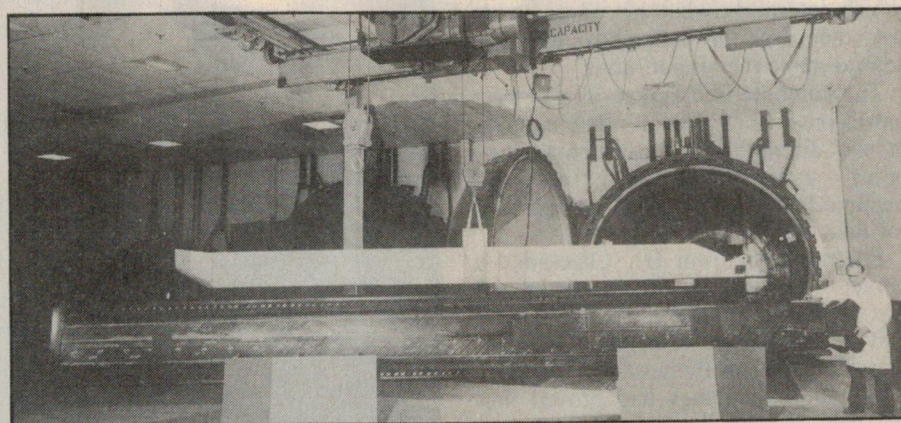

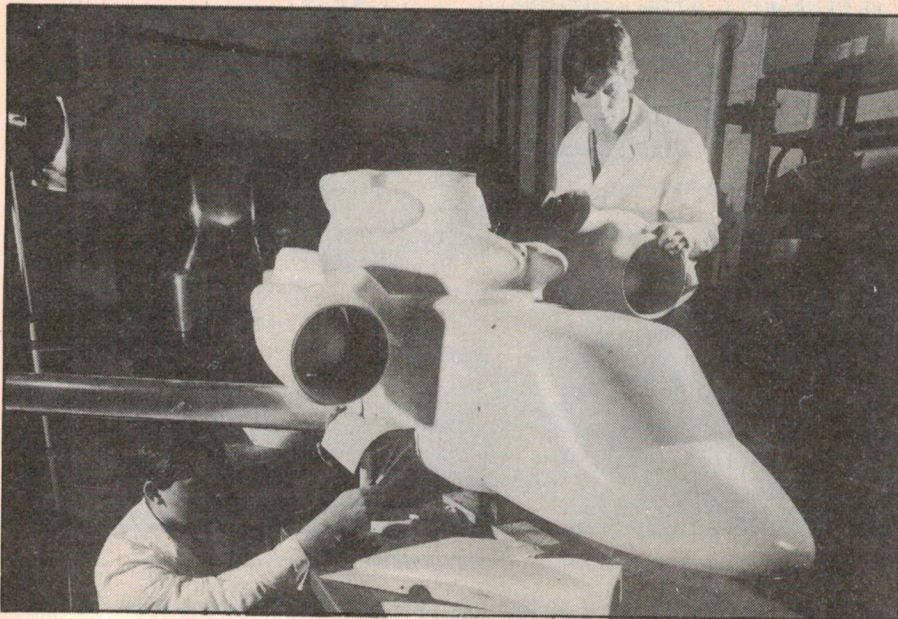This comparison of a conventional helicopter rotor blade (top) and an X-wing rotor/wing (bottom) gives some idea of its size and substantial construction. Without its final aerodynamic skin in place, the air slots are clearly visible along each edge of the rotor/wing.



A one-sixth scale model of the Rotor Systems Research Aircraft that will test-fly X-wing, being prepared for wind-tunnel tests.

roll by regulating the air blowing through the wing edges. Although X-wings are extremely stiff and resistant to bending up and down, they have some flexibility when it comes to twisting. Blowing air through one wing edge and not the other makes the wing twist and changes the amount of lift it generates. By creating more lift in one part of the X-wing's rotation than in other places, pitch and roll can be controlled very accurately indeed. Shaping the air-flow like this is called Circulation Control Aerodynamics or "Pneumodynamics".

It is such a complicated control technique that a pilot could not possibly handle it manually. As a result, an X-wing aircraft must be flown "by-wire". The pilot's movements of the control column are fed into a computer, which interprets what he wants to do and then uses the pneumodynamic system to make the aircraft do it.

The computerised system also detects unwelcome vibrations or other motions in the aircraft — almost before they occur — and automatically uses the pneumodynamic system to compensate for them.

Following on from Dr. Cheeseman's pioneering work, the X-wing technique was further developed at the US Navy's David Taylor Ship Research and Development Centre in Bethesda, Maryland.

In 1983, when they had proved that the vehicle could be built, NASA and the Defence Advanced Research Projects Agency contracted with Sikorsky to design, build and test-fly a full scale X-wing aircraft.

Flight testing

Sikorsky has built an X-wing rotor-head onto one of the Rotor Systems Research Aircraft (RSRA) that they supplied to the US government ten years ago. Its extra wings and engines allow the X-wing stop-start procedures


and performance to be tested safely. If lift from the X-wings is lost at any time, the aircraft can switch to conventional fixed wing flight.

The RSRA has a unique crew escape system, the only operational crew escape system in use in a helicopter. The problems of ejecting upwards from a helicopter with sword-like blades spinning directly above the crew must be obvious. In an emergency, the RSRA crew can fire explosive charges to blow the blades off and away from the aircraft, blow the cockpit roof apart and then eject the crew safely.

The modified RSRA will be flight tested throughout 1987 at NASA's Dryden Flight Research Facility at Edwards, California.

When X-wing aircraft eventually come into service, they will most likely be used for missions which neither helicopters nor fixed wing planes are presently capable of accomplishing efficiently — missions where it is vital to get to a location swiftly and then stay there for long periods. Air/sea rescue, anti-submarine sonar dipping and electronic intelligence all require this versatility and should benefit from X-wing technology at the beginning of the next century.


EA

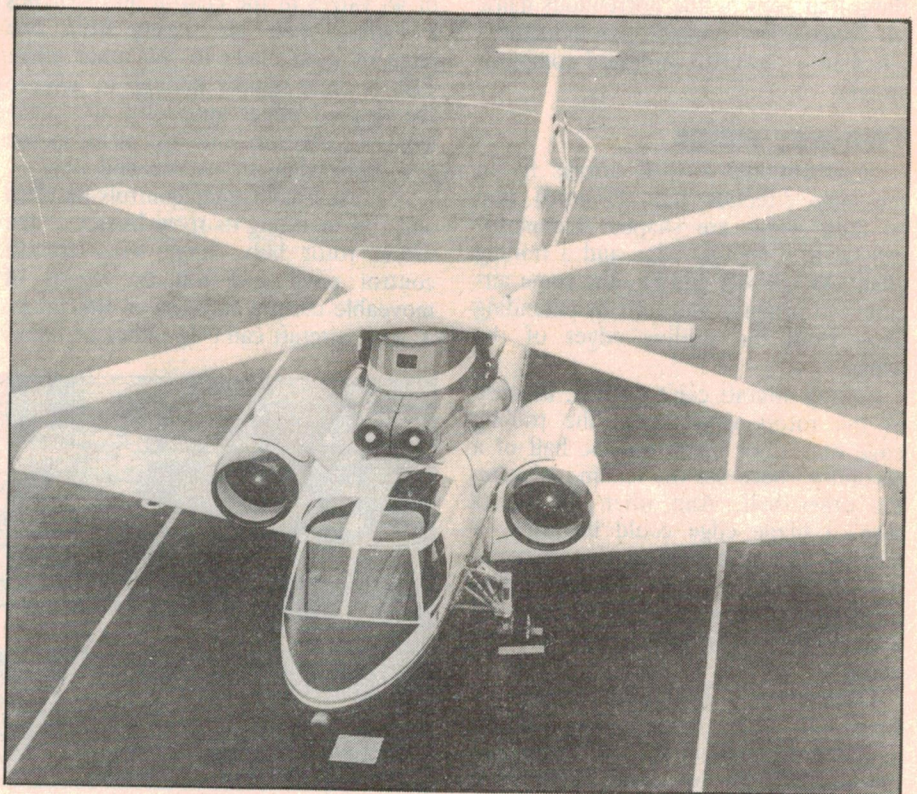

The full-size X-wing Rotor Systems Research Aircraft. Once the RSRA proves X-wing to be technically feasible and safe, the next aircraft, a technology demonstrator, will dispense with unnecessary wings and engines and rely totally on the X-wing for lift in the hover and forward flight modes.

Two of our best Performers

**NOW
TURBOCHARGED
TO 5MHz**

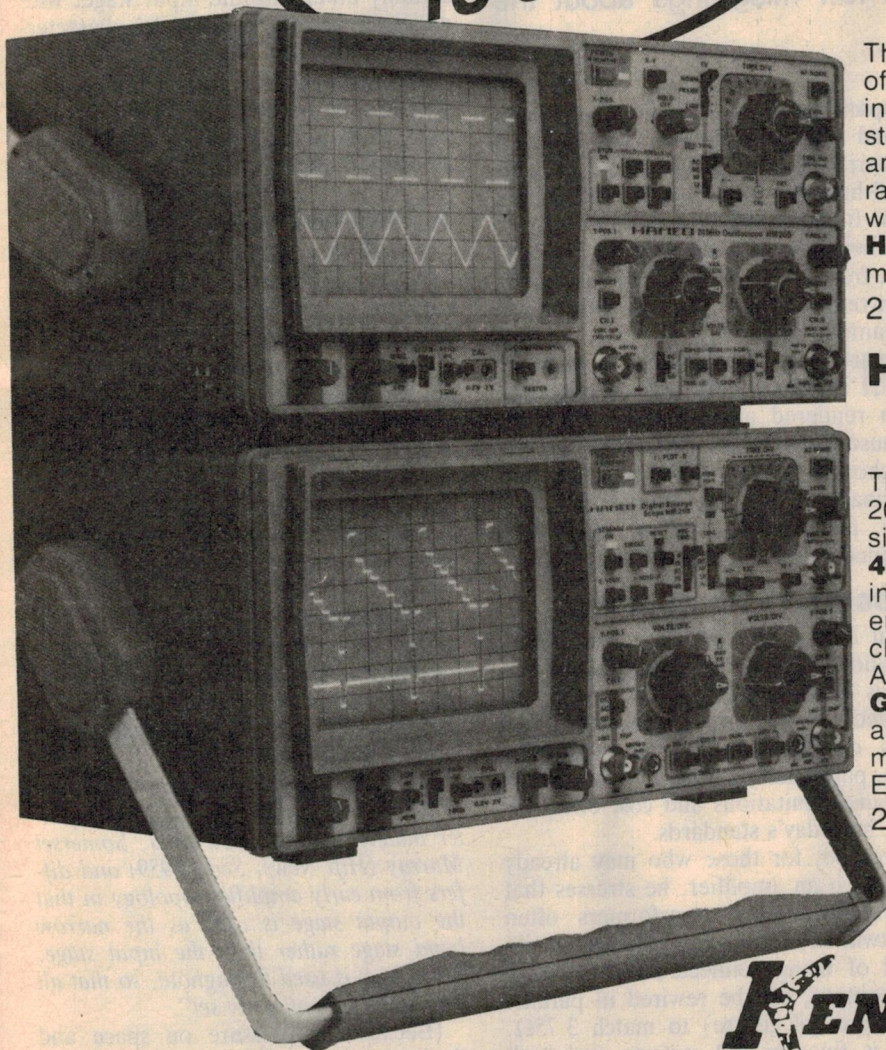

HM205

an outstanding Oscilloscope with
digital storage

This new oscilloscope offers all the features of a state-of-the-art **20MHz** realtime instrument. In addition it provides digital storage capability for signals between **50s** and **0.3ms** duration, with a max. sampling rate of **5MHz**. Especially when working with comparatively slow phenomena, the **HM205** can easily replace considerably more expensive digital storage scopes.

2 Probes \times 1/ \times 10 incl.

HM208

the high tech Storage Scope with
20MHz sampling rate


The **HM208**'s high sampling rate of max. 20MHz facilitates storing of relatively fast single shot events. Max. memory is **4096 \times 8** bit, conveniently divided into two independent blocks. **XY-storage** capability enables easy viewing and recording of characteristic curves and Lissajous figures. An XY-recorder output and the optional **GPB-Interface** allow full integration in automatic measurement systems. With more than **5000** units sold, this is one of Europe's best selling digital storage scopes.

2 Probes \times 1/ \times 10 incl.

KENELEC PTY. LTD.
(INCORPORATED IN VICTORIA)

VIC. (03) 560 1011, FAX (03) 560 1804 NSW (02) 439 5500
QLD (07) 393 0909 SA (08) 223 2055 WA (09) 322 4542

WorkSouth 293

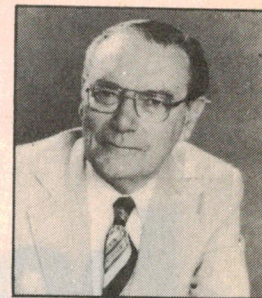

Gilding the lily: is it worthwhile?

A reference in the December issue to the possible up-dating of old valve amplifiers seems to have prompted correspondence not just on the original subject, but on "improving" hifi equipment generally, including near-new compact disc players. While I don't wish to be totally negative, I do have more than a few misgivings about the idea.

The urge to "improve" the performance of consumer audio/radio equipment is at least as old as my own awakening interest in what was then called "wireless".

Back in the 1920s, the popular choice, for those who could afford it, was a "neutrodyne" type receiver, featuring provision to neutralise the grid-plate capacitance of the triode RF amplifier stages, in the interests of stability.

The setting-up procedure involved disabling each RF amplifier valve in turn, by disconnecting one side of the filament and then, with the receiver tuned to a strong local station, carefully adjusting the associated neutralising condenser (capacitor) for minimum signal feedthrough.

Heaven alone knows how many such receivers were subsequently de-stabilised by owners who couldn't resist the temptation to screw the neutralising condensers this way and that in a quest for improved performance.

Which reminds me of a brand new superhet receiver, returned for service to the factory where I worked in the early '30's. On taking delivery, the purchaser had apparently checked it over to see that everything was firm and shipshape. And, sure enough, he found it necessary to tighten quite a few "loose screws" (trimmer, &c) visible on the tuning gang and IF transformers!

Then there was the manager of a

company handling a leading line of imported hifi loudspeakers. He was still muttering into his glass when I encountered him at a trade function during the '70's. It seems that a customer had just returned one of their systems for service, from which the original wiring had been removed and replaced with bits of gargantuan cable.

Apart from the fact that it involved an 8 Ω circuit anyway, the exercise had been rendered all the more ridiculous because the oversize cable could not be attached directly to the various lugs and terminals — so the connections had been made with bits of thin wire wrapped around its bared ends!

Those 17W Playmasters

But enough of that. A reader, B.A. (Ivanhoe, Vic), writes to say that, based on his own experience with yesterday's "valved" amplifiers, he heartily supports our remarks in the December issue, particularly in regard to their performance limitations and cost effectiveness, by today's standards.

Even so, for those who may already have such an amplifier, he stresses that yesterday's output transformers often had twin secondary windings which, instead of being connected in series for 15 Ω output, can be rewired in parallel (in phase, of course) to match 3.75 Ω . This is fine for 4 Ω systems and both safe and usable with 8 Ω loads.

If such a change is made, however,

the feedback series resistor must be reduced by about 2:1 to maintain the feedback factor and gain at the original level. But, he says, when using a modern preamplifier, it is often possible to further reduce the power amp gain by suitably modifying the input stage, with a view to improving the noise characteristic, stability and bandwidth.

The once popular EL37 output valves are now in very short supply but he finds that the EL34/6CA7 is an available and practical substitute.

A Playmaster/LEAK?

It's all very matter-of-fact but, at that point in his letter, B.A. the pragmatist becomes B.A. the enthusiast, with cost effectiveness thrust aside. I quote:

"Since most component parts in an old Playmaster are bound to be suspect, a complete rebuild/redesign project in the context of the December 1986 article may be worthwhile for valve enthusiasts, collectors or just plain hobbyists".

He goes on to say that, some years ago, he had to update a couple of LEAK TL12 class-A mono amplifiers — a project that involved changing the power stage over to class-AB ultralinear, for increased power, and replacing the original 12W output transformers with larger Australian A&R/Playmaster types. I quote again:

"Overall, the final circuit addresses problems of bandwidth and phase splitter balance as described by J. Somerset Murray (Hifi News, Sept. 1959) and differs from early amplifier topology in that the output stage is used as the narrow band stage rather than the input stage. Fixed bias is used throughout, so that all stages can be optimally set".

(Because of pressure on space and draftsman's time, it was not practical to include the actual circuit, so that discussion can only be of a general nature).

In respect to the 6CA7/EL34 output valves, there is no special cause for argument. While cathode bias is simple and automatic, valve application data clearly indicates that, in the quest for maximum power output from a push-pull class AB stage, separate fixed bias has the edge — assuming that the power supply can provide the requisite HT voltage and peak current.

Moreover, with cheap and reliable solid state rectifiers at hand, it is no great hassle, these days, to derive a supplementary negative potential from an existing power transformer.

But he doesn't stop there. To counter Miller effect capacitance losses, along with possible grid blocking effects — "a bane in fixed-bias output stages", he says — B.A. adds a pair of cathode followers (a 12AX7/ECC83) ahead of the output valves, DC coupled to the grids. Presets in the 12AX7 grid returns determine the voltage and current levels in the now composite stage.

RC coupling is used between the cathode followers and the 12AX7 long-tailed phase inverter that precedes them but the phase inverter itself is DC coupled to the input voltage amplifier, a parallel connected 12AT7/ECC81, again with external adjustable bias.

I wondered about his choice of a 12AT7 for the input stage. In the days when I used to be involved with valves, we avoided recommending the 12AT7 for low-level audio amplification like the plague. Being intended initially for RF service, it lacked the special antimicrophonic construction used for its 12AU/AX/AY7 contemporaries.

That aside, B.A. says that the addition of the cathode followers, along with the use of DC coupling and externally applied bias, was aimed at extending the front-end bandpass to 200-odd kHz and minimising low-end phase rotation. The approach reflects modern solid-state design thinking but one can argue that it offers less advantage in a valve type amplifier, where a multi-wound output transformer remains as the dominant and limiting component in the signal/feedback path.

(Perhaps I should add that B.A. claims also to have taken considerable care in selecting the small components used throughout, and in the provision of a 30-second time delay for the HT circuitry, to minimise stress on the EL34 cathodes during the warm-up period).

Was it worthwhile

Clearly, an exercise of this magnitude would add up to a complete strip, refurbish and rebuild, complicated by a

possible difficulty in accommodating the extra components in an existing stereo chassis. Add to this the need to set up or check voltage and current levels initially, occasionally and each time a valve is changed.

Personally, I'm not convinced about the importance of fixed bias in other than the output stage but, overall, B.A. appears to have handled the assignment with as much attention to circuit detail as one could wish for, ending up with 35W (per channel) of clean power up to 20kHz, although diminishing through 20W at 25Hz — a limit attributable to the output transformers.

But was the effort to "gild the lily" worthwhile? Decide for yourself. Here's how the result was summed up by the man who did all the work.

"For what matters to most people, a listening test against a similar power solid-state amplifier revealed very little difference in overall sound, when fed from the same preamplifier with levels set precisely to be identical. (Monitoring via very high quality 3-way loudspeakers).

"The only area where the solid-state amplifier was marginally superior was in the bass attack, control, extension and clarity. Anyone surprised?"

"In passing, I must remark that I have had some recent valve amps for auditioning which sounded hard and glassy by comparison".

I'm afraid that B.A.'s verdict doesn't provide much incentive to get on with what we proposed last December; dust off one of the old Playmasters . . . &c.

The current scene

A couple of rather lengthy letters, one from NSW, the other from Victoria, express curiously parallel opinions — this time about present-day components and CD players, inspired, I rather imagine, by parallel reading.

A.K. of Turrumurra, NSW leads off with the contention that consumer audio equipment stands to benefit considerably by the substitution of more suitable capacitors, most obviously: "styroseals in lieu of greencaps or ceramics". To support his findings, he refers to work by Walter Jung and Richard March reported some years ago in *Audio* magazine.

Yes, Jung and Marsh did devise a test set-up capable of demonstrating behavioural differences between capacitors of various kinds but it does not follow that all such differences will show up in routine audio circuits. The matter was subsequently checked out in the EA lab, the chief practical observation at

the time being the need for discretion in the use of electrolytic types and, most certainly, ceramics.

By way of contrast, A.K. then details an "improvement" that didn't work out in his case, arising from the substitution of 120-strand cable for the 79-strand type supplied with a pair of loudspeakers. Far from improving matters, he says, (gilding the lily?) the heavier cable over-damped the drivers, causing an apparent and unacceptable increase in brightness.

This rather surprising result seemed, however, to be consistent with a statement which he came across in a QED loudspeaker brochure (enclosed) to the effect that:

"QED's are designed to be properly damped with 0.25Ω resistance in the speaker wire between them and the amplifier."

Something doesn't add up, A.K., because loudspeaker damping is a function of the circulating current when the voice coil tends to behave independently of the drive, effectively acting as a generator. Assuming that the voice coil itself has a resistance of 4Ω or more, even the complete elimination of 0.25Ω cable resistance would not markedly affect the damping — predominantly a bass-end phenomenon, anyway.

It seems to me that you have misunderstood the QED brochure, because it goes on to say:

"Using heavier wire will not significantly overdamp the woofers and can, of course, increase the power delivered to the speakers by as much as 5%".

We would interpret that to mean that QED loudspeakers will be adequately damped provided the cable resistance is not greater than 0.25Ω. A 5% difference in power, by the way, is very small in decibel terms.

If your observation about "an apparent increase in brightness" is correct, the more likely explanation is a rather nasty one, namely that there is a region in the top end where the system impedance falls well below the rated figure — a not unusual occurrence. A reduction in lead resistance might then show up as increased output and added brightness.

The "nasty" part is that, under high drive conditions, the resulting peak current could wreck the output stage.

That aside, in the area of amplifier interconnecting leads, A.K. is an uncompromising supporter of the heavy duty, low capacitance shielded cable sold by Tandy, as distinct from (I quote) "the 100pF-per-foot rubbish" often supplied and currently sold by most electronic retailers.

Fair enough, A.K. If you don't mind the extra cost and bulk, reduced cable capacitance is a commendable quality. Whether it confers a practical advantage, however, depends on the length of the interconnect and the impedance of the particular circuit.

Operational amplifiers

That brings A.K. to "the replacement of operational amplifiers such as 4558s, &c, by TL072/LF353 in cassette decks and CD players (Nakamichi BX1, BX2, Dragon; also TEAC PD230 CD player, and the Marantz CD65 CD player's headphone amplifier section)". He adds:

These are only a few examples. I do not claim to have "golden ears" (I suffer from industry related loss in my left ear) but I, along with most of my workmates and acquaintances, have been able to hear most of these changes. In many cases, they have modified their own equipment accordingly (often with readily measured improvements).

The Victorian reader mentioned above, P.R. of Puckapunyal takes up much the same theme. He owns a Marantz CD-65 CD player and considers that, even though it is "designed to a price", it achieves "much better than average (audible) performance by attention to component quality and power supply design".

But that's still not good enough for P.R.:

"It can be and will be improved by the substitution of a different dual op amp in the analog stage, by further attention to component quality and to power supply design".

If P.R. is confident that he can show Marantz/Philips engineers a thing or two, so be it, but I would hesitate to encourage readers generally to dive into commercial consumer equipment with a hot soldering iron — especially readers without a service manual, without adequate test equipment and without sufficient experience or knowledge of what it's all about.

In the early days of compact disc, it was noticeable that most of the actual circuit criticism was focussed on the analog bit at the output end — the one bit, I would venture to suggest, that most critics could comprehend at the time. This was despite the fact that the signal being delivered through the analog output stage was way ahead in measured quality of any signal source they'd previously had access to.

It was almost as if, faced with an electronic lily, they felt duty bound either to ridicule it or gild it!

I do not deny that it may be possible to nominate new operational amplifiers or other small components which, on paper, have somewhat better performance parameters than those found in last year's CD player. But it does not follow that the differences will show up in existing adequately designed circuitry, especially if the said components operate inside a feedback loop.

Really, with a flat frequency response, a rated THD through the entire system of 0.01% or less, and an S/N ratio of 90dB or more, there isn't a lot of scope in a CD player for gee-whiz improvement — not from fiddling with the analog bit, anyway.

Justified or not, speculation and criticism, these days, has focussed on less accessible areas like data errors, correction, concealment, sample and hold, and filters.

As far as cassette decks are concerned, they have been around for a longer period and it is more likely that some at least could benefit from a revamp. Whether that would apply to the Nakamichi models mentioned, I am not able to say. Frankly, I doubt it.

Warranty and service

When preparing this article, I made a point of talking to the service managers for a couple of the companies concerned. Perhaps predictably they assured me that there was no pattern of complaint, or of manufacturer's modification notes, that would support the need for anything other than the direct replacement of failed components.

They emphasised, however, that any modification to new equipment would automatically invalidate the manufacturer's warranty.

After the warranty period, owners could obviously make whatever changes they like at their own risk but, if a modified unit had to be returned for service, the repair bill could well be higher, especially if the changes were not properly documented. Time that a service mechanic may have to spend working out who has done what, and with what effect, would have to be paid for!

P.R. raises other matters in his letter which we may follow up later but I do want to make one other point. The foregoing discussion is not directed, even obliquely, at those who specialise

in modifying commercial equipment on a professional basis. One assumes that they would have the experience, information and facilities necessary and be able to provide adequate back-up service.

Whether the end result justifies the cost is for their clients to say.

4-channel DADs and DATs

To change the subject, I would like to round off the article with yet another mention of 4-channel sound on compact disc and digital tape cassettes.

In a letter which also refers to a number of other matters, A.J. of City Beach, WA, comes up with further evidence that I was not suffering from a too-active imagination when I recollected early references to 4-channel discrete sound on compact disc.

He encloses a photostat of a page from an unspecified Philips publication which poses the following query and comment, without any qualification as to track speed:

Usefulness for future developments?

Decoding circuit can also be used for four-channel version (quadraphonic reproduction).

In a recent reference to the DAT (Digital Audio Tape) cassette format, I drew attention to the fact that the literature to hand from Sony and Matsushita had made no mention of provision for other than 2-channel stereo recording and replay. This prompted the remark that, if we were ever to get 4-channel sound from either CD and DAT, it would be of the encoded compatible variety.

However, further information to hand indicates that DAT planning provides for no less than six operating modes, of which three are mandatory in hardware:

- Record and playback, 16-bit linear, 48kHz sampling, normal speed.
- Playback only, 16-bit linear, 44.1kHz sampling, normal speed.
- Playback only, 16-bit linear, 44.1kHz sampling, 1.5 times normal speed, two-thirds playing time.


Three other optional modes, record and playback, all involve the 32kHz sampling rate.

- 16-bit linear, normal speed, normal playing time;
- 12-bit non-linear, half speed, double playing time;
- 12-bit non-linear, normal speed and playing time, 4-channel discrete stereo.


Well what do you know! If and when all these facilities are taken up, DAT cassettes will have to be distinguished by quite an array of mode information and cue slots for automatic sensing. ⑦

REGULATED DC POWER SUPPLIES

- Single and dual models. Duals can be series, parallel, independent or dual tracking
- Duals also have fixed 5V supplies with overload indication
- Fine and coarse voltage controls
- High and low current ranges
- Fully short circuit protected
- Auto constant voltage - constant current indication
- High line and load regulation typically 0.01%+3mV
- High quality 4mm binding posts
- Economical and robust
- Ripple and noise typically 0.5mV or 1mVrms
- Class 2.5 Analog meters

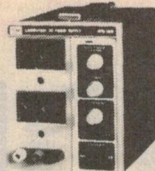

GPR3030

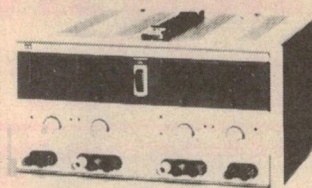

GPQ3020

GPQ3030

Model	GPR3030	GPQ3020	GPQ3030
Type	Single	Dual	Dual
Outputs	0 - 3V 0 - 3A	0 - 30V x2 0 - 2A x2 5V 1A 5V 3A	0 - 30V x2 0 - 3A x2 5V 1A 5V 3A
Price ex tax	\$210	\$530	\$561
inc tax	\$244	\$617	\$654

NOW STOCKING COLINE PROBES

Update your scope with the switch selectable x1/x10 Coline SP100 probes. As used by industry, research labs, universities etc. BNC connectors and selection of tips. Complete in deluxe heavy duty plastic pouch. **\$45.50**



COLINE SP100

passive probe incorporates a 3-position slide switch in the head and has a cable length of 1.5 metres.

SPECIFICATION: Position x1 Bandwidth: DC to 10MHz • Input R: 1M (scope input) • Input C: 40pF + scope cap. • Working Voltage: 600Vdc (inc peak ac)

Position Ref Scope input grounded. Probe tip grounded through 9M. **Position x10** Bandwidth: DC to 100MHz • Risettime: 3.5nS • Input R: 10M when used with scopes having 1M input (probe 9M + 1%) • Input C: 11.5pF when used with scopes having 30pF input capacitance • Compensation Range: 10-60pF • Working Voltage 600V dc (inc peak ac)

Supplied complete in deluxe heavy duty plastic pouch

LMC 7660 SWITCHED CAPACITOR VOLTAGE CONVERTER

This handy CMOS IC converts positive voltages into negative voltages in the range 1.5V to 10V. Circuits can be cascaded to increase output voltage. **\$2.97**

QUALITY BELLING LEE IEC-TYPE CONNECTORS



L1950A
Appliance Inlet **\$2.20**



L2157
Right angled PCB Inlet **\$2.50**



L2723
Switched and fused Inlet **\$10.76**



L2728
Fused inlet **\$4.60**



L2212A Fused inlet with voltage selector **\$28.35**



L2292 Appliance outlet **\$2.60**




L2298
Rewireable connector **\$4.00**

8.30 to 5 Monday to Friday, 8.30 to 12 Sat.
Mail Orders add \$5.00 to cover postal charges.

All prices INCLUDE sales tax.

Tax exemption certificates accepted if line value exceeds \$10.00.

BANKCARD, MASTERCARD, VISA, CHEQUES

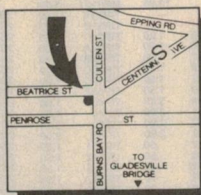

GEOFF WOOD ELECTRONICS P/L (02) 427 1676

INC IN NSW

229 BURNS BAY RD.
(CORNER BEATRICE ST.)
LANE COVE WEST N.S.W.


TWX 71996
P.O. BOX 671
LANE COVE N.S.W. 2066

OR CASH CHEERFULLY ACCEPTED

specialising in electronic components for the professional and hobbyist.

CHOOSE FLUKE® MULTIMETERS FOR FEATURES, QUALITY AND VALUE

70 Series Low Cost
Analog/Digital
Multimeters

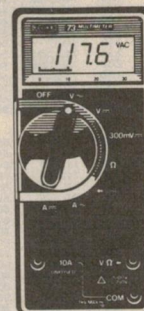

FLUKE 73

Analog/digital display
Volts, ohms, 10A diode test
Autorange
0.7% basic dc accuracy
2000+ hour battery life
3-year warranty

ex tax \$159
inc tax \$183

FLUKE 75

Analog/digital display
Volts, ohms, 10A mA diode test
Audible continuity
Autorange/range hold
0.5% basic dc accuracy
2000+ hour battery life
3-year warranty

\$219
\$252

FLUKE 77

Analog/digital display
Volts, ohms, 10A, mA, diode test
Audible continuity
"Touch Hold" function
Autorange/range hold
0.3% basic dc accuracy
2000+ hour battery life
3-year warranty
Multipurpose holster

\$279
\$321

20 Series For Toughest Applications



FLUKE 25 & 27

Charcoal or yellow case colour
Analog/Digital display
Touch Hold™ function
-15°C to 55°C operation
0.1% basic accuracy
100 µV to 1000V ac and dc
0.1 µA to 10A, all fused
Relative (difference) mode (27)
MIN/MAX recording mode (27)

Model 25 27
Price ex tax \$472 \$543
inc tax \$543 \$625

Ruggedized, waterproof case
Two-year warranty

Radio Shack Electronics

For semiconductors



MELBOURNE 48 A Beckett Street, Phone (03) 663 6151.

NORTHCOTE 425 High Street, Phone (03) 489 8866.

MAIL ORDER HOTLINE: (03) 543 7877

IC SPECIALS!

8087 CHIPS!
from \$279

8087-3 (4.77MHz) \$279
8087-2 (8MHz)... \$399
8087-1 (10MHz)... \$649
80287-6 (6MHz)... \$499
80287-7 (8MHz)... \$699
8087-3 (4.77MHz) \$279

SPO256A-AL2 SPEECH CHIP

Speech synthesiser chip, needs programming to work.

1-9 10+ 100+
\$15.00 \$14.50 \$14.00

CTS256-AL2 SPEECH CHIP

Contains the code recognition circuit to enable the project to plug directly on to the printer port, or into an IBM PC.

1-9 10+ 100+
\$27.00 \$26.50 \$26.00

41256-15

1-9 10+ 100+
\$7.95 \$7.50 \$6.95

4164

1-9 10+ 100+
\$3.95 \$3.50 \$2.95

27128

1-9 10+ 100+
\$9.95 \$8.95 \$7.95

27512

1-9 10+ 100+
\$19.50 \$18.50 \$17.50

CA3130E

1-9 10+ 100+
\$1.95 \$1.75 \$1.50

6116 LP-3

1-9 10+ 100+
\$3.95 \$3.75 \$3.50

NE5534AN

1-9 10+ 100+
\$1.95 \$1.85 \$1.75

INS8250

1-9 10+ 100+
\$29.95 \$27.95 \$26.95

AM 7910

(WORLD MODEM CHIP)
\$24.95

4000 .50	74150 1.50	74F533 4.84	74LS298 1.20	74S473 9.90	NE555 .60	2101 (5101)	BC559 .20	2N1613 1.20	2SK45 3.95
4001 .50	74151 1.20	74F534 4.84	74LS299 3.90	74S474 9.90	NE556 1.20	(8101) 7.90	BC560 .50	2N2102 1.90	2S449 7.95
4002 .350	74152 2.75	74HC SERIES	74LS300 3.95	74S475 9.90	NE557 5.00	BC639 .50	BC639 .50	2N2218 1.90	2S456 17.50
4006 1.90	74161 1.20	74HC00 .60	74LS301 3.95	74S476 9.90	NE560 4.60	8101 7.90	BC790 .190	2N2222A 1.90	2SK134
4007 .40	74163 1.40	74HC02 .60	74LS302 2.20	74S477 9.90	NE561 2.00	2532 12.50	BCY71 .190	2N2369 1.00	2SK176
4008 1.20	74164 1.20	74HC04 .60	74LS303 2.20	74S478 9.90	NE562 2.00	7235 11.50	BD140 .60	2N2484 1.00	
4010 1.90	74165 1.20	74HC08 .60	74LS304 2.20	74S479 9.90	NE563 2.00	7252 11.50	BD140 .60	2N2484 1.95	DIODES
4011 .40	74166 1.70	74HC11 .60	74LS305 2.20	74S480 9.90	NE564 2.00	41256 5.95	BD232 .90	2N2484 3.95	1N4002 .15
4012 .40	74174 1.45	74HC14 1.40	74LS306 2.20	74S481 9.90	NE565 2.00		BD232 .90	2N2484 3.95	1N4007 .20
4013 .60	74175 1.20	74HC16 1.40	74LS307 2.20	74S482 9.90	NE566 2.00		BD232 .90	2N2484 3.95	1N4048 .40
4014 1.90	74180 1.20	74HC27 .60	74LS308 2.20	74S483 9.90	NE567 2.00		BD232 .90	2N2484 3.95	1N4048 .40
4015 1.90	74190 1.00	74HC32 .60	74LS309 2.20	74S484 9.90	NE568 2.00		BD232 .90	2N2484 3.95	1N4048 .40
4016 1.00	74191 1.45	74HC36 1.10	74LS310 2.20	74S485 9.90	NE569 2.00		BD232 .90	2N2484 3.95	1N4048 .40
4017 1.50	74192 1.45	74HC37 1.10	74LS311 2.20	74S486 9.90	NE570 2.00		BD232 .90	2N2484 3.95	1N4048 .40
4018 1.90	74193 1.80	74HC38 1.40	74LS312 2.20	74S487 9.90	NE571 2.00		BD232 .90	2N2484 3.95	1N4048 .40
4019 1.90	74194 1.20	74HC39 1.40	74LS313 2.20	74S488 9.90	NE572 2.00		BD232 .90	2N2484 3.95	1N4048 .40
4020 1.50	74195 1.10	74HC40 1.40	74LS314 2.20	74S489 9.90	NE573 2.00		BD232 .90	2N2484 3.95	1N4048 .40
4021 1.50	74196 1.10	74HC41 1.40	74LS315 2.20	74S490 9.90	NE574 2.00		BD232 .90	2N2484 3.95	1N4048 .40
4022 1.50	74197 1.10	74HC42 1.40	74LS316 2.20	74S491 9.90	NE575 2.00		BD232 .90	2N2484 3.95	1N4048 .40
4023 1.50	74198 1.10	74HC43 1.40	74LS317 2.20	74S492 9.90	NE576 2.00		BD232 .90	2N2484 3.95	1N4048 .40
4024 1.50	74199 1.10	74HC44 1.40	74LS318 2.20	74S493 9.90	NE577 2.00		BD232 .90	2N2484 3.95	1N4048 .40
4025 1.50	74200 1.10	74HC45 1.40	74LS319 2.20	74S494 9.90	NE578 2.00		BD232 .90	2N2484 3.95	1N4048 .40
4026 1.50	74201 1.10	74HC46 1.40	74LS320 2.20	74S495 9.90	NE579 2.00		BD232 .90	2N2484 3.95	1N4048 .40
4027 1.50	74202 1.10	74HC47 1.40	74LS321 2.20	74S496 9.90	NE580 2.00		BD232 .90	2N2484 3.95	1N4048 .40
4028 1.50	74203 1.10	74HC48 1.40	74LS322 2.20	74S497 9.90	NE581 2.00		BD232 .90	2N2484 3.95	1N4048 .40
4029 1.50	74204 1.10	74HC49 1.40	74LS323 2.20	74S498 9.90	NE582 2.00		BD232 .90	2N2484 3.95	1N4048 .40
4030 1.50	74205 1.10	74HC50 1.40	74LS324 2.20	74S499 9.90	NE583 2.00		BD232 .90	2N2484 3.95	1N4048 .40
4031 2.95	74206 1.10	74HC51 1.40	74LS325 2.20	74S500 9.90	NE584 2.00		BD232 .90	2N2484 3.95	1N4048 .40
4032 2.95	74207 1.10	74HC52 1.40	74LS326 2.20	74S501 9.90	NE585 2.00		BD232 .90	2N2484 3.95	1N4048 .40
4033 2.95	74208 1.10	74HC53 1.40	74LS327 2.20	74S502 9.90	NE586 2.00		BD232 .90	2N2484 3.95	1N4048 .40
4034 2.95	74209 1.10	74HC54 1.40	74LS328 2.20	74S503 9.90	NE587 2.00		BD232 .90	2N2484 3.95	1N4048 .40
4035 1.95	74210 1.10	74HC55 1.40	74LS329 2.20	74S504 9.90	NE588 2.00		BD232 .90	2N2484 3.95	1N4048 .40
4036 1.95	74211 1.10	74HC56 1.40	74LS330 2.20	74S505 9.90	NE589 2.00		BD232 .90	2N2484 3.95	1N4048 .40
4037 1.95	74212 1.10	74HC57 1.40	74LS331 2.20	74S506 9.90	NE590 2.00		BD232 .90	2N2484 3.95	1N4048 .40
4038 1.95	74213 1.10	74HC58 1.40	74LS332 2.20	74S507 9.90	NE591 2.00		BD232 .90	2N2484 3.95	1N4048 .40
4039 1.95	74214 1.10	74HC59 1.40	74LS333 2.20	74S508 9.90	NE592 2.00		BD232 .90	2N2484 3.95	1N4048 .40
4040 1.95	74215 1.10	74HC60 1.40	74LS334 2.20	74S509 9.90	NE593 2.00		BD232 .90	2N2484 3.95	1N4048 .40
4041 1.95	74216 1.10	74HC61 1.40	74LS335 2.20	74S510 9.90	NE594 2.00		BD232 .90	2N2484 3.95	1N4048 .40
4042 1.95	74217 1.10	74HC62 1.40	74LS336 2.20	74S511 9.90	NE595 2.00		BD232 .90	2N2484 3.95	1N4048 .40
4043 1.95	74218 1.10	74HC63 1.40	74LS337 2.20	74S512 9.90	NE596 2.00		BD232 .90	2N2484 3.95	1N4048 .40
4044 1.95	74219 1.10	74HC64 1.40	74LS338 2.20	74S513 9.90	NE597 2.00		BD232 .90	2N2484 3.95	1N4048 .40
4045 1.95	74220 1.10	74HC65 1.40	74LS339 2.20	74S514 9.90	NE598 2.00		BD232 .90	2N2484 3.95	1N4048 .40
4046 1.95	74221 1.10	74HC66 1.40	74LS340 2.20	74S515 9.90	NE599 2.00		BD232 .90	2N2484 3.95	1N4048 .40
4047 1.95	74222 1.10	74HC67 1.40	74LS341 2.20	74S516 9.90	NE600 2.00		BD232 .90	2N2484 3.95	1N4048 .40
4048 1.95	74223 1.10	74HC68 1.40	74LS342 2.20	74S517 9.90	NE601 2.00		BD232 .90	2N2484 3.95	1N4048 .40
4049 1.95	74224 1.10	74HC69 1.40	74LS343 2.20	74S518 9.90	NE602 2.00		BD232 .90	2N2484 3.95	1N4048 .40
4050 1.95	74225 1.10	74HC70 1.40	74LS344 2.20	74S519 9.90	NE603 2.00		BD232 .90	2N2484 3.95	1N4048 .40
4051 1.95	74226 1.10	74HC71 1.40	74LS345 2.20	74S520 9.90	NE604 2.00		BD232 .90	2N2484 3.95	1N4048 .40
4052 1.95	74227 1.10	74HC72 1.40	74LS346 2.20	74S521 9.90	NE605 2.00		BD232 .90	2N2484 3.95	1N4048 .40
4053 1.95	74228 1.10	74HC73 1.40	74LS347 2.20	74S522 9.90	NE606 2.00		BD232 .90	2N2484 3.95	1N4048 .40
4054 1.95	74229 1.10	74HC74 1.40	74LS348 2.20	74S523 9.90	NE607 2.00		BD232 .90	2N2484 3.95	1N4048 .40
4055 1.95	74230 1.10	74HC75 1.40	74LS349 2.20	74S524 9.90	NE608 2.00		BD232 .90	2N2484 3.95	1N4048 .40
4056 1.95	74231 1.10	74HC76 1.40	74LS350 2.20	74S525 9.90	NE609 2.00		BD232 .90	2N2484 3.95	1N4048 .40
4057 1.95	74232 1.10	74HC77 1.40	74LS351 2.20	74S526 9.90	NE610 2.00		BD232 .90	2N2484 3.95	1N4048 .40
4058 1.95	74233 1.10	74HC78 1.40	74LS352 2.20	74S527 9.90	NE611 2.00		BD232 .90	2N2484 3.95	1N4048 .40
4059 1.95	74234 1.10	74HC79 1.40	74LS353 2.20	74S528 9.90	NE612 2.00		BD232 .90	2N2484 3.95	1N4048 .40
4060 1.95	74235 1.10	74HC80 1.40	74LS354 2.20	74S529 9.90	NE613 2.00		BD232 .90	2N2484 3.95	1N4048 .40
4061 1.95	74236 1.10	74HC81 1.40	74LS355 2.20	74S530 9.90	NE614 2.00		BD232 .90	2N2484 3.95	1N4048 .40
4062 1.95	74237 1.10	74HC82 1.40	74LS356 2.20	74S531 9.90	NE615 2.00		BD232 .90	2N2484 3.95	1N4048 .40
4063 1.95	74238 1.10	74HC83 1.40	74LS357 2.20	74S532 9.90	NE616 2.00		BD232 .90	2N2484 3.95	1N4048 .40
4064 1.95	74239 1.10	74HC84 1.40	74LS358 2.20	74S533 9.90	NE617 2.00		BD232 .90	2N2484 3.95	1N4048 .40
4065 1.95	74240 1.10	74HC85 1.40	74LS359 2.20	74S534 9.90	NE618 2.00		BD232 .90	2N2484 3.95	1N4048 .40
4066 1.95	74241 1.10	74HC86 1.40	74LS360 2.20	74S535 9.90	NE619 2.00		BD232 .90	2N2484 3.95	1N4048 .40
4067 1.95	74242 1.10	74HC87 1.40	74LS361 2.20	74S536 9.90	NE620 2.00		BD232 .90	2N2484 3.95	1N4048 .40
4068 1.95	74243 1.10	74HC88 1.40	74LS362 2.20	74S537 9.90	NE621 2.00		BD232 .90	2N2484 3.95	1N4048 .40
4069 1.95	74244 1.10	74HC89 1.40	74LS363 2.20	74S538 9.90	NE622 2.00		BD232 .90	2N2484 3.95	1N4048 .40
4070 1.95	74245 1.10	74HC90 1.40	74LS364 2.20	74S539 9.90	NE623 2.00		BD232 .90	2N2484 3.95	1N4048 .40
4071 1.95	74246 1.10	74HC91 1.40	74LS365 2.20	74S540 9.90	NE624 2.00		BD232 .90	2N2484 3.95	1N4048 .40
4072 1.95	74247 1.10	74HC92 1.40	74LS366 2.20	74S541 9.90	NE625 2.00		BD232 .90	2N2484 3.95	1N4048 .40
4073 1.95	74248 1.10	74HC93 1.40	74LS367 2.20	74S542 9.90	NE626 2.00		BD232 .90	2N2484 3.95	1N4048 .40
4074 1.95	74249 1.10	74HC94 1.40	74LS368 2.20	74S543 9.90	NE627 2.00		BD232 .90	2N2484 3.95	1N4048 .40
4075 1.95	74250 1.10	74HC95 1.40	74LS369 2.20	74S544 9.90	NE628 2.00		BD232 .90	2N2484 3.95	1N4048 .40
4076 1.95	74251 1.10	74HC96 1.40	74LS370 2.20	74S545 9.90	NE629 2.00		BD232 .90	2N2484 3.95	1N4048 .40
4077 1.95	74252 1.10	74HC97 1.40	74LS371 2.20	74S546 9.90	NE630 2.00		BD232 .90	2N2484 3.95	1N4048 .40
4078 1.95	74253 1.10	74HC98 1.40	74LS372 2.20	74S547 9.90	NE631 2.00		BD232 .90	2N2484 3.95	1N4048 .40
4079 1.95	74254 1.10	74HC99 1.40	74LS373 2.20	74S548 9.90	NE632 2.00		BD232 .90	2N2484 3.95	1N4048 .40
4080 1.95	74255 1.10	74HC00 1.40	74LS374 2.20	74S549 9.90	NE633 2.00		BD232 .90	2N2484 3.95	1N4048 .40
4081 1.95	74256 1.10	74HC01 1.40	74LS375 2.20	74S550 9.90	NE634 2.00		BD232 .90	2N2484 3.95	1N4048 .40
4082 1.95	74257 1.10	74HC02 1.40	74LS376 2.20	74S551 9.90	NE635 2.00		BD232 .90	2N2484 3.95	1N4048 .40
4083 1.95	74258 1.10	74HC03 1.40	74LS377 2.20	74S552 9.90	NE636 2.00		BD232 .90	2N2484 3.95	1N4048 .40
4084 1.95	74259 1.10	74HC04 1.40	74LS378 2.20	74S553 9.90	NE637 2.00		BD232 .90	2N2484 3.95	1N4048 .40
4085 1.95	74260 1.10	74HC05 1.40	74LS379 2.20	74S554 9.90	NE638 2.00		BD232 .90	2N2484 3.95	1N4048 .40
4086 1.95	74261 1.10	74HC06 1.40	74LS380 2.20	74S555 9.90	NE639 2.00		BD232 .90	2N2484 3.95	1N4048 .40
4087 1.95	74262 1.10	74HC07 1.40	74LS381 2.20	74S556 9.90	NE640 2.00		BD232 .90	2N2484 3.95	1N4048 .40
4088 1.95	74263 1.10	74HC08 1.40	74LS382 2.20	74S557 9.90	NE641 2.00		BD232 .90	2N2484 3.95	1N4048 .40
4089 1.95	74264 1.10	74HC09 1.40	74LS383 2.20	74S558 9.90	NE642 2.00		BD232 .90	2N2484 3.95	1N4048 .40
4090 1.95	74265 1.10	74HC10 1.40	74LS384 2.20	74S559 9.90	NE643 2.00		BD232 .90	2N2484 3.95	1N4048 .40
4091 1.95	74266 1.10	74HC11 1.40	74LS385 2.20	74S560 9.90	NE644 2.00		BD232 .90	2N2484 3.95	1N4048 .40

ROD IRVING ELECTRONICS

Nº1 FOR COMPONENT SPECIALS!




TAG TANTALUM CAPACITORS SPECIALS!

Cat. No.	Description	Price
R16124	16V 4.7uF	\$0.48
R16125	16V 10uF	\$0.52
R16126	16V 15uF	\$0.75
R16128	16V 22uF	\$0.85
R16216	25V 2.2uF	\$0.40
R16220	25V 4.7uF	\$0.70
R16222	25V 6.8uF	\$0.70
R16224	25V 10uF	\$0.60
R16228	25V 22uF	\$2.40
R16300	35V 0.1uF	\$0.30
R16302	35V 0.15uF	\$0.30
R16304	35V 0.22uF	\$0.30
R16306	35V 0.33uF	\$0.30
R16308	35V 0.47uF	\$0.30
R16310	35V 0.68uF	\$0.35
R16311	35V 0.82uF	\$0.35
R16312	35V 1.0uF	\$0.30
R16314	35V 1.5uF	\$0.50
R16316	35V 2.2uF	\$0.50
R16318	35V 3.3uF	\$0.35
R16320	35V 4.7uF	\$0.70
R16322	35V 6.8uF	\$0.80
R16324	35V 10uF	\$0.80
R16326	35V 15uF	\$1.40
R16328	35V 22uF	\$3.50



ECONOMY TRANSFORMERS

Cat. No.	Description	Price
2155	240V 6-15V 1A	\$8.95
Cat. M12155		\$9.95
2156	240V 6-15V 2A	\$13.95
Cat. M12156		\$14.95
2840	240V 9V CT	\$4.95
Cat. M12840		\$5.95
2851	240V 12-6V CT 150mA	\$5.50
Cat. M12851		\$5.95
2860	240V 15V CT 250mA	\$4.95
Cat. M12860		\$5.95
6672	240V 15-30V 1A tapped	\$13.95
Cat. M16672		\$14.95

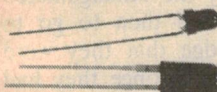

QUALITY LEDs

Cat. No.	Description	Price
Z10140	3mm Red	\$0.15
Z10141	3mm Green	\$0.20
Z10143	3mm Yellow	\$0.20
Z10145	3mm Orange	\$0.20
Z10150	5mm Red	\$0.15
Z10151	5mm Green	\$0.20
Z10152	5mm Yellow	\$0.20

HIGH INTENSITY RED LED BAR GRAPH

Dimensions:
Overall: 63mm across, 5mm high.
LEDs: 10 x 5mm x 1mm

Cat. No.	Price
Z10180	\$2.95
Z10181	\$2.75



1/2" HIGH INTENSITY RED LED DISPLAYS

(Available in Common Cathode and Common Anode)

Dimensions:
Overall: 12.7mm(H) x 7.3mm(W)
Segment Width: 1.2mm
Brightness: 3400 ucd, I_a = 10mA

COMMON CATHODE:

Pin 1 Segment E	Pin 6 Segment B
Pin 2 Segment D	Pin 7 Segment A
Pin 3 CC	Pin 8 CC
Pin 4 Segment C	Pin 9 Segment F
Pin 5 Segment Op	Pin 10 Segment G
Cat. No.	Price
Z10190	\$1.95
Z10191	\$1.75
Z10192	\$1.50

COMMON ANODE:

Pin 1 Segment E	Pin 6 Segment B
Pin 2 Segment D	Pin 7 Segment A
Pin 3 CA	Pin 8 CA
Pin 4 Segment C	Pin 9 Segment F
Pin 5 Segment Op	Pin 10 Segment G
Cat. No.	Price
Z10190	\$1.95
Z10191	\$1.75
Z10192	\$1.50



NUMERIC KEYPAD

Unencoded keypad, 10 digit keys plus two utility keys. Light grey in color.

OUTPUT ARRANGEMENT:

Output Pin No.	Symbol
1	N.A.
2	Shield plate
3	Column 2
4	Row 4
5	Column 3
6	Row 1
7	Column 1
8	Row 2
9	Row 3
10	N.A.

Cat. C19030	Price
1-9	\$2.95
10+	\$2.50
100+	\$1.95

6.35mm STEREO PLUGS

UNBELIEVABLE PRICES!!
P10121 (plastic plug) Normally \$1.00

Cat. No.	Price
1-9	\$0.50
10+	\$0.45
100+	\$0.40



ELECTROLYTICS (PCB MOUNTING)


Cat. No.	Description	Price
R15461	10uF	\$0.25
R15481	22uF	\$0.25
R15511	33uF	\$0.25
R15521	47uF	\$0.25
R15531	100uF	\$0.30
R15541	220uF	\$0.60
R15551	330uF	\$0.75
R15561	470uF	\$0.75
R15571	640uF	\$0.90
R15581	1000uF	\$0.90
R15601	2200/2500uF	\$1.20

Cat. No.	Description	Price
R15422	2.2uF	\$0.25
R15432	3.3uF	\$0.25
R15442	4.7uF	\$0.25
R15462	10uF	\$0.25
R15502	25uF	\$0.30
R15512	33uF	\$0.30
R15522	47uF	\$0.30
R15532	100uF	\$0.40
R15542	220uF	\$0.70
R15552	330uF	\$0.75
R15562	470uF	\$0.75
R15582	1000uF	\$1.00
R15602	2200/2500uF	\$1.40

Cat. No.	Description	Price
R15443	4.7uF	\$0.30
R15463	10uF	\$0.30
R15483	22uF	\$0.30
R15513	33uF	\$0.40
R15523	47uF	\$0.40
R15533	100uF	\$0.60
R15543	220uF	\$0.60
R15563	470uF	\$0.70
R15583	1000uF	\$1.20
R15593	2200/2500uF	\$1.50

Cat. No.	Description	Price
R15404	0.47uF	\$0.25
R15414	1uF	\$0.25
R15424	2.2uF	\$0.30
R15434	3.3uF	\$0.30
R15444	4.7uF	\$0.40
R15464	10uF	\$0.40
R15484	22uF	\$0.40
R15514	33uF	\$0.40
R15524	47uF	\$0.50
R15534	100uF	\$0.60
R15544	220uF	\$0.90
R15564	470uF	\$1.00

Cat. No.	Description	Price
R15405	0.47uF	\$0.30
R15415	1uF	\$0.30
R15425	2.2uF	\$0.30
R15435	3.3uF	\$0.30
R15445	4.7uF	\$0.40
R15465	10uF	\$0.40
R15485	22uF	\$0.40
R15505	25uF	\$0.50
R15525	47uF	\$0.50
R15535	100uF	\$0.60
R15545	220uF	\$0.90
R15555	330uF	\$1.20
R15565	470uF	\$1.40

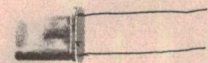

CRYSTALS SPECIALS!

Description	Cat. No.	Price
1MHz	Y11000	\$7.50
4.433618MHz	Y11023	\$2.95
8.867238MHz	Y11055	\$2.95
12MHz	Y11070	\$2.95
14.31818MHz	Y11072	\$2.95



CHROME LED BEZELS

9mm hole, available 3 colours

Cat. No.	Description	Price
S14030	Red	\$1.20
S14032	Green	\$1.45
S14034	Yellow	\$1.45



5 PIN DIN PLUG

UNBELIEVABLE PRICE!

Cat. No.	Price
P10157	Normally \$1.00
1-9	\$0.50
10+	\$0.45
100+	\$0.40



ULTRASONIC TRANSDUCERS


Designed to transmit at 40kHz (L19990) and receive at 40kHz (L19991) with up to 20V I/P on the transmitter. These units can't be heard and so are ideal for TV remote controls, water level detectors, burglar alarms, motion detectors and information carriers as they can be either pulsed or used in the continuous wave mode. Full specifications below for design purposes.
Maximum Input Voltage: 20V rms
Centre Frequency (kHz): 40 ± 1.0
Sound Pressure Level 10V RMS: 110dB min.
Sensitivity (dB/V/ubar) min.: -65 min.
Bandwidth (kHz):
Transmit: 4.0 (at 100dB)
Receiver: 5.0 (at -73dB)
Impedance:
Transmit: 500
Receiver: 5000
Cat. L19990 (Transmitter) \$4.75
Cat. L19991 (Receiver) \$4.75



MINI JUMPERS

• Contact terminal: Phosphor bronze
• Material: P.B.T. 94V-0
• Gold plated

Qty.	Cat. No.	Price
10	P12053	\$ 2.95
25	P12055	\$ 4.95
100	P12057	\$21.95

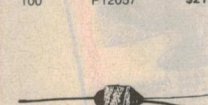

TRIGGER TRANSFORMERS


Cat. M10104 \$1.45



10 AMP RELAY

S.P.D.T. 12V Coil, 240V (S14114)

Cat. No.	Price
1-9	\$4.95
10+	\$3.95
100+	\$3.75

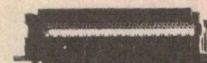

CENTRONICS PLUG SPECIAL!

36 WAY MALE (P12200)


Cat. No.	Price
1-9	\$3.95
10+	\$3.50
100+	\$3.00



DB STAND OFFS

At incredible prices! No need to pay absurd prices because we import them direct and pass on the savings to you!

Cat. No.	Price
2 Pack P10930	\$1.00
10 Pack P10932	\$3.95
100 Pack P10934	\$20.00

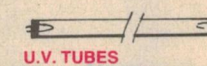

U.V. TUBES

Fits into standard 15W fluoro holder. Suitable for Scotchcal, Epsom erasing etc. As used in ETI Epsom Erasing Kit.

WARNING: Do not look directly into UV Tubes.

Cat. H28600 \$24.95

*If ordering by mail please include an extra \$2 for "special" packing.



SPECTROL MULTIALDIS


MODEL 15-1-11

Number of turns: 10
Minor Scale Division: 1/500 turn
Shaft Bore: 6.35mm (1/4")
Finish: Satin Chrome
Body Size: 25.4 x 44.45mm (1 x 1 3/4")
Depth: 25.4mm (1")
Weight: 45.4g (1.6oz.)
Cat. R14405 \$45.95




MODEL 16-1-11

Number of turns: 15
Minor Scale Division: 1/50 turn
Shaft Bore: 6.35mm (1/4")
Finish: Clear Anodize
Body Size: 22.2mm diameter (875")
Depth: 22.2mm (875")
Weight: 19.8g (0.7oz.)
Cat. R14400 \$26.95

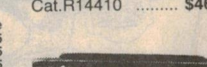

MODEL 21-1-11

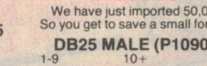Number of turns: 15
Minor Scale Division: 1/100 turn
Shaft Bore: 6.35mm (1/4")
Finish: Satin Chrome
Body Size: 46.04mm diameter (1.812")
Depth: 25.4mm (1")
Weight: 85.9g (3oz.)
Cat. R14410 \$46.95



DB25 CONNECTOR SPECIALS!

We have just imported 50,000. So you get to save a small fortune!

DB25 MALE (P10900)

1-9 \$1.50 10+ \$1.20 100+ \$1.00

DB25 FEMALE (P10901)

1-9 \$1.70 10+ \$1.40 100+ \$1.20

S.P.D.T. TOGGLES

We have 15,000 to clear!

Cat. S11010 Normally \$1.75


1-9 \$0.80 10+ \$0.75 100+ \$0.65

RCA GOLD PLATED CHASIS SOCKET

For the ultimate connection!

Cat. P10229 Normally \$1.95

1-9 \$1.00 10+ \$0.90 100+ \$0.85

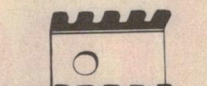


MINIATURE HEATSINK!

A great little fellow if you are short of space. Great price too, because we import direct so you save!

Dimensions: 19(L) x 13(W) x 9(H)mm

Cat. No.	Price
H10606	\$0.40
10+	\$0.35

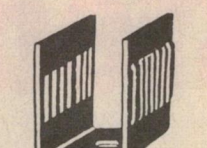

MINI "U" HEATSINK

Used extensively on PCB's this heatsink suits most flat (plastic type) semiconductors. Has vertical flutes for maximum thermal efficiency.

Cat. No.	Price
H10602	Normally \$1.25
1-9	\$0.65
10+	\$0.55
100+	\$0.50



UNIVERSAL HEATSINK

Universal because of the hole pattern which allows it to be mounted to most "power" type semiconductors. Features vented sides and black anodised finish for maximum efficiency.
Dimensions: 60(L)x35(W)x30(H)mm
Cat. H10601 Normally \$1.75

1-9 \$0.75 10+ \$0.65 100+ \$0.60



CANNON TYPE CONNECTOR SPECIALS

Cat. No. Description Price

P10960 3 pin line male. Was \$3.90 NOW \$2.90

P10962 3 pin chassis male. Was \$3.00 NOW \$2.40

P10964 3 pin line female. Was \$4.50 NOW \$3.25

P10966 3 pin chassis female. Was \$4.95 NOW \$3.45

P10968 3 pin chassis female. Was \$4.95 NOW \$3.45

P10970 3 pin chassis female. Was \$4.95 NOW \$3.45

P10972 3 pin chassis female. Was \$4.95 NOW \$3.45

P10974 3 pin chassis female. Was \$4.95 NOW \$3.45

***65TH BIRTHDAY FEATURE:**

A dream that lasted 65 years

— and is still going strong!

Sixty-five years ago this month, on August 4, 1922, Messrs W.J. Maclardy, of Castlereagh Street, Sydney launched what they claimed to be the first-ever publication to be produced in Australasia, wholly devoted to wireless . . . This present copy of Electronics Australia is a direct descendent of that first issue of Wireless Weekly.

by NEVILLE WILLIAMS



We don't have a copy of the very first issue (August 1922) good enough to reproduce, but here is the cover of the issue for September 2, 1927 — plus a typical advert of the time.

At the time, regular officially endorsed public broadcasting was something about which would-be listeners were still dreaming and agitating.

An article on page 3, headed: "OUT-BACK — As It Should Be" pictured "Dad Wayback" coming inside for the evening, hanging up his hat, and switching on the wireless in time to catch the weather forecast and daily market reports. A few minutes later the whole family would gather round to enjoy a concert "sent out by the Amalgamated Wireless". They would then go to bed, in the knowledge that they were no longer as isolated as once they had been.

At the time, AWA was in fact broadcasting demonstration "wireless concerts" each week in Sydney and Melbourne, while other transmissions could be heard from enterprising amateur stations. But a whole year was to elapse before the Federal Government would implement formal broadcasting provision (August 1, 1923) with the first official broadcast station 2SB Sydney (later 2BL) later, 3AR Melbourne in January 1924, and 6WF Perth in June.

A clear objective

But, with all that still in the future, the writer of the introductory editorial in 1922 identified the objective of the new publication with rare insight — even if rather awkward punctuation. I quote the key paragraph, exactly as published:

"It will be the wholehearted endeavour of this journal to give its readers reliable news of the latest developments in the science from all parts of the world; keep the experimenter informed on all matters

concerning his hobby, and help him to put his case for the relaxation of restrictions under proper control; and generally deal with the science in an understandable way, from the elementary stages to the super-technical".

Sixty-five years on, that statement of intent is still relevant even though, in the meantime, the science of "wireless" has expanded at a speed, and to an extent, that is nothing short of mind-boggling.

The practical items in that first issue of 1922 were elementary in the extreme:

- A circuit for a one-valve regenerative radio receiver.

- A plug-in mounting system for honeycomb tuning coils;
- Constructional details for a fool-proof molybdenite signal detector.

This plus technical tips, news items, wireless club notes, advertisements and intriguing little snippets like the following:

"A well known Adelaide jeweller, who is interested in wireless, puts his hobby to an interesting use. At noon each day, he checks his chronometers by radio time signals received on a set at his shop. He finds this method more reliable than the telephone system".

By March 1923, with public broadcasting still eight months away, *Wireless Weekly* was sporting a colour cover, a new business address in Regent Street, Sydney and, more importantly, an array of titillating advertisements for an emerging of wireless hobbyists. Here's a sampling:

GRACE BROS, Sydney: "Send for our free booklet: 'All About Wireless'. Broadcasting will soon be in full swing."

ANTHONY HORDERNS, Sydney: "Murdock's double head sets. Myers' valves" . . . &c.

HEMOCRAFTS, Melbourne: "Closed core interval transformers 45/-, postage 6d".

COLVILLE-MOORE, Sydney: "Receiving sets, AC 'Homecharger'. Charge your own A or B battery."

O.H.O'BRIEN & NICHOLL, Sydney: "The Trimm Professional head set. A quality phone at a quantity price".

With the commencement of public broadcasting, interest in wireless — or radio — grew rapidly, with receivers being variously bought and sold, built and rebuilt, in a seemingly tireless quest for any signals, more signals and louder signals.

In those days, broadcast stations using horizontal transmitting antennas tended to spray signals randomly far and wide, especially at night, and half the fun of owning a wireless set was to have listened to and logged more sta-

The KLOTZ 2-Valve RECEIVER

Described in This Issue.

	£	s.	d.
1 Radion Panel, 14 x 8 x 3-16	0	11	8
2 Eco Centreline Condensers, .0005, 10/-	1	0	0
2 Emmco Bakelite Vernier Dials, 7/6	0	15	0
3 Radiokes R.F. Chokes, at 8/6	0	4	0
1 Wetless Reinartz Coil	1	5	6
2 Kelford Anti-vibration Sockets, U.X., at 3/-	0	12	6
1 Single Circuit Jack (Pilot)	0	6	0
1 Wetless Mica Condenser, .0003	0	2	0
1 Wetless Mica Condenser, .001	0	1	6
2 Wetless Mica Condensers, .0001, 1/6	0	1	6
1 Crescent Audio Transformer	0	3	0
1 Doz. Square Buswire	0	13	6
2 Lengths Spaghetti, 3d.	0	0	10
1 Standard Terminal Board	0	0	6
	0	2	9

This Set of Quality Parts costs £6/0/3

A very popular build-it-yourself project described in 1927 was the "Klotz" two-valve regenerative receiver. Built on a wooden "breadboard" and with a bakelite panel, its kit of parts could be yours for only six pounds and thirpence (about \$12).

tions — especially distant ones — than anyone else in the street. A card with callsigns and dial settings was routine.

Wireless Weekly catered for all this with a comprehensive menu of programs, articles on stations, sessions and personalities, products and trade information, technical assistance and — last but certainly not least — how-to-build articles dealing with domestic receivers and accessories.


Prominent, too, was "The Safety Valve", the fore-runner of today's "Letters to the Editor".

A couple of years back, EA reprinted examples of this now historic material in a publication entitled "The Best of Australia's Wireless Weekly in 1927" — a vintage year that saw something of a

peak in the initial growth phase, involving mainly battery-powered receivers.

The dozen-odd projects which were reproduced covered receivers ranging from 1 to 8 valves, including a reflex circuit, a neutrodyne and a superhet. These, plus a crystal set, a B-battery eliminator and a selection of audio amplifier stages.

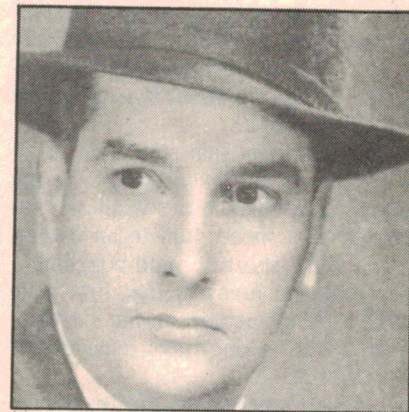Interest in radio broadcasting reached even greater heights in the early and mid '30s, with more stations coming on-air and more imaginative programming. The same period saw the emergence of practical and reliable mains powered receivers, and a growing consciousness of sound quality as properly driven moving coil loudspeakers took over from the old "horn" and "cone" models.



When editor Ross Hull left the magazine to go the USA in the early 1930s, his brother 'Braith Hull (above) took his place. One of 'Braith Hull's other interests was motor racing, as shown in the shot at left. (Courtesy Ron Bell)

It was at this stage that *Wireless Weekly* set an industry lead with receivers for home construction like the "1933 Standard" and the "1934 Champion" superhet, which clearly outclassed most contemporary commercial designs. In a very real way, those receivers set the scene for the journal's later commitment to high fidelity sound reproduction.

Technical writers

For some obscure reason, few of the articles in *Wireless Weekly* carried by-lines. But one name that did become legendary in those early days was that of Ross Hull — an avid experimenter and "Ham", and a capable technical writer. I never met him personally, mainly because he was a decade ahead of me but his reputation remained for years as a standard against which his successors were measured.

In the early '30s, Ross Hull resigned from *Wireless Weekly* to take up a position with "QST", an amateur radio magazine published by the ARRL (American Radio Relay League). Tragically, his career was cut short when he was electrocuted while working on his latest interest — a developmental TV receiver.

Ross was succeeded in the editorial chair of *Wireless Weekly* by his brother A.G. Hull, whose immediate skills were administrative and mechanical rather than electronic. But according to his lifelong friend Ron Bell, founder of RCS Radio, 'Braith (Galbraith) Hull adapted quickly to his new role.

He engaged as technical assistant a

youth, fresh out of Scots College, Melbourne who, over and above music and literature, had one dominating passion: radio. His name was John Murray (Johnny) Moyle.

Like Ross Hull before him, John already held an amateur licence and, as early as 1936, was to be found tearing around the countryside with mobile 5-metre (60MHz) equipment, talking back to fellow amateurs from remote mountain outcrops around Sydney. This interest was to be taken up again ten years later.

But, for the magazine itself, the winds of change were freshening. With radio receivers being accepted as a routine consumer appliance, the traditional nexus between programs, personalities and technical matters was eroding, placing a large question mark over the basic format of *Wireless Weekly*.

Between them, 'Braith Hull and John Moyle managed to talk their parent company into a completely new concept: *Wireless Weekly* would continue as a purely program and personality publication, produced by non-technical journalists. The technical team would concentrate on a new national monthly magazine, devoted mainly to radio and allied technology, but with a generous helping of science and hobbies.

It sounded like a good idea and, in April 1939, the first issue of *Radio and Hobbies* appeared on the streets. It sold quickly and, over the next few issues, gave all the indications of being a runaway success!

But then the scene changed when Australia joined Britain in declaring war

on Germany. Braith Hull left to take up other activities, and I myself became involved with "R&H" — first as a contributor, then as a full-time technical editor. John Moyle accepted a commission with the RAAF as a radio/radar instructor, and I suddenly found myself with the job of running the magazine with the help of a junior assistant and a shared typist.



John Moyle (right) was editor of the magazine, then *Radio & Hobbies*, from 1939 until his untimely death in 1960. Here he is shown with Ron Bell, founder of RCS Radio.

With paper, facilities and radio components virtually frozen, it was essentially a holding operation, although the magazine was eagerly sought by service personnel, who were being introduced to radio technology for the first time in the armed forces.

A whole new team

Following the war, John Moyle and I set about assembling a technical team and organising new facilities to tackle the job ahead. Our aim was to find people with a range of skills, likely to complement the diverse interests of a whole new generation of readers.

And what unlimited scope for initiative there seemed to be, especially in view of the thousands of enthusiasts re-entering civilian life:

A huge backlog of ordinary receivers to be built; an urge to come to grips with better quality sound reproduction; a reopening of the amateur bands, and the promise of a mountain of surplus components through military disposals; the possibility of acquiring or building some real test equipment; and, further down the track, tape recording, a vastly improved disc format and television!


Far from being a daunting prospect, it was like a bunch of "carrots" out front, exasperating only because one couldn't tackle everything at once. I'm not exaggerating to say that John and I, along with newly recruited staff members, were like overgrown kids in a toyshop — incredulous that somebody was willing to pay us wages to pursue our collective hobby!

We would pore over disposals adverts and jostle with other enthusiasts every lunchtime at Price's Radio in Angel Place. "Two-bob for this . . . a quid for that!"

We worked during the day in the office and, for the most part, went off home and kept right at it. John set up a ham shack and workshop in a spare (?) bedroom where, amongst other things, he spent countless hours grinding and etching crystals; I had a desperately overcrowded "shack" in the backyard; hifi gear dominated our respective living rooms. That was around 1947.

First radio newsgathering

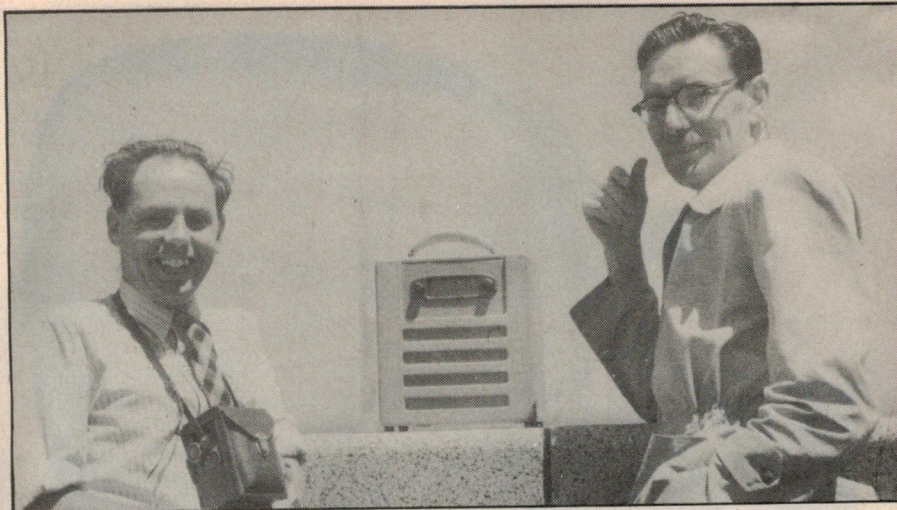As a measure of this immediate post-war enthusiasm, one of the projects tackled by the R&H technical team was only remotely connected to the magazine itself. Remembering his mobile radio activities in 1936, John saw the opportunity to set up what would be Australia's first mobile radio news gathering service, in association with our



Former assistant editor Philip Watson (left) with Neville Williams, author of this article, in mid-1948 on the roof of the Sun newspaper building in Sydney. They were trying out a VHF newsgathering system.

parent company's "Sun" newspaper.

The PMG Radio Branch obliged with a licence for 70.46MHz, and the race was on to rework what was essentially 50MHz amateur equipment for the higher frequency. The base transmitter and receiver were installed on the roof of the old Sun building in Elizabeth Street (Sydney), with a control and copy reception centre in a disused studio on the 12th floor. It had been installed for 2UE in the early '30s, for simulated test cricket broadcasts.

With the vibrator-powered transmitter/receiver mounted in a (fortunately) capacious Chevrolet, and with yours-truly aboard to make sure it all worked, we made the first radio-controlled news sortie on July 2, 1948. Backing up was Ray Howe (ex RAAF) and Maurice Findlay, who, in later years, was to found his own company specialising in 2-way radio. (The exercise was described in the August, 1948 issue of EA).

Perhaps I should add that, at a later stage, Philip Watson — ultimately EA's assistant editor — was involved in the on-going mobile news-gathering project, as also was Ian Pogson, a long-term staff member, probably best remembered for the "Deltahet" series of high-tech, communication receivers.

On the amateur bands

Getting back to the magazine, most of the once well-known "2JU" amateur transmitter and receivers were built in John Moyle's bedroom/shack and checked out on air, in the late evenings. We would compare notes on the then 6-metre band, with occasional interruptions from as far afield as Arch Cox in Canberra (240km) and Alan Thackeray

in Young (320km). This was long before the days of VHF repeaters.


Around 1950, we began to use 2 metres or 2/5metre crossband — made possible, in my case, by modifying a British made ex-disposals 1143 transceiver. Of necessity, it had been designed around components that always were ill-suited to VHF service but, as I remember, it had been coaxed up to around 120MHz. To get it up to 144MHz was quite an assignment.

It was a multi-channel unit, with a fierce ratchet type stepping motor to change crystals and re-tune a bank of variable capacitors. In a plane, with a couple of Rolls Royce Merlins going full bore, the noise of the stepping mechanism would have been of no great consequence but, to change channels in an amateur shack in the dead of night, it was something else!

Audio-hifi activities

Interesting though these activities were, I doubt that they held the fascination of our on-going quest for even higher audio quality; this against a background of argument, during meal breaks in the cafeteria, between John Moyle the recorded music exponent and Julian Russell, more recently an EA record reviewer but, in those days, resident concert critic for our parent company. I can assure you that Julian upheld very capably the views of the "golden ear" fraternity!

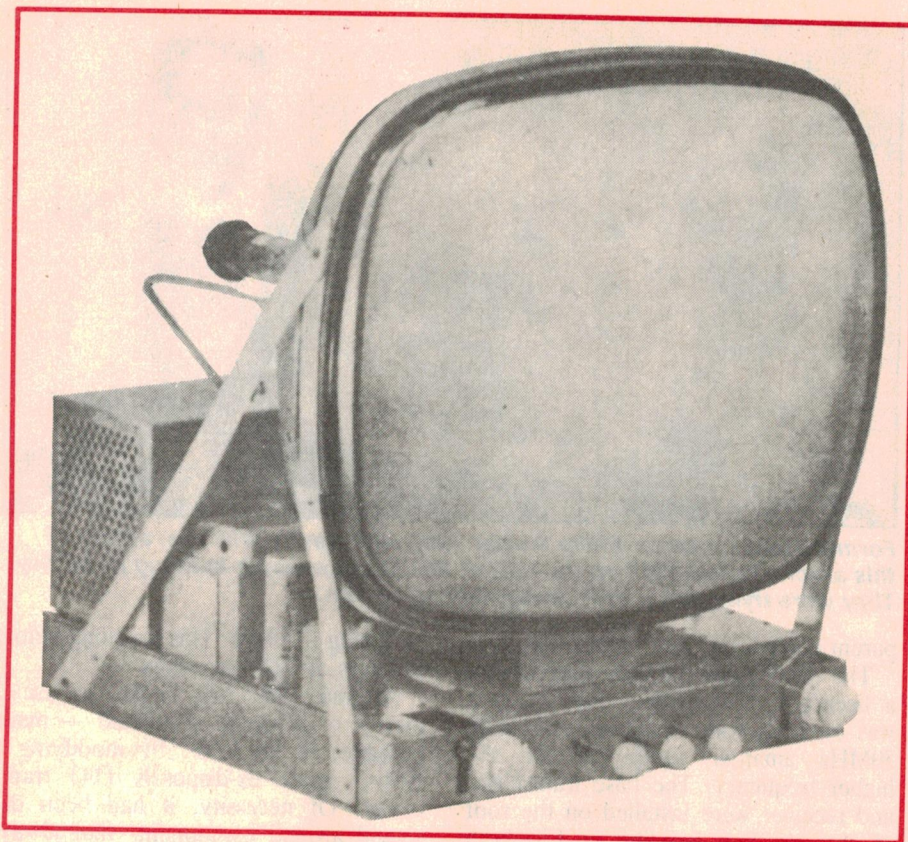I can recall our valiant efforts to win better sound from 78rpm records, the exercises in frequency compensation, the many lightweight — but often frail — pickups and the sad shake of the head by Fritz Langford-Smith, a guest at some of our listening sessions. As au-



The famous 1957 17-inch TV receiver, which Neville Williams himself designed. The first large-screen set described for home construction, it was extremely popular.

thor of the famous Radiotron Designer's Handbook, and a hifi fan with a keen ear for distortion, he had been my immediate superior in former days with the Amalgamated Wireless Valve Company.

Then along came microgroove LP records, marked by king-size commercial gaffes that left more than a few industry executives with egg on their corporate faces. For us, LP records marked a new era, but one that involved us in still more test runs in the search for a reliable microgroove magnetic pickups or, alternatively, for a suitably hifi ceramic cartridge. But it provided welcome copy for a technical magazine.

Meantime, domestic tape recorders had also made their appearance, backed up by a cloak-and-dagger tale of how they had been surreptitiously developed by the Germans, used secretly to further the Nazi War effort and discovered by chance by the rapidly advancing occupation troops.

In truth, German recording engineers had proudly demonstrated an early model tape deck to Sir Thomas Beecham in Ludwigshafen in 1936, and had used his orchestra to make the first-ever tape recording of a major concert. Far from being kept a secret, all rele-

vant patents had been systematically filed in Switzerland, a neutral country. They were there for anybody to study.

Tape, and then stereo

The first tape recorder to reach us for inspection and comment was the "Magictape", a basic half-track model marketed by AWA. We had more fun with it in our lab than with any other "new toy" that I can remember, duly offering to prepare a lecture on the subject for the WIA (Wireless Institute of Australia).

The formal words and diagrams were prepared in good time but, on the morning of the lecture, we decided to make a send-up tape of an amateur transmission, with all the editing tricks that one could pull with such gear. For good measure, we added a home-grown, inlab version of the old comedy classic "The Crazy Pantomine".

For most of that day, our not-very-soundproof lab re-echoed to outlandish sound effects, grunts and guffaws that must have seemed slightly peculiar to other occupants of the floor. It must have appeared even more so to the spirits of the long-departed scientific fathers whose solemn portraits, on the night, gazed down from the walls of a

packed Science House in Gloucester Street, Sydney.

As a tape recorder, the "Magictape" was no great shakes but one thing I know: From every point of view, it was far more affordable and practical as a recording device than the plastic coated aluminium recording discs and the Byer decks that some of us had been using previously to record interesting QSO's.

As for stereo LP discs, one could write a very long article about the philosophical arguments that they prompted. Many established hifi enthusiasts didn't want to pension off their prized mono pickup and amplifier, and they certainly couldn't afford or accommodate a duplicate of the massive mono loudspeaker enclosure they had fought to justify in the living room.

So any plausible anti-stereo argument was worth a run if it served to postpone the evil day: stereo was unnatural, artificial; it traded genuine quality for an illusion of spread; it could only work for someone sitting in one critical position; it was a gimmick, which wouldn't last, etc.

One man who didn't see it that way was a longstanding friend, Ernest (now Dr) Benson. At the time, he was a leading development engineer with AWA, who showed unusual interest when I mentioned that John and I would be auditioning a couple of advance-sample stereo records with a prototype ACOS cartridge. It had just arrived from the UK, and Max Cutts of Amplion had invited us to check it out.

Ernie B. duly joined us in John's lounge room and listened intently, saying scarcely a word. Finally, to our question "what do you think?" he drew breath and came up with what must be the most unbiased, matter-of-fact reply that I have ever heard:

"Gentlemen, you have just written off twelve months work!"

He went on to explain that he had been quietly researching simulated stereo sound, culminating in a prototype radiogram that would hopefully have stolen a march on AWA's competitors. In the light of what he had just heard, it would have been released just in time to be rendered obsolete!

Electronic organs

That same Ernest Benson was the man who, years before, had got me all steamed up about electronic organs. Together with EA science writer, Calvin Walters, I had visited his home and heard an organ in his lounge room that, in those days, sounded nothing short of magnificent. Then he took us

downstairs to where a Hammond-like mechanism was purring away, generating waveforms for the console above.

I even went as far as having the blanks punched for a set of tone wheels, but that's as far as it went. Anyone who addresses himself to an organ on that scale may as well forget everything else for an indeterminate period!

Further involvement in the subject had to wait until around 1960, when Stromberg-Carlson Australia collapsed, following the failure of their unbranded receiver production. On the side, they had just previously begun to manufacture and market their version of a single-manual Thomas electronic organ and this, too, was doomed.

However, through the good offices of Neville Oates and Bob Swan — respectively Stromberg's organ engineer and sales executive — an arrangement was reached whereby the entire organ parts inventory would be cleared as kits and we would devise and publish a matching series of constructional articles.

In fact, we went well beyond the original Thomas/Stromberg design, adding optional 16' and 2' voices and reverberation. In so doing, we established something of a record in publishing about nine separate instalments, to the best of our knowledge without a single presentation error!

Admittedly, it was an essentially basic instrument but it allowed quite a few enthusiasts and small churches to acquire an electronic organ that they would not otherwise have been able to afford.

It also whet the appetites of quite a few others for something more pretentious but, apart from a few "ideas" articles, the Stromberg/Playmaster organ featured in and after December '61, remained a one-off exercise. The economics of designing, publishing, kitting-up for and supporting a complex organ for home construction simply don't stand up.

Home built hifi

But that's fortunately not the case with home-built hifi equipment, notably amplifiers, tuners and loudspeaker systems. Readers in Australia and New Zealand have built them in their tens of thousands, in many cases in numbers which would have delighted companies marketing name-brand products.

Quite early in the piece, John Moyle came up with the idea of adopting the name "Playmaster" for all audio-related projects which we might otherwise describe — at the time — as high fidelity.



Another EA "milestone" project was the Stromberg-Playmaster organ of December 1961 and following issues, which was a very popular project. Here it was shown being played by Stromberg sales executive Bob Swan.

It was a brilliant idea, almost too good because, in short order, it was adopted for a whole range of audio related products. The Stromberg/Playmaster organ was an obvious example.

It would require a whole article even to scan the Playmaster projects over the years, but my mind turns automatically to the memorable last generation of all-valve amplifiers, using tetrode output valves in ultralinear configuration, with overall negative feedback.

The ultralinear connection, with the screens returned to tapings on the output transformer, was an ingenious way to combine the efficiency of a beam tetrode with the low output impedance of a power triode. You were halfway there even before the application of negative feedback!

Mathematicians had long since known that overall negative feedback could turn nasty at high frequencies and cause instability — but they didn't build amplifiers. Manufacturers knew that their output transformers were the main source of phase rotation — but they didn't have to solve circuit problems!

It fell to people like Williamson in "Wireless World", Mullard in their "Outlook" and us with our "Playmasters" to bring together the maths, the transformer winding options, and circuit practicalities, in devising amplifiers that would work well and behave themselves in terms of high frequency stability.

There were many occasions when we could have done with "hotlines" from our lab to the valve manufacturers, along with Ferguson in Chatswood, Bramco in Newcastle, and A&R and RedLine in Melbourne. Those were days when Australians produced their own indigenous components, and we could consult directly with the engineers responsible. You'll have to pardon my nostalgia.

The television boom

Fortunately, and fairly obviously, that situation applied in the late '50s and early '60s when we had to meet reader clamour for home-built TV receivers. So much so that we changed our name from the original *Radio and Hobbies* to *Radio, TV and Hobbies* — a

The Best of Australia's Wireless Weekly

It may look like a book, but don't let its appearance fool you. There are no whirling dials and control levers; but once you open the cover, it'll take you on an incredible journey backwards in time. You'll find yourself back in the 1920's, when Australia's first new radio stations were just getting established and typical radio set cost ten weeks' wages. We've chosen a collection of highlights from the 1927 issues of "Wireless Weekly".

Send your order to:


**Freepost No.4,
Federal Publishing
Book Sales**

PO Box 227

Waterloo NSW 2017

(No postage stamp required if mailed within Australia)

Price: \$3.95 plus \$1.00 p&p

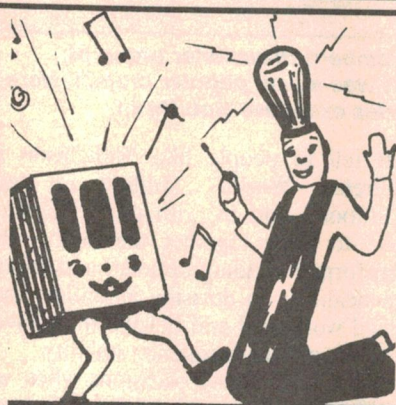

RESURRECTION RADIOS

(WE BUY, SELL AND REPAIR
ANTIQUATED RADIOS)

Are proud to announce the recent restoration of various valve radios from the period 1920 to 1950. These attractive units combine function with style, in some cases having been converted to receive FM Broadcasts. Units of particular quality are to be sold from our display area at:

53 LANG ST., SOUTH YARRA, 3141.

We also wish to announce the availability to the public of full servicing and original parts replacement, plus FM conversion at reasonable rates.

FOR INFORMATION OR ADVICE,
TELEPHONE 820 1315.

DEALERS AND REPAIRERS OF
ANTIQUATED VALVE RADIOS



**Neville Williams joined the magazine, then "Radio and Hobbies" in December 1941 — as Technical Editor. He held that position until April 1960, also serving as Acting Editor during the illness of the then Editor, John Moyle. After Mr Moyle's death he was appointed editor and served in this position until April 1971. He then became Editor-in-Chief and continued to guide the destiny of the magazine until his retirement in July 1983. His total length of service with the magazine is thus almost 42 years — more than any other individual. Since his retirement, Neville has remained very active and is still a regular contributor, with columns and articles coming from him each month in a steady stream. We're delighted he was able to write this article to celebrate our 65th birthday.*

mouthful if there ever was one!

Our attention turned initially to junk boxes and disposals stores, crammed alike with surplus cathode ray tubes and other radar remnants, hoarded against just this eventuality. After all, they were descendents of pre-war British television and who cared if the images were small and green, or blue? They would move and talk, wouldn't they?

John Moyle and I became involved in a two-horse race to devise a workable receiver, using one of the available 5-inch tubes — a 5BP1 or its somewhat more bulky English equivalent. The EHT supply was a problem, but someone had worked out that the need could be met with a voltage multiplier using 1000V paper capacitors and, of all things, a handful of 6H6 metal shell twin-diode valves.

Some would inevitably develop internal shorts, but who cared? There were thousands of otherwise useless 6H6s in the disposals stores, at "two bob" a time!

I managed to get hold of a prototype IF strip from Bob Steane of Q-plus, but I then had to devise my own tuner using a conventional Oak switch, incremental tuning and a box folded from sheet brass. It wasn't all that efficient but, given a reasonable location and antenna, it worked.

John chose to devise his own IF strip, as I remember, in collaboration with Ron Bell of RCS Radio. Phil Watson, meanwhile, was doing his best to devise suitable test gear, including a 36MHz FM generator or "wobulator".

In due course, we were both rewarded with little green pictures that moved and talked — and it's debateable

whether any single project ever gave us greater satisfaction. You could even reduce the walking/talking picture to postage stamp size, much to the intrigue of visitors.

Attempts to blow up the picture weren't always quite so successful, particularly when the circuitry was re-worked for one or other of the larger tubes that could be picked up in those days.

Apart from their awkwardness and the sheer hazard of handling them, few of those early tubes were designed to have their total screen area brightly illuminated. Unable to drain away, the electrostatic charges inside and outside the glass would tear and distort the picture into grotesque shapes.

But then, just when we had had our fill of green pictures, the Manufacturers' Special Products (MSP) branch of AWA came up with a full kit of deflection components for their companion 17-inch (43cm) tube and my overcrowded shack in the backyard saw the birthpangs of what was the first modern TV receiver to be described in this country for home construction: The 1957 TV Receiver. It was finished and working before it even saw the inside of our lab.

Larger-screen models followed in successive years, but the urge to "roll your own" was gradually overtaken by the attraction of the factory-built product, off the shelf, at a cut price, on time payment.

Moreover, a new challenge had appeared on the horizon — the transistor — which was clearly going to change the whole scene. but that is another story.



Weller

New Generation Soldering Stations



WTCPS

Weller, the leader in precision soldering, introduces the ultimate in state-of-the-art soldering tools with four new stations that can handle anything from sophisticated electronic or industrial needs, to technical production for the discerning hobbyist. The WTCPS for constant use, the WTCPT Thermolok with the unique "key" for temperature selection, the EC2001D with the "set/read" digital read-out and the EC3001D for micro soldering.



WTCPT



EC2001D



EC3001D

Check with your electronics distributor now for the latest release of Weller Soldering Stations.

CooperTools

Cooper Tools Pty. Limited, P.O. Box 366, Nurigong Street, Albury, NSW 2640, Australia

TEST INSTRUMENTS

NEW

KIKUSUI 60 MHz-TRIPLE TRACE OSCILLOSCOPE — COS5060



Total Performance, multi-purpose, 3CH-Multi Trace. Dome-mesh type 12KV P.D.A. CRT. A and B Alternate sweep. Hold-Off function. VERT MODE trigger function. Energy-Saving design (PAT. Pending). Designed for Laboratory, Production line, Maintenance and Field service use.

\$1904 + tax


INCLUDES 2 HIGH QUALITY PROBES

NEW GW 20 MHz, DUAL TRACE OSCILLOSCOPE

— GOS522

A heavy duty and accurate scope for service as well as production use. Features include • Wide freq. bandwidth • Optimal sensitivity • Extremely bright display • Auto trigger level • Variable hold off • Alternate triggering • DC trigger coupling.

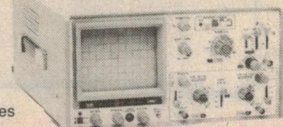\$745 + tax Includes 2 high quality probes




10 MHz SINGLE CHANNEL CRO \$412 + tax

GOS-3310

Features:

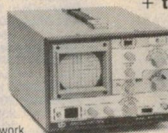- 5mV/div sensitivity
- Light & compact
- Easy to operate
- Low cost
- High performance
- TV sync. mode
- Ideal for education, hobby and service work



5MHz OSCILLOSCOPE GOS-955

Features:

- Low cost
- High performance
- User friendly
- 10mV/div Sensitivity
- Ideal for education, hobby and service

\$396 + tax



FREQUENCY COUNTERS

A whole range of Lab-quality freq. counters at a breakthrough price!

GFC 8010F (120 MHz) \$276 + tax

GFC 8055F (550 MHz) \$471 + tax

GFC-8100G (1GHz)

- Microprocessor controlled
- High resolution
- Self diagnosis routine


\$656 + tax

- 8 digit display
- Overflow indicator
- High sensitivity
- High stability

GUC-2010 UNIVERSAL COUNTER \$414 + tax

* From 5 Hz to 100 MHz

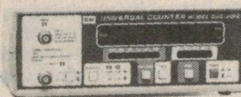* Frequency, period, totalize, freq. ratio and time interval



DIGITAL MULTIMETERS

CHECK OUR RANGE OF PROFESSIONAL MULTIMETERS

GDM-8035F

- 6 Functions (AC/DC) Volt & Current Resistance & Diode Test
- 3 1/2 Digit
- High resolution, 0.1mV, 0.1uF
- High accuracy 0.1%

\$252 + tax



GDM 8035T

- High Voltage 1200V, 20A
- Auto Zero Circuit
- Range Protection
- Diode Test Function

\$345 + tax

GDM 8045

- 6 Function
- 1/2 Digit
- High accuracy 0.03%
- High range — 1200V, 20A
- Auto zero
- True RMS


\$462 + tax

Escort EDM 1111A DIGITAL MULTIMETER

\$98 + tax

Features:

- High accuracy in measuring
- One rotary range switch allows fast and convenient operation
- Diode check DC/AC, 10A
- Instant continuity check
- Low battery indication
- 200 hrs long battery life
- Overload protection on all ranges
- Capacitance measuring
- Transistor hFE test
- 4 feet drop proof durability

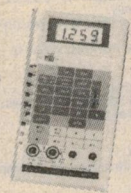


EDM 1105A

- 3 1/2 digits LCD display
- Diode testing

V DC 0-2-1000 V, 5 ranges
100 μ V max resolution, 0.8%
V AC 0-2-750 V, 5 ranges
100 μ V max resolution, 1.5%
A DC 2 mA-10 A, 5 ranges
1 μ A max resolution, 1.25%
A AC 2 mA-10 A, 5 ranges
1 μ A max resolution, 2%
Ohm 200 Ω - 20 M Ω , 6 ranges
0.1 mA max resolution, 1.0%
Auto zero & polarity indication

\$83 + tax

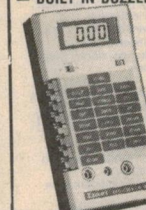ANALOGUE MULTIMETERS — SOLID PERFORMER — BUILT IN BUZZER




ELC-120

- 3 1/2 digit LCD display
 - Wide measuring ranges
 - 3 inputs: hi, lo & guard
- RANGES**
Capacitance: 200pF-200 μ F, 7 ranges
0.1pF max resolution, 1%
Inductance: 2mH-200H, 6 ranges
0.1 μ H max resolution, 2%
Resistance: 20 Ω -20M Ω , 7 ranges
10M Ω max resolution, 1%
Accessories included: Test clips, spare fuse, Instruction Manual.

\$211 + tax

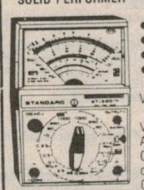ANALOGUE MULTIMETERS — SOLID PERFORMER — BUILT IN BUZZER



\$30.66 + tax

- Transistor checker
- Mirror scale
- Fuse & diode protection
- 20k Ω /V sensitivity

V DC: 0-0.1, 0.5, 2.5, 10, 50, 250, 1000
V AC: 0-10, 50, 250, 1000
A DC: 0-50 μ A, 2.5mA, 25mA, 250mA
Ohm: Rx1, Rx10, Rx100, Rx1k, 10k, 100k, 1M Ω
dB: -10 to -50 dB
Continuity buzzer.
Dim: 106 x 149 x 55 mm.

CORRESPONDENCE:
BOX K21,
HAYMARKET, NSW 2000



EMTRONICS
Retail Division of EMONA ELECTRONICS P/L

WE WELCOME
BANKCARD, VISA
& MASTERCARD

MAIL ORDERS
WELCOME

NSW & HEAD OFFICE:

92-94 Wentworth Ave,
Sydney NSW 2000.
TLX: AA 73990
P.O. BOX K21,
Haymarket, NSW 2000.
Ph: (02) 211 0988
FAX: (02) 281 1508


VICTORIA:

288-294 Queen St,
Melbourne Vic 3000.
(Entrance from
Lt. Lonsdale St)
Ph: (03) 670 8551
or 670 0330
FAX: (03) 670 0671

QUEENSLAND:

416 Logan Road,
Stone's Corner
Qld 4120
Ph: (07) 394 2555
FAX: (07) 394 4316

12 months warranty!

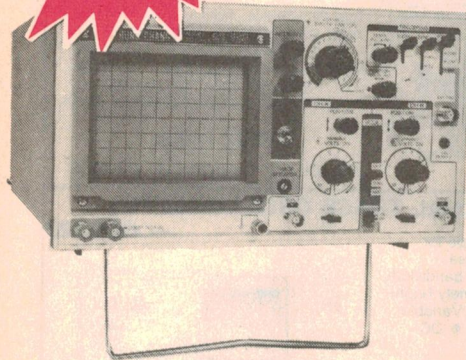

HUNG CHANG (RITRON) 20 MHz DUAL TRACE OSCILLOSCOPE

- Wide bandwidth and high sensitivity
- Internal graticule rectangular bright CRT
- Built in component tester
- Front panel trace rotator
- TV video sync filter
- Z axis (Intensity modulation)
- High sensitivity X-Y mode
- Very low power consumption
- Regulated power supply circuit

COMPONENT TESTER is the special circuit with which a single component or components in circuit can be easily tested. The display shows faults of components, size of a component value, and characteristics of components. This feature is ideal to troubleshoot solid state circuits and components with no circuit power. Testing signal (AC Max 2 mA) is supplied from the COMPONENT TEST IN terminal and the result of the test is fed back to the scope through the same test lead wire at the same time.

CRT
CRT: 6" (150mm) Flat-faced high brightness CRT with Internal Graticule.
Effective display area: 8 x 10 div (1 div = 10 mm)
Acceleration potential: 2KV

VERTICAL
Operating Modes: CH-A, CH-B, DUAL, ADD (CH-B can be inverted.)
Dual modes: Alter: 0.2u/s - 0.5ms/div, Chop: 1ms - 0.5s/div.
CHOP frequency 200KHz approximately.
Deflection factor: 5mV/div 20V/div $\pm 3\%$, 12 ranges in 1-2-5 step with fine control.
Bandwidth: DC, DC - 20MHz (-3dB), AC: 10Hz - 20MHz (-3dB).
Rise Time: Less than 17ns.
Overshoot: Less than 3%.
Input Impedance: 1M ohm $\pm 1\%$, 20pF $\pm 3\%$.
Maximum Input Voltage: 600Vp-p or 300V (DC+AC Peak).
Channel Isolation: Better than 60 dB at 1KHz.

HORIZONTAL
Sweep Modes: NORMAL, and AUTO
Time Base: 0.2u/s - 0.5s/div $\pm 3\%$, 20 ranges in 1-2-5 step with fine control.
Sweep Magnifier: 5 times (5X MAG).
Linearity: 3%.

TRIGGERING
Sensitivity: INTERNAL: 1 div or better for 20Hz - 20MHz (Triggerable to more than 30MHz). EXTERNAL: 1Vp-p or better for DC - 20MHz (Triggerable to more than 30MHz).
Source: INT, CH-A, CH-B, LINE and EXT.
Slope: Positive and Negative, continuously variable with level control PULL AUTO for free-run.
Coupling: AC, HF-REF and TV. TV SYNC Vertical and Horizontal Sync Separator Circuitry allows any portion of complex TV video waveform to be synchronized and expanded for viewing TV-H (Line) and TV-V (Frame) are switched automatically by SWEEP TIME/DIV switch.
TV-V: 0.5s/div to 0.1ms/div. TV-H: 50u/s/div to 0.2u/s/div.

X-Y OPERATIONS
X-Y Operations: CH-A: Y axis. CH-B: X axis Highest Sensitivity: 5mV/div.

COMPONENT TESTER
Component Tester: Max AC 9V at the terminal with no load. Max current 2mA when the terminal is shorted. (Internal resistance is 4.7K ohm)

OTHER SPECIFICATIONS
Intensity Modulation: TTL LEVEL (3Vp-p): Positive brighter.
BANDWIDTH: DC - 1MHz MAXIMUM INPUT VOLTAGE: 50V (DC+AC Peak)
Calibration Voltage: 0.5Vp-p $\pm 5\%$, 1KHz $\pm 5\%$ Square wave.
Trace Rotation: Electrically adjustable on the front panel.
Power Requirements: AC: 100, 120, 220, 240V 20W
Weight: 7kg approximately.
Size: 162(H) x 294(W) x 352(D)mm.

Cat. Q12105 only \$849
(tax exempt only \$695)
Bulk orders, schools, please phone (03) 543 2166 for special low pricing

METEX M-3650 MULTIMETER

20A, 3 1/2 digit frequency counter multimeter with capacitance meter and transistor tester.

This spectacular, rugged and compact DMM has a bright yellow high impact plastic case. It features a frequency counter (to 200kHz), diode and transistor test, continuity (with buzzer), capacitance meter, up to 20 amp current measurement and comprehensive AC/DC voltage, current and resistance ranges.

- CHECK THESE FEATURES....**
- Push-button ON/OFF switch.
 - Audible continuity test
 - Single function, 30 position easy to use rotary switch for FUNCTION and RANGE selection.
 - Transistor test
 - Diode test
 - Quality probes
 - 1/2" High contrast LCD.
 - Full overload protection
 - 20 Amp
 - Built in tilting ball
 - Capacitance meter
 - Instruction manual

SPECIFICATIONS:
DC VOLTAGE:
Range: 200mV, 2V, 20V, 100V
Resolution: 100uV, 1mV, 10mV, 100mV, 1V
Accuracy: 200mV - 1000V $\pm 0.3\% + 1$ digit
AC VOLTAGE:
Range: 200mV, 2V, 20V, 200V, 750V
Resolution: 100uV, 1mV, 10mV, 100mV, 1V
Accuracy: 200mV - 200V $\pm 0.8\%$ rdg + 3 digits.
750V $\pm 1.2\%$ rdg + 3 digits
Input Impedance: 10M ohm


DC CURRENT:
Range: 200uA, 2mA, 20mA, 200mA, 20A
Resolution: 100nA, 1nA, 10uA, 100uA, 10mA
Accuracy: 200uA - 20mA $\pm 0.5\%$ rdg + 1 digit
200mA $\pm 1.2\%$ rdg + 1 digit
10A $\pm 2\%$ rdg + 5 digits (10A range unfused)

Max. I/P Amps: 10A (20A up to 60 seconds)
AC CURRENT:
Range: 2mA, 20mA, 200mA, 10A
Resolution: 1uA, 10uA, 100uA, 10mA
Accuracy: 20mA - 20mA $\pm 1\%$ rdg + 3 digits
200mA $\pm 1.8\%$ rdg + 3 digits
10A $\pm 3\%$ rdg + 7 digits (10A range unfused)

RESISTANCE:
Range: 200, 2k, 20k, 200k, 2M, 20M ohms
Resolution: 0.1, 1, 10, 100, 1k, 10k ohms
Accuracy: 200 ohm $\pm 0.5\%$ rdg + 3 digits
2k ohm - 2M ohm $\pm 0.5\%$ rdg + 1 digit
20M ohm $\pm 0.5\%$ rdg + 2 digits

Overload: 200 ohm 250V DC/AC rms, 2k-20M ohm 500V
Protection: DC/AC rms

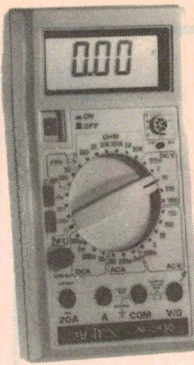CAPACITANCE:
Range: 200nF, 2uF, 20uF
Resolution: 100pF, 1nF, 10nF
Accuracy: 200nF $\pm 3\%$ + 5 digits
FREQUENCY RANGE: 0.2KHz - 0.200KHz
Cat. Q91550 only \$165



METEX 4500H MULTIMETER

10A, 4 1/2 digit multimeter with digital hold, transistor tester and audible continuity tester.

The Metex 4500H is perfect for the technician, engineer or enthusiast who requires the higher accuracy of a 4 1/2 digit multimeter. This meter is exceptionally accurate, (just look at the specifications), and yet, still retains an exceptionally low price!

The Metex 4500H features digital hold which is normally only found on very expensive multimeters. This enables you take a reading and hold that reading on display even after you have removed the probes, simply by pressing the hold button.

CHECK THESE FEATURES...

- Readout hold
- Transistor Tester
- 4 1/2 digit x 1 1/2" (H) LCD
- Audible continuity tester
- Push-button ON/OFF switch.
- Quality set of probes
- Single function, 30 position easy to use rotary switch for FUNCTION and RANGE selection.
- Built in tilting ball
- Instruction manual
- Full overload protection
- hFE test
- Battery and Spare fuse
- Diode Tester
- Vinyl case

SPECIFICATIONS:
DC VOLTAGE:
Range: 200mV, 2V, 20V, 100V
Resolution: 10uV, 100uV, 1mV, 10mV, 100mV
Accuracy: 200mV - 100V $\pm 0.05\%$ rdg + 3 digits
Input Impedance: 10M ohms

AC VOLTAGE:
Range: 200mV, 2V, 20V, 200V, 750V
Resolution: 10uV, 100uV, 1mV, 10mV, 100mV
Accuracy: 200mV - 200V $\pm 0.8\%$ rdg + 10 digits
750V $\pm 0.8\%$ rdg + 15 digits

Input Impedance: 10M ohm
DC CURRENT:
Range: 200uA, 2mA, 20mA, 200mA, 2A, 10A
Resolution: 10nA, 100nA, 1uA, 10uA, 100uA, 1mA
Accuracy: 200uA - 20mA $\pm 0.3\%$ rdg + 3 digits
200mA - 2A $\pm 0.5\%$ rdg + 3 digits
10A $\pm 1\%$ rdg + 5 digits (10A range unfused)

Max. I/P Amps: 10A (20A up to 60 seconds)
AC CURRENT:
Range: 200uA, 2mA, 20mA, 200mA, 2A, 10A
Resolution: 1nA, 10nA, 1uA, 10uA, 100uA, 1mA
Accuracy: 200uA - 20mA $\pm 0.8\%$ rdg + 10 digits
200mA - 2A $\pm 1\%$ rdg + 10 digits
10A $\pm 1.5\%$ + 5 digits (10A range unfused)

Max I/P Amp: 10A (20A up to 60 seconds)
RESISTANCE:
Range: 200, 2k, 20k, 2M, 20M ohms
Resolution: 10m ohm, 100m ohm, 1, 10, 100, 1k ohms
Accuracy: 200 ohm $\pm 0.2\%$ rdg + 5 digits
2k ohm - 2M ohm $\pm 0.1\%$ rdg + 3 digits
20M ohm $\pm 0.5\%$ rdg + 5 digits
OVERLOAD PROTECTION: 200 ohm 250V DC/AC rms, 2k-20M ohm 500V DC/AC rms

Cat. Q91560 only \$175



METEX 3800 MULTIMETER

This instrument is a compact, rugged, battery operated, hand held 3 1/2 digit multimeter for measuring DC and AC voltage, DC and AC current, Resistance and Diode, for testing Audible continuity and transistor hFE. The Dual-slope A-D Converter uses C-MOS technology for auto-zeroing, polarity selection and over-range indication. Full overload is provided. It is an ideal instrument for use in the field, laboratory, workshop, hobby and home applications.

- Features....**
- Push-button ON/OFF power switch.
 - Single 30 position easy to use rotary switch for FUNCTION and RANGE selection.
 - 1/2" high contrast LCD.
 - Automatic over-range indication with the "1" displayed.
 - Automatic polarity indication on DC ranges.
 - All ranges fully protected plus Automatic "ZERO" of all ranges without short circuit except 200 ohm range which shows "000 or 001".
 - High Surge Voltage protection 1.5 KV-3 KV.
 - Diode testing with 1 mA fixed current.
 - Audible Continuity Test.
 - Transistor hFE Test.

SPECIFICATIONS
Maximum Display: 1999 counts
3 1/2 digit type with automatic polarity indication.
Indication Method: LCD display.
Measuring Method: Dual-slope in A-D converter system.
Over-range indication: "1" Figure only in the display.
Temperature Ranges: Operating 0°C to +40°C
Power Supply: one 9 volt battery (006P or FC-1 type of equivalent)
Cat. Q91530 Normally \$109
SPECIAL \$79



METEX 3500 MULTIMETER

This instrument is a compact, rugged, battery operated, hand held 3 1/2 digit multimeter for measuring DC and AC voltage, DC and AC current, Resistance and Diode, Capacitance, Transistor hFE and Continuity Test. The Dual-slope A-D Converter uses C-MOS technology for auto-zeroing, polarity selection and over-range indication. Full overload is provided. It is an ideal instrument for use in the field, laboratory, workshop, hobby and home applications.

- Features....**
- Push-button ON/OFF power switch.
 - Single 30 position easy to use rotary switch for FUNCTION and RANGE selection.
 - 1/2" high contrast LCD.
 - Automatic over-range indication with the "1" displayed.
 - Automatic polarity indication on DC ranges.
 - All ranges fully protected plus Automatic "ZERO" of all ranges without short circuit except 200 ohm range which shows "000 or 001".
 - High Surge Voltage protection 1.5 KV-3 KV.
 - Capacitance measurements to 1pF
 - Diode testing with 1 mA fixed current.
 - Audible Continuity Test.
 - Transistor hFE Test.

SPECIFICATIONS
Maximum Display: 1999 counts
3 1/2 digit type with automatic polarity indication.
Indication Method: LCD display.
Measuring Method: Dual-slope in A-D converter system.
Over-range indication: "1" Figure only in the display.
Temperature Ranges: Operating 0°C to +40°C
Power Supply: one 9 volt battery (006P or FC-1 type of equivalent)
Cat. Q91540 Normally \$139
SPECIAL \$109



WELLER WTCPN SOLDERING STATION


The WTCPN Features:
• Power Unit 240 V AC
• Temperature controlled iron, 24 V AC
• Flexible silicon lead for ease of use
• Can be left on without fear of damaged tips!
The best is always worth having.
Cat. T12500 R.R.P. \$149
SPECIAL, ONLY \$129



SCOPE 60W SOLDERING SYSTEM

- Infinitely adjustable temp. 200 C to 470 C. Sliding control selects desired tip temperature (LED readout monitors tip temp.)
- Safety holder features ceramic burn-proof bush and can be converted to left-hand-side
- Cool and cool hand grip in pliable rubber.
- Screw type connector prevents accidental plug removal and guarantees solid contacts.
- Temperature lock allows production supervisors to control soldering temperatures.
- Anti seize tip retention design reduces risk of thread seizure by removing locking nut to cooler end of barrel.
- Optional 30W soldering pencil is available for finer work.

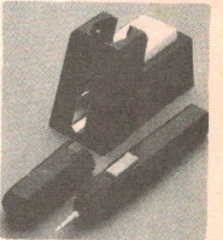
Cat. T12900 Normally \$229
SPECIAL, \$199



CORDLESS RECHARGEABLE SOLDERING IRON


- Built in solder point illumination
- Easy replacement of solder tip
- Protective stand which also functions as charging unit
- Sponge pad attach to stand
- Plug pack power adaptor
- Includes Nicad battery
- Instruction manual
- 12 months warranty

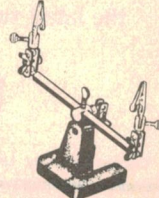Cat. T12480 Normally \$79.95
SPECIAL, \$69.95




PC BOARD HOLDER

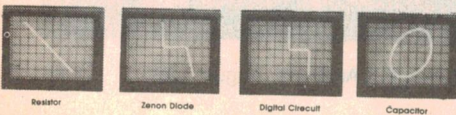Better than an extra pair of hands!
A must for all PCB work.
Cat. T12444 \$9.95



Audio Audio Audio Audio

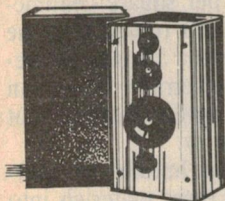TOLL FREE
008 33 5757
MAIL ORDER NUMBER
(STRICTLY ORDERS ONLY)
INQUIRIES TO (03) 543 7877



VIFA/AEM 3 WAY SPEAKER KIT!

This superb 3 way speaker kit competes with systems that cost 2-3 times the cost of these units! (which may even be using VIFA drivers etc.) Never before has it been possible to get such exceptional value in kit speakers! Call in personally and compare for yourself!

The system comprises...
2 x D19 dome tweeter
2 x D75 dome midrange
2 x P25 woofers
2 x pre-built quality crossovers
The cabinet kit consists of 2 knock-down boxes in beautiful black grain look with silver baffles, speaker cloth, innerbaffle, grill clips, speaker terminals, screws and ports.

D19 DOME TWEETER SPEAKER SPECIFICATIONS

Nominal Impedance: 8 ohms
Frequency Range: 2.5 - 20kHz
Free Air Resonance: 1.700kHz
Sensitivity 1W at 1m: 89dB
Nominal Power: 80 Watts
(to: 5,000Hz, 12dB/oct)
Voice Coil Diameter: 19mm
Voice Coil Resistance: 6.2ohms
Moving Mass: 0.2 grams
Weight: 0.28kg


D75 DOME MIDRANGE SPECIFICATIONS

Nominal Impedance: 8 ohms
Frequency Range: 350 - 5,000Hz
Free Air Resonance: 300Hz
Sensitivity 1W at 1m: 91dB
Nominal Power: 80 Watts
(to: 500Hz, 12dB/oct)
Voice Coil Diameter: 75mm
Voice Coil Resistance: 7.2ohms
Moving Mass (incl. air): 3.6 grams
Weight: 0.65kg

P25 WOOFER SPECIFICATIONS

Nominal Impedance: 8 ohms
Frequency Range: 25 - 3,000Hz
Free Air Resonance: 25Hz
Operating Power: 5 watts
Sensitivity 1W at 1m: 89dB
Nominal Power: 100 Watts
Music Power: 100 Watts
Voice Coil Diameter: 40mm
Voice Coil Resistance: 5.7ohms
Moving Mass (incl. air): 44 grams
Thiele/Small Parameters:
Qm: 3.15
Qe: 0.46
Qt: 0.40
Vas: 180.1
Weight: 1.95kg

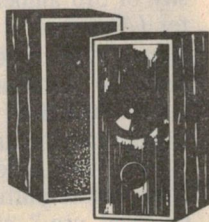Complete Kit Cat.K16030 **\$1,199**
Speaker Kit Cat.K16031 **\$949**
Cabinet Kit Cat.K16032 **\$349**



VIFA/AEM 2 WAY SPEAKER KIT!

This exciting new speaker kit, designed by David Tillbrook (a name synonymous with brilliant design and performance) uses VIFA's high performance drivers from Denmark. You will save around \$800 when you hear what you get from this system when compared to something you buy off the shelf with similar characteristics. Call in personally and compare for yourself!

The system comprises...
2 x P21 Polycone 8" woofers
2 x D25T Ferrofluid cooled dome tweeters with Polymer diaphragms
2 pre-built quality crossovers
The cabinet kit consists of 2 knock-down boxes in beautiful black grain look with silver baffles, speaker cloth, innerbaffle, grill clips, speaker terminals, screws and ports.

D25T SPEAKER SPECIFICATIONS

Nominal Impedance: 6 ohms
Frequency Range: 2 - 24kHz
Free Air Resonance: 1500Hz
Operating Power: 3.2 watts
Sensitivity 1W at 1m: 90dB
Nominal Power: 90 Watts
Voice Coil Diameter: 25mm
Air Gap Height: 2mm
Voice Coil Resistance: 4.7ohms
Moving Mass: 0.3 grams
Weight: 0.53kg

P21 WOOFER SPECIFICATIONS


Nominal Impedance: 8 ohms
Frequency Range: 25 - 4,000Hz
Free Air Resonance: 33Hz
Operating Power: 2.5 watts
Sensitivity 1W at 1m: 92dB
Voice Coil Diameter: 40mm
Voice Coil Resistance: 5.8ohms
Moving Mass: 20 grams
Thiele/Small Parameters: Qm: 2.4
Qe: 0.41
Qt: 0.35
Vas: 80.1
Weight: 1.65kg

Complete Kit Cat.K16020 **\$799**
Speaker Kit Cat.K16021 **\$649**
Cabinet Kit Cat.K16022 **\$209**



OMNI-DIRECTIONAL WIRELESS MICROPHONE

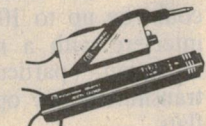Tunable: 92 - 104MHz
Freq. Response: 50 - 15kHz
Range: Over 300 feet in open field.
Modulation: FM
Power Source: 9V Battery
Type: Electret Condenser
Dimensions: 185 x 27 x 38mm
Weight: 160 grams
Cat. A10450 **\$19.95**



CRYSTAL LOCKED WIRELESS MICROPHONE AND RECEIVER

MICROPHONE SPECIFICATIONS:
Transmitting Frequency: 37.1MHz
Transmitting System: crystal oscillation
Microphone: Electret condenser
Power Supply: 9V battery
Range: 300 feet in open field
Dimensions: 185 x 27 x 38mm
Weight: 160 grams
RECEIVER SPECIFICATIONS:
Receiving Freq: 37.1MHz
Output Level: 30mV (maximum)
Receiving System: Super heterodyne crystal oscillation.
Power Supply: 9V Battery or 9V DC power adapter.
Volume control
Tuning LED
Dimensions: 115 x 32 x 44mm
Weight: 220 grams
Cat. A10452 **R.R.P. \$113**
Our price, **\$99**



SUPERB NEW VIFA/EA 60+60 SPEAKER KIT!

The new Vifa EA 60+60 loudspeaker kit has been designed to completely outperform any similarly priced speakers. This is a 2-way design incorporating drivers which give a deeper, more natural bass response and 19mm soft-dome ferro fluid cooled tweeters which provide clear, uncoloured sound reproduction.

These Vifa drivers are identical to the ones used in such fine speakers as Mission, Rogers, Bang & Olufsen, Monitor Audio and Haybrook just to name a few. Some of which cost well over \$1,000 a pair!

The dividing network is of the highest quality and produce no inherent sound characteristics of their own; they simply act as passive devices which accurately distribute the frequency range between both drivers in each speaker.

The fully enclosed acoustic suspension cabinets are easily assembled. All you need are normal household tools and a couple of hours and you've built yourself the finest pair of speakers in their class!

D19 TWEETER SPECIFICATIONS

Nominal Impedance: 8 ohms
Frequency Range: 2.5 - 20kHz
Free Air Resonance: 1.700kHz
Sensitivity 1W at 1m: 89dB
Nominal Power: 80 Watts
(to: 5,000Hz, 12dB/oct)
Voice Coil Diameter: 19mm
Voice Coil Resistance: 6.2 ohms
Moving Mass: 0.2 grams
Weight: 0.28kg
Cat. C10301 **\$38**

C20 WOOFER SPECIFICATIONS

Nominal Impedance: 8 ohms
Frequency Range: 35 - 6,000Hz
Resonance Frequency: 39Hz
Sensitivity 1W at 1m: 90dB
Nominal Power: 50 Watts
(12dB/oct)
Voice Coil Diameter: 25mm
Voice Coil Resistance: 5.5 ohms
Moving Mass: 15 grams
Cat. C10322 **\$89**

Kat. K86092 (speakers only) **\$379**
Kat. K86091 (complete kit) **\$449**



PHILIPS SPEAKERS

This month we are offering 20% off these prices! But, you'd better be quick as this offer is limited.
Description Cat.No. Price
AD0161078 (C12030) **\$24.95**
AD021605Q8 (C12040) **\$69.95**
AD80652W8 (C12042) **\$69.95**
AD070620M8 (C12045) **\$69.95**
AD12250W8 (C12050) **\$129.00**



PORTABLE MINI P.A. AMPLIFIER

A completely portable system, sets up anywhere in seconds. Inputs for microphone, electronic organ and cassette players. Variable echo makes this an ideal unit for buskers and budding singers.
SPECIFICATIONS:
Output power: 1W RMS, 2W max.
Frequency Response: 100-15kHz
Speaker: 5" full range, 4 ohms
Echo Time: Variable 5-52m/sec
Power Source: 6 x "D" size batteries (position for power adaptor also)
Size: 280(H) x 120(W) x 180(D)mm
Weight: 1.3kg
Cat. A12022 **\$89.95**

SENNHEISER HEADPHONES!!

The worlds best headphones are now available from Rod Irving Electronics! 3 models to choose from, other models are available on request! (Phone Tony DiPaolo on (03) 543 2166)



SENNHEISER HD 40

The HD40 is feather light, at just 60g! This HiFi stereo headphone is uncommonly convenient to use. Its systems can be rotated so it can fit into any drawer. It is also available as a TV headphone.
SPECIFICATIONS:
Frequency Range: 22 - 18,000Hz
Impedance: 600ohm
Distortion Factor: Approx. 1.5%; pressure on ear, approx. 1.3 N
Weight: Approx. 60g
Length of lead: 3 metres
Cat. A10515 **\$49.95**



SENNHEISER HD 410 SL

The HD 410 SL embodies all the advantages of the new "Slim-line" concept: brilliant sound characteristics with an optimum of sound volume combined with high wearer comfort.
SPECIFICATIONS:
Frequency Range: 20 - 18,000Hz
Impedance: 600ohm
Distortion Factor: Less than 1%; pressure on ear, approx. 2.5 N
Weight: Approx. 82g
Length of lead: 3 metres
Cat. A10518 **\$74.95**




SENNHEISER HD 540 REFERENCE

The HD 540 reference headphones are open dynamic stereo headphones. They are among the best ever made. Designed according to latest findings in acoustics, their reproduction is of extraordinary transparency and the highest transients fidelity. The test with a CD player shows: their acoustic properties are outstanding. The ear cushions play a major role. They provide a completely resonance-free treble reproduction up to 25 kHz and assure an impressively clear bass reproduction down to 16 Hz.
SPECIFICATIONS:
Frequency Range: 16 - 25,000Hz
Impedance: 600ohm per capsule
Harmonic Distortion Factor: Less than 0.4%
Contact Pressure: Approx. 3 N
Weight: Approx. 250g
Length of lead: 3 metres
Cat. A10519 **\$199**



1" DOME TWEETER SPEAKER

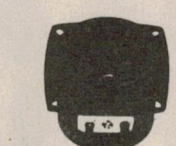Mylar diaphragm
SPECIFICATIONS:
Sensitivity: 95dB
Frequency Response: 2-20 kHz
Impedance: 8 ohms
Power RMS: 15 watts RMS
Magnet Weight: 5.4c.z.
Size: 96mm diameter
Cat. C10234 **\$10.95**



2" HORN TWEETER SPEAKER

Mylar diaphragm, aluminium voice coil
SPECIFICATIONS:
Sensitivity: 95dB
Frequency Response: 1.5-20 kHz
Impedance: 8 ohms
Power RMS: 10 watts RMS
Magnet Weight: 2.5oz.
Cat. C10232 **\$8.95**



5" MIDRANGE SPEAKER

Sealed back, foam edge, black cone, silver dust cap.
SPECIFICATIONS:
Sensitivity: 98dB
Frequency Response: 500-8 kHz
Impedance: 8 ohms
Power RMS: 10 watts RMS
Magnet Weight: 5.4oz.
Cat. C10230 **\$12.95**



6 1/2" TWIN CONE FULL RANGE SPEAKER

Foam edge, black cone, black whizzer cone
SPECIFICATIONS:
Sensitivity: 89dB
Frequency Response: 60-15 kHz
Impedance: 8 ohms
Power RMS: 10 watts RMS
Magnet Weight: 5.3oz.
Cat. C10222 **\$14.95**



8" TWIN CONE FULL RANGE SPEAKER

Foam edge, black cone, black whizzer cone
SPECIFICATIONS:
Sensitivity: 95dB
Frequency Response: 45-16 kHz
Impedance: 8 ohms
Power RMS: 30 watts RMS
Magnet Weight: 13oz.
Cat. C10224 **\$23.95**



8" WOOFER HIGH POWER SPEAKER

Cloth edge, dark grey cone, rubber mounting seal, cloth dust cap.
SPECIFICATIONS:
Sensitivity: 90dB
Frequency Response: 60-4 kHz
Impedance: 8 ohms
Power RMS: 50 watts RMS
Magnet Weight: 20oz.
Cat. C10226 **\$34.95**



10" WOOFER HIGH POWER SPEAKER

Cloth edge, dark grey cone, rubber mounting seal, cloth dust cap.
SPECIFICATIONS:
Sensitivity: 93dB
Frequency Response: 50-2.5 kHz
Impedance: 8 ohms
Power RMS: 100 watts RMS
Magnet Weight: 30oz.
Cat. C10228 **\$59.95**



12" WOOFER HIGH POWER SPEAKER

Cloth edge, dark grey cone, rubber mounting seal, cloth dust cap.
SPECIFICATIONS:
Sensitivity: 97dB
Frequency Response: 28-4 kHz
Impedance: 8 ohms
Power RMS: 50 watts RMS
Magnet Weight: 30oz.
Cat. C10229 **\$69.95**



Rod Irving Electronics

48 A Beckett St. MELBOURNE
Phone (03) 663 6151
425 High St. NORTHCOTE
Phone (03) 489 8866
Mail Order and Correspondence:
P.O. Box 620, CLAYTON 3168
Telex: AA 151938



MAIL ORDER HOTLINE

008 335757
(TOLL FREE)
(STRICTLY ORDERS ONLY)

LOCAL ORDERS & INQUIRIES

(03) 543 7877

POSTAGE RATES:
\$1 - \$9.99 **\$2.00**
\$10 - \$24.99 **\$3.00**
\$25 - \$49.99 **\$4.00**
\$50 - \$99.99 **\$5.00**
\$100 - \$199 **\$7.50**
\$200 - \$499 **\$10.00**
\$500 plus **\$12.50**

The above postage rates are for basic postage only. Road Freight, bulky and fragile items will be charged at different rates.


All sales tax exempt orders and wholesale inquiries to: RITRONICS WHOLESALE, 56 Renner Rd, Clayton, Ph. (03) 543 2166 (3 lines)

Errors and omissions excepted

*Apple and IBM are registered trade names



News Highlights

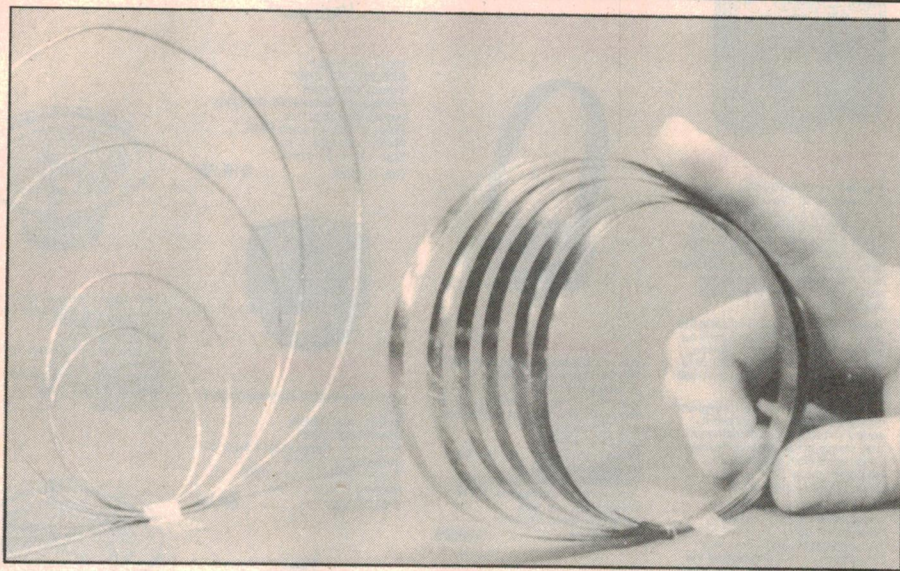

Toshiba produces wires and tapes of superconductor

Scientists working at Toshiba Corporation in Japan have developed superconducting wires and tapes, using the yttrium-barium-copper oxide superconductive ceramic material recently developed in various laboratories throughout the world (see EA July 1987, page 10).

Toshiba not only has helped to de-

velop the new material, but also marked another important step forward in the practical application. The company molded this material into thin wire rods with ceramic cores 0.6mm in diameter, and tape formulation 5mm wide, 0.1mm thick.

Moreover, the company's researchers processed these thin wires into silver-

covered coils of 2 centimetres in diameter and attained the critical current density of 510 ampere per square centimetre (A/cm^2) — a world record in these forms. Critical current density represents the maximum electricity which can be conducted in a given area without losing superconductivity.

"We have a lot of hurdles to overcome before putting these materials into practical use," says Fumio Miyashiro, manager of Toshiba's Metals and Ceramics Laboratory, "Ceramic superconductors are currently too brittle for practical applications. Also, critical current density is too small. We need to achieve at least 10,000 A/cm^2 ".

Mr Miyashiro says, however, that the exciting discoveries in the past few months regarding superconductors now make it possible to think about the previously unthinkable dream. "Who would have imagined a man could land on the moon forty years ago? We may, ultimately, be able to find superconductors that can operate at room temperature."

Toshiba has been pursuing research and development work on superconductivity for over 25 years.

The fruits of this research and development have already been applied in the company's magnetic resonance imaging (MRI) system — advanced medical equipment for image diagnosis. Toshiba is also a key participant in national projects in Japan for developing magnetically levitated trains and fusion power generators.

New software for Jindalee OTH radar

Computer Sciences of Australia has begun work on a \$6 million project to convert experimental software developed for the Federal Government's Jindalee Over-The-Horizon Facility into an operational system.

Up to 30 CSA software engineers will be employed on the contract over the next three years at the Defence Research Centre in Adelaide.

Jindalee is a revolutionary radar technique that enables surveillance over immense areas far beyond the limits of conventional radar. It detects targets by bouncing high frequency radio waves off the ionosphere.

The reflected radio energy is gathered by very large antenna arrays and analysed by a computer system that takes into account the frequently changing characteristics of the ionosphere.

The Department of Defence intends to build three operational Jindalee systems which will become an integral part in Australia's defence program.

CSA has worked on Jindalee for the past four years. The company has carried out software studies and made recommendations of future software and computer systems needs to the Defence Research Centre which is part of the Defence Science and Technology Organisation.

Wireless video transmitter standard

A draft standard that aims to protect television reception against interference from wireless video transmitters has been released by the Department of Communications.

The new standard is designed to cover video transmitters which provide

a "wire-free" connection between video recorders and television receivers.

According to DoC, any video transmitter connected to a power supply can cause interference to television receivers and to other types of radio communications equipment. In the case of a video transmitter with an excessive output power level, the "wire-free" link between the recorder and a receiver could be up to 100 metres. This could interfere with a neighbour's television reception, particularly where video transmitters are operated in a block of flats.

The new draft standard specifies the performance and effective range for video transmitters and, once it comes into force, all video transmitters sold in Australia would have to comply with the requirements.

Copies of the draft standard may be obtained by writing to the Assistant Secretary, Operations Branch, Department of Communications, Canberra.

Perth Electronics Show heading for a "sellout"

At the time of going to press with this issue, the 1987 Perth International Electronics Show was heading for a complete sellout in terms of exhibitors. According to Show manager Chris Gulland, this year looks like being at least as good as last year's show, if not better. There seems to be no doubt that the Perth Show has become the premier annual showcase for the Australian electronics industry.

Last year some 218 companies were represented at the show, in one capacity or another, and 93,600 trade and consumer visitors passed through the turnstiles. Of the latter, some 9,700 visitors were from overseas.

This year's show is being held from July 29 to August 2, at the Claremont showgrounds.

Philips CD players to be made in China

Philips of the Netherlands has established a 50%-50% joint venture with the Shenzhen Advanced Science and Technology Company (S.A.S.T. Ltd) of the People's Republic of China to manufacture and market laser optical systems including Laservision players and CD players and discs.

The signing of the joint venture contract and other main contract documents took place in Shenzhen on 16th May, 1987. The signing ceremony was attended by Mr Zhou Qie Wu, First Executive Vice Mayor of Shenzhen, Mr Zhu Yueh Ning, vice Mayor of Shenzhen and Mr Ye Hua Ming, Director of S.A.S.T., as well as Mr R.H. van Meurs, Managing Director of the product division Consumer Electronics of Philips and Mr C.J. Seelen, Senior Managing Director of Philips International, responsible for Philips activities in China.

Total investment for equipment will amount to 80 million Dutch guilders. The factory and the offices of the joint venture, named Shenzhen Shen Fei Laser Optical Systems Co. Ltd, are presently under construction and will be completed by the end of this year. Production facilities are being built to meet international requirements for high technology process industry. Personnel employed will eventually reach 500 persons. The products of the company will be mainly destined for the domestic market and will be sold under the Philips brandname. The remaining part of the production will be exported.



Australian data logger monitors body temperature of Antarctic researchers

An Australian-made electronic data logger will record the body temperature of survey staff during field work on the ice plateau beyond Casey station during 1987.

The temperature recordings will be used to probe a possible link between low body temperature and gastro-intestinal disorders in traverse personnel. The project is directed by Dr Peter Gormly, Senior Medical Officer, and Dr Des Lugg, Assistant Director, or the Polar Medicine Branch, in the Antarctic Division of the Department of Science, which is based near Hobart. At Casey Station the program is supervised by Dr Vernon Moo.

Dr Gormly said that for some years there had been reports of gastro-intestinal disease in polar survey teams. He said it was known that moderate hypothermia (34-35 degrees C) disturbs the function of the stomach, reducing the quantity of gastro-intestinal secretions. Below normal body temperature was a possible cause of the gastro-intestinal problems, Dr Gormly said. Normal body temperature is 38.4 degrees C.

During the project, members of a glaciological survey team will "wear" a DT100 **Datataker** for 24 hour periods in turn. The **Datataker** will record temperatures sensed by two YSI number 401 probes. One probe will emerge from the outer clothing near the neck, and will measure air temperature. The

other probe will be inserted rectally, and will measure deep body temperature.

Readings from both probes will be recorded automatically every five minutes by the **Datataker**, which has an inbuilt power supply and 24K of memory for storing information.

At the end of each 24-hour period, the team will answer a questionnaire about gastro-intestinal symptoms. The questions will be asked impersonally by a portable computer previously programmed with the questionnaire, and the answers entered directly by the team member. At the same time, the temperature records from the **Datataker** will be downloaded into the computer and, together with the data from the completed questionnaire, transferred to cassette tape for storage. The **Datataker** will then pass to the next team member for another 24-hour periods.

Dr Gormly expects that after two major traverses scheduled for 1987, there will be enough information to establish whether low body temperature is a factor in the gastro-intestinal problems.

One of the **Datataker's** designers, Mr Graham Henstridge, spent two years at Casey and Mawson working as an electronics engineer. Mr Henstridge is now a partner in Data Electronics, the Melbourne-based manufacturer of the **Datataker**.

News Highlights

Plessey to make Army's communications system

A \$350 million contract has been signed between the defence manufacturer Plessey Australia and the Australian Government. Plessey will now begin Australian production of some 2000 HF and 3900 VHF radios, plus associated ancillary and frequency management systems.

All equipment, including computerised battlefield service and repair facilities, is currently being field trialled by the Australian Defence Force.

Code named RAVEN, the system incorporates the latest advances in tactical communications systems including highly sophisticated state of the art technology to prevent eavesdropping or

jamming during field operations.

RAVEN is designed to perform in a wide variety of harsh climatic and electronic warfare situations, and provides simple "user friendly" operations for soldiers whether on foot, in four wheel drive, armoured vehicles or in command posts. It has been developed in Australia by Plessey in co-operation with its UK parent.

Welcoming the contract — the largest Australian defence contract ever received by the company, the Managing Director of Plessey (Australia), Mr Edwin Matiuk said RAVEN would provide a substantial impetus to Australia's electronics industry.

"Jobs, export opportunities and the further development of technology at the highest levels will all result from the Government's decision to proceed with RAVEN," he said. "We have already established advanced production facilities at our Sydney manufacturing plant.

"With this as a base, Plessey will now be able to manufacture state of the art defence communications systems to friendly nations throughout the Pacific Region."

Mr Matiuk said that to enhance RAVEN's development, Plessey had encouraged the manufacture of locally produced high technology components, many of which were now being evaluated for suitability in like projects overseas.

In total it is expected that more than 600 jobs will result at Plessey's Meadowbank plant and through the provision of components and assemblies by external manufacturers.

Shown here signing the Army contract are (left to right) Duncan Spencer and Edwin Matiuk of Plessey, Fred Bennett and Bill Drysdale of the Department of Defence, and Major General Duncan Francis, Chief of Army Materiel.

Freezeframe video camera

A new device which freezes video images and delivers a choice of high quality instant colour prints or 35mm slides from a range of video sources, is now available in Australia. The Polaroid FreezeFrame Video Recorder, a joint Polaroid and Toshiba design and

development project, captures and digitises an image field at the touch of a single button. Pushing a second button produces the instant prints and slides.

Currently available only in an NTSC configuration, FreezeFrame is the first relatively low cost device which simply

and quickly delivers photographic still images from video.

Polaroid believes that when the PAL version of FreezeFrame is in production, the new recorder will satisfy a broad range of previously unfulfilled video imaging needs in Australia.



The NTSC FreezeFrame has so far been proven to work with video sources which operate at 15.75kHz in the RGB analog or TTL mode, or can be converted to do so, such as computers and high technology medical video imaging devices.

The current model FreezeFrame Video Recorder digital freeze field device captures NTSC television signals off air, or from such standard video sources as cameras, VCRs or disc players and computers. It comprises an imaging unit with interchangeable instant print and 35mm film backs, and a keyboard type control unit.

The recorder produces instant 4x3 inch self-developing colour prints on Type 339 AutoFilm, at the push of a button, from its Polaroid CB-33 AutoFilm camera back. AutoFilm prints match the 4:3 aspect ratio of standard video displays and once ejected from the BC-33 back, develop themselves in ordinary light.

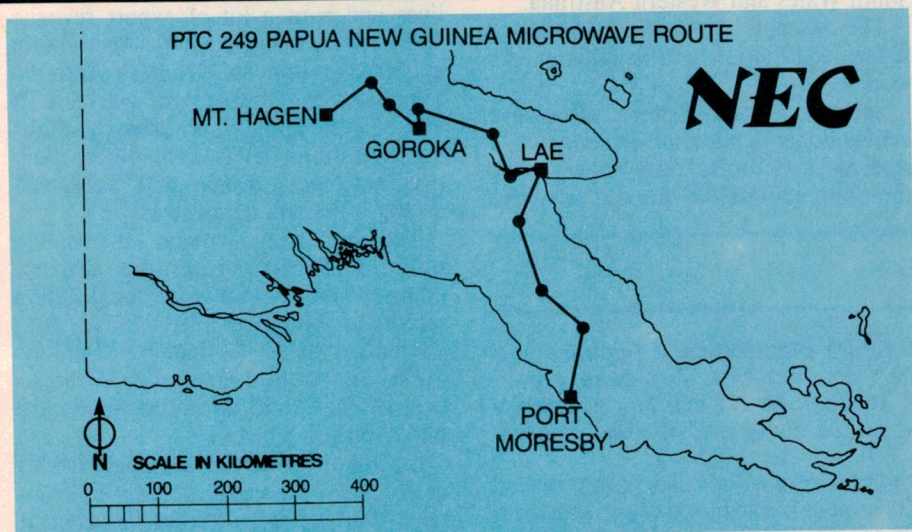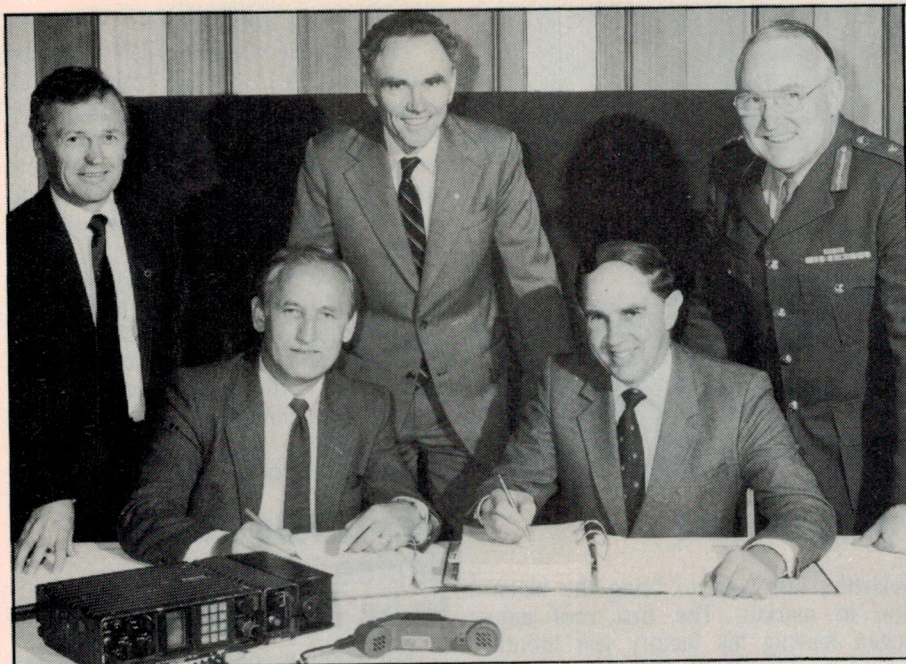With its alternate 35mm motorised camera back, the system produces Polaroid instant 35mm slides or conventional 35mm images. Polaroid instant slide films are developed in a minute, in the Polaroid AutoProcessor and ready immediately after for cutting, mounting and projection.





NEC to supply microwave system for PNG telephones

NEC Australia has been awarded an export contract worth several million dollars to supply a turnkey microwave system across the rugged mountains of Papua New Guinea.

Average altitude of the microwave repeater stations along the 677 kilometre route will be 2800 metres (9,000 ft). Access to all but two of the repeater sites is by helicopter.

The system, ordered by the Post and Telecommunication Corporation of Papua New Guinea, will upgrade and expand telephone communications between Port Moresby, Lae, Goroka and Mount Hagen.

It will use NEC's 550 Series low power consumption equipment, with 960 channel capacity on each bearer. This equipment is specially designed for remote solar powered sites such as occur in the Papua New Guinea highlands.

The project also involves the establishment of a network control centre which will eventually gather data from all major microwave bearers in Papua New Guinea.


The Export Manager of NEC Australia, Mr John Norton, said this week: "Our success in this project shows that NEC Australia can be competitive in export markets. It is also a demonstration of the high level of cooperation and support between NEC Australia and NEC Corporation, Japan, in developing into new areas".

BYTEK[®]

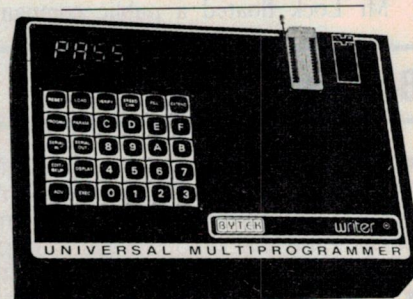(E) EPROM PROGRAMMER WRITER — 1[™]

The WRITER-1[™] is a low cost fully Stand Alone (E) EPROM Multi Programmer. (E) EPROM programming is achieved internally within the main unit. All voltages and wave forms required are generated under software control — No personality modules or adapters are required.

The WRITER-1[™] provides serial data input and output through its RS232 Port. Both downloading and uploading to a host computer are supported.




Features

- Single 28 pin ZIF Socket
- 30 Key Full Travel Keyboard
- 6 Character 0.6" 7 Seg LED
- 32K BYTE x 8 RAM (256 K Bit)
- Programs all popular single voltage EEPROMs & EPROMs from 2716-27256.
- Fast Intelligent Algorithms
- Formats: 12 Popular Formats
- Baud Rates: 110-9600
- PromSoft[™] IBM-PC Compatible Software Driver Available

SCIENTIFIC DEVICES AUST P/L

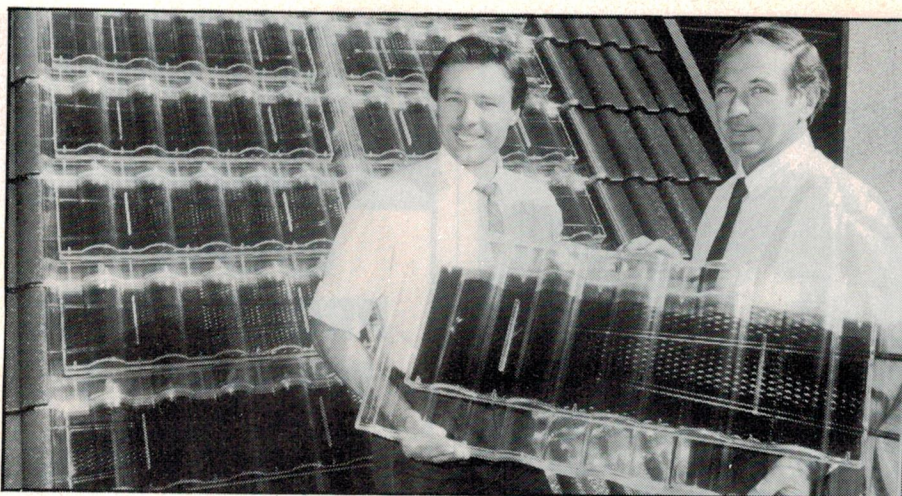- MELBOURNE 03-579 3622
- SYDNEY 02-95 2064
- ADELAIDE 08-255 6575



Australian solar invention goes on sale

An award winning Australian inventor has begun selling his highly acclaimed Solartile solar roofing system. Ken Lock won the Esso Energy Award for his unique design, which places solar panels within the normal roof line of a house or commercial building.

The panels are claimed to be more energy efficient than conventional solar collection units, as well as being more attractive.

Mr Lock floated a public company,

Solartile, last year to bring the invention to market. The first roof units began leaving his factory last month, bound for markets in Queensland, New South Wales and Western Australia.

The Solartile system is backed by a strong distribution and installation network.

Solartile panels replace sections of conventional ceramic or cement tiles or steel decked roofs. They fit flush with the roof material to present a normal

weather proof surface.

The Solartile is made of UV stabilised toughened clear acrylic with a black chrome solar collection panel mounted beneath it. Each Solartile takes the place of three conventional concrete tiles. Twelve Solartiles are sufficient to service a 300 litre (60 gallon) storage tank.

"The idea came to me because of the number of people who like the idea of solar-heating, but wanted less obvious collection units", said Mr Lock, a Sydney builder. "It's taken several years to perfect the technique of flush-mounting solar panels to make them virtually invisible on the roof".

Life-saving aviation device to be developed in SA

An aviation collision avoidance system with the potential to save many lives and earn a lot of export revenue will be developed in South Australia in a joint venture by Duntech International and the University of Adelaide. It will prevent mid-air collisions by allowing aircraft to detect each other, identify each other's courses and speeds and establish the risk of collision.

The increasing volume of aviation traffic worldwide makes the development of the system vital for aviation safety. In September 1986 a survey conducted by the 39,000 member Air Line Pilots' Association in the United States showed that "mid air collisions are the pilots' biggest concern."

Mr John Dunlavy, Managing Director of Duntech International and the inventor of the system, said it was anticipated that the air to air collision avoidance system would be flight tested within two years. "If successful, it will represent the only known system in the world affordable for both commercial and private aircraft."

The South Australian system is expected to cost between \$5,000 and \$10,000 compared to an expected \$80,000 for a system being proposed by the US Federal Aviation Agency. "Furthermore, we believe our system is technologically superior to the American system," Mr Dunlavy said.

The development of the system by Duntech International and the University of Adelaide's Electrical and Electronic Engineering Department will take place under the National Teaching Company Scheme sponsored by the Department of Industry, Technology and Commerce.

Business Briefs

- Mike Wilson, managing director of **Dick Smith Electronics** in Australia and New Zealand since March 1984, resigned on 25th May. He gave parent company Woolworths Ltd three months' notice. Mr Wilson is apparently considering the various ways to capitalise on his considerable experience in the computer and electronics industries.

- **Atari Corporation** is to set up its own subsidiary in Australia, to handle all Australian and Asia Pacific business. Existing distributor Mobex is to become a shareholder in the new subsidiary, which will be headed by Nigel Shepherd — recently president of Commodore in the USA.

- **Austral Standard Cables**, a division of Metal Manufacturers, has won the \$6.2 million Telecom contract for stage 2 of the east-west optical fibre cable link between Perth and Port Augusta. ASC will be supplying 75% of the 1500km long 14-fibre single mode non metallic fibre optic cable. Two of the fibres will be carrying information for the Australian National Railways, the remaining 12 an estimated 50,000 simultaneous telephone connections and data for Telecom.

- **E.S. Rubin Marine** is now the Australian agent for Marconi's Oceanray satellite communication system, and also for "Francis" searchlights.

- **Scalar Industries**, manufacture of a wide range of antennas for UHF, VHF, HF, marine and CB, has changed its name to Scalar Antennas.

- **Anitech** is now the exclusive Australian distributor for Keyence, Japanese maker of photoelectric sensors.

- **Oliver J. Nilsen (Aust)** has acquired the New Zealand test and measuring equipment company GTS Engineering, continuing the expansion begun earlier in the year with the acquisition of Datac Digital Systems.

- **Solar '87**, a conference to examine the use of renewable energy resources, will be held in Canberra at the Australian National University, from November 26-28 1987. Further information is available from John Balingier, School of Architecture, the University of NSW, PO Box 1, Kensington 2033.

Who said Men don't cry?

To say that men don't cry is to say that men don't have emotion. It is to say that man is not moved by the birth of a child; by the visual splendour of nature, or the sensitivity of a song.

It was the emotional desire of Saul Marantz which set him on the mission of establishing standards in the science of sound reproduction that were to surpass laboratory levels of excellence and become the statement in technical superiority.

For 35 years Marantz has maintained that proud tradition whilst elevating the concept of sound reproduction to an art form.



The PM94 Stereo Amplifier, the latest in a line of new era Marantz audiophile components, has won Australia's highest award for excellence, the CESA Hi Fi Grand Prix, and is consistently winning acclaim from internationally prestigious publications like "Hi Fi News and Record Review" of the U.K.

So listen with your heart and experience the expression of emotion through the science of sound: Marantz.



marantz®

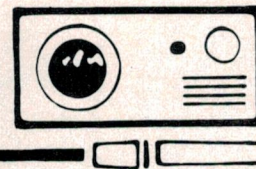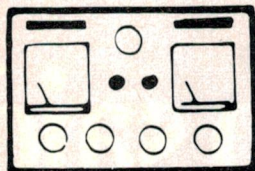For your nearest Marantz Audiophile Dealer and a brochure, phone Marantz on (02) 939 1900.



A journey into unfamiliar territory

Like many doctors, the majority of electronics service technicians find themselves dealing with fairly familiar problems most of the time. But every so often, there are jobs that take you into areas where you really don't have much experience at all.

I'm sure that to the average consumer nowadays, one home appliance is much like another. They all tend to have knobs and switches on the front, and generally there's at least some electronics inside. So when they become faulty, where else would you seek help but from the local serviceman?

Of course this is not at all unreasonable, because often there isn't anywhere else to go apart from the service department run by the manufacturer or importer. And in the case of fairly exotic equipment, there may be only one such place in the country — so sending back a costly or bulky piece of equipment may well be impractical.

From the customer's point of view, taking it to the local serviceman is entirely logical. But for those of us on the other side of the counter, it can provide some real challenges.

In a lot of cases, you may never have seen one of these gadgets before, and quite possibly may never see one again. So before you can tackle the actual job of finding the fault, there's often a need to familiarise yourself with the equipment and how it works. This can make the job very time consuming, and consequently run up a sizeable bill for labour alone.

There's also the possibility that the equipment will contain some unusual components (perhaps not even electronic, but mechanical), which will not be part of your normal replacement stock. So you may have to order them in, even to try making a few substitutions. Not an entirely happy prospect, especially when Murphy's Law generally operates to ensure that the fault turns out to be somewhere else!

All in all then, for the serviceman this kind of job can turn out to be anything but straightforward. Yet when a customer fronts up with one, there's a natural desire to try and help out — despite the likely hassles.

Faulty projector

But enough preamble. The actual story which illustrates what I've been talking about concerns a home movie projector, and a fairly fancy one at that. It was a French make, a Beaulieu model 708EL super-8 sound machine. One of my old colleagues who was fairly keen on home movies before the coming of video tells me that at one stage (not all that long ago), it was regarded as pretty close to the "Rolls Royce" of such machines. It apparently sold for a lot of money — two or three times that of the more popular makes.

The story began when a chap rang up to ask if I did repairs on movie equipment. I was a bit light on for work at the time, and although I had the vague feeling that I might be letting myself in for something I might regret, I volunteered that I did so occasionally. In an effort to be helpful, I enquired as to the nature of the problem.

It turned out that he was a professional man, and had bought the projector overseas on a business trip. As a movie enthusiast he'd always wanted to own "the best", and it had been a good opportunity to pick one up at a good price.

Apparently it had operated perfectly up until a few weeks before, with excellent pictures and sound. But then, the customer explained, it started to play up and "mince the film" — losing its loops

and ripping sprocket holes. But only when you were projecting sound films, he stressed; for silent projection it was still fine.


It sounded as if it could well be a mechanical problem rather than electronic, so I offered this as a possibility. Perhaps it would be better, I added, if he contacted the Australian distributor for Beaulieu. Presumably they would have a suitably equipped service department, with technicians more familiar with this equipment than I — plus a suitable stock of whatever special parts might be required.

But he was one jump ahead. He'd already found out that the distributor, Interdyn, was based in Melbourne. In order to have them look at it, he would need to pack it all up in a suitable box, well padded, and send it for hundreds of miles. As it had cost a lot of money and was a fairly delicate piece of equipment, he wasn't too keen on the prospect. Couldn't I have a look at it, and at least advise whether or not the problem was one that justified sending to Melbourne?

That didn't seem too unreasonable, so I agreed. Consequently a couple of days later, the said item was gingerly placed on my counter together with the driving manual and a reel of not-too-valuable film. I had explained to the customer that the last named of these would be necessary, because not tackling this kind of job very often, I had no test films on hand.

Needless to say the first thing I did was attempt to thread up the film and try it out. This should have been simple, because the machine was one of those fitted with automatic threading. You poke the end of the film in a slot, whereupon the projector grabs it and takes it around the various sprockets, through the picture gate, around the sound drum and out the other end ready to clip onto the takeup reel.

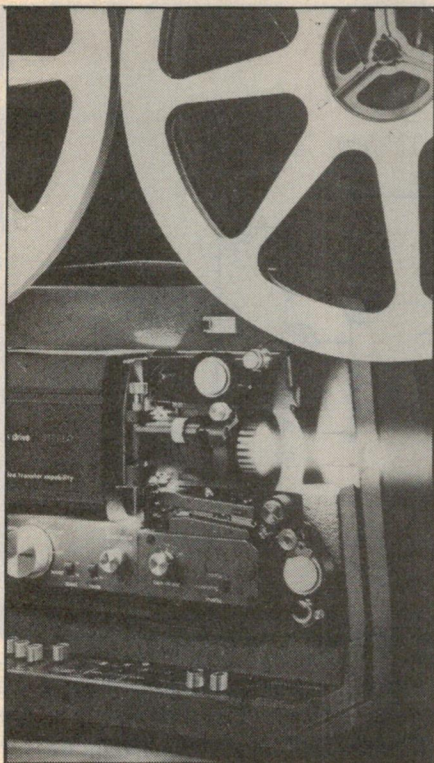But here I struck the first snag, because when I tried it, the front of the film seemed to hit some obstacle just below the gate, and begin buckling out. After checking carefully that there was no obvious mechanical problem, I finally discovered that the leading end of the film had to be cut square but with chamfered corners, and even kinked



A close-up of the Beaulieu 708EL projector. The capstan, pinch wheel, sensing roller and lower sprocket described in this month's story are visible at lower right, below the lens.

over slightly. Then it would at least thread up correctly.

Next I tried turning the machine on for silent projection. As the customer had noted, everything seemed to operate normally. The picture was bright and steady, and the film loops seemed perfectly stable. No problems at all . . .

Graunching noises

Then I turned the main control knob to the last running position, for sound projection. Everything seemed OK for about 30 seconds, but then the film loop between the picture gate and the sound heads started shrinking and finally disappeared. In the few seconds before I could turn everything off the picture started jumping madly, the sound became badly distorted and there was the awful sound of film being graunched and its sprocket holes torn.

Obviously the customer was right — something was definitely wrong when the projector was set for sound projection. It was time to take off the back cover and look for some clues as to the cause.

The first thing I noticed when the cover came off was that instead of a single drive motor, as in most of the projectors I had seen before, there were

two. The larger of the two was obviously driving the main picture projecting mechanism: the sprockets, shutter and intermittent "claw", plus the cooling fan for the lamp. This was of the modern quartz-halide type, complete with its own built-in mirror.

The other, much smaller motor appeared to be a DC type, which was arranged to drive the sound smoothing flywheel via a small rubber belt. The flywheel was on the end of a spindle, which on the other end formed what was effectively a capstan, just as in a tape recorder. There was even a very familiar looking pinch roller, to press the film against the capstan.

So far so good. By careful inspection with the power off, I discovered that when the projector was set for silent projection, the pinch roller did not press the film against the capstan. Aha — that must mean that in this mode of operation, the film was driven through the machine purely by the sprockets, from the main motor.

But when you switched the main control to the sound position, the pitch roller moved over to force the film against the capstan. So obviously this was where the second motor and sound flywheel came into the picture (sorry for the pun!).

Somehow the sound motor must normally be synchronised with the main motor, or vice-versa. Otherwise, the film would be trying to run at two different speeds, with all sorts of horrible effects rather like those we were actually getting. The question was, how were the two motors supposed to be locked to the same speed?

A bit of further investigation revealed that a film guide roller that was rigidly locked in position between the sound capstan and the final drive sprocket, for silent projection, became moveable in sound mode. It could swing in a small arc, against a tension spring, and was able to sense the length of film between the capstan and the sprocket.

By peering behind the sound flywheel inside the bowels of the machine, I could see a small strip of metal passing through a block. When I moved the film sensing roller back and forth through its arc, the strip slid to and fro inside the block. Since the block had a small terminal strip with six wires attached, leading back to the most visible PC board, it was evident that the metal strip and the block it passed through formed a sensor that was used to feed back the film loop size and control the speed of one of the motors.

This discovery prompted me to turn

on the projector without any film, and switch the main control to the sound position. I then moved the sensing roller back and forth gently by hand, listening to see if I could hear or see any change in speed by either of the motors. There wasn't a skerrick.

Fairly obviously this was the real cause of the trouble. Without any ability to vary motor speed, there was no possibility of locking the two motors to run at the same speed. But what had gone wrong to stop this simple "servo mechanism" from working?

By this time I realised that it must be the main picture motor whose speed must be controlled, not the sound motor. Simple really, because if the sound motor were to be controlled the sound speed would be varying up and down either way to match the average picture motor speed, and you'd hear a most awful "wow" in the sound. So it must be the sound motor that stayed fixed as the reference, and the picture motor that was brought into lock with it. Normally, that is . . .

Circuit wanted


Unfortunately it was now also becoming clear that I was going to need a circuit schematic, and preferably at least a basic rundown on circuit operation, if I were to track down the fault without spending a huge amount of time. And by now I was pretty well "hooked" on the challenge of finding it — the idea of packing it all up and telling the customer to send it to Melbourne just wasn't on.

So the next thing was to ring up the Interdyn people in Melbourne, to see if they could provide any circuits or other service information. They could, it turned out, and would send them by priority mail. I left the projector with a dust cover over it on the end of the bench, and went on with a few other jobs that had turned up.

When the envelope turned up a couple of days later, it had some photocopies of circuits plus a description of the operation of the motor locking system and how it was normally adjusted. There were also a few suggestions as to the likely cause of the trouble, from the friendly Interdyn service guy.

It didn't take long to see that my initial deductions were on the right track (whew — haven't entirely lost the knack!). It was indeed the main picture motor whose speed was controlled in the sound projection mode, and the mysterious little block and sliding strip turned out to be a photo sensor.

The sliding metal strip had a central

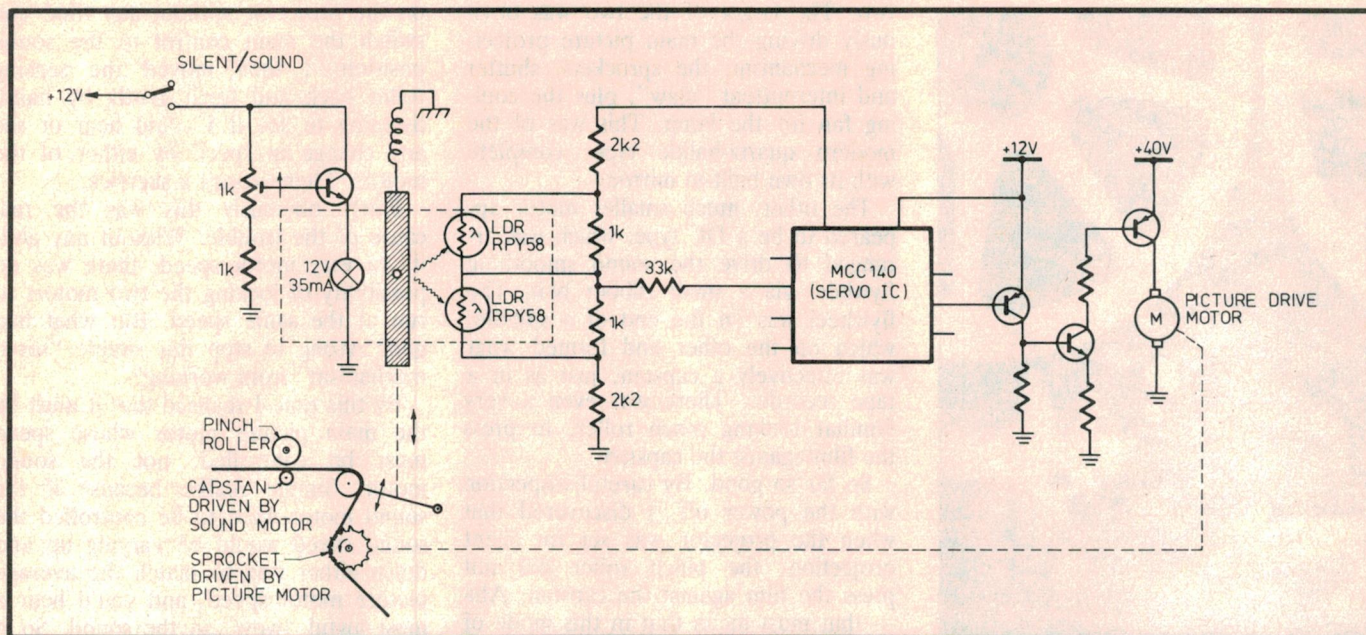

Here is the basic idea of the motor locking system used in the Beaulieu 708EL projector. For sound projection, a capstan and pinch wheel driven by one motor pulls the film past the magnetic heads at a constant speed. To lock the picture motor to the same speed, a sensing roller is used to monitor the size of a film loop between the capstan and the final sprocket. A simple position sensor using two LDRs and a lamp, is used to drive a servo IC and control the speed of the picture drive motor — normally that is!

hole about 3mm diameter, and slid between a small filament lamp and a pair of light dependant resistors. These were arranged so that when the metal strip was in the mid position, they each received a small amount of light from the lamp. This corresponded to the correct "locked" position of the film sensing roller, with the film loop neither too big nor too small.

But when the film loop size varied up or down, the metal strip was pushed one way or the other, and one LDR received more light while the other got less. The circuit was obviously arranged to correct this by bringing about an opposing change in the speed of the picture drive motor. The service information even showed how to achieve the correct swing in motor speed, in response to swinging the sensor roller through its arc, by setting a pot which adjusted the brightness of the sensing lamp.

The screed also explained how to measure picture motor speed with a CRO, by taking advantage of a reed switch and magnet setup which was attached to the main drive shaft. This was apparently used for synchronising the projector with a tape recorder, when required.

Of course when I tried it all out again, following the approved procedure, I got the same results as before. You could swing the sensing roller back

and forth through its full arc, and the speed of the picture motor didn't vary one iota.

Checking with the circuit showed that the two LDRs were connected into a resistive divider, and the divider point voltage was fed into one input of a rather unfamiliar looking IC with the designation "MCC140". This looked to be fairly complex, controlling not only the picture motor but the sound motor as well. It had inputs for signals from not only the LDRs and a set of pots for adjusting the various speeds, but from what appeared to be alternators built into each motor as well. Presumably these were for feedback and maintaining the correct speeds.

There's no point in worrying about the full circuit, as most of it didn't turn out to be relevant. The essential part from the point of this story is shown in the diagram.

The whole setup around the MCC140 was a bit daunting, and I didn't like to think about the possibility that the IC itself could be faulty. It looked a special purpose device, and there could well be a problem tracking down a replacement.

Still, there was no point in crossing bridges before I came to them. The first thing was to check if the optical sensing scheme was working. Who knows, it might be something simple, like a blown lamp. This would certainly be capable of causing the trouble.

But when I identified the leads to the lamp and gingerly disconnected them, a quick check with the multimeter showed that the lamp filament was intact. The emitter follower circuit feeding the lamp also checked out normally. So there was nothing amiss on the lamp side of the circuit.

The next thing was to look at the midpoint of the voltage divider, between the two LDRs, with the power on. There should be a variation in voltage when the film sensing roller was moved back and forth. Aha — nothing at all!

In fact the voltage stayed as steady as a rock, even on the LDR side of the 33kΩ resistor. This suggested that the problem was right at the LDRs themselves, not inside the input circuit of the IC. I started to breathe a sigh of relief — but rather prematurely, as it happened.

Turning off the power again, I delved into the back again and lifted the leads from the LDR connections on the sensor block. A quick check with the meter showed that the resistors of the divider itself were OK. That left the LDRs themselves, but these were not easy to check buried as they were inside the block.

Strange LDRs

Still, by connecting some temporary leads and turning on the power again, I was able to determine that there was

definitely something very strange about those LDRs. Moving the film sensing roller back and forth produced a modest change in resistance for one of them, but none whatever in the other. It was completely open circuit.

Even the one that did respond only came down to an "illuminated" resistance of about 15kΩ, which would hardly be capable of producing much voltage change with a parallel resistor of 1kΩ. Obviously they were both faulty.

So I had at last found the cause of the trouble, but I was not out of the woods yet, by a long chalk.

From the circuit I learned that the LDRs were type RPY58, apparently a miniature cadmium sulphide type made originally by Philips. But a quick check with Philips Elcoma revealed that this type had not been made for years. Nor was there any current replacement type available — apparently no-one uses LDRs much anymore.

What to do now? For a few minutes I gave thought to the prospect of re-designing the circuit, so it would accept some alternative components to the LDRs. One possibility was a pair of silicon photodiodes, driving junction FETs.

Then I suddenly remembered an old colleague, who had worked at Philips Elcoma for quite a few years earlier in his career. Perhaps he might be able to suggest where to try looking for a pair of the long-lost LDRs.

When I rang him, he did better than that. In fact, by sheer good luck he happened to have a small number of RPY58s, which he had bought some years ago for a project that fell flat. They were brand new and unused, and I could have them if they would help!

But before I could relax, he warned me they might not be much better than the two already in the projector. Apparently he had had quite a bit of experience with cadmium sulphide cells like the RPY58, and recalled that some of them seemed to suffer from a long-term "poisoning" or breakdown effect. It seemed quite likely that the two in the projector were in fact victims of this effect, and also entirely possible that the "brand new" units in his own junk box might have quietly succumbed to the same malady during the years since they were made.

Still, if I cared to pop over at a convenient time, he would be happy to dig them out and we could run the meter over them. Perhaps I might be lucky.

So it was that I called in at his place a couple of days later, multimeter in hand but without a great deal of optimism.

After the inevitable greetings we sat down over a welcome cup of coffee and had a pleasant chat to catch up on what we'd both been doing since last we crossed paths. Then he produced the little stock of surviving RPY58s, and we began to check them out.

My spirits sank with the first we tried, which had an illuminated resistance even higher than 15kΩ. Obviously, it too had fallen prey to the same disease as the two in the projector.

But all was not lost. Among the others we found no less than three which seemed to have survived intact, with an illuminated resistance of well below 1kΩ. We were in luck! After offering my eternal thanks, I bid my old friend adieu and drove back to the workshop, the precious LDRs in an envelope.

Getting the faulty ones out and replacing them with two of the "new" ones turned out to be quite a job. To get at the sensor block in which they were mounted, I found I had to remove the sound drive motor carefully, along with the smoothing flywheel. Then when I did get access to the block and could remove it, I found that the old RPY58s were cemented into a shallow recess with some kind of epoxy. Removing them and cleaning out the recess ready to cement in the new parts took quite a while.

In fact the whole job took a surprising amount of time, but when it was all back together again it all paid off in terms of satisfaction. With the power on, moving the sensing roller back and forth now produced the expected healthy variation in the speed of the picture motor. Everything looked a lot better.

Just to make sure, I went through the speed adjustments as described in the Beaulieu service information. As expected, it all fell into place. Before long I was able to thread up the customer's film again, and project it together with excellent sound — with the motors obviously locking together nicely.

A happy owner

Needless to say, the owner was delighted that I had fixed his pride and joy. I decided not to charge him for all the time it had taken, because I felt that to a certain extent this had been the result of my own lack of experience with this kind of equipment.

As far as the LDRs were concerned, I simply charged him what I had offered my friend for them. Since it was unlikely that I would ever need the third

one, I gave it to the customer with the suggestion that he put it in a safe place, just in case it might ever be needed. You never know, and if there was a next time they would probably be even harder to obtain than now.

As I said at the start, this kind of job can be quite a challenge for a "GP" serviceman like myself, because you're never likely to get enough experience with unusual equipment to be able to service them really efficiently.

Still, when a customer's in strife, you have to help out — even if you lose on the deal in terms of time and money. At least you end up with a grateful customer, who will hopefully call you next time their TV set plays up. EA

TETIA Fault of the Month

G.E. TC20T1 (Hitachi Pal3-A chassis)

Symptom: Low height, north/south pincushion distortion, no colour, 12 and 20V rails both low.

Cure: C753 (100μF 25 volt electro) open circuit. This is the main 20 volt rail filter cap, and its loss is seen in all parts of the set.

MicroGram COMPUTERS

IC TEST CARD

- Designed for IBM PC/XT/AT
- Tests 54/7400, CD45/4000 and MC145/140 series chips.
- Will identify unknown chips from its library.
- To test simply insert chip in ZIF socket and press space bar.

\$295 EACH including sales tax

8 BIT A/D-D/A CARD

- 64 8 bit A/D channels
- 2 8 bit D/A channels
- 24 digital I/O lines programable as input or output
- 3 independent 16 bit counters
- 12 and 14 bit A/D-D/A cards also available

\$349 EACH including sales tax

DEALER ENQUIRIES WELCOME

Ph (043) 328 651

17 Barry St, Bateau Bay, NSW, 2261

Educational video

Funway: first the books and kits, now a movie!

The Dick Smith Electronics "Funway" series of introductory kits has already helped large numbers of young people discover the fun and excitement of electronics, as both a hobby interest and a career. Now the company has produced a Funway Into Electronics video, to take the concept one stage further.

You've got to hand it to the people at Dick Smith Electronics. Most companies would have been fairly happy with something as successful as the Funway series, which has sold by the tens of thousands and helped beginners of all ages discover the excitement and satisfaction of electronics. But not DSE.



Explaining the story behind the new video, DSE's marketing manager Howard Needleman says that despite the success of the kits, his company still believed that they were not reaching their full potential.

"We realised that this wasn't likely to happen unless we used modern video communications technology, to attract the attention of young people and actually show them how interesting and enjoyable electronics can be", he added. "Nowadays, kids are very sophisticated, and they're bombarded daily with a lot of dynamic audio-visual material. You can't just show them a book and a kit, and expect them to suddenly get all excited and jump into electronics."

So the Funway Video concept was born. It's not meant to replace the existing Funway books or kits, but to precede and supplement them. It's basically a "sampler", designed to give you a quick overview of what the Funway books and kits cover, and how easy it is to use them as an enjoyable introduction to electronics.

Howard Needleman loaned me a copy of the video, and I was able to take it home and watch it a couple of times. I was most impressed.

A friendly young male presenter is

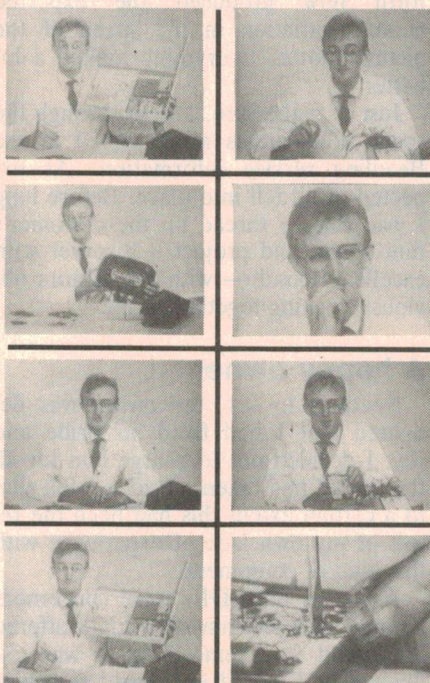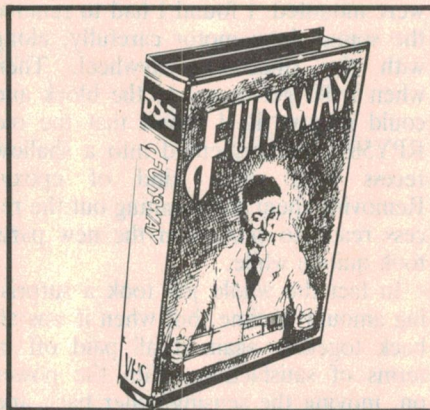

used, and he begins the 19-minute show with a quick introduction to the various basic electronic components and their functions. He then leads the viewer gently and easily through the assembly and checkout of one of the simpler Funway kits, a soil moisture checker.

From here, he passes to a more elaborate kit, the beer-powered small radio receiver. As with the first kit, we see the circuit being put together, and the "big moment" when it begins working.

Finally, the presenter explains how various kits may be combined to produce more impressive circuits, and illustrates this by adding a two-transistor amplifier and speaker to the beer-powered radio, to produce a more practical and satisfying radio.

All of this is done with good humour, and in a relaxed and informal fashion. There's no suggestion of a formal classroom approach, which would no doubt be an instant turnoff for many of today's kids.

The camerawork in the video leaves a little to be desired in odd places, with not quite as many closeups as one might wish and a few spots where the focussing might have been better. But on the whole, the subject matter and presentation more than make up for these slight rough edges.

It's a very worthwhile production, and one that extends and enhances the original Funway concept. I feel sure it is likely to attract many more people — particularly young people — into the exciting world of electronics.

You'll be able to see the Funway Video in action at any Dick Smith Electronics store, by the time you read this story. Copies are also available for sale, at a very reasonable \$19.95 each. I gather DSE is also offering a special pack of the Funway Video, the Funway Into Electronics No.1 Pack (book plus kits) for \$39.95, but this is available through DSE's mail order department, not through the stores.

A good one DSE — congratulations! (J.R.)

EA

**One standard.
Zero defects.
From IC people
committed to quality.**

Some IC companies talk about defect standards of 500 ppm as if they were proud of them. At Philips, we have a different philosophy: one defect is one too many. So zero defects is the standard we've set for our ICs. And the warranty for that standard goes like this: when you receive ICs from Philips, if you find a single defect in that batch, we'll take them all back for re-screening or replacement. The reason we can offer this warranty is that after 100% testing, we sample every batch. If we find a single defect, that batch isn't delivered.

The Philips IC activity is absolutely committed to a standard of zero defects. We have been for some time, in fact. In 1980, we instituted a rigorous 14-point program aimed at preventing mistakes – rather than correcting them. Since then, the program has evolved until it's now more than a program: it's a state of mind.

By working with you and examining rejects, we'll carry zero defects beyond a standard to a reality. You'll find that same commitment to quality throughout Philips, whether we're designing a VLSI chip containing more than 100,000 transistors, or a simple gate.

So while many IC companies are bragging about a standard of 500 defects per million, we at Philips are working our way towards zero. And when you put your trust in that kind of individual commitment, you can't lose.

**When you're offered zero,
why settle
for less?**

One standard.  defects.

Sydney (02) 439 3322 Melbourne (03) 542 3333 Adelaide (08) 243 0155 Perth (09) 277 4199 Brisbane (07) 44 0191

the UN 428




**Electronic
Components
and Materials**

PHILIPS

Circuit & Design Ideas

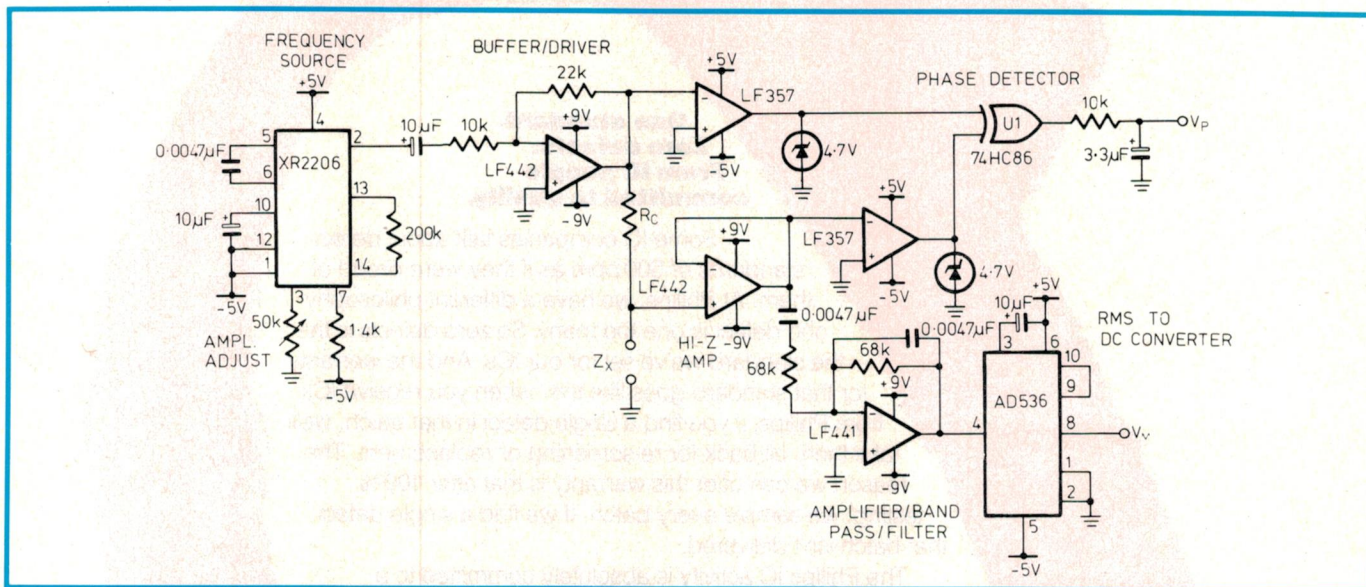Interesting circuit ideas from readers and technical literature. While this material has been checked as far as possible, the circuits have not been built and tested by us. As a consequence, we cannot accept responsibility, enter into correspondence or provide constructional details.



Complex impedance meter

No, not an impedance meter that's complex, but a meter to measure complex impedances.

Impedance meters are extremely useful test instruments. Despite this they are rarely seen, most likely due to their exuberant price tags. Likewise the need for measuring impedance is often seen as an unnecessary complication, and so is waived in favour of more familiar measurements.

By measuring impedance, both the resistance and reactance of a circuit can be determined. Similarly taking capacitance and inductance measurements is a

breeze with an impedance meter.

This circuit calculates the impedance magnitude and argument (phase) of a circuit placed across the terminals Z_x . The frequency of operation is 25kHz.

Impedance magnitude is calculated using a voltage divider network formed by the calibration resistor R_c and the unknown circuit element. R_c has not been assigned a value because its value depends on the range of impedances measured. A basic guideline is that R_c should be about 10 ohms. Values up to about 1M work well.

The phase circuit simply compares the


phases of the signals before and after they have been passed across the circuit element. A basic rule here is

Phase Angle (degrees)
= $(36 \times V_p \text{ (volts)})$.

Calibration of the meter is performed simply using a few impedance elements (e.g., resistors and capacitors joined in series), to produce calibration graphs of impedance magnitude and impedance argument versus V_m and V_p respectively.

Andrew J. Stewart,
Pialba, Qld.

\$20

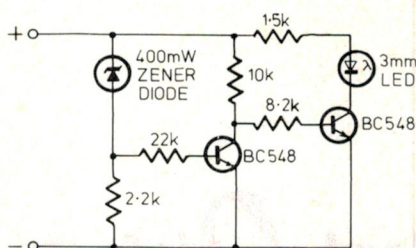

Low battery indicator

This circuit will let the users of electronic equipment powered by zinc-carbon and similar cells know when the batteries are nearing the end of their useful life.

When the supply falls to within 0.8

volts of the voltage across the zener diode, the LED will light.

Using a 10 volt zener diode the LED will light when the supply voltage falls to 10.8 volts, which is suitable for use with a 12 volt battery supply. The current drawn rises from 2mA to 7mA when the LED lights.

For a 9 volt battery supply the zener diode could be 7.5 volts and the resistor in series with the LED could be reduced from 1.5k to 1.0k ohms.

Because zener diodes are not made to strict tolerances, it may be necessary to try several before the desired operating point is obtained.

Note also that because zeners do not have a sharp "knee" below 6 volts, this

circuit is not very suitable for lower voltages.

This circuit can also be used to warn the user that Ni-Cad batteries require re-charging, but because they have a fairly flat discharge characteristic the working voltage of the zener diode becomes much more critical. A suitable re-charge point for Ni-Cad batteries would probably be 1.2 volts per cell or a little less.

If used with Ni-Cad batteries, the circuit may help reduce the risk of "reverse-charging" one or more of the cells, which can occur if the voltage is allowed to fall too low.

J. Emery,
Bullcreek, WA.


\$10

El cheapo frequency reference

A cheap way of calibrating DMFs, with sufficient accuracy for most purposes is to use the 15625Hz line frequency of a TV set locked to say the local ABC channel.

Construction is 50 turns of B&S of enamelled wire on an AFT3743 toroidal core, slipped over a 25mm piece of spaghetti. The 0.1 μ F capacitor and coil are fastened with silicone 780 sealant to the spaghetti. The capacitor pigtails are used to terminate the winding and the two connecting leads are also silasticed for support.

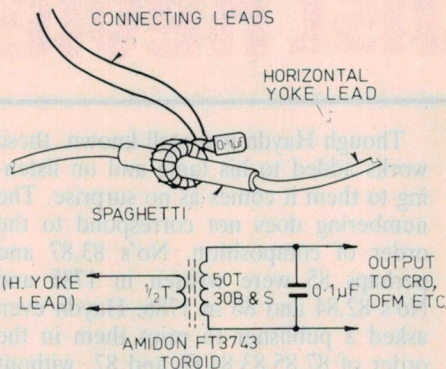The assembly is slipped over one of the horizontal yoke leads, and the connecting leads passed through ventilation holes in the back of the



TV set. This will give a known 15625Hz reference signal whenever the set is locked to a program.

Tim Wellstead,
Borden, WA.

\$10

Simple doorbell

Rather than paying the inflated prices for a commercial doorbell circuit, I decided to make up a simple one myself using this oscillator circuit.

The capacitor and resistor values can be changed to alter the sound it produces. I used a small pushbutton from Dick Smith Electronics, Cat. No.S-1102, but you could easily use an existing doorbell button, or even a reed switch if desired.

Total cost of the complete circuit was less than \$10.

Ben Buxton,
Edgecliff, NSW.


\$10

24V/12V regulator

If efficiency is not too important, this simple arrangement can be used to operate 12V car equipment from a 24V truck electrical system. It will deliver up to 10 amps.

Basically two 78H12A three-terminal TO-3 power regulators are used, with resistors R to ensure that they share the load equally. The resistors were each made from a piece of toaster element 0.5 inches long. To the ends of these I crimped lengths of thick copper wire, to form pigtails for connecting into circuit.

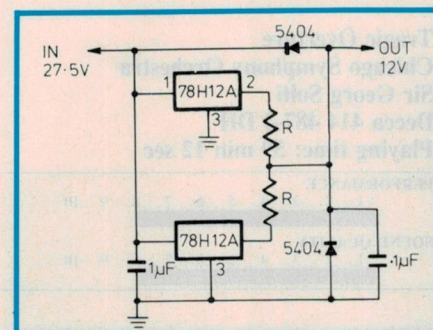Needless to say, the regulators need to be provided with good heatsinking —



particularly if the circuit is to be used to deliver higher currents.

G.B. Wolfe,
Bombala, NSW.

\$10

SCOPE TOOLS


60W SOLDERING SYSTEM

NEW INFINITELY ADJUSTABLE 200° - 470° C

Illuminated Temp. readout monitors actual tip temperature.

Zero Voltage switching for maximum component safety.

Select the tip temp. required.

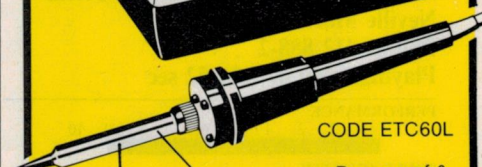

CODE ETC60L

60 Watts of back-up power - 30W Pencil optional.

Burnproof & flexible lead.


Ceramic encapsulated element for lowest earth leakage

SOLDER REMOVER METAL BODY - SELF CLEANING

CODE SR



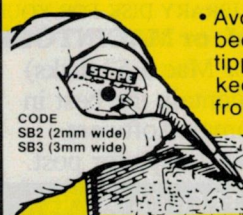SOLDER BLOTTER 2 M IN WIND BACK DISPENSER



CODE SB2 (2mm wide) SB3 (3mm wide)

• Avoid burnt fingers because metal tipped container keeps fingers away from iron tip

• Dispenser locates tape positively



DAVID REID ELECTRONICS LIMITED
127 York Street, Sydney. 2000
Telephone: (02) 267 1385

Compact Disc Reviews

by RON COOPER



HAYDN SYMPHONIES 86 & 87

Academy of St. Martin-In-The-Fields
Neville Marriner
Philips 412 888-2
Playing time: 47 min 52 sec

PERFORMANCE										
1	2	3	4	5	6	7	8	9	10	
SOUND QUALITY										
1	2	3	4	5	6	7	8	9	10	

These two lesser-known works belong to a group known as the "Paris Symphonies" (No's 82-87) which were commissioned from Haydn by Claude-Francois-Marie Rigoley, Comte d'Orgny (1757-1790).

Though Haydn was well known, these works added to his fame and on listening to them it comes as no surprise. The numbering does not correspond to the order of composition. No's 83,87 and perhaps 85 were written in 1785 and No's 82,84 and 86 in 1786. Haydn even asked a publisher to print them in the order of 87,85,83,84,86 and 82, without success.

The two works on this disc have quite profound slow movements, the No. 86 being probably the greatest of the group, with excellent use of trumpet and tympani.

Here again, the Academy under Marriner is merely magnificent — very spirited playing which I feel makes these works just that little bit more exciting. This is the music the Academy are really renowned for and their brisk tempos capture your interest right from the first hearing, coupled as they are with an almost perfect mike balance from the un-named Philips recording team.

As with other recordings of the Academy, my usual comment is that they are not large-scale works and should therefore not be played too loud — the strings may sound a trifle edgy. This is front-row seat sound but only from a chamber orchestra, and a superb one at that. (R.L.C.)

GRIEG/SCHUMANN PIANO CONCERTOS

Piano Concerto in A minor (Grieg)
Piano Concerto in A minor (Schumann)
Stephen Bishop Kovacevich
BBC Symphony Orchestra
Sir Colin Davis
Philips 412 923-2
Playing time: 60 min 30 sec

PERFORMANCE										
1	2	3	4	5	6	7	8	9	10	
SOUND QUALITY										
1	2	3	4	5	6	7	8	9	10	

The problem with popular concertos such as the Grieg A minor, Tchaikovsky No. 1 and so on is the fact that being popular they become labelled as hackneyed and apparently less worthy than others. Over-exposure can blunt the tastes of a refined public. Both the concertos here could be labelled as such, but fortunately the Schumann hasn't quite fallen into this category yet.

Grieg was an admirer of Schumann and his A minor concerto was first performed on April 3rd, 1869 in Copenhagen, with the composer as soloist. It is as much a reflection of Grieg's background as the earlier concerto was of

MICRO-EDUCATIONAL P/L
8/ 235 Darby St NEWCASTLE 2300
Australia's largest computer mail-order company.

FREE

OUR LATEST LIBRARY DISK FOR YOUR
APPLE, IBM, or MACINTOSH
(Add \$10 for Mac 3.5" disks)
These disks contain the best in
public domain software.
Send 6 x 36c stamps for post.

Ask for your **FREE CATALOG**

Dear George,

Please rush me a free library
disk for my IBM/ APPLE/ MACINTOSH
(Add \$10 for Mac disks)
Enclosed please find 6 x 37c stamps.

NAME: _____

ADDRESS: _____

P/CODE: _____

BRAHMS SYMPHONY NO.2

Tragic Overture
Chicago Symphony Orchestra
Sir Georg Solti
Decca 414 487-2 DH
Playing time: 59 min 12 sec

PERFORMANCE										
1	2	3	4	5	6	7	8	9	10	
SOUND QUALITY										
1	2	3	4	5	6	7	8	9	10	

While it had taken Brahms well over a decade to compose his first symphony, possibly due to the thought of the mighty Beethoven looming over him, the second symphony was composed within the following year.

It was an immediate success and has



gained wider appeal than the first. An influential critic of the period, Hanslick, wrote: "Seldom has there been such a cordial public expression of pleasure in a new composition. Brahms Symphony No.1 was a work for earnest connoisseurs capable of constant and micro-

Schumann's.

There are similarities between these works, mainly in the first movement. They both start with a short cadenza-like section for the soloist, after which the first subject appears, played initially by the winds and then by the soloist.

The performances here by Stephen Bishop-Kovacevich are excellent indeed and leave little room for comment, other than to say they are "traditional" versions (read that how you like!).

The analogue recording is slightly dated, but still very good, even though it has a rather wide left-right effect and a slightly higher background hiss. However, with CD's such as this, it is easy to play the music louder than it would normally be heard in a concert hall, so increasing the awareness of background hiss. Overall, this is first rate music with almost first rate sound. (R.L.C.)



scopic pursuit of its minutely ramified excursions; the Symphony No.2 extends its warm sunshine to connoisseurs and laymen alike".

Like the first symphony, this work is one of great feeling, particularly the 3rd and 4th movements, which appear to have a paradoxical air of complicated simplicity about them.

The Tragic Overture was first performed some four years after the second symphony and, I feel, shows Brahms in a somewhat different vein but still retaining his great orchestral skill.

Solti's handling of these works leaves little to be desired and almost defies comment. The overall balance is very good, with a very slight edginess to the strings and some minor background hiss, but on first-rate playback equipment the overall effect is verging on excellent — maybe just a little too much reverb. (R.L.C.)

MOZART PIANO SONATAS

Andras Schiff

Piano Sonata in A major, K331/300i

Piano Sonata in A minor, K310/300d

Piano Sonata in D major, K576

Decca 417 571-2 DH

Playing time: 54 min 26 sec

PERFORMANCE

1 2 3 4 5 6 7 8 9 10

SOUND QUALITY

1 2 3 4 5 6 7 8 9 10


Of the three sonatas on this disc the earliest is the A minor K310/300d, composed in 1778 in Paris. Apart from that, little is known about it. Mozart was in Paris for six months and the early good intentions of this stay culminated in grief at the death of his mother. The "Paris" symphony and this sonata, his first keyboard work in a minor key, were the most substantial compositions of this stay.

The beginning of the disc shows Mozart's genius, in the quiet, masterly K331 composition. The third movement, often performed as a separate piece, is familiar to all — the rondo "Alla Turca". Played here by Andras

Schiff, it is excellent.

The first movement of the D major K576 shows influences of Haydn by being somewhat dominated by the opening theme. Elsewhere there are influences of the great Bach.

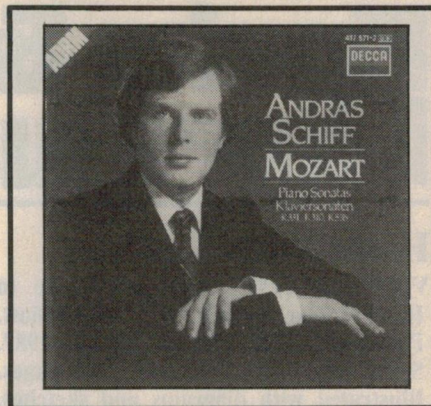The performance on this disc is exhilarating. It shows a strong sense of purpose without any hesitancy, yet a sensitivity also seems to prevail. Sound-wise, the recording is quite live and there is a constant faint background hiss, due, I gather to the original analogue recording, but as this is a quietly even noise, it does not really intrude. A very worthwhile disc. (R.L.C.)





DEEP, TIGHT, BASS IN KIT FORM

**\$1199
PAIR**

vifa

AEM-6103

KIT SPEAKERS.

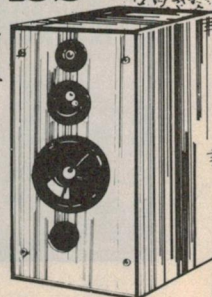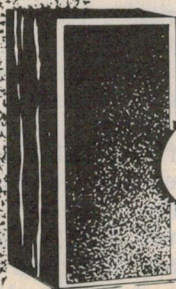

In the past, buying high quality loudspeakers has necessitated selecting a fully imported product, together with its increasingly high price tag. Today, if you can use a screwdriver and solder a few connections, those pecuniary problems are far behind.

Tilbrook's AEM6103 is a kit speaker designed to incorporate the world famous Vifa drivers. A 10" woofer is housed in a solid diecast chassis on which a huge magnet is fitted.

A most unusual 3" soft textile dome mid-range with magnificent dispersion and transient qualities ensures perfect reproduction of the critical mid-band area.

The classic Vifa 19mm dome tweeter with ferro fluid-cooled voice coil provides extremely clear and well balanced treble.


The crossover is a very advanced 18dB/octave design with impedance correction for the woofer. In the tweeter

and mid-range section, only polyester capacitors are used.

Many hundreds of these speakers have already been built with superb results. Capable of handling 130 watts, these masterpieces of quality retail at \$1199 a pair including drivers, pre-built crossovers and flat pack cabinets. On the other hand, you could spend an additional \$2000 or more for a comparable imported speaker! Which is why VIFA drivers are used and preferred as original equipment by many of the world's most acclaimed loudspeaker manufacturers.

For full details of Vifa speaker kits, priced from as low as \$449, please contact the Sole Australian Distributor: **SCAN AUDIO Pty. Ltd.** 52 Crown Street, Richmond, 3121. Telephone (03) 429 2199. Stocked by leading electronic stores throughout Australia.

Books & Literature

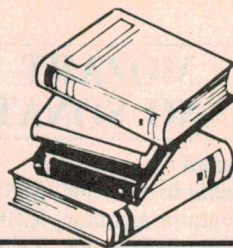

Home Video Guide


VIDEO ACTIVE: An Easy Guide to Home Video Making, by Geoff Elliott. Published by BBC Books, London 1987. Soft covers, 199 x 124mm, 168 pages. Illustrated with diagrams and sketches. ISBN 0 563 21314 0. Recommended retail price \$14.95.

A very down to earth and friendly little book, this one. It was apparently written to accompany a series of TV programs with the same title, produced by BBC-TV and broadcast in the UK earlier this year.

Essentially it's a primer on making home video movies, using either a camera and VCR combination or one of the newer "camcorder" combined units. And although it is fairly clearly meant to be augmented by demos and other supplementary information provided in

the TV programs, it's so well done that it can easily stand on its own feet.

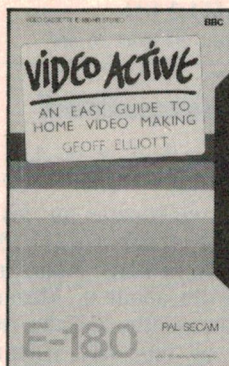It's divided into two main sections. The first covers choosing a camcorder or camera/VCR combination, how to set them up and basic operating techniques. It also provides a chapter on



ideas for video movie projects, for those who need a few pointers to head them in the right direction.

Part 2 then deals with topics of interest once you've mastered the basics: things like adding accessories and other equipment (such as lights, titlers, editing gear etc.), creative production techniques, and ideas for more advanced video movie projects.


The emphasis throughout is on practical operation, rather than a lot of technical theory, and it's written in a concise, easy to read style.

If you're looking for a good no-nonsense guide to getting into video movie-making, either from scratch or as a transition from traditional home movies on film, it would make a good choice — particularly in view of the attractive price.

The review copy came from Heinemann Publishers Australia, the local distributors for BBC Books, but copies should be available from most bookstores by the time you read this. (J.R.)

Semiconductor circuits

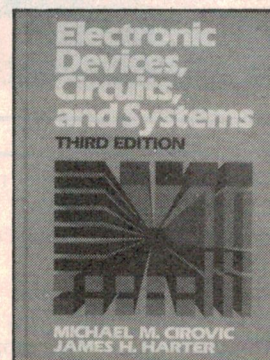
ELECTRONIC DEVICES, CIRCUITS AND SYSTEMS, by Michael M. Cirovic and James H. Harter. Third Edition, published by Prentice-Hall Inc., New Jersey 1987. Hard covers, 243 x 184mm, 444 pages, with many diagrams and circuits. ISBN 0 13 250655 6. Recommended retail price \$83.50.



This is the third edition of a textbook that is now something of a classic, first published in 1974 and then in 1979 under the title Basic Electronics. For the third edition it has been extensively revised and updated, to include material on new linear ICs, power MOSFETs, fibre optic devices, IC thyristor devices and other recently developed devices.

As the title itself suggests, it is divided into three main sections dealing in turn with the various semiconductor devices themselves, the main kinds of basic electronic circuit employing them,

Continued on page 125

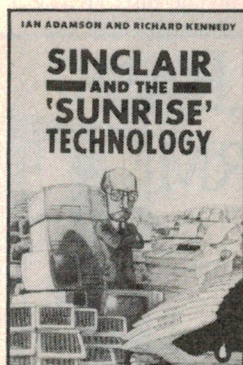

An entrepreneur examined

SINCLAIR AND THE 'SUNRISE' TECHNOLOGY, or The Deconstruction of a Myth, by Ian Adamson and Richard Kennedy. Penguin Books, 1986. Soft covers, 199 x 130mm, 263 pages. ISBN 0 14 008774 5. Recommended retail price \$12.95.

I first heard about this book from Dick Smith, who was apparently sent an advance copy by one of his friends in England. Dick found it fascinating, because apart from anything else he met Sir Clive Sinclair a number of times and did business with him (or tried) for years. As soon as Dick read it he rang up, saying "You'll have to get hold of a

copy of this new book as soon as it's released here — it's incredible!"

Thanks to the Penguin people, I now know why Dick was so enthusiastic. It certainly makes intriguing reading, for anyone who has ever heard of Sir Clive and his career as entrepreneur, visionary boffin and self-styled saviour of the British electronics industry. If you've ever bought any of the Sinclair products, or checked them out (as I have), you'll find it irresistible.

It really is a splendid study of a complex man, undoubtedly gifted and with enormous energy — but with almost equally serious shortcomings. A man of vision who can grasp new technology and use it to build new enterprises, but who also tends to destroy both vision and enterprise through mistrust, self deception and amazing mismanagement.

The book indeed makes fascinating reading, tracing through the ups and downs of 'Uncle Clive' and his companies right from the very early days of amplifier and watch kits, through the ZX80 and ZX81 computers to the C5 electric trike and beyond. For me there's also a few parallels there, with would-be Australian entrepreneurs I've come across recently (no, not Dick!).

The review copy came direct from Penguin Books Australia, but it's now available at major bookstores. (J.R.)

LISTEN & LEARN, Software made Simple

Why spend time and money on training courses for your computer programs? Now a revolutionary new training program is available exclusively through Dick Smith Electronics!

The Listen & Learn audio cassette system lets you TEACH YOURSELF to master those complex programs such as MS-DOS, Lotus 1-2-3, Multimate, dBase3+, Wordstar, Displaywrite3 and many more.

Simply by playing the audio tapes and following the simple colour coded exercises you can learn to master even the most complex programs in as little as 10 hours. You'll save a fortune on training courses, seminars, etc. PLUS you can use the tapes over and over again!

Executives as well will find this system invaluable! In your own time you can master the programs used in your office — and it's fun!

What you get

Each Listen & Learn pack comes with audio cassette tapes and colour coded instruction manual. Or, you can buy the Professional Pack which includes a portable cassette player and quality, lightweight headphones. For the new common sense approach to learning programs. Listen & Learn eliminates the need for heavy, hard to follow manuals. With DSE, Multitech and Listen & Learn — you've got the problem solved!

MS DOS Cat X-9800

\$99

Lotus 123 Prof Pack Cat X-9801

Multimate Prof Pack Cat X-9803

dBase 3+ Prof Pack Cat X-9805

Wordstar Prof Pack Cat X-9807

Display WRT3

Prof Pack

Cat X-9809

\$199

Lotus 123 Executive Pack

Cat X-9802

Multimate Executive Pack

Cat X-9804

dBase 3+ Executive Pack

Cat X-9806

Wordstar Executive Pack

Cat X-9808

Display WRT3 Executive

Pack Cat X-9810

\$129



DSE Multitech All the best for less!!

The DSE Multitech PC-500 System 1 started the Affordable PC compatible revolution by being the first to break the \$1000 price hurdle. It's still the leader when it comes to quality, versatility and value! With 256K memory (expandable to 512K), single 360K disk drive, 4.77MHz clock speed, CGA card, parallel and serial ports and MS-DOS — it's not hard to see why!

Specifications:

- IBM PC standard 4.77MHz clock speed
- On-board memory 512K maximum (256K fitted)
- 8088 CPU chip
- CGA card, parallel and serial ports fitted
- 67W power supply
- Supplied with MS-DOS 3.20, plus software depending on model.

System 1: Single 360K disk drive, 256K memory. Cat X-8000

DSE Diskettes

Why pay more? Top quality computer media at a realistic price, made exclusively for Dick Smith Electronics by one of the world's leading disk manufacturers. They're so good we use them ourselves! Double sided disks, soft sector, in 5 1/4" (13cm) standard size.

Single density: **\$27⁵⁰**

Double density: **\$29⁵⁰**

Box 10 disks

Box 10 disks

Cat X-3500

Cat X-3501




Does not include monitor

\$995

Protect those disks!

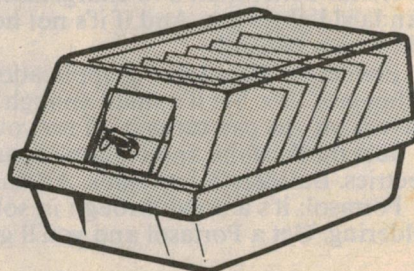Your disks need help... and protection. Look after your data and software properly by storing your disks away in a disk box.



50 disk hinged box, lockable with 5 movable dividers.

180 x 160 x 250mm Cat X-3531

\$22⁵⁰

100 disk hinged box, lockable with 9 movable dividers.

180 x 160 x 380mm Cat X-3534

\$24⁹⁵

3 1/2" (9cm) format. 40 disk hinged box, lockable with 4 movable dividers.

125 x 130 x 250mm Cat X-3533

\$28⁹⁵


DICK SMITH ELECTRONICS COMPUTERSTOP

Don't shop at DSE...
Unless of course,

you want the best value, largest range and professional service!

Want a Hot Tip?

PORTASOL won't let you down.

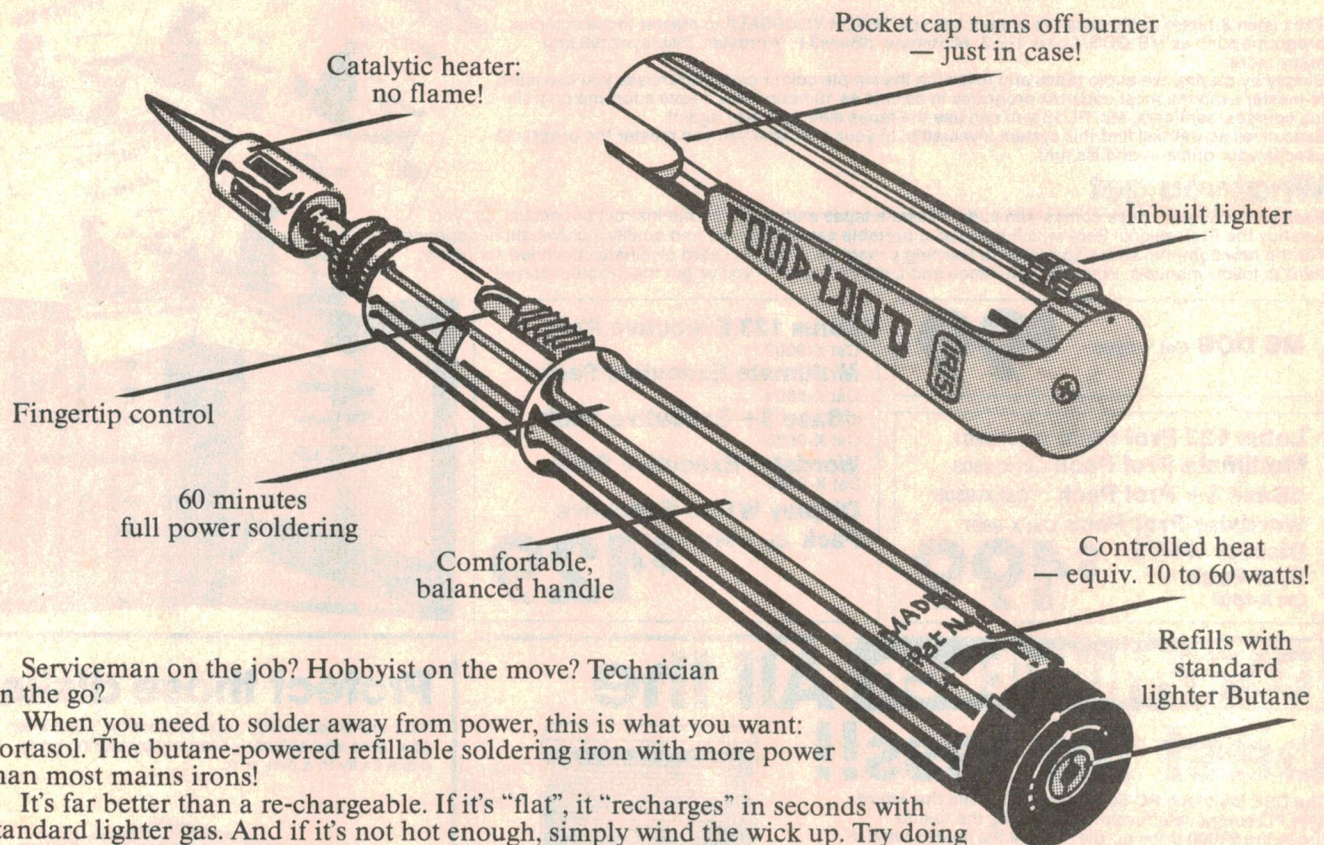

Serviceman on the job? Hobbyist on the move? Technician on the go?

When you need to solder away from power, this is what you want: Portasol. The butane-powered refillable soldering iron with more power than most mains irons!

It's far better than a re-chargeable. If it's "flat", it "recharges" in seconds with standard lighter gas. And if it's not hot enough, simply wind the wick up. Try doing that with a NiCad!

Perfect for all soldering applications — even those heavy jobs you'd normally want a "big gun" for. Yet it's small enough to slip into the shirt pocket (and in case you leave it on, the cap turns it off for you!)

Just think of the applications apart from electronics: Boat wiring and repairs. Auto electrics. Builders/electricians. Antenna installers. And so many more.

Portasol: it's a breakthrough in soldering. Throw away your old ideas about soldering. Get a Portasol and you'll get the difference. Cat T-1370

**Spare tips
including
Catalytic
Heater**

\$12⁹⁵

Cat T-1371

Only \$59⁹⁵ at

**DICK SMITH
ELECTRONICS**
PTY LTD

Available at all DSE stores . . . or phone DSXpress
on (008) 22 6610 (Sydney 888 2105)

ARLEC

Famous Aussie brand from
the famous Aussie stores:
Dick Smith Electronics!


ARLEC'S FAMOUS SUPERTOOL!

What versatility! It sands. It polishes. It engraves. It mills. It's one of the handiest tools you can have in your arsenal! This fantastic hobby machine is a 10,000 RPM power head which does all of the above with the attachments supplied. And because it operates from low voltage (240V plugpack included!) it's safe. Includes the Supertool and plugpack, 2 milling cutters, 1 wire brush, 1 grinding wheel, 4 high speed drills, 5 chuck collets (0 to 4mm), eraser sticks and instructions. Cat T-4754

ONLY
\$59⁹⁵

Supertool: for • Hobbyists • Model
Makers • Technicians • Gem & Lapidary
• Antiques • You name it!

**INCLUDES
CASE!**

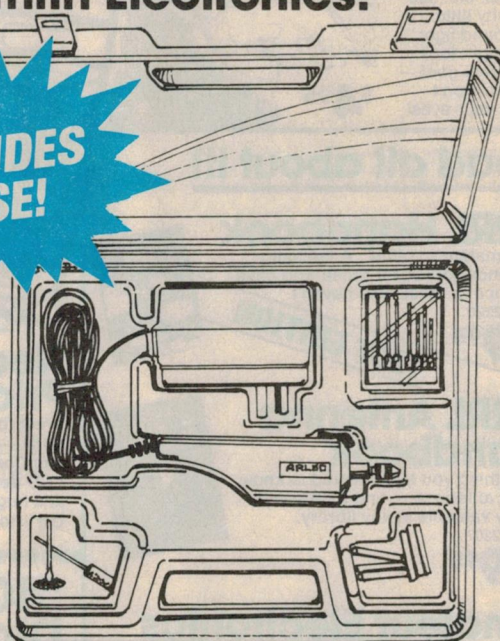

SUPERTOOL ACCESSORIES:

Cutting Discs

Set of 6 mini cutting discs, with arbor, for cutting metal and plastic. Essential for the serious hobbyist. Cat T-4766

\$11⁹⁵

Grinding Bits

Shape, sand and grind your projects to perfections. 3 piece, different shapes. Cat T-4758

\$11⁵⁰

Wire Brushes

Pack of 3 wire brushes for polishing, cleaning, etc. Cat T-4768

\$15⁹⁵

Set 4 PCB Drills

Top quality high speed steel twist drills in all popular PCB sizes: 1.2, 1.0, 0.8, and 0.6mm. Cheaper than buyer singly! Cat T-4756

\$7⁹⁵ set

Erasers

Make short work of rubbing out! Two different types to cover both ink and pencil!

Set 5 ink \$5¹⁵
Cat T-4760

Engraving/Milling Bits

Set of three cutters designed to make short work of any engraving or milling job. Fine and medium hex head plus fine round head. Cat T-4764


Set 5 pencil \$2⁹⁵
Cat T-4762

\$9⁹⁵

OTHER FINE ARLEC PRODUCTS...

ARLEC MINI VICE

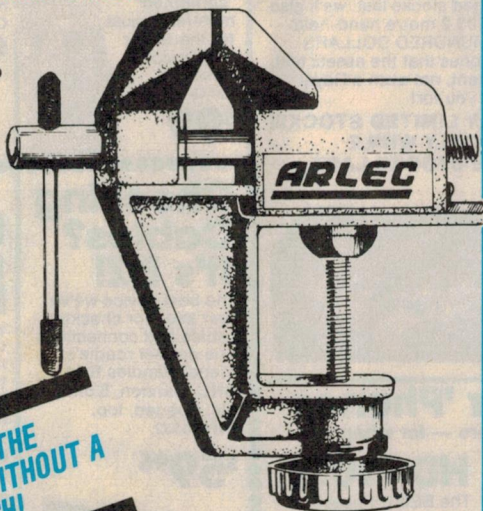Need a third hand? Here's one that won't let go! The mini vice from Arlec attaches to any table, desk, bench, etc. (up to about 40mm thick). 50mm wide jaws hold tight — opens up to around 60mm for those big jobs. More than strong enough for cutting, filing and other testing applications. Cat T-4748



**A MUST FOR THE
HOBBYIST WITHOUT A
WORK BENCH!**

ONLY **\$12⁹⁵**

ARLEC NICAD CHARGERS

"D" Charger

Want to charge "D" NiCads? This one will handle two or four D size cells — even the heavy duty 4A types (the ones most chargers take forever doing!) Perfect for radio control cars, video cameras, etc — anything with a D size NiCad. Rated at 2x 3V, 400mA. Cat M-9400

Multi Current Arlec Charger

In-situ charger for all NiCad types (AAA to 9V) with 4 different charging currents and 6 different connector types to suit all device sockets. Handles up to 10 NiCads at one time. Cat M-9510

M-9521

Universal model accepts all types, automatically adjusts charging current to suit type. Includes battery tester. M-9521



\$39⁹⁵

\$29⁹⁵

\$39⁹⁵

DICK SMITH ELECTRONICS

PTY LTD

When you need a third hand...

To hold the light, that is! Don't strain your eyes with small pcb's, circuits, etc: use our nifty little headband light. You might look like a real goof — but you won't strain your eyes!



\$4⁹⁵

Cat Y-1073

Read all about it!

ARRL Handbook

The amateur's "bible". A fantastic reference source for those who have a licence or those who haven't.

Cat B-2220

\$49⁹⁵

1987 EDITION

ARRL Antenna Handbook

Everything you ever wanted to know about antennas — and then some! Highly valuable in any library.

Cat B-2207

\$29⁹⁵

Amateur Electronics and Study Guide

"Students own notes" format makes it so easy to understand. A must for the beginner — right through to full licence level. Cat B-2319

\$16⁹⁵

VHF/UHF Manual

Recommended for "Z" calls and all others interested in working above DC! One of our most popular manuals. Cat B-2054

\$29⁹⁵

Magnavox is Back!

Famous Magnavox speakers are back in production, and back at DSE stores. Build your own speaker systems with these superb models:

80mm Tweeter

30W maximum rated, 8 ohms impedance. Frequency response to 18kHz. Cat C-2070

\$9⁹⁵

100mm Midrange

Superb high quality speaker for smaller systems. 3W, 8 ohms. Ideal replacement speaker, too. Cat C-2062

\$9⁹⁵

125mm Midrange

High power version: 30W rating, with 800 to 7000Hz. Smooth and precise. Cat C-2060

\$19⁹⁵

200mm Woofer

Huge 80W rating with excellent bass response. Frequency response to 500Hz. Cat C-2054

\$29⁹⁵

250mm Woofer

Similar to above, but slightly lower (65W) rating, lower resonant frequency. Cat C-2052

\$39⁹⁵

300mm Woofer

The Big Gun! 80W rating, 30Hz resonant frequency. Also 8 ohms. When you want the best... Cat C-2050

\$49⁹⁵



Buy in bulk and \$\$\$ave

Every hobbyist, every technician knows that a well-stocked "junk box" is one of life's biggest assets. You never know when you want a... and a good junk box should be able to yield one! Stock your junk box with DSE bulk bargain packs. Prices up to 50% and more off single prices!

1/4 Watt Resistor Pack Ceramic Pack

300 computer selected carbon resistors, at huge savings. Cat R-7010

\$8⁷⁵

Over 60 ceramics of various values, with voltages as high as 630VW! Cat R-7050

\$6²⁵

Metal Film Resistor Pack

300 1% tolerance metal films. A great buy! Cat R-7015

\$17⁵⁵

Diode Pack

100 pieces signal diodes in both Ge and Si. From OA90 to 1N914's. Cat Z-3005

\$13¹⁵

LED Pack

100 premium quality (matched brightness & colour) LEDs in red, green & yellow Cat Z-3015

\$26³⁵

Greencap Pack

60 greencaps from .001 to 0.22uF. All 100V types. Cat R-7040

Around \$22 worth \$12⁶⁰

Electro Pack

55 quality pcb mounting electros from 2.2 to 470uF. Cat R-7030

Around \$15 worth! \$8⁷⁵

Near Half Price!

Great for computer buffs — or just as a gift! Computer shaped LCD desk clock now at a huge saving. Cat Y-1039



\$6⁹⁵

One for the Girls...

Cat Y-1010



Big savings too on this travel alarm. It's pink, so it's just right for mum or sis! Last year sold for \$14.95 — now look!

\$6⁹⁵

Value!

No, we don't know what they're from, but they're great! 240V AC motor, geared to 5RPM, with can driving microswitch 3 times each rev. So you get the motor and microswitch for this crazy price! Cat J-1041

\$1⁵⁰

"4000 Count" Bargraph Digital Shows Analog!

\$249

The usual complaint with a digital multimeter is you can't see changes. Problem Solved: this new LCD gives you the best of both worlds: digital accuracy, with an analog indication AS WELL which shows both magnitude AND variation at the same time. But there's even more than that: this outstanding design counts to 4000, rivalling the accuracy of 4.5 digit meters, while keeping the price down to 3.5 digit types! 4000 counts means it has double the resolution of 2000 count meters. One of the best meters we've ever seen! Cat Q-1666



Bargain of the Century


BUY AN FT757GX

Yaesu's superb all mode, all band HF transceiver with 100 watts out from the size of a (small) shoebox. Already one of the greatest buys in amateur radio. . . Cat D-2940

\$1799 AND GET A HANDHELD FREE!!!

Yes while strictly limited stocks last, we'll also throw in a Yaesu FT203 2 metre hand-held. That's around FIVE HUNDRED DOLLARS saving! Yes, 500 big ones that the assets test, the taxation department, not even a Royal Commission can get you for!

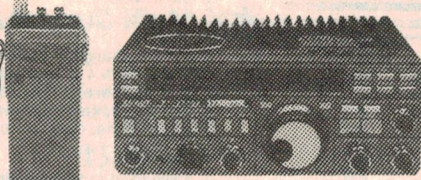HURRY! STRICTLY LIMITED STOCK!!! OFFER APPLIES ONLY WHILE CURRENT STORE STOCKS LAST.



Sennheiser 'Phones

Top quality Sennheisers — for when you want REAL quality.

HD40

The budget model. Lightweight and comfy, 22-18000Hz response. Complete with 6.5/3.5 multi-plug & cable. Cat C-4120

\$49⁹⁵

HD410SL


The BEST! Superb sound reproduction, 20-18000Hz response and generous 3 metre cable. Highly comfortable, ideal for monitoring 'phones. Cat C-4115

\$74⁹⁵

Digital Capacitance Meter Too!

Few pF to 200uF range — very handy to sort through "unknowns" (saves you having to remember codes too!) Much more accurate than "combined" meters. A must for the lab or the service bench. Cat Q-1221

\$99

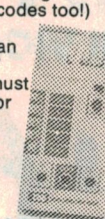

At Last! DSE's Dipper

Budget priced dipper with 1.5 to 250MHz range (6 plug-in coils) for all those amateur and communication uses. Inbuilt xtal oscillator (1-15MHz), 2kHz sine wave modulation. Cat Q-1335

\$129



Checking Cables? It's E-Z!

The best device we've ever seen for checking cables and connections. The perfect roadie's friend. Handles RCA, BNC, Cannon, 6.5mm etc. Rugged, too. Cat Q-1532.

\$59⁹⁵



Bench meter Bargains

When you want high visibility and don't want to tie up a multimeter, try these. DCV and DCA, huge scale and two ranges. Ideal for techs, schools too.

0-1A, 0-10A DC

Cat Q-2130

0-10V, 0-20V DC

Cat Q-2140

EACH \$29⁹⁵



Fuses



We've got the LOT!

Whatever your requirement in fuses, see DSE. You'll save! And if you buy in bulk, you'll save even more!

Fast Blow

3AG	
100mA	S-4494
150mA	S-4451
250mA	S-4453
350mA	S-4455
500mA	S-4457
1A	S-4461
1.5A	S-4465
2A	S-4467
3A	S-4469
5A	S-4471
7.5A	S-4473
10A	S-4475
15A	S-4477
20A	S-4479
25A	S-4481
30A	S-4485
35A	S-4487

M-205

ALL

250mA	S-4412
500mA	S-4415
1A	S-4421
2A	S-4423
5A	S-4425

45¢
EACH

Slo Blo Fuses

3AG	M205
250mA	S-4350
500mA	S-4355
1A	S-4360
2A	S-4365
5A	S-4370
250mA	S-4300
315mA	S-4305
500mA	S-4310
1A	S-4315
2A	S-4320

Auto (Blade Type) Fuses



5A	S-4505
7.5A	S-4507
10A	S-4510
15A	S-4515
20A	S-4520
25A	S-4525
30A	S-4530

ALL 50¢ each

Mains Circuit Breakers

Plug-in replacements for "Federal" type fuses in your fuse box. Saves ever having to search for fuse wire again!

16A	P-5920
20A	P-5925
10A	P-5910
15A	P-5915

ALL \$10.95 each



THE ROLLS-ROYCE OF HAND TOOLS: PIERGIACOMI

You asked for quality - you've got quality. Around the world, Piergiacomini tools are known for their outstanding performance and precision. Stainless steel, beautifully honed cutting edges - you owe it to yourself to try them!

Standard Cutter

Just feel the precision! 4mm blade opening. Cat T-3262



\$16.95

Shears

Cut through metal, plastics, even RG213 coax! Cat T-3265



\$22.95

Back Angled Cutter

Reverse to normal cut especially for fine pcb work. Cat T-3261



\$16.95

Needle Nose Pliers

Really a needlet! Ultra fine with flat blades. Cat T-3266



\$17.95

Inclined frontal cut.

Full frontal! Leaves 1.5mm lead length for soldering. Cat T-3263



\$19.95

Inclined cutter and bender

Bends pcb leads as well as cutting them. Clever! Cat T-3264



\$18.95

Building Or Renovating?

Find the power cable or pipe before your drill or saw does! Hand held detector detects metal to several cm; a must for builders & handymen Cat Y-1060



WAS \$17.95 NOW \$14.95

Assorted Metric Screw Pack

Over 200 pieces of the most popular small sizes: M2.5, 3 and 4 nuts and screws - cross, round and counter-sunk head. Plated finish.



\$9.95 10 up \$8.77

BOXES AND CASES FOR PROJECTS

No matter what your project, there's a DSE box just right for it. Professional finish, made to last. Here are just two styles from our large range:

Extruded Aluminium Plastic


High degree of RF shielding, close fitting ends. Extrusion size 76 x 102mm, supplied in three lengths:

76mm length	H-2420	\$10.95
102mm length	H-2425	\$12.95
153mm length	H-2430	\$14.95

As used by world-wide manufacturers. Three different styles of case, one to suit your requirements.

155 x 65 x 160mm	H-2508	\$9.45
200 x 95 x 140mm	H-2506	\$15.00
200 x 65 x 100mm	H-2505	\$16.75

(illustrated)

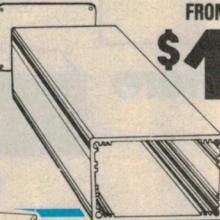

FROM \$10.95



FROM \$9.45

Slimline UHF CB: Royce

Slimline so we've given it a slim price! It's superb - electronic control, full 40 channels - and add the optional carry case for go-anywhere type. Cat D-1810


Optional Carry Case (turns mobile CB portable) Cat D-1812 \$189.95
Optional Tone Squelch (ideal for business use) Cat D-1808 \$129

\$599

Less than \$1 per piece!

Our T-4830 tool kit is outstanding value! 21 pieces including mini spanners, screwdrivers, spiritlights, etc etc. Handy plastic carry pack. Cat T-4830

\$14.95

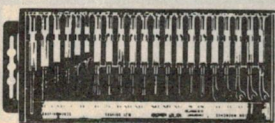

Stick it by Gum!

Glue nearly anything to anything with a hot melt glue gun. Easy to use, makes a really strong, tough bond. Great for the hobbyist, ideal for the serviceman.



Cat T-4840

\$19.95

Own a Frog 8800?

want wide band FM? Here's how to get it: fit an FM wide module. We ordered hundreds more than we needed so you save! Normally around \$50, now almost half price! Cat D-2824

\$29.95

Protect those Mags!

Electronics magazines are too expensive to throw away. And they make good reference too. So protect them with DSE's magazine binders. Holds up to 12 copies of your favourite mag (fit EA, ETI, AEM, AR, ARA, etc etc). Cat B-4045



VALUE!

\$6.95


NEEDA TRANSFORMA? SEE DSE

Our range will get you the voltage and power you want. All electricity authority approved, versatile, ready-to-go-to-work transformers just right for a hobby project or a commercial design - and anything in between!

DSE2851. Primary: 240V, 50Hz. Secondary voltage: 6.3-0-6.3V. Secondary current: 150mA. Terminations: Flying leads. Cat M-2851

10 up \$4.70

\$5.50

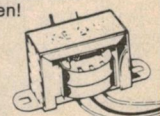

DSE2155. Primary: 240V, 50Hz. Secondary voltage: 6.3, 7.5, 8.5, 9.5, 12 & 15V. Secondary current: 1 amp. Terminations: Flying leads. Cat M-2155

10 up \$6.80


\$7.95



DSE6672. Primary: 240V AC. Tapped: 15, 17.5, 20, 24. Secondary voltages: 27.5 & 30V. Secondary current: 1amp. Terminations: Solder lugs. Cat M-6672

10 up \$10.95


\$11.95

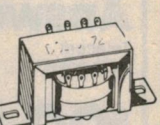

DSE2000. Primary: 240V AC. Secondary: 18 volts @ 6A. Terminations: Flying leads. Cat M-2000

10 up \$28.35


\$29.50

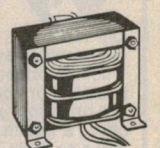

DSE0144. Primary: 240V AC. Secondary: 28-0-28V. Secondary current: 2A. Cat M-0144

\$29.50

\$29.50

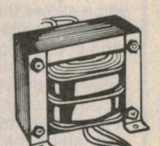

DSE0153. Primary: 240V AC. Secondary voltage: 35-0-35V. Secondary current: 2.5A. Cat M-0153

\$29.50

\$29.50



FERGUSON Low Profiles Too

Famous Ferguson low profile transformers offer low levels of flux leakage (very quiet!) as well as their small profile. All 20VA models, all with twin windings which can be paralleled or seriesed for greater current or voltage output.



2 x 6V@1.7A	M-3596
2 x 7.5V@1.3A	M-3597
2 x 9V@1.1A	M-3598
2 x 12V@.85A	M-3599
2 x 15V@.69A	M-3600
2 x 20V@.51A	M-3601

ALL ONE PRICE! \$24.75 EACH

PLUG-PACKS AS WELL


Plug packs make great sense. The bulky transformer is left on the power point while the whole of the case can be devoted to the circuitry! And your choice of AC or DC output - depending on application.

12V AC at 500mA
Cat M-9555 \$19.95

16V AC at 900mA
Cat M-9567 \$14.95

9V DC at 200mA Cat M-9514 \$11.95

\$11.95

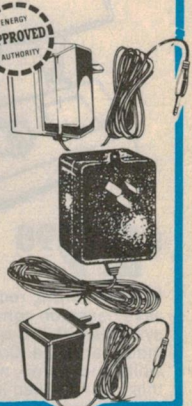

DICK SMITH ELECTRONICS

PTY LTD

The Perfect Answer At The Right Price!

Budget-Priced Answerer

Telecom Authorised

\$99

Our most affordable answering machine priced for the small business or home. But don't let the low price fool you... new technology offers a wealth of features. An amazing 'built-in' female synthesized voice allows the single tape to record more messages than other single tape answering machines. • 40 second recording time permits callers to deliver a full message. PLUS: 8 second VOX auto-off • 3 ring delayed trigger • Call screening and telephone monitor • Volume control • 'Power' and 'Auto Answer' LEDs. All this packed into a compact unit which uses standard size cassettes. Includes power adaptor and Telecom approved phone plug. Cat F-6125



Phone & Answer Machine

Telecom Authorised

\$269

It's a full function push-button phone AND answering machine. Takes up less space, doesn't need two phone sockets or double adaptors, yet gives all the features of both. Single tape unit uses standard audio cassettes, and you only need record your outgoing message once. Retrieve messages left from any phone — anywhere. Cat F-6140



NEW PRODUCT Call Forwarding 2 Tape Answering Machine

\$349

You won't believe that an answering machine could offer so much — at such a low price. But then it's much, much more than an answering machine. Look at the incredible features this state-of-the-art machine has to offer:

- Call forwarding
- "Memo" function
- Emergency message sending
- Answer delay
- Total remote control
- Security coded control

Plus all the "usual" answering machine features. Cat F-6145




16 Memory Hands-free Loudspeaking Phone

\$179

The ideal office companion — even at home! It's the perfect telephone for busy people. Features 16 single touch memories so those important calls are always at your finger tips. Loudspeaking mode allows you to make or answer calls without interrupting your work. Features include adjustable speaker volume, mute switch, 16 single touch memories, handsfree operation, Hookflash for PABX use, adjustable ringer level, Tone/Pulse switchable, battery backup facility, desk or wall mountable and more! Cat F-5136



Deluxe 3 Band Indoor

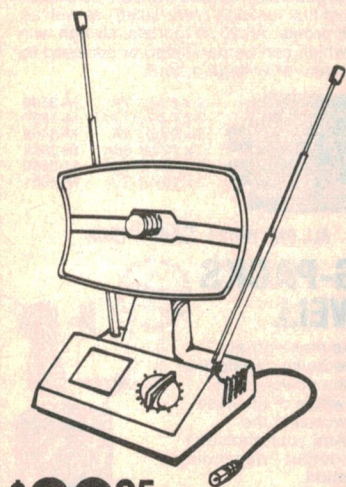


\$29⁹⁵

Ideal for strong reception areas, you'll save heaps on complex outside systems with this quality UHF, FM, VHF indoor antenna. Colour, black and white and stereo, nothing's a worry for this one. Installed in seconds for the perfect picture. Cat L-4005

Get A Clear Picture!!


Indoor UHF/VHF Diplexer

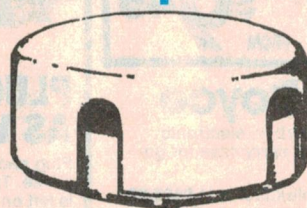

\$9⁹⁵

Many TV sets and videos have only one antenna input: tough luck if you're running VHF and UHF antennas! Now there's a solution — the Diplexer. Accepts lead-ins (75 ohm) from both antennas and combines them without the normal losses associated with couplers used at UHF. Then you can run one lead-in to the TV/Video. Cat L-4470

Go Anywhere FM/TV

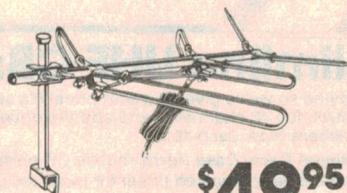


\$49⁹⁵

Here's a go anywhere TV/FM antenna that's small enough to be packed up and put in the camper or van. It even comes with a special 'gutter gripper' bracket for caravan use, plus a mini mast and 7 metres of 300 ohm ribbon. Single folded dipole for maximum performance over wide frequency range, suits horizontal or vertical mounting. Cat L-4026

Even from your old set you can now get...

Stereo TV!

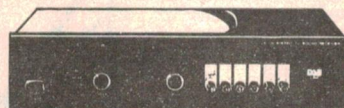


\$199

Your old telly can have the best qualities of the modern ones — without spending a thousand dollars or more on a new model! You can have full stereo sound from your existing set. Just plug in the DSE Stereo Sound Receiver and quality stereo is at your fingertips (and buzzing around the room as well). You can put it through your existing stereo amplifier and speakers for true hi-fi and the 6 preset stations make tuning a breeze. Its handsome design and compact size mean it'll be at home anywhere. 6 preset stations, video and audio output with terminals, mono/stereo mode selection, LED stereo indicator and more! Yes, it's fully compatible with Australian "two carrier" TV system. Comes complete with adaptor plug and connecting leads. Cat L-4905

Metal Line Plug

Cat L-4508

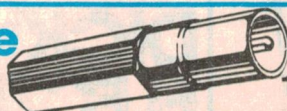

\$1²⁰

10 up 85¢

Metal Line Socket

Cat L-4509



\$1²⁰

10 up 85¢

DICK SMITH ELECTRONICS

PTY LTD

Because you're technical...

Install your own alarm system or second phone, etc, and save a fortune. Put your technical knowledge to work for you instead of someone else!




Control 44444444...!

The Affordable Professional System

The latest in electronic technology and concept, versatile enough for commercial use yet affordable for home use. The Control 4 is a complete 4 sector alarm panel with panic or emergency sector, with provision for a wide range of options which can turn it into a formidable and secure alarm package. Advanced features include adjustable entry, exit and alarm times, 4 inputs PLUS 2 end of line, allows connection to remote keyswitch or codepads for added security, monitors both mains power and standby battery against failure, emergency/panic button, allows silent access for authorised people, allows 24 hour circuits to be monitored (fire, medical, hold-up, freezers, etc), provision for 'At Home' Entry Guard feature, provision for dialler and just about every feature you're likely to ever want! Comes complete with DC adaptor. With Control 4 — you won't need any more! Cat L-5106

\$299

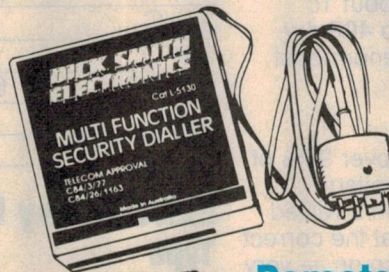


Alarm Phone Dialler


Your home alarm can 'phone' you at work, phone a relative or friend to alert them. Telecom authorised, dial two numbers. Suitable for most alarm types. Cat L-5130

Remote Keyswitch

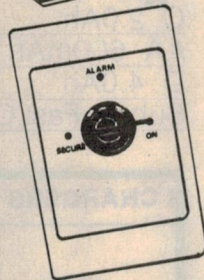Help eliminate accidentally setting off the alarm! The CP1 remote key-switch can be mounted out of the surveillance field of your alarm sensors (eg. in the garage, garden, verandah) so you can arm and disarm your system remotely. With tamper switch and three LED status report. Cat L-5104



\$79⁹⁵

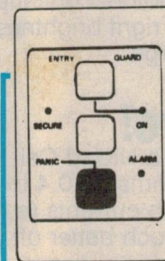


\$249

Entry Guard

Designed for use in conjunction with the Control 4 security system Entry Guard allows you to use your alarm while you're at home. It allows you to monitor one or more sectors of the house (say the perimeter sensors) while others are ignored. Incorporates 24 hour panic button for emergency use. You can even activate an optional plug-in dialler! Cat L-5107

\$79⁹⁵

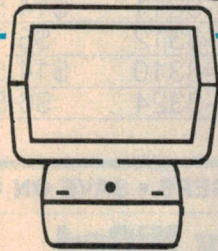

Passive infrared detector

Wide angle protection of rooms, hallways, etc. Adjustable swivel head for precise line of detection. Convenient wall or ceiling mounting. Cat L-5009


\$89⁹⁵

15 metre Phone Extension!



Take the phone from room to room, or out to the patio or pool! With the Telephone Extension Reel you get 15 metres of cable on a retractable spool — so you can keep it tidy! Cat F-5113

\$18⁹⁵

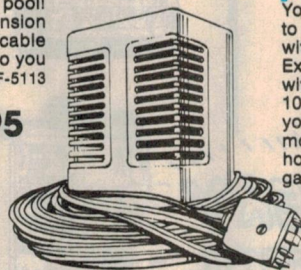


Is that the phone??

You won't have to strain to hear the phone ring with the Telephone Extension Bell. Comes with socket adaptor and 10 metres of lead. All you do is plug it in and move it anywhere in the house, workshop or garden, etc. Cat F-5119

\$19⁹⁵

Hands-Free Telephone with Clock Radio!

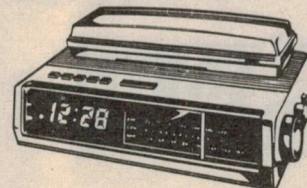Perfect for the bedside table! Alarm Clock Radio with all the features PLUS push-button Telephone with hands-free capability. Sure makes those early morning (or late night) calls easy! Cat F-5109



\$65

Economy Phone!

The economical way to a second phone or replace that clumsy old thing with a modern push button model. Features automatic last number redial, mute switch and ringer On/Off! Cat F-5185


\$19⁹⁵



Double Adaptor

Get away with it! Connect two phones or a phone and an answering machine without disconnecting and reconnecting. Cat F-5112

\$7⁹⁵

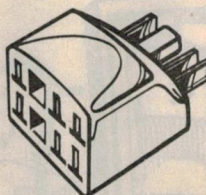

Plugs/Sockets

DSE's phone plugs — identical to Telecom type 605 — as used in all phones, etc. Cat L-5117

\$4⁵⁰



Our 610 phone sockets are designed to Telecom standard... and DSE's versatility. Cat F-5118

\$4⁵⁰



DICK SMITH ELECTRONICS

PTY LTD

• NSW • Albury 21 8399 • Bankstown Square 707 4888 • Blacktown 671 7722 • Blakehurst 546 7744 • Bondi Junction 387 1444 • Brookvale (Warringah Mall) 93 0441 • Campbelltown 27 2199 • Chatswood Chase 411 1955 • Chuliora 642 8922 • Gore Hill 439 5311 • Gosford 25 0235 • Hornsby 477 6633 • Liverpool 600 9888 • Maitland 33 7866 • Miranda 525 2722 • Newcastle 61 1896 • North Ryde 86 3855 • Parramatta 689 2188 • Penrith 32 3400 • Railway Square 211 3777 • Sydney City 267 9111 • Tamworth 66 1711 • Wollongong 28 3800 • ACT • Fyshwick 80 4044 • VIC • Ballarat 31 5433 • Bendigo 43 0388 • Box Hill 890 0699 • East Brighton 592 2366 • Coburg 383 4455 • Essendon 379 7444 • Frankston 783 9144 • Geelong 43 8804 • Melbourne City 67 9834 • Richmond 428 1614 • Ringwood 879 5338 • Springvale 547 0522 • QLD • Brisbane City 229 9377 • Buranda 391 6233 • Chermide 359 6255 • Redbank 288 5599 • Rockhampton 27 9644 • Southport 32 9863 • Toowoomba 38 4300 • Townsville 72 5722 • Underwood 341 0844 • SA • Adelaide City 232 1200 • Darwin 298 8977 • Elizabeth 255 6099 • Enfield 260 6088 • Salisbury 281 1593 • WA • Cannington 451 8666 • Fremantle 335 9733 • North Perth 328 6944 • Perth City 481 3261 • TAS • Hobart 31 0800 • NT • Stuart Park 81 1977

• NICAD SAVINGS • NICAD SAVINGS • GET UP TO 400 CHARGES OUT OF OUR HEAVY DUTY NICADS.

Ideal for all your toys, radios...

Why buy Nicads?

You should expect at least 400 charges from a NiCad battery. If looked after, this can easily be doubled. Taking worst case, each charge for a "AA" cell costs about 1c (electricity costs are negligible). Compare this to 400 dry batteries at about 60c each. . . the savings are enormous!

But there's more!

A NiCad cell holds its voltage virtually constant over 90% of the discharge cycle. A dry cell starts dropping voltage immediately. You don't get the same "drop off" in a NiCad as a dry cell. Therefore motors continue to run at the correct speed, lamps glow at the right brightness, and so on — very close to complete discharge.

And even more!

The internal resistance of a NiCad Cell is much lower than a dry cell. (less than 0.05 ohms Vs 0.4 to 0.8 ohms) Therefore devices which require high currents (e.g. photoflashes, high torque motors, etc) are much better off with NiCad cells than dry cells.

Still not convinced?

You can get much higher continuous current ratings in a NiCad cell than a dry cell. While not rated the same way, a dry cell discharged at 90mA is considered "flat" (1.1V) after approx. 2.5 hours. A NiCad cell lasts almost 5.5 hours under the same conditions. Even under non-continuous discharge conditions, the NiCad cell wins hands down: because the NiCad can be re-charged between uses!



Information supplied courtesy
Plessey Ltd & SAFT (Pte) Ltd


Battery Packs

Qty	Type	Cat No.	Price
4 x AA	500mAh	S-3150	\$16.95
2 x C	1.2Ah	S-3152	\$15.95
2 x D	1.2Ah	S-3154	\$16.50
4 x AA	600mAh	S-3160	\$19.95
2 x C	2.0Ah	S-3162	\$24.95
2 x D	4.0Ah	S-3164	\$27.95

Extra Heavy Duty NiCads

Type	Cat No.	Price
C 2.0Ah	S-3311	\$14.50
AA 600mAh	S-3312	\$5.50
D 4.0Ah	S-3310	\$14.50
Sub C Fast Charge	S-3324	\$6.50


CHARGERS • SAVE ON CHARGERS • SAVE ON CH

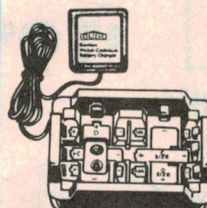

Eveready NiCad Charger

Multi-size (AA, C, D or 9V) NiCad battery charger. Takes two 1.2V cells at a time or one 9V. Complete unit including plug-pack: nothing extra to buy. Cat M-9515

\$27⁵⁰

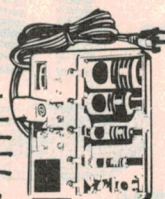


Multi-cell Charger

Charge up to 4 batteries at a time — AA, C, D, 6V or 9V. AND you can also charge AAA, and button cells too! But there's more: a test meter to check NiCad voltage under load — the only way to check your battery properly. Fully approved plug-pack included.

\$34

Cat M-9518

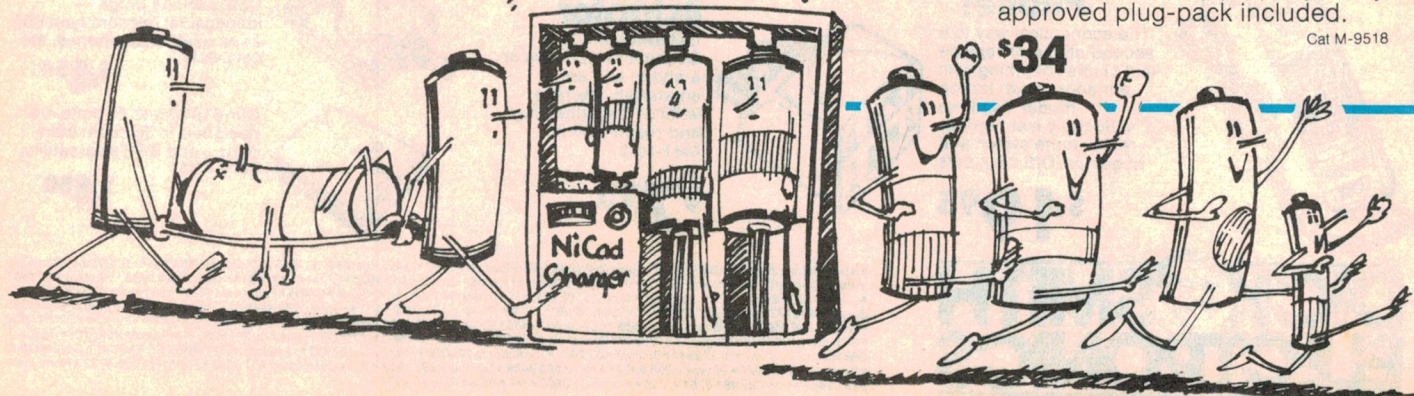

Build this low-cost wireless guitar link

You don't have to run long leads between your guitar and the amplifier or mixer unit. This professional quality FM wireless transmitter plugs into your instrument and transmits the signal to the amplifier via an FM receiver.

by BRANCO JUSTIC

The FM wireless transmitter published in the September 1986 issue was described simply as a printed circuit board with optional microphone preamplifier. We left it to the readers to house it in a box to suit their particular

application.

Since then, many readers have asked us to publish the full details on this circuit, showing how the module could be housed in a suitable case complete with battery, on/off switch and input socket.



As described, the original transmitter has sufficient sensitivity for line level inputs such as from a guitar and various other electronic musical instruments. The sensitivity level is set by means of a trimpot (VR1) at the input. The optional microphone preamplifier is unnecessary in this application and can be deleted from the circuit.

A plastic case measuring 120 x 65 x 40mm houses the transmitter and 9V battery for the power supply. At one end of the case is a 6.5mm panel socket for the signal input and an on/off power switch. The 600mm antenna wire for the module is fed through a hole drilled in the opposite end of the case.

A clip can be attached to the case lid to allow the unit to be attached to a trouser belt.

The circuit diagram (Fig.1) is very simple, and involves just a few external connections to the FM wireless transmitter PCB. These are for the audio input socket, the antenna and the power supply connections. The 9V battery supply is switched using a SPDT toggle switch (S1).

Construction

The transmitter uses the FM wireless transmitter module described in September 1986. This should be constructed as described in the article but, as noted above, the optional microphone preamplifier stage (Q6, Q7) is deleted.

In fact, the preamplifier section of the PCB should be separated from the rest of the PCB so that the completed module will fit in the recommended case.

Once the module has been completed, drill the necessary holes in the case to accommodate the on/off switch, audio socket and antenna lead. Fig.2 shows the details. The belt clip is secured to the lid of the case using a screw and nut. Follow the wiring diagram when wiring up the connections to the transmitter module. It is not necessary to use screened cable between the socket and PCB because of the short distance involved. The antenna lead should be about 600mm long and can be made by trimming one end of


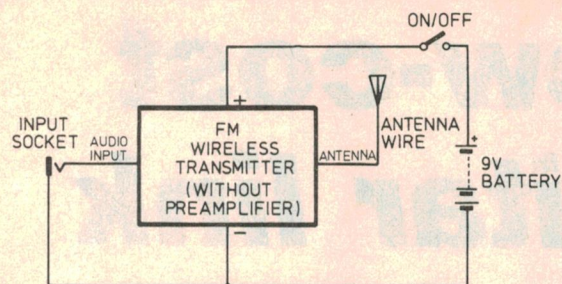
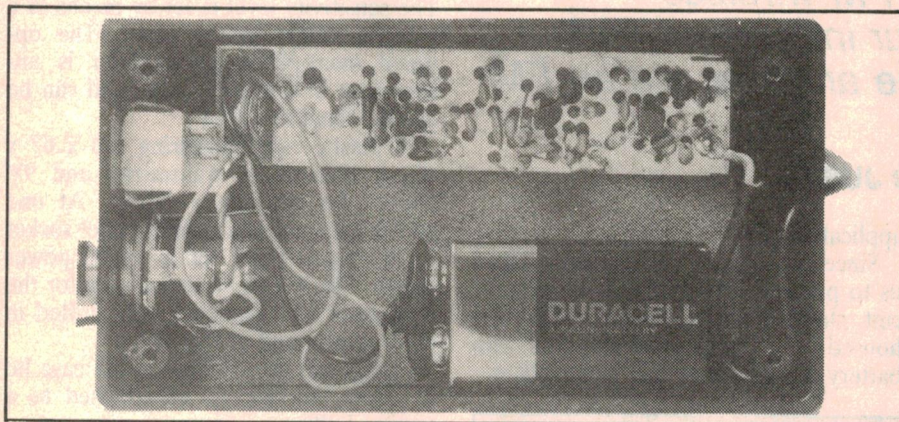


Fig.1 (above): the schematic, and Fig.2: the wiring diagram of the wireless guitar link, which is based on the FM wireless transmitter of September 1986.

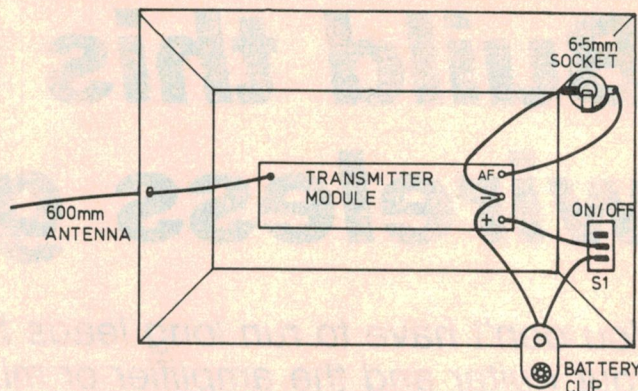

Inside the box. There's not a great deal involved, apart from the transmitter module.

the 2-metre coax cable supplied with the kit. It can be hooked around one of the support pillars in the case to provide strain relief.

Note that the inside and outside conductors of the antenna lead should be soldered together at the transmitter module.

The PCB and battery are secured in

the case using several pieces of foam rubber. Make sure that the battery cannot move and short out any of the connections before screwing the lid down.

Finally, an FM Walkman-style receiver makes an ideal companion unit to the Musolink. We showed you how to connect such a receiver to your amplifier in the October 1986 edition.

PARTS LIST

- 1 FM wireless transmitter (September 1986)
- 1 plastic case, 120 x 65 x 40mm
- 1 SPST rocker switch
- 1 6.5mm panel mounting mono socket
- 1 moulded plug with 2-metre coax lead
- 1 6.35mm jack plug
- 1 belt clip

Miscellaneous

Screw, nut, foam plastic, hookup wire, solder etc.

Note: a complete kit of parts for the Musolink is available for \$23.90 (incl. p&p) from Oatley Electronics, 5 Lansdowne Parade, Oatley, NSW 2223. Phone (02) 579 4985. Send mail orders to PO Box 89, Oatley, NSW 2223.

AVAILABLE NOW IN AUSTRALIA

★ AUDIO DRIVE BELTS ★ TURNTABLE BELTS ★ PINCHROLLERS ★ VIDEO BELTS



TURNTABLES

Turntable belts are available in 5 mm & 6 mm with diameters commencing from 122 mm up to 292 mm.

TRADE & WHOLESALE ENQUIRIES WELCOME

Imported & Distributed by WES COMPONENTS PTY. LTD.
For a comprehensive catalogue send your company or business details to: PO. Box 451 Ashfield NSW 2131 Aust.,
Phone: (02) 797 9866 Fax: (02) 799 7051

VIDEO

Over 60 Video Belt Kits in stock to suit most popular video machines. Other video parts also available ie: pinchrollers, heads, etc.


AUDIO CASSETTE

A range of belts is available in 1.2 mm square & 1.4 mm square, from the 19 mm diameter up to 136 mm diameter. These will suit most audio products. If a flat belt is required our range includes 3 mm, 4 mm, 5 mm & 6 mm belts in an assortment of lengths. An assortment of pinchrollers is also available.

Please call for a stocklist or bring in your sample belt and we will match it.

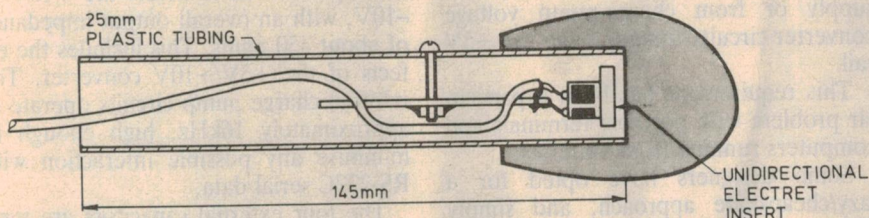WAGNER ELECTRONIC SERVICES PTY. LTD.,
305 Liverpool Rd., Ashfield, N.S.W. 2131. Aust.,
Phone: (02) 798-9233





Adding a microphone to your musolink

Many readers who have made the FM transmitter module (EA Sept. 1986) have asked how to connect an electret microphone to the unit. Here we describe how this can be done easily. We also show two different microphone assemblies which can be added to the original transmitter or the musolink transmitter.

The two units shown here are:

1. A clip-on omnidirectional microphone.
2. A hand-held unidirectional microphone.

As one reader pointed out (EA May 1987), the microphone is especially useful as an aid for people with hearing difficulties. The transmitted signal can be picked up by an inexpensive "walkman" type of receiver. The required microphone can be assembled on an alligator clip so that the unit can be easily attached near the sound source.

The alternative hand held microphone was assembled into a short length of 25mm plastic tubing. The microphone was supported by soldering its negative terminal to a small piece of unetched single sided

printed circuit board. Two holes drilled on the PCB were used as a means of clamping the cable whilst a nut which was soldered to the PCB attaches it to the plastic tube by means of a single screw.

Depending on your application you may choose from the omnidirectional insert or the unidirectional insert. For a description of the two inserts refer to a project called "The Microphone" which was featured in the November 1986 issue of EA.

The construction of the microphones should be self explanatory from the accompanying photographs. They are mainly intended to give some ideas on inexpensive materials which can be effectively used. However to accommodate for the necessary combination of an AC signal and a DC supply on the one lead ("phantom power supply") a resistor and a capacitor have to be added to the transmitter circuit.

We have used the unidirectional insert in the hand held microphone shown.

The various bits and pieces used in the microphone are available from Oatley Electronics.

KALEX

UV MATERIALS

3M Scotchcal Photosensitive

		Pack Price	
		250 x 300 mm	300 x 600 mm
8001	Red/Aluminium	\$70.15	\$80.75
8005	Black/Aluminium	\$70.15	\$80.75
8007	Reversal film	\$38.20	\$51.40
8009	Blue/Aluminium	\$70.15	\$80.75
8011	Red/White	\$63.20	\$72.70
8013	Black/Yellow	\$63.20	\$72.70
8015	Black/White	\$63.20	\$72.70
8016	Blue/White	\$63.20	\$72.70
8018	Green/White	\$63.20	\$72.70
8030	Black/Gold	\$88.90	\$108.00
8060	Black/Silver	\$63.20	\$72.70

UV PROCESSING EQUIPMENT

KALEX LIGHT BOX

- Autoreset Timer
- 2 Level Exposure
- Timing Light
- Instant Light Up
- Safety Micro Switch
- Exposure to 22in x 11in

\$599.00 + ST

KALEX "PORTU-VEE"

- UV Light Box
- Fully Portable
- Exposure to 10in x 6in

\$199.00 + ST

PCB PROCESSING

KALEX ETCH TANK

- Two Compartment
- Heater
- Recirculation (by Magnetic Pump)
- Two Level Rack • Lid

\$595.00 + ST

RISTON 3400 PCB MATERIAL

SIZE INCHES	SINGLE SIDED	DOUBLE SIDED
36 x 24	\$90.00	\$117.00
24 x 18	\$45.00	\$ 58.50
18 x 12	\$22.50	\$ 29.25
12 x 12	\$15.00	\$ 19.50
12 x 6	\$ 8.00	\$ 10.00

All prices plus sales tax if applicable


KALEX 40 Wallis Ave.
East Ivanhoe 3079
(03) 497 3422
497 3034
Telex AA 37678



ELECTRONIC COMPONENTS & ACCESSORIES
• SPECIALIST SCHOOL SUPPLIERS

Solid State Update

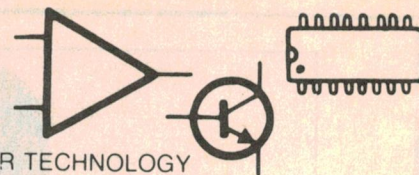KEEPING YOU INFORMED ON THE LATEST DEVELOPMENTS IN SEMICONDUCTOR TECHNOLOGY



Introduction

Hi! This is the first appearance of a new regular column, designed to keep you up to date on the latest developments in semiconductor technology. Each month we're going to discuss interesting new ICs or discrete components, new ways to use semiconductor devices, or new developments in the manufacture of these devices. Anything timely and to do with semiconductors and solid state electronics, in other words.

New chip simplifies RS-232C interfacing

In the spotlight this month we have a chip designed to take a lot of the hassle out of providing interface circuits for RS-232C serial communications ports in computers, modems, terminals, instruments or whatever. It's the MAX232 from Maxim Integrated Products, a dual RS-232C receiver/transmitter.

What's so new about an RS-232 receiver/transmitter? After all, RS-232 receiver and transmitter chips have been around for quite a while — chips like the trusty MS1488 and MC1488, and their clones.

The catch is that up until now, in order to use these existing chips to pro-

vide a true RS-232C interface, you needed to supply the transmitter chip in particular with bipolar power supplies — usually $\pm 12V$. This was to allow the chip to provide the bipolar output voltage swing needed for true RS-232C operation.

In many modern digital circuits this can be quite a nuisance, because often the rest of the circuit runs on a single $+5V$ supply. So it may well become necessary to provide $\pm 12V$ supply rails purely for the RS-232C interface, generating them either from the main power supply or from charge-pump voltage converter circuits running from the $+5V$ rail.

This requirement has been a particular problem with portable terminals and computers running from batteries.

Some designers have opted for a lazy/cheapskate approach, and simply ignored the need for a bipolar RS-232 output. But this produces a circuit that is non-standard, and often won't work reliably with other nominally standard RS-232C equipment.

The new MAX232 chip solves all of these hassles, providing true bipolar output signals which meet all of the RS-232C specs. Yet the chip runs from a single $+5V$ supply, generating the necessary bipolar voltages ($\pm 10V$) itself via a pair of on-chip charge pump converters.

Only a handful of external components is needed, as you can see from the diagram.

One charge pump circuit uses external capacitor C1 to double the $+5V$ input to $+10V$, with an output impedance of approximately 200 ohms. As well as being used internally by the RS-232C output drivers, this can also be used as a pullup supply for resistors used to terminate the DTR and DSRS lines.

The second charge pump uses external capacitor C2 to invert the $+10V$ to $-10V$, with an overall output impedance of about 450 ohms. This includes the effects of the $+5V/+10V$ converter. The internal charge pump circuits operate at approximately 16kHz, high enough to minimise any possible interaction with RS-232C serial data.


The four external capacitors are typically 22uF as shown, but their values are not critical. They can be low cost aluminium electrolytics, or tantalums if size is critical. Increasing the value of C1 and C2 to 47uF will lower the output impedance of the $+10V$ output by about 5 ohms, and that of the $-10V$ output by about 10 ohms. Increasing the value of C3 and C4 lowers the 16kHz ripple on the RS-232C outputs.

In systems where size is critical, all four capacitors can be reduced in value to 1uF, at the expense of an additional 20 ohms impedance in the $+10V$ output and 40 ohms in the $-10V$ output. The 16kHz ripple on the $-10V$ output also rises to 250mV.

Each of the two RS-232C transmitter drivers on the MAX232 is a CMOS inverter powered by the $\pm 10V$ internally generated supplies. The inputs are TTL and CMOS compatible, with a logic threshold of about 26% of V_{CC} (1.3V for a 5V rail). The input of an unused transmitter section can be left unconnected; an internal 400k pullup resistor connected between the transmitter input and V_{CC} will pull the input high, forcing the unused transmitter output low.

The open circuit output voltage swing is from $+9.4V$ ($V^+ - 0.6V$) to $-10V$. The outputs are guaranteed to meet the RS-232C specification of $\pm 5V$ minimum output swing, under the worst case conditions of both transmitters

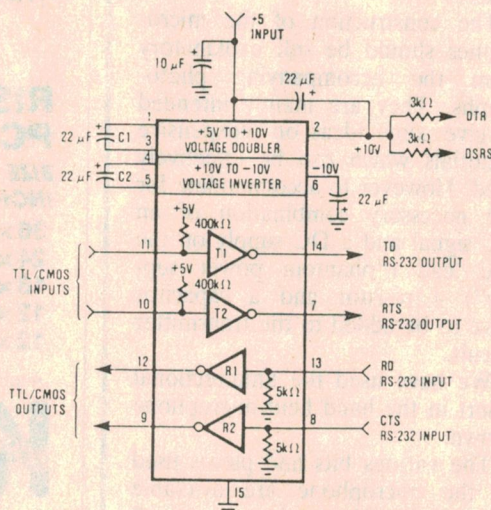How the MAX232 chip is used in a typical communications interface. It provides two RS-232C receivers and two transmitters with true bipolar outputs — but works from a single $+5V$ supply.



driving a 3k minimum load impedance, the Vcc input at +4.5V and maximum allowable ambient temperature. The outputs are limited to the RS-232C maximum slew rate of 30V/us, and are short-circuit protected.

The two receivers on the MAX232 fully conform to RS-232C specs. They have a 5k input impedance and can withstand up to +/-30V inputs, either with or without 5V power applied to the chip. The receivers are inverters; i.e., their TTL/CMOS outputs are low whenever the incoming RS-232C line concerned is more positive than +2.4V. Conversely they swing high whenever the input is floating or driven more negative than +0.8V.

As shown in the circuit, a single MAX232 chip can handle most signal requirements for a normal RS-232C interface. However if additional signal lines must be implemented, a second MAX232 can be coupled to the first. In this case the +10V and -10V outputs of both chips are tied together, to ensure correct operation.

All this from a little CMOS chip which runs on little more than the smell of an oily rag — well, only about 5mA quiescent current! It's also available in a 16-pin outline package for surface mounting, as well as a normal plastic or ceramic 16-pin DIP.

MAX232 chips are available locally for \$12.96 each from Geoff Wood Electronics, of 229 Burns Bay Road, Lane Cove West 2066. (J.R.)

FUNDAMENTALS OF SOLID STATE

Inside this book you'll find a wealth of basic information on the theory and operation of semiconductors — diodes, transistors, thyristors, FETs and integrated circuits. It's for anyone who wants to know that little bit more about solid state devices and the way they work.

only \$4.50

plus \$1.00 post and handling

Send your order to:

Freepost No.4

Federal Publishing Book Sales,

PO Box 227

Waterloo NSW 2017

MINIMUM 50% OFF

Boschert SWITCHING POWER SUPPLIES

At the end of the financial year, we identified several areas of overstocking. The following power supplies are brand new but old stock. Our normal 12 months warranty applies.

	List Price	Sale Price
MULTIPLE OUTPUTS		
Input voltage: 90-132V/180-264VAC		
XL50-4602 60 watt	\$198	\$ 98
Outputs: +5V 6A, +12V 0.7A, -12V 0.7A, +24V 2A		
XL50-4603 60 watt	\$198	\$98
Outputs: +5V 6A, +12V 3A, +12V 1.5A, -12V 0.7A		
XL53-4603 65 watt	\$225	\$100
Outputs: +5V 6A, +12V 0.6A, -12V 0.6A, 24V 1.25A		
XL80-4601 80 watt	\$260	\$120
Outputs: +5V 8A, -5V 0.7A, +12V 3.5A, -12V 0.7A		
OL153-2033 180 watt (240V input only)	\$500	\$250
Outputs: +5V 20A, +12V 4A -12V 4A, +24V 4A		
OL200-4024 200 watt	\$500	\$250
Outputs: +5V 25A, +12V 4A, -12V 4A, +24V 4A		
XL200-4501 200 watt	\$500	\$250
Outputs: +5V 25A, +12V 4A, -12V 4A, -5V 4A		
OL301-4026 300 watt	\$647	\$320
Outputs: +5V 20A, +12V 4A, -12V 4A, +15V 4A, -15V 4A, +24V 4A		
SINGLE OUTPUTS		
Input voltage: 90-132V/180-264VAC		
ES50-4605 Eurocard 50 watt	\$210	\$98
Output: +5V 10A		
SL120-4612 120 watt	\$265	\$130
Output: 11.5-15V adjustable		
DC-DC DOWN CONVERTERS		
3T5AN-6030		
Input: +20 to 60 VDC	\$200	\$100
Output: -4.5 to -30VDC adjustable 5A		
3T5AN-4030		
Input: +10 to 40 VDC	\$200	\$80
Output: -4.5 to -30 VDC adjustable 5A		

Add 20% Sales Tax if applicable.
Freight: \$7 per order

**ONLY WHILE CURRENT
STOCKS LAST**

AMTEX
ELECTRONICS


A DIVISION OF METAL MANUFACTURES LIMITED

36 LISBON STREET, FAIRFIELD, NSW 2165. AUSTRALIA
TELEPHONE: (02) 728-2121, 727-5444
TELEX: AA27922 ATTN AMTEX
FACSIMILE: (02) 728-6908, 728-2837
MELBOURNE TEL: (03) 890-6999

A really BIG LED display module!

Need to produce an LED display that can be seen from a long way off? This single digit 153mm high seven segment LED display module is just what you need. It can be used as a replacement for both common anode and common cathode LED displays, can be either multiplexed or DC driven, and can be provided with a decimal point on either the right or left.

by JOHN CLARKE

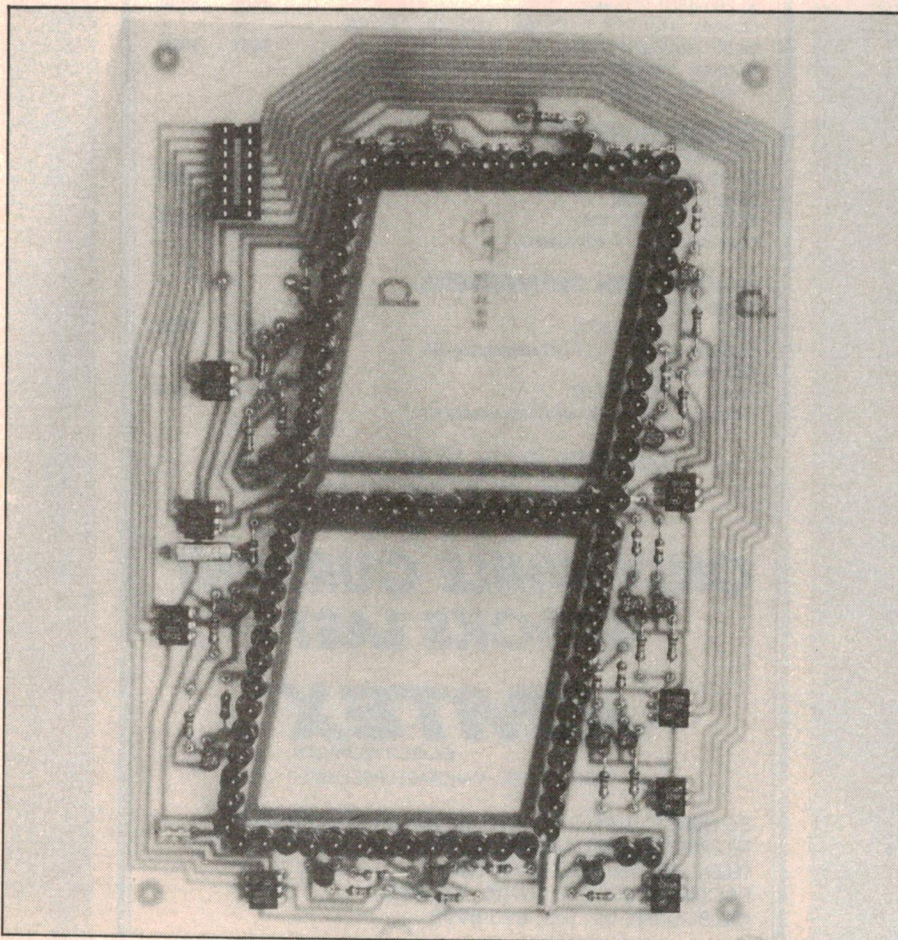

You'll need one of these for each digit of a display.

The large LED display module to be described should find use in classrooms and lecture theatres, so that a demonstration can be seen by everyone. A set of the modules can display voltage, temperature or any other parameter simply by using them to replace the LED display in the piece of measuring equipment concerned.

The module should also have application in industry, to indicate process parameters which are important enough to be prominently displayed so that they will be visible over a large area (say a control room). No doubt there will also be novelty applications, such as a large digital clock and an event or elapsed timer for sports grounds and functions.


The display module has been designed to be fully compatible with standard smaller seven segment LED displays, of either the common cathode or common anode type. However the display is separately powered, so that its considerably higher power requirements do not cause additional drain on the original LED display circuit.

No modifications are necessary to the original LED display circuit to enable incorporation of the large display. The original display is removed and the inputs of the large display module connected in its place. The secret of this direct compatibility is the use of optocouplers, to isolate the segment and decimal point drivers of the large display.

An optocoupler consists internally of an LED which optically drives a phototransistor. Since it is the optocoupler LED which is driven, instead of the original small LED display, there is direct compatibility between the displays.

The LED terminals to the optocoupler are left free, so that all the optocoupler anodes can be connected to simulate a common anode display or all the cathodes connected for simulation of a common cathode display.

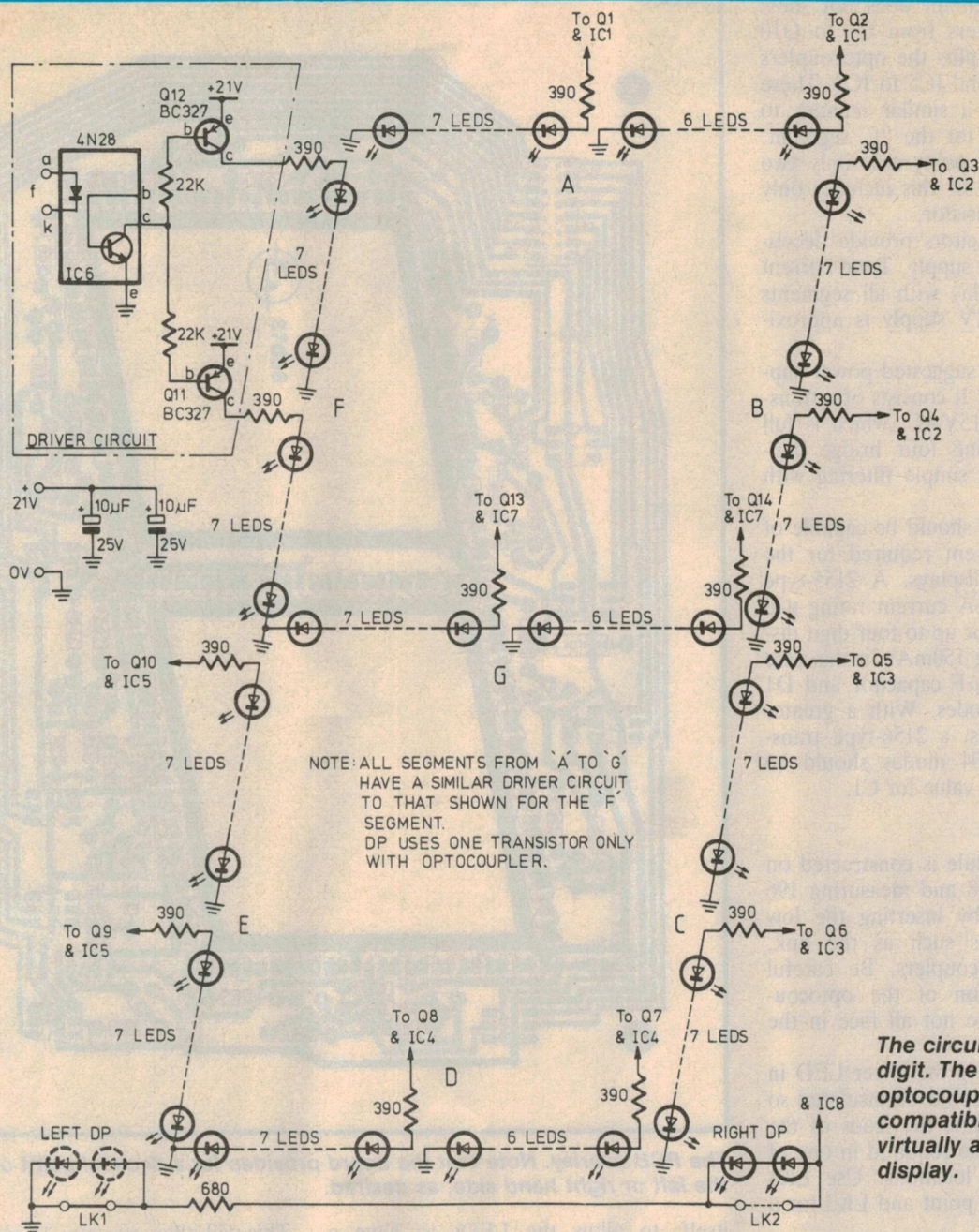The module's display can be configured for left or right hand decimal points, to match displays with either a



The circuit for each digit. The inputs use optocouplers to provide compatibility with virtually any existing display.

left or right channel decimal point.

The large LED display module has a digit which consists of 95 LEDs, arranged in a standard seven segment format. Two further LEDs are used for the left or right decimal point. The LEDs are arranged on a printed circuit board, with the associated LED driving circuitry located around these LEDs. It is quite easy to mount several of the modules side by side to produce a multi-digit display.

Circuitry

The circuit for the module comprises eight optocouplers which provide the interface between a conventional LED

display and the circuit. These optocouplers drive transistors which in turn drive the LEDs forming each large display segment.

As shown in the circuit schematic, the "f" segment comprises two sets of seven series connected LEDs. Each set is driven by a BC327 transistor with current limiting using a 390Ω resistor. The base of each transistor is driven via a 22kΩ resistor at the collector of the optocoupler transistor. When the optocoupler LED is powered, the optocoupler transistor turns on to allow base current flow to the BC327 transistors. These transistors switch on and drive the series connected LEDs.

PARTS LIST

- 1 PCB coded 87ds8, 196 x 141mm
- 97 5mm red LEDs
- 15 BC327 PNP transistors
- 8 4N28 optocouplers
- 2 10uF 25VW axial electrolytic capacitors
- 15 22k ohm 0.25W resistors
- 1 680 ohm 0.25W resistor
- 14 390 ohm 0.25W resistors
- 15mm of insulated link wire
- 1 16 pin socket (optional)
- 1 16 pin header plug (optional)

Note that the circuit does not show the transistor drivers from Q1 to Q10 and Q13 to Q15, plus the optocouplers from IC1 to IC3 and IC5 to IC8. These are connected in a similar manner to the circuit shown for the "f" segment. Since the decimal point uses only two LEDs, the circuit for this includes only a single driver transistor.

Two 10 μ F capacitors provide decoupling of the power supply. Total current drain for the display with all segments lit and using a 21V supply is approximately 150mA.

Fig.1 shows the suggested power supply for the display. It consists of a transformer providing 15VAC, which is full wave rectified using four bridge connected diodes and simple filtering with C1.


The transformer should be capable of supplying the current required for the total number of displays. A 2155-type transformer with 1A current rating will supply the needs for up to four digit displays each drawing 150mA. In this case C1 can be a 1000 μ F capacitor and D1 to D4, 1N4002 diodes. With a greater number of displays, a 2156-type transformer and 1N5404 diodes should be used, with a larger value for C1.

Construction

The display module is constructed on a PCB coded 87ds8 and measuring 196 x 141mm. Begin by inserting the low profile components such as the link, resistors and optocouplers. Be careful with the orientation of the optocouplers, since they do not all face in the same direction.

The link straddling the lower LED in the "b" segment should be insulated so that it does not short the leads of the LED. Linking is also required in one of the decimal point locations. Use LK1 for a right decimal point and LK2 for a left decimal point.

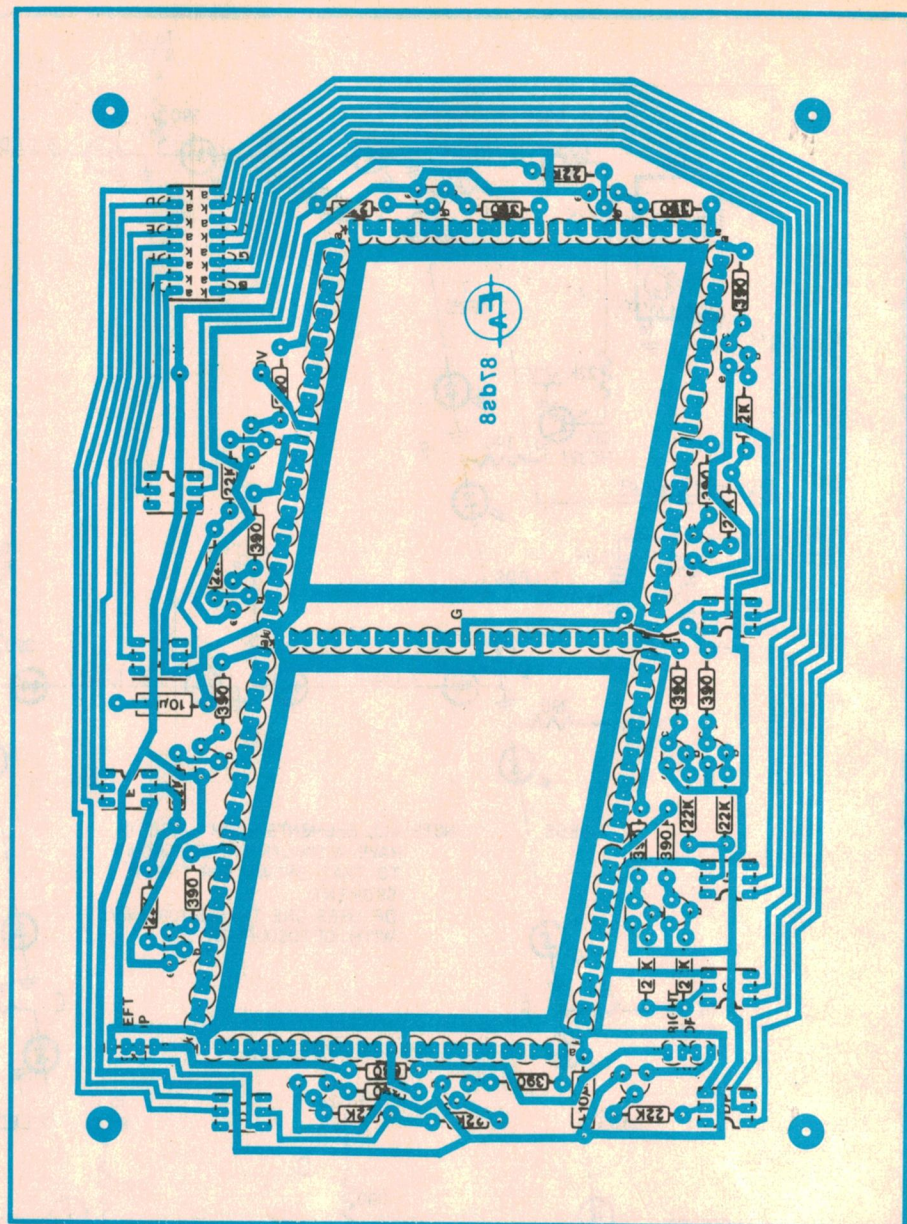The two capacitors can be installed at this stage, taking note of the correct polarity. The transistors should be installed as closely as possible to the PCB



The PCB overlay. Note that the board provides for a decimal point on either the left or right hand side, as desired.

itself, to allow the LEDs to have a higher profile above the PCB.

A 16-pin IC socket can be used for the seven segment and decimal point inputs at the top left side of the PCB.

This will allow use of a 16 pin header to be inserted for external connections.

Finally, the LEDs can be installed. Begin by inserting every second LED fully down onto the PCB, taking care that they are orientated correctly. The longer lead is the anode while the flat side on the LED body is the cathode. Solder only one lead for the present, to allow adjustment of the LEDs in a straight line.

Now the in-between LEDs can be inserted. Full insertion onto the PCB for these LEDs is prevented by the plastic rim around the LED base. This is a reasonably attractive arrangement, however some readers may prefer to snip off the rim with side cutters to allow full


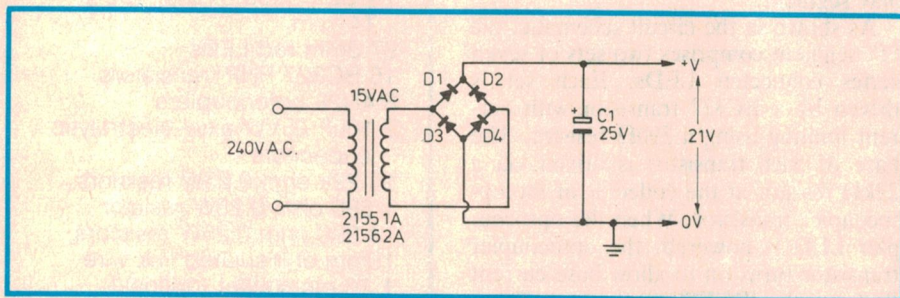


Fig.1: A suggested power supply, capable of running up to 4 digit modules with a 1A transformer or 8 modules with a 2A type.

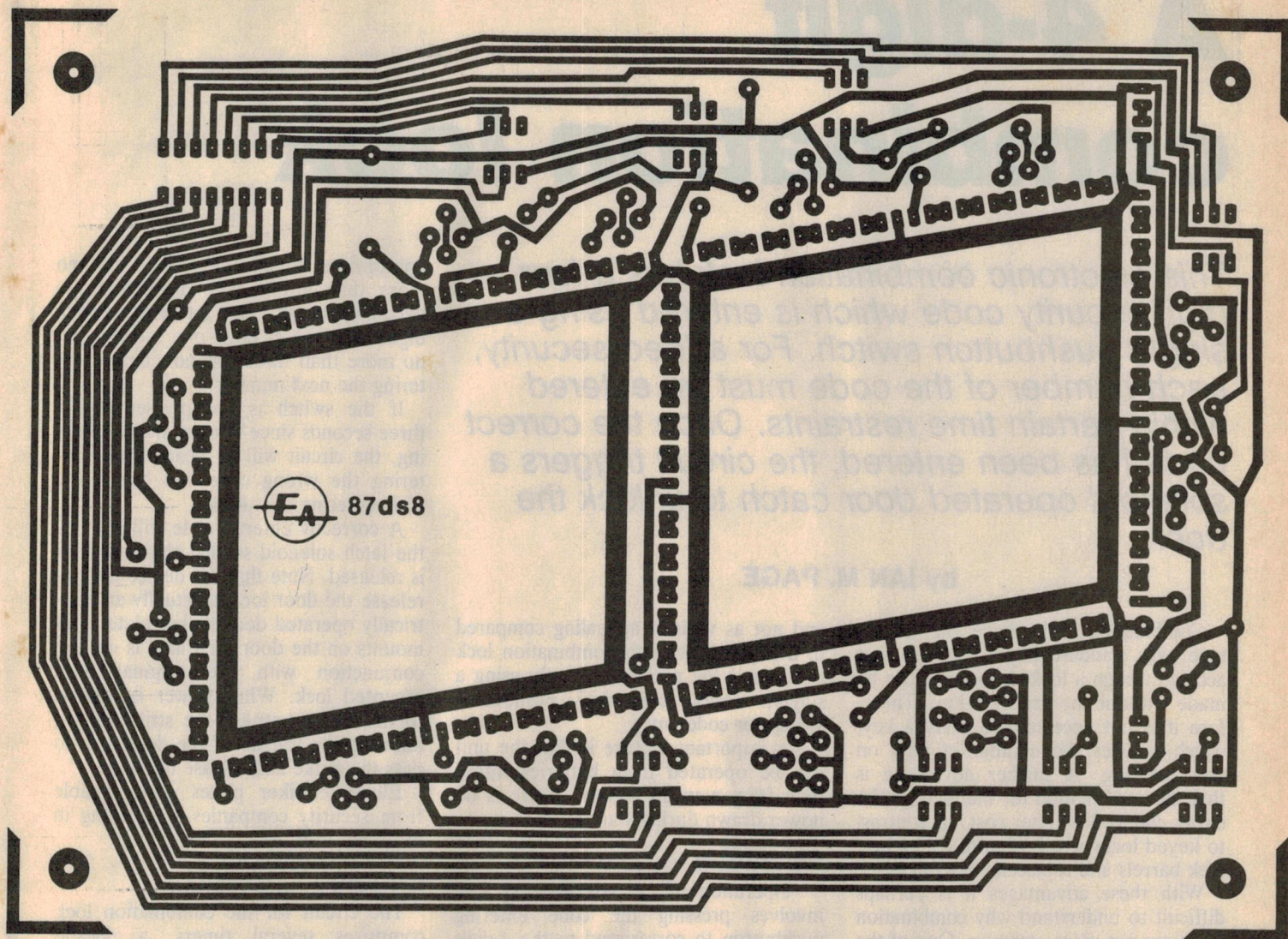

The PCB pattern itself, reproduced actual size (we just made it!).

insertion on the PCB.

Solder these in position for one lead only and align the LEDs so that each segment is in a straight line. The remaining leads on all the LEDs can now be soldered.

That completes work on the display module PCB.

Testing requires a power supply of about 21V with current capability of at least 150mA. Connect the positive (+) and ground power terminals for the large display module to the power supply and the cathodes of the optocoupler LEDs to ground. To light a segment, connect a 3.9kΩ resistor between the anode of an optocoupler and the positive supply. This should light the large segment associated with that optocoupler.

Should the segment not light, check

for incorrectly orientated or faulty LEDs. Similarly check that all the remaining segments operate.

When the display is used in a multiplexed situation, the resistor values specified will be suitable to give sufficient brightness for up to four digits. To give greater LED brightness, the resistor values for limiting the LED current and base drive to the transistors can be reduced. LED current is calculated assuming that there is a 2V drop across each LED, leaving about 7V across the resistor. The current through the transistor base should be 20 times less than the LED current, to ensure saturation of the transistor.

Note that we are assuming that the current through the optocoupler LED is sufficient to ensure saturation of the phototransistor. This should normally

be the case.

Installation

There are four holes located in the corners of the PCB suitable for mounting the display. When more than one digit is used, each PCB can be secured at regular spacing onto a backing plate. To give protection for the diodes and ensure greater visibility, a red Perspex screen can be secured over the front of the display.

Connection of the large LED display to a seven segment LED driver circuit requires knowledge of the pinouts and polarity for the particular LED display involved. The Dick Smith catalog shows pinouts for several of the LED displays, but for greater detail and information on other displays, refer to the manufacturers' optoelectronic data books. EA

A 4-digit combination lock

This electronic combination lock has a four digit security code which is entered using a single pushbutton switch. For added security, each number of the code must be entered within certain time restraints. Once the correct code has been entered, the circuit triggers a solenoid operated door catch to unlock the door.

by IAN M. PAGE

Combination locks have the advantage over standard keyed locks in that access through a locked doorway can be made without the use of a key. Therefore it is not necessary to carry a key, which reduces the number of keys on your keyring. A further advantage is that the combination for the lock can be easily changed without cost, in contrast to keyed locks which require fitting new lock barrels and replacement of keys.

With these advantages it is perhaps difficult to understand why combination locks are not more common. One of the reasons could be that the keypad used to enter the code is usually obtrusive,

and not as visually appealing compared to a keyed lock. This combination lock overcomes the problem by only using a single, easily concealed pushbutton switch for code entry.

An important feature is that the unit can be operated from batteries rather than from a mains supply. There is no power drawn during standby.

Operation

Operation of the combination lock involves pressing the code entering pushbutton to correspond to the 4-digit code. Each digit of the code is entered separately by pressing the button the

appropriate number of times, with no more than a one second interval between pressings. The interval between digits must be at least one second, but no more than three seconds, before entering the next number.

If the switch is not pressed within three seconds since the last switch pressing, the circuit will be deactivated. Entering the wrong code will cancel the code entering operation.

A correctly entered code will activate the latch solenoid so that the door lock is released. Note that the device used to release the door lock is actually an electrically operated door striker plate. This mounts on the door jamb and is used in conjunction with the original door mounted lock. When power is applied to the electric strike, the strike opens, allowing the tongue of the door lock to pass the strike and release the door.


Electric striker plates are available from security companies specialising in locks.

Circuitry


The circuit for the combination lock comprises several timers, a decade counter, latches and a solenoid driver. The decade counter is used to count the input pulses from the switch and produce an output at one of its ten pins corresponding to the number of pulses received. When a correct code number is entered, an SCR switches on preparing the circuit for the next number in the code. As each number is correctly entered, the corresponding SCR triggers on. Finally, on the last entered code the solenoid SCR fires to power the door lock solenoid.

An incorrect number or wrong timing will cause all the SCRs to drop out of the circuit, cancelling the counting operation.

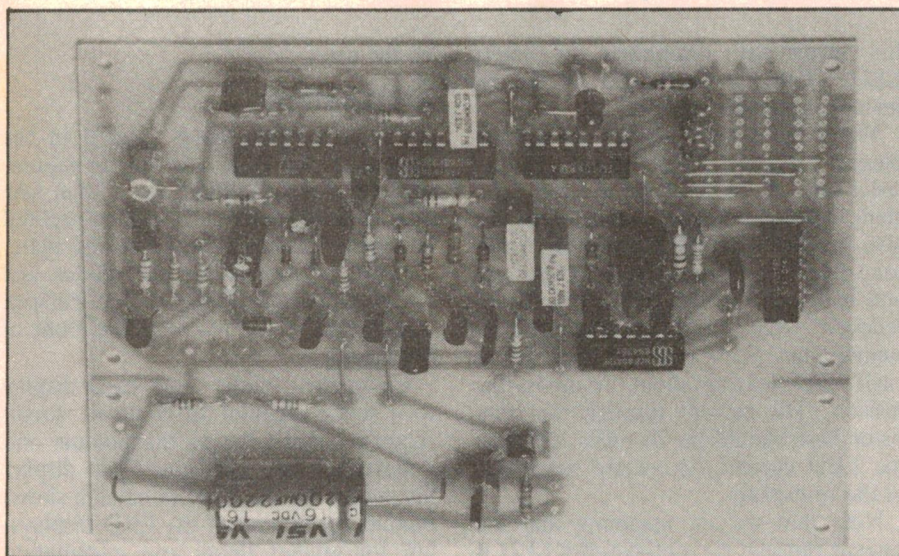Let's take a look at the circuit in more detail. Initially, capacitor C1 is charged to the supply voltage via R1. When S1 is first closed, C1 is discharged via D1 and turns on Q1 due to the base current through R2. Q1 switches on Q2, which supplies power to the remainder of the circuit.



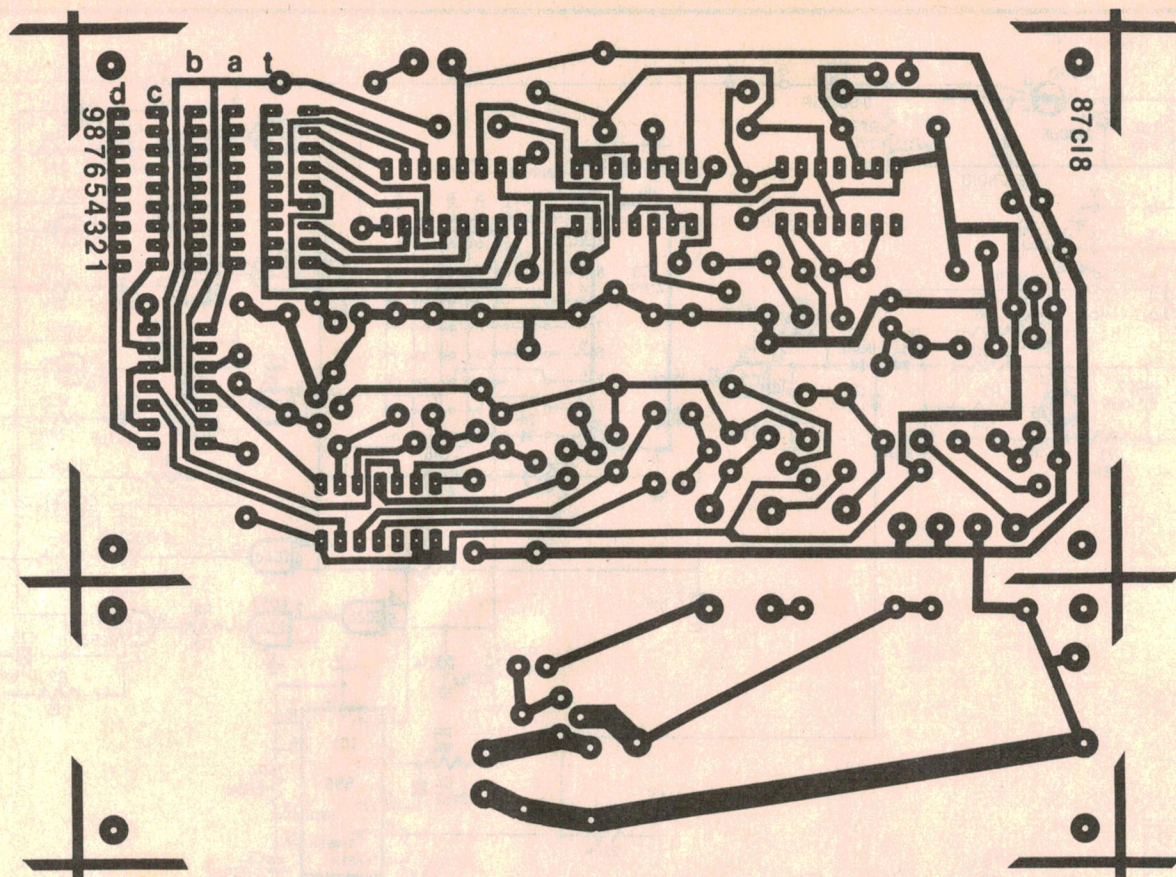The PC board for the combination lock. Programming for the code digits is carried out using the diodes and links in the top right hand corner.



The PCB, reproduced actual size. The latch unit driver section can be separated if required.

D2. Capacitor C1 charges up via R1 and base resistor R2 when S1 is open. If S1 is not pressed within about three seconds, C1 will charge sufficiently to switch off Q1 and disconnect power to the circuit.

Capacitor C5 remains held in the discharged state, provided that S1 is pressed more often than once per second. This is the timing period for the first timer of IC1.

Capacitor C6 at the input to Schmitt trigger IC2c charges via R9 to provide about a 10ms debounce period for switch S1. Whenever S1 is pressed, the output of IC2c goes high and clocks IC3. This sets the "1" output of IC3 high. At each pressing of S1, the next output of IC3 goes high. The switch should be pressed the same number of times as the first number in the combination code. After completing code entry of the first digit, capacitor C5 begins to charge on the first timer of IC1. After about one second, the second timer of IC1 is triggered via C4 and the output at pin 9 goes high. This enables the gates IC2b, IC4c, IC4d, IC4a and IC4b.

IC2 and IC4 are quad AND gates. These operate so that the output goes

high when both inputs are high, and stays low otherwise. Consequently, when the inputs at pins 9, 12, 5 and 2 are low the AND outputs are always low and when these inputs are high, each output follows the a, b, c or d input.

The high output at pin 9 of IC1 allows the outputs of IC4 to follow the inputs at a, b, c and d. If the a input to IC4c is high, indicating that the correct first digit of the code has been entered, the output of IC4c will go high and triggers SCR T1.

Note that T2, T3 and T4 cannot be triggered even if one of the b, c or d inputs are high. This is because the IC5 AND gates are disabled via the pull down resistors R18, R17 and R16 respectively at their inputs.

With T1 conducting, the pin 2 input of IC5a is pulled high. This enables IC5a, so that the next code number entered can trigger T2 via the b input through IC4d and gate IC5a.

The pin 9 output of the second timer in IC1 remains high for about 30ms, enough to trigger the SCR and then reset IC3 via the delay formed by C7 and R10 at pin 15.

After the second digit is correctly entered,

the b input to IC4d goes high at pin 13. SCR T2 is then triggered via IC5a and enables IC5b at pin 6. When the third digit is selected at c, SCR T3 is triggered enabling IC5c at pin 12. Similarly, entering the fourth digit brings the d input of IC4b high and triggers T4 via IC5c.

When T4 switches on, it supplies a positive pulse to the gate of T5 to switch it on. T5 powers the solenoid door latch mechanism. Note that the relatively heavy transient current required for the solenoid is drawn from a 2200 μ F capacitor, which is supplied via R21 and D4. Diode D5 removes the reverse voltage spike when the solenoid current is switched off.

To assist in data entry, LED D6 is lit briefly during resetting. This indicates that the next code can be entered.

If a digit that is not in the code is fed in, one of the diodes at D7 to D11 will go high and pull the pin 6 input of IC2b high. This sets the outputs of IC2b low and IC2a high respectively, to remove base bias to Q3. Q3 removes the positive power supply from the anodes of the SCRs and thus resets them. Note that C14 is used to remove glitches that can cause all the SCRs to latch on when

S1 is pressed. If code entry for each digit is entered before IC3 resets, any entered number will be added to the previous count, causing an incorrect code.

Construction

The circuitry for the 4-Digit Combination Lock is constructed on a PCB coded 87cl8 and measuring 137 x 110mm. Note that the PCB can be cut in two, so that the latch unit circuit on the PCB can be mounted close to the electric strike.

This has the advantage that the high transient current required for the solenoid can be supplied directly from the large storage capacitor C14, using short connecting leads. Alternatively, heavy duty wiring will be needed between the solenoid and latch unit PCB if this sec-

tion of the PCB is located far from the solenoid.

Begin construction by deciding on the code required for the combination. Linking is required between the a, b, c and d inputs of IC4 and the outputs from IC3, while diodes (D7 — D11) are inserted between the unused outputs of IC3 and the "t" input to pin 6 of IC2b.

A special area at the top right side of the PCB has been reserved for combination coding and the overlay shows encoding for the example combination code of 1234. For this combination, the "1" output from IC3 is linked to the "a" bus, the "2" output to the "b" bus, the "3" output to the "c" bus and the "4" output to the "d" bus. The D7 to D11 diodes connect between the "t" bus and the "5, 6, 7, 8 and 9" outputs of IC3. These diodes will need to be mounted upright.

Note that it is also possible to duplicate a number in the code simply by linking between one output of IC3 and two of the a, b, c or d inputs. In this case an extra diode will be necessary for the free output from IC3.

Continue with construction by installing the low profile components such as the links, resistors, diodes and ICs. Take care with the orientation of the diodes and ICs. Now the transistors, SCRs and capacitors can be installed. Note that these with the exception of the non-electrolytic capacitors, must be orientated correctly as shown on the overlay diagram.

After installation of the components, check your work for the correct placement of components, for dry solder joints and shorts. The circuit is now ready for testing.

Connect S1 between the "P" terminal and "0V" on the PCB and interconnect the latch unit PCB to the main PCB if the two have been separated. A 12V power supply or battery can be connected to the +12V and 0V terminals.

Use a multimeter to check that Q2 switches power to pins 14 of IC1, IC2, IC4 and IC5 and pin 16 of IC3 when switch S1 is pressed. After S1 is released, the power should remain on the ICs for about 3 seconds.

Press S1 again and check that LED D6 flashes for a very short time one second after S1 is released. After this time, S1 can be pressed again and the "1" output of IC3 should go high. Pressing S1 again should bring the "2" output high. The pressing of S1 can be continued to check that each output

PARTS LIST

- 1 PCB coded 87cl8 measuring 137 x 110mm
- 8 AA size cells
- 1 8 x AA battery holder
- 1 momentary contact pushbutton switch
- 1 12V electrically operated striker plate

Semiconductors

- 1 556 dual timer
- 1 4093 quad NAND Schmitt
- 1 4017 decade counter
- 2 4081 quad AND gate
- 1 5mm LED
- 2 BC557 PNP transistors
- 1 BC547 NPN transistor
- 4 C103Y SCRs
- 1 C106D SCR
- 8 1N914 small signal diodes
- 2 1N4002 1A diodes

Capacitors

- 1 2200uF 16VW PC electrolytic
- 1 47uF 16VW PC electrolytic
- 1 10uF 16VW PC electrolytic
- 1 4.7uF 16VW PC electrolytic
- 1 0.15uF metallised polyester
- 3 0.1uF metallised polyester
- 1 0.047uF metallised polyester
- 1 0.039uF metallised polyester
- 1 0.01uF metallised polyester
- 5 0.0047uF metallised polyester

Resistors (0.25W, 5%)

- 1 x 680kΩ, 2 x 220kΩ, 2 x 100kΩ, 5 x 27kΩ, 1 x 18kΩ, 1 x 10kΩ, 1 x 5.6kΩ, 1 x 1.8kΩ, 5 x 1.2kΩ, 2 x 560Ω

Miscellaneous

Solder, tinned copper wire, hookup wire.

FOR EXCLUSIVE AND SELECTED KITS:

OATLEY ELECTRONICS

5 LANDSDOWNE PDE

OATLEY WEST 2223

PH. (02) 579 4985


POSTAL ADDRESS: P.O. BOX 89

OATLEY NSW 2223

UHF KEY CONTROLLED ULTRASONIC ALARM

E.A. JAN./APR. 87

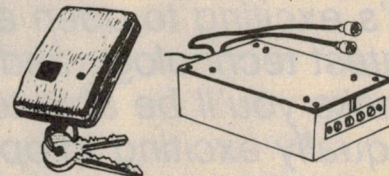Why pay more than \$500?? Do it yourself for under \$100!! * HIGH QUALITY UNIT * Has provision for wiring bonnet boot etc.: For total "INSTANT" protection!



Transmitter P.C.B. Kit \$11.90, Receiver P.C.B. Kit \$29.90, Ultrasonic P.C.B. Kit \$16.90, Suitable Ultrasonic Transducers \$13.50 pair, Piezo Siren \$16.00, Metal Siren \$25.00, Pin Switches (Bonnet, Boot) \$1 ea, 12V Lighter Batteries (Alkaline) \$3.40 a pair!

THE "MUSOLINK" WIRELESS GUITAR TRANSMITTER

- * Professional quality F.M. transmitter
- * Performs equal if not better than those expensive commercial units.
- * Can also be used for microphones
- * Complete to the last detail:

Even the belt clip and the lead is provided for only: \$24.95



MUSOLINK
STICKER
INCLUDED

What to use for a receiver?? Why not adapt an F.M. walkman (EA OCT. 86) Conversion kit only: \$8.95

BE HEARD WITH: THE MICROPHONE

E.A. NOV. 86

- * Professional quality * Touch controlled
- * Up to 0.5V R.M.S. output! (drives any amplifier)
- * Battery check function * Low battery consumption
- * Easy to construct



SPECIAL
THIS MONTH
ONLY

Only \$15.95 with Omnidirectional insert OR \$20.95 with Unidirectional insert. Try both for only \$21.95

WHAT ABOUT THESE GIVEAWAY KITS?

"Dashboard Flasher"	\$9.95
"Ignition Killer"	\$11.50
Professional Quality V.H.F./U.H.F.	
"Distribution Amplifier" P.C.B. kit	\$33.90
"Mini Mixer" P.C.B. kit	\$27.95

* ALL PRICES INCLUDE P&P *

BANKCARD AND MASTERCARD PHONE
ORDERS WELCOME
PERSONAL CHEQUES AND POSTAL MONEY
ORDERS ALSO ACCEPTED WITH MAIL
ORDERS.

Continued on page 129

Putting old video gear to good use:

Home movies on the (very) cheap

It's exciting to open a box containing the very latest technology and to wonder what new tricks you'll be able to make it do. It can be equally exciting to open up some old technology and to learn about how it was done in days gone by. When the learning also results in a useful end product, the whole exercise can be very worthwhile . . .

by JIM LAWLER



Although the AV3420-CE is quite heavy at 8.5kg, it is not so heavy that it can't be used on a roof, to record closeup features of a television antenna.

When my younger son mentioned that he wanted to do "Film and TV" at college, I had a fleeting thought about getting a video camera and portable recorder so that he could practice at home. But we need a new car before spending two or three thousand dollars on new video gear, so the idea lasted about ten seconds before it disappeared in a tiny "pooff".

A few days later a colleague mentioned that the local University was selling off a lot of old audio/visual gear, and that there was a monochrome portapak and other video gear (all reel-to-reel) amongst it. Without realising just what I was getting myself into, I made an offer for a selection of the equipment and the offer was accepted.

Now before I go on, I should make it clear that I'm a qualified technician. I knew what I was getting into and was prepared to write off my expenses at any time. I learned early on that I could expect no help from the manufacturers or distributors of this equipment and that anything I learned would have to be from my own experience or from my fellow technicians.

So read on for entertainment, but don't expect to emulate my achievement unless you have the technical expertise or clever friends who can fix whatever might break!

The principal item of the gear concerned was a Sony model AV3420-CD portapak, with camera and AC power adapter. The second video item was a Sony model AV3670-CE recorder, a large desk type machine with what turned out to be a surprisingly effective editing function. Both of these items were supposed to be in working order, an opinion which proved quite accurate.

An item which *wasn't* working but was bought, anyway, for its curiosity value was an Akai quarter-inch video recorder. This funny little machine used ordinary quarter-inch audio tape for helical scan recording of monochrome

video signals. The recorder had one unique feature that would not be amiss on modern VCR's, a built-in three inch monitor screen.


My purchase worked out to be something like \$40 each for the two half inch Sony recorders and \$20 for the Akai curiosity. (This last was not really a waste, because the kit included a black and white video camera which must be worth at least \$20, when I can find out how to use it!)

Before the machines could be properly tested, I needed a monitor (or monitors). Initially, I borrowed a couple of colour sets from the workshop but this seemed a wasteful way to go. Then among my junk I found an old Kriesler monochrome portable, a model PT2 that had been discarded because its power transformer had failed.


It was easy enough to find and fit a suitable replacement transformer. Then I removed the tuner and IF stage, devised a suitable video input configuration and fitted two BNC sockets on the back panel. I retained the audio stage and gave that a suitable input using 3.5mm phono jacks. I finished up with a monitor that matched the recorders for both appearance and vintage.

Later, I inherited two more of these little Krieslers, junked because simple faults had been considered uneconomical to repair at the time. I found the repairs easy enough, if a trifle time consuming. They were modified the same way as the first set, so now I have three ideal monitors, for a total cost of something like thirty dollars. They look quite impressive, sitting on the shelf above the recorders.

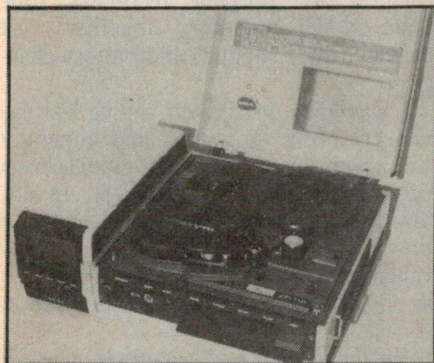The portable recorder contained a Sony BP2 12 volt lead-acid battery pack. It was no surprise to find that the battery was flat, and it was so old that it would not hold any useful charge. The



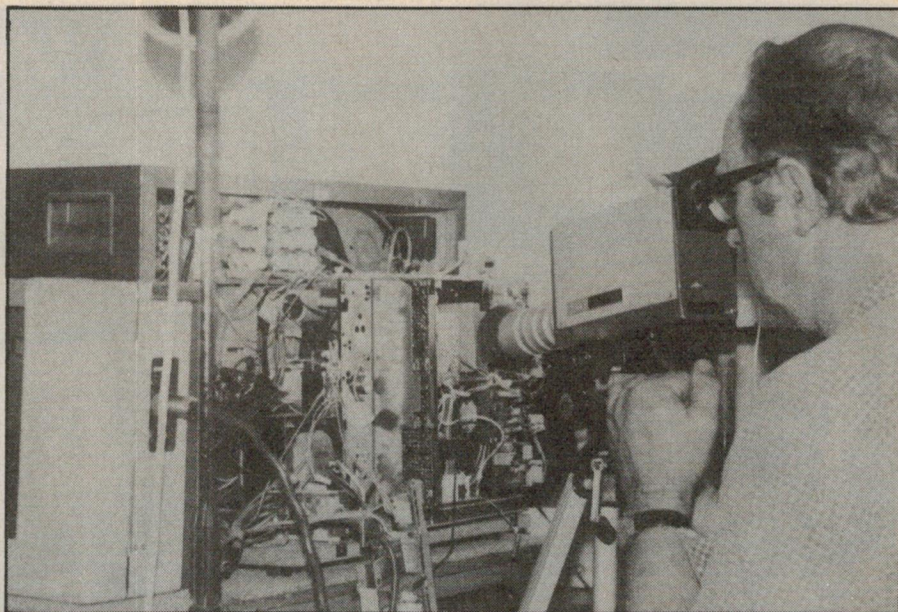The Akai VT110 quarter inch portable video-recorder. It includes most of the functions of larger machines, as well as a built in monitor seen here on the left of the deck.



The author at work recording a fault inside a television set. The portapak unit is sitting upright on the left of the bench and one of the 150W floods can be seen on its microphone stand, over the TV.

pack contained two six volt batteries which are still available as standard items. I ordered two replacements from the Yuasa distributors and got quite a surprise when I got a bill for \$41. That's as much as the recorder they were to be used in!

Still, it was worth it because the old Sony started up and recorded near perfect pictures. The machine had come with a 5-inch reel of tape, enough for half an hour's recording. This was soon used up, and the search began for a supply of tape to fuel the machines.

Both of these recorders used half-inch video tape, of a grade described in their time as "High Density". I eventually found a source of tape which turned out to be "low density" and quite unsuitable. I spoke with a lot of people in an attempt to learn about the difference in these tapes but nobody seemed to know anything. It seems that when these machines were current models, they required no service and thus nobody learned anything about them (well that's the story anyway . . .).

I did hear dire warnings about a tape characteristic called "striction" which makes the tape stick to any polished surface. It was supposed to be particularly vicious on these machines but turned out to be a minor problem, and then only with tape made by or for Sony. Other brands gave no trouble at all.

Anyway, fate must have had its eye on me because the local college learned about my search and offered a quantity of old tape which proved to be ideal for


both machines. Later experiments showed that tape from Philips N1500 cassettes suited these Sony machines perfectly, as does modern VHS or Beta tape. So there is unlikely to be any shortage of tape in the future.

So now I had one camera, two recorders, three monitors, a supply of tape, and no immediate subject to use them on. My son had lost interest now that we were working in thrilling black and white! Like most people he had decided that it was to be colour or nothing.

It came to pass that at this time I had a television set in my workshop with a most unusual fault. A full replacement of the faulty parts would have been very expensive for the customer. But I was able to devise a repair that has proved most reliable and cheap for the customer. So I decided to film the exercise and to distribute copies to my colleagues in the trade, in the hope that they could save their customers the cost and delays of getting scarce and expensive parts.

Then another odd fault showed up, and another, and soon I had enough material to make a 20 minute News tape for distribution among my friends in TETIA. The *Electronics Australia* "Fault of the Month" might soon be circulated on video!!

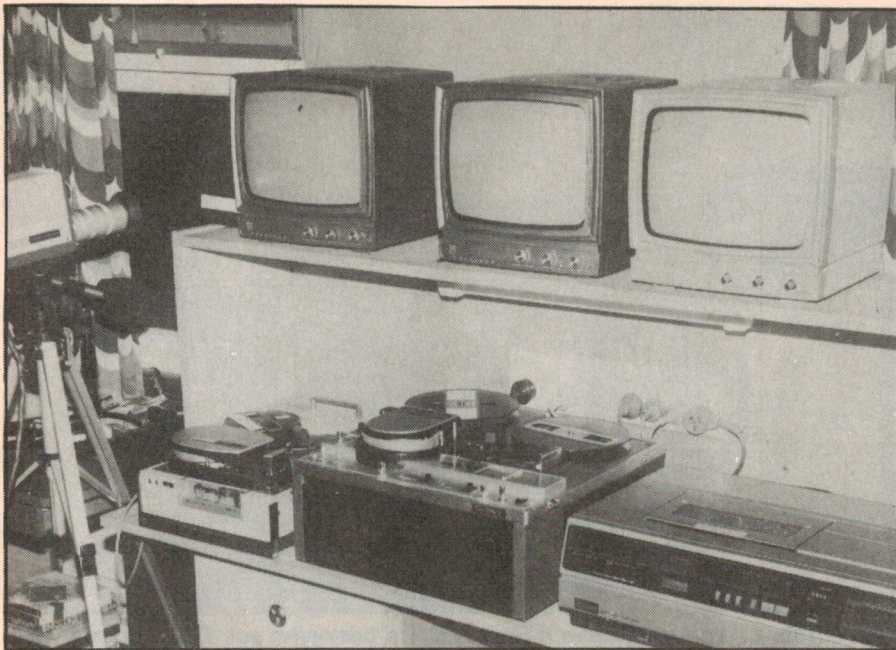A very useful accessory (that also cost more than the portable recorder) was a set of closeup lenses. These allow me to film right down to an inch or so from the subject. I can fill the screen with a single dry joint, or display the type number on a transistor.



Showing the equipment set up in the "Editing" mode. The Portapak is on the left of the bench, then the 3670 editing machine and the VHS unit on the right. The three modified Kriesler monitors are on the shelf, and the AVC3420 camera on a tripod on the extreme left of the picture.


I spent \$12 on a movie titling set and made up some quite smart titles for my creation, then added a personal introduction and a visit to the workshop of a couple of our members. All in all, the programme turned out to be surprisingly effective.

The final edited tape was copied onto VHS cassettes for distribution. (My colleagues are not yet lucky enough to have their own mono recorders). Even the VHS machine was bought on the cheap — \$250 ex-rental. The entire studio has not yet cost \$500 . . .

One advantage of working in monochrome is that any light source is suit-

able for black and white. Colour video needs proper colour corrected movie lights and lots of them. Mono video can use any kind of light (tungsten, fluoro, daylight or even sodium street lights) and even a mixture of different light sources.

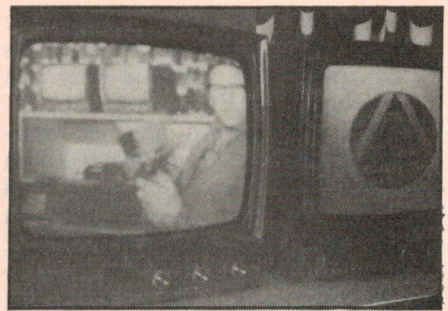Although the monochrome camera can work in extremely low light levels, I found I needed more light when working close up inside a TV set. To solve this problem I bought two 150 watt "Portafloods" and mounted them on ordinary microphone stands. This gave me effective studio lighting for less than \$20.



Two of the monitors displaying pictures during an editing session.

Another advantage of working with this old equipment is the remarkable quality of multi-generation copies. The VHS print of my Newstape is three and four generations from the original, and still has almost all the sharpness and gradation of the original camera material.

So there it is. A quality amateur production, assembled on the kind of equipment that is now being sold off for a "song". At which point I should remind readers that the song could go very flat. While the old gear is in good order it runs well, but any breakdown could be the end. Considering that the Sony recorders are only 13 years old (1973), it clearly demonstrates the rapid advance of modern technology.

The sad thing about this is that the thousands of dollars worth of taxpayer-funded equipment was very little used, before the advent of colour made it all redundant and therefore worthless. I hope that my exercise in the production of training and information films can squeeze a little more value out of the gear before it is finally put away.

FOOTNOTE: Since writing the bulk of this article, TETIA has been successful in tendering for more of this video equipment from the Tasmanian Education Department. The lots include seven cameras and portable recorders, four table model recorders, together with various power supplies and battery chargers.


It has been distributed among Tasmanian members of TETIA and hopefully will result in a flood of video service tips for our TETIA Newstape. In all, the gear has cost the Division \$300, a tiny fraction of its original value, but invaluable in the possibilities it opens for us to develop our technical information service.

We have managed to secure a selection of spare parts to suit the old machines. With a few heads and a range of belts, we should be able to keep the old equipment running for many years into the future.



Closeup views of the monochrome decks.

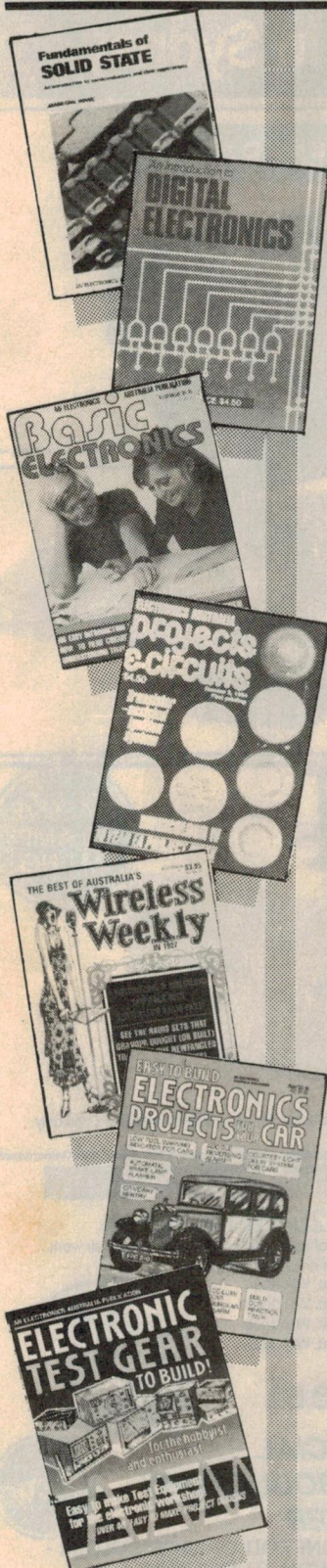Special Publications from Electronics Australia



FUNDAMENTALS OF SOLID STATE. Now in its second reprinting — which shows how popular it has been! It provides a wealth of information on semiconductor theory and operation, delving much deeper than very elementary works but without the maths and abstract theory which make many of the more specialised texts heavy going. Starting with a background chapter on atomic theory, the book moves easily through discussions on crystals and conduction, diode types, unijunction, field effect and bipolar transistors, thyristor devices, device fabrication and microcircuits. A revised glossary of terms and index complete the book. *Fundamentals of Solid State* has also been widely adopted in colleges as recommended reading — but it's not just for the student. It's for anyone who wants to know just a bit more about the operation of semiconductor devices. **\$4.50**

DIGITAL ELECTRONICS. Electronic equipment plays an important role in almost every field of human endeavour and every day, more and more electronic equipment is 'going digital'. Even professional engineers and technicians find it hard to keep pace. In order to understand new developments, you need a good grounding in basic digital concepts and *Introduction to Digital Electronics* can give you that grounding. Tens of thousands of engineers, technicians, students and hobbyists have used this book to find out what the digital revolution is all about. This new fourth edition has been updated and expanded to make it of even greater value. No previous knowledge of digital electronics is necessary — The book includes an excellent coverage of basic concepts. **\$4.50**

BASIC ELECTRONICS. This popular text has now been re-issued. *Basic Electronics* is almost certainly the most widely used reference manual on electronics fundamentals in Australia. Written as a basic text for the electronics enthusiast, it is also being used by radio clubs, secondary schools and colleges, and WIA youth radio clubs. It begins with the electron, introduces and explains components and circuit concepts and progresses through radio, audio techniques, servicing instruments, television, etc. If you've always wanted to know more about electronics, but have been scared off by the mysteries involved, let *Basic Electronics* explain them to you. Easily understood diagrams and text make this the perfect introduction to the growing and exciting world of electronics. We've even included five electronic projects for the beginner. **\$4.50**

PROJECTS & CIRCUITS. If you like building electronic projects in your spare time, you can't afford to miss out on this exciting book of popular projects from *Electronics Australia*. Just look what's inside! **Audio and Video Projects:** Video Amplifier for Computers and VCRs, Video Enhancer, Vocal Canceller, Stereo Simulator for Tuners and VCRs, Guitar Booster for Stereo Amplifiers. **Automotive Projects:** Transistor-assisted Ignition System, Breath Tester, Low Fuel Indicator, Speed Sentry, Audible Turn Indicator. **Mains Power Control Projects:** Musicolor, Photographic Timer, Driveway Sentry, Touch-lamp Dimmer. **Power Supplies and Test Equipment:** Battery Saver for Personal Portables, Dual Tracking $\pm 22V$ Power Supply, 3 1/2-Digit LCD Capacitance Meter, In-Circuit Transistor Tester. **Plus EA's 10-year project index.** **\$4.50**

WIRELESS WEEKLY. Our own time machine! It may look like a book, but don't let its appearance fool you. There are no whirling dials and control levers; but once you open the cover, it'll take you on an incredible journey backwards in time. You'll find yourself back in the 1920's, when Australia's first few radio stations were just getting established and a typical radio set cost ten weeks' wages. We've chosen a collection of highlights from the 1927 issues of 'Wireless Weekly': You'll find some front covers, a few editorials, the best new items, a collection of typical do-it-yourself radio set designs, and some selected pages from the programme listing. Plus a sprinkling of the original advertisements, of course. These are particularly fascinating because they show prices and put everything into proper context. Send today for *The Best of Australia's Wireless Weekly in 1927* ... A fascinating and nostalgic trip into our radio past. **\$3.95**

ELECTRONIC PROJECTS FOR YOUR CAR. How can you extend the performance of your car without it costing an arm and a leg? With these selected projects from *Electronics Australia* you can add all of the gadgets you've dreamed of: Cruise Control, Courtesy Light Delay, Deluxe Burglar Alarm, Headlight Reminder, Audible Reversing Alarm, Transistor-assisted Ignition with Optoelectronic Trigger, Driveway Sentry, Speed Sentry, Tacho/Dwell Meter, Breakerless Ignition, Audible Turn Signal and more easy-to-build projects to add value, interest and safety to your pride and joy! **PLUS** Feedback from those who have built the projects themselves and Bright Ideas for you to develop yourself: Automatic Antennae Retraction, 6V Car Adaptor, Fuse-Failure Indicator and more ... **\$3.95**

ELECTRONIC TEST GEAR TO BUILD. Why buy it? These valuable projects from *Electronics Australia* will add a new dimension to your workshop! Detailed, step-by-step instructions guide you through the construction of the most useful of electronic workshop test gear: 500 MHz 7-digit Frequency meter, Wheatstone Bridge and Resistance Box, AC Millivoltmeter, DC Voltmeter, LCR Bridge, Modulated Signal Injector, Audio Prescaler. **PLUS** Feedback from those who have built the projects themselves and Bright Ideas for you to develop yourself: Linear Frequency Controller, Dummy Loads, General Purpose Counter Timer and more ... **Never built a project before?** What better way to get started than by building the test instruments needed to begin a workshop? **Build it yourself to save and learn at the same time!** **\$3.95**

Send your order to — **Freepost No.4** **PO Box 227,**
Federal Publishing Book Sales, **Waterloo NSW 2017**
(no postage stamp required if mailed within Australia)

JAYCAR ELECTRONICS NOW AT 8 LOCATIONS

• 2 in Melbourne • 1 in Brisbane • 5 in Sydney

MASSIVE SCOOP PURCHASE

Yes, we've made another scoop purchase. The imported contacted us with his dilemma and we purchased a quantity of these fully imported fully guaranteed air purifiers. These units are 240 volt operated, draw about 1/2 watt, deliver about 250 billion ions per second, and cover about 25 square metres. It's even supplied with a Testor PC board and spare needles. If you've ever wondered about negative ion generators, this MUST be the time to buy one. These were selling for about \$80. Jaycar has a limited quantity available for:

Cat. YX-2905

\$29.95
SAVE \$50.00

ALMOST
2/3
OFF!

NEW

ROVER NEGATIVE ION GENERATOR




NEW WELLER WTCPS SOLDERING STATION

At last, the old WTCPS has been upgraded and replaced by the new WTCPS. This station incorporates the famous Weller "closed loop" temperature control system. New features include a detachable iron stand that clips on either side of the station, which incorporates a "water well" which keeps the sponge constantly damp. Uses the well known PT range of tips.

Cat. TS-1002

\$149.50

NEW

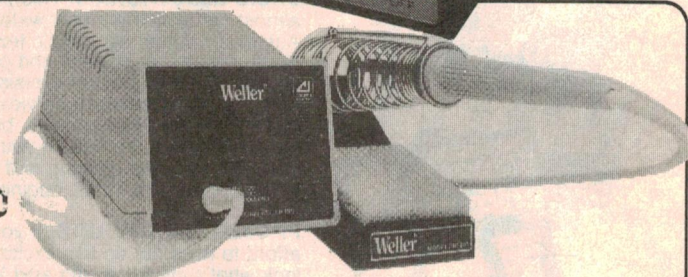

SQUEAKY CLEAN MAINS FILTERS

TWO BRAND NEW MODELS, BOTH FULLY APPROVED BY THE ELECTRICITY AUTHORITY.

4 OUTLET

The MS-4020 will supply up to 4 appliances. Each 240V socket is independently filtered from the other, i.e. interference from disk drives is de-coupled from the CPU power supply, etc. The filter will suppress interference from RF sources, spikes, transients and lighting, and supply up to 4 outlets with a total load of 10 amps.

Cat. MS-4020

\$269.00

NEW

2 OUTLET

The two outlet will handle up to 7.5 amps and will suppress interference from RF sources, spikes, transients and lighting. The two sockets are not independently filtered, although.

Cat. MS-4025

\$99.00

AUSSIE
MADE

BEWARE: There are many mains filters on the market. One sample we evaluated had only one capacitor in it!



MASSIVE
10 AMP
RATING

INSTRUMENT CASE


A proud addition to our range. This very attractive case is Instrument blue in colour, made in ABS plastic, has removeable front and rear panels, vented and looks extremely smart. Its along the same lines as our HB-5912 box, but not as high.

Measures: 180(W) x 230(D) x 40(H)mm. Accepts PCB vertically 170 x 34mm and horizontally 220mm x 145mm.

Cat. HB-5915

ONLY \$16.95

AUSSIE MADE

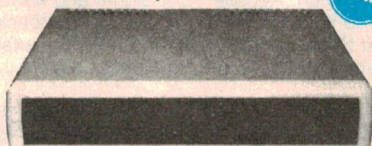

NEW

AT LAST

DIRECT IMPORT

HOOK-UP WIRE ON 25 metre ROLLS

Now all hobbyists can afford to have a roll of each colour hook-up wire by their work bench. Quality 13/0, 12 tinned hook-up wire on plastic spools.

Red	Cat. WH-3000	Yellow	Cat. WH-3004
Black	Cat. WH-3001	Green	Cat. WH-3005
Brown	Cat. WH-3002	Blue	Cat. WH-3006
Orange	Cat. WH-3003	White	Cat. WH-3007

\$2.95 per reel




ILLUMINATED ROCKER SWITCH

- Great for amps
- SPDT, 8A, 240V
- Illuminated actuator
- As used in P/Master 60/60
- Size 21 x 15mm
- Panel cutout 13 x 19.5mm

Cat. SK-0985
Catalogue Price
\$7.50 ea


AUGUST SPECIAL
\$3.95 ea 10 up \$3.25 ea

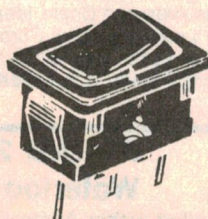

TWEETY PIE

This incredibly little piezo screamer measures 57(L) x 33(H)mm emits a 116dB wall. It's deafening! As used in the screamer car alarm kit. Cat. LA-5255

ONLY
\$16.95

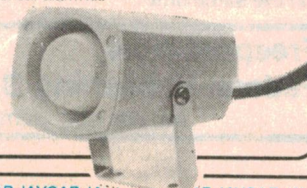

SPECIAL INTRODUCTORY OFFER

BUY ONE ROLL OF EACH COLOUR - 8 ROLLS IN ALL FOR ONLY

\$19.95 - SAVE \$3.65

Cat. No for pack of 8 rolls WH-3009

NEW

MIXED COMPONENT PACKS - SAVE HEAPS!!

We reserve the right to make changes to these packs
if stock shortages occur

NEW ELECTROLYTIC PACK

- Contains over 80 assorted electrolytics
- Most are normal stock lines
- Types supplied: 1, 2.2, 10, 22, 25, 47, 100, 150, 220, 470, 680, 4700, 10,000uF
- Voltages 6.3, 10, 16, 25, 35, 40, 50, 63, 250V
- At our current prices these caps are worth \$85.00
- That's only 12¢ per capacitor

Cat. RE-6260
**80 PRIME SPEC ELECTROS FOR
\$10.00
SAVE 88%**

MIXED CAPACITOR PACK

Don't miss this bargain!

This pack contains approx. 150 assorted capacitors. Not junk values, most are normal stock lines. Here's what you get:

RT Electro 1, 4.7, 25, 100, 220, 470uF most 63V
RB Electro 1, 2.2, 25, 47uF
GreenCap 100V - 0.0022, 0.01, 0.22, 1uF
GreenCap 630V - 0.022, 0.1uF
Ceramic 4.7, 47, 220, 470pF, 0.022uF
Polystyrene 220, 820, 2200pF
1kV Ceramic 330, 470, 680pF
PLUS LOTS MORE

**150 PRIME SPEC CAPACITORS
FOR \$10.00**
Cat. RE-6260

POT PACK

After the huge success of our Plessey pot pack, we present our new one.

This pack includes trimpots of various styles, switchpots and expensive slider pots. There is a minimum of 10 sliders, dual sliders sell for \$5.50 each. If you only use two sliders, you will be in front, not to mention the trimpots. Typical values included are: 500, 2k, 5k, 20k, 100k, 250k, and 500k ohm. The pack includes at least 35 items. We estimate the current retail price of pots in the pack to be over \$82.

Cat. RP-3902
**SAVE 87%
35 POTS/TRIMMERS FOR
ONLY \$10.00**


OLFA KNIVES - CUTTERS

Jaycar proudly introduces a range of high quality Japanese made cutters from Olfa. We are very impressed with these products, and we are sure you will be too!

ART KNIFE

Precision art knife supplied with not one or two spare blades, but a massive 25 replacements and a plastic storage box which houses both used and unused blades. Less than half the price of other art knives with comparable blades.


Cat. TH-1950 **\$9.95**

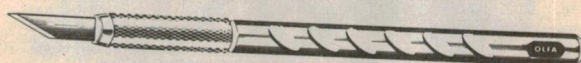

SMALL UTILITY KNIFE

When the blade becomes blunt, snap it off! Housed in a metal holder (not plastic). Fully retractable blade, one hand operation.

Cat. TH-1952

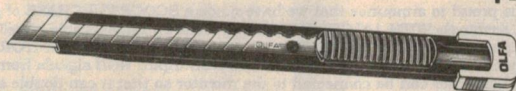


\$2.99

MEDIUM UTILITY KNIFE

Supplied with two blades, one snap off type and one saw blade, which will saw timber, plywood, plastic, etc. Retractable blade.

Cat. TH-1954

\$14.95

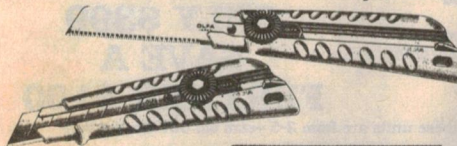

NEW

TOUCH KNIFE

Measures only 40mm long and 4.5mm wide, and is ideal for cutting fruit, opening letters and parcels, cutting string, a million uses. Every handbag pocket, desk, glovebox, keyring should have one.

Cat. TH-1955

\$1.99



ULTRASONIC PEST INSECT REPELLER

(full details 1987 Jaycar Catalogue.)


Cat. YS-5510

**SAVE Less than 1/2 price
\$30.05
ONLY \$24.95**



LOWER PRICES ON DIL IDC's

Cat	Pins	Was	Now	10 up
PI-6549	14	2.75	1.95	1.75
PI-6550	16	2.95	2.25	2.00
PI-6555	24	4.50	3.95	3.70
PI-6558	40	5.75	4.95	4.60

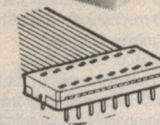

**CARLINGFORD OPEN
SATURDAYS TIL 2pm**

"SPY-IN-THE-SKY" SENSOR

Jaycar is proud to announce that we stock a Pyroelectric Infra-Red Sensor Element. This is the 'eye' of a passive infra-red detector.

The Murata IRA.F001-P is tiny! It measures 10mm high, 9mm wide and only 6.2mm deep. The element is a ceramic-ferroelectric (modified Lead Zirconate Titanate) which is very stable with VERY high sensitivity and wide spectral response - (1-20um)! The IRA.F001-P comes complete with full technical data including performance graphs, information on the operating principle and two typical application circuits!

Typical Applications:

- Burglar Alarms
- Proximity Detectors
- Automatic door/shutter switch
- Toys, robotics
- Accident prevention/machine guard
- Electronic appliances
- Automatic lighting (in toilet?)

Jaycar (once again!) has purchased this item at a stunning low price so (once again!) we pass the savings on to you!

Cat. ZR-9500

The IRA.F001.P comes complete with all data mentioned above for:

ONLY \$19.95



SCOOP BUY!! 240V - 6V 300mA PLUG ADAPTOR

- Genuine scoop purchase
- Extra long lead with 4 way connector
- Below HALF PRICE!!
- Incredible bargain

Cat. MP-3008

**ONLY
\$7.95 ea**




DIGITAL MULTIMETER WITH FREQUENCY COUNTER

A compact DMM which not only has impressive voltage, current and resistance range BUT a digital frequency and capacitance meter to boot! Not to mention the diode and transistor checker as well.

You will be proud to own this attractive meter moulded in yellow high impact plastic. Quality shrouded test leads, instructions and battery. See the Jaycar 1987 Catalogue for full details.

Cat. QM-1555

**ONLY
\$169.00**

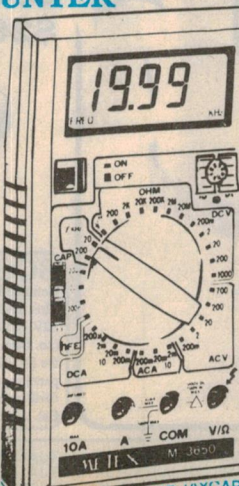

41/2 DIGIT MULTIMETER

including transistor & diode tester
Cat. QM-1550

\$179.00

10A DIGITAL


with transistor tester & capacitance meter
Cat. QM-1540

\$129.00

10A DIGITAL

with transistor tester
Cat. QM-1530

\$89.95

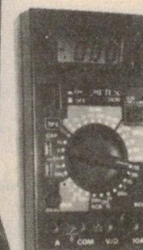

**GET YOUR COPY
OF THE 1987
JAYCAR
CATALOGUE
ONLY \$1.00**

TWO MELBOURNE LOCATIONS

- 45 A'Beckett Street City 663 2030

- 887 Springvale Road Mulgrave 547 1022

MASSIVE SCOOP PURCHASE

SAVE OVER 50%

The most sensational personal robot we have EVER SEEN!!


- NOT ONLY does this robot TALK to you, it has an LCD 'face' with lips that move in synchronisation! How would you like a robot to have these features?
 - Up to 206 words of speech
 - Tactile bumper sensors
 - Infra red sensor - sees in the dark!
 - MOBILITY. Forward AND backwards in 2 speeds! Right and left turning AS WELL AS curved right and left turning!
 - 25 key TALKING keypad with 16 blinking lights
 - Individual security code. Supplied with individual plastic ID card!
 - LCD face. 4, yes FOUR expressions, happy, surprised, angry and sleepy, and remember the lips move too!
 - Other blinking LEDs on head and chest which work with the voice
 - TWO mechanical arms with grippers - up, down, open, close
 - 8 bit microprocessor
 - 4k RAM for operations
 - 16k speech processor, 2 x 128k ROM chips for vocabulary!
 - Full alphanumeric programming keypad
 - Comprehensive programming and troubleshooting manual
- Well! See what we mean? We trust that you are as convinced as we are!! Once again (boring isn't it), we have made a SCOOP PURCHASE from an importer. The LANDED COST plus sales tax is well above the price that we offer these goods to you. The original recommended price of the goods was \$199. You can have an "ELAMI Jr" running around your lounge room for only \$99!! Once again (boring!) we only have a limited number of Elami Jr's - ACT NOW!
- Cat. XR-1030
(Requires 4 x "AA" & 4 x "C" batts - not included). SIZE 300(H)x 175(D) x 235(W)mm

ONLY \$99.00

SEE REIVIEW AEM DEC '85! (page 33)



25 Key talking keyboard

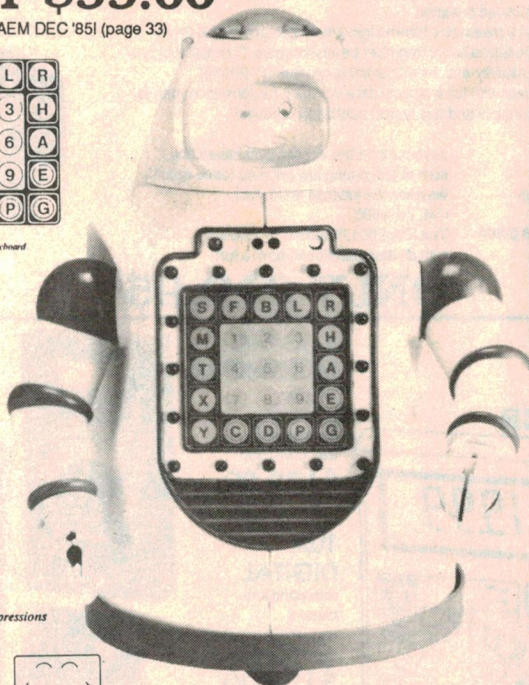

Facial expressions



Sleepy



Happy

Dynamic talking



Angry



Surprised



Static talking



Dynamic talking



SENSATIONAL BUY OF 1987!!!

Jaycar is proud to announce that we have made a SCOOP PURCHASE of genuine VIATEL terminals WITH 14" COLOUR MONITOR at an unbelievable price!! We can pass ENORMOUS SAVINGS on to you as a result. RGB MONITOR. Such is the quality of this system the monitor has RGB input. RGB signals from a suitable computer can be connected to the monitor so that it can double as a high res COLOUR computer monitor! With a composite RGB adaptor you can use virtually any computer!

VIATEL ADAPTOR. The adaptor is professionally made by Phillips and INCLUDES an inbuilt modem to Viatel standard (1200/75). It features:

- Detachable remote keypad
- Keylock on/offswitch
- Centronics type printer port
- Telecom approved (C82/39/489)
- Full keyboard port
- Instructions

**ONLY \$399
SAVE A
FURTHER \$100**

We must emphasise that these units are from 3-5 years old but are in a very clean and good condition.

WANT TO KNOW MORE? Ring (02) 747 2022 and ask for "Mr Viatel" for full details.

INPHONE Cordless Phone

FEATURES:

- Simple to use and easy to install - just plug in
 - Operating range up to 250 metres (800ft)
 - Security code system with 16,348 combinations
 - Call function at base unit to alert handset
 - Pulse dialling with audible tone feedback at the touch of a key
- Cat. YT-7065

ONLY \$269



TRANSISTOR BARGAIN 2N5415

PNP, 200V, 1A, metal TO-5 case Cat. ZT-2365


**NORMALLY 50¢ ea
AUGUST SPECIAL
10 for \$1.00
50 for \$3.50
100 for \$6.00**



SCOOP BUY - VEHICLE BACK-UP BEEPER

Genuine Mallory 'Sonalert'. This device mounts near the rear of any 12V vehicle. When +12V is connected (i.e. from reverse gear switch) it will give the familiar 'beep-beep' noise. Simple panel mount fixing. (Operates 4-28V) 69dB min - 80dBA max. Cat. AB-3442

ONLY \$9.95

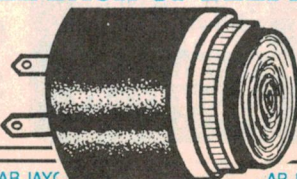

JAYCAR No1 for New Kits

100 WATT MOSFET MODULE

REF AEM April 1987

Upgrade your ETI 5000 power amp. Kit supplied with all parts less the 4 MOSFETs. (Use the ones you already have).

Cat. KM-3056

ONLY \$99.50

HIGH PERFORMANCE MICROPHONE PREAMPLIFIER

REF: AEM August 1987

Here's a top-line mic preamp that's fully DC coupled. PC board and components supplied. No box or power supply supply.

Cat. KM-3061

\$36.95

DIGITAL PHOTO TIMER

REF EA August 1986

Precisely time your photographic processing from one second up to 9 minutes 59 seconds in increments of one second.

Complete kit.
Cat. KA-1674

**VALUE
AT
\$89.95**



LOW COST ELECTRONIC FLASH

REF EA August 1987

This project allows a low cost electronic flash to be used as an electronic stroboscope.

Cat. KA-1688

**ONLY
\$13.95**



BALANCED LINE DRIVER

REF AEM August 1987

Accepts unbalanced inputs and converts them to balanced outputs! This device enables you to convert unbalanced line level signals to balanced line level signals. It is stereo (2 channel) and has a noise floor of -100dB and 0.005% distortion. Great for PA applications when long signal lines in noisy environments are commonly encountered. Can also be used to bridge amps for greater power!

The Jaycar kit includes all board components, case, etc. Requires 30V AC power, i.e. 6672 type transformer.

Cat. KM-3060

\$99.50

AUDIO CLIPPING FAULT INDICATOR

Ref: AEM June 1987

* Indicates overload condition * PCB and all components * Use with amps 5 - 250W * Mono

Cat. KM-3054

\$19.95

CUSTOM TELEPHONE RINGER

Ref: ETI June 1987

Connect this to your phone (with double adaptor \$7.50) and generate your own variable space age ring tone.

Cat. KE-4728

\$39.95

**TOLL FREE ORDER LINE 008 022888
MELBOURNE STORES OPEN FRIDAYS
UNTIL 8.30 p.m.**

COMMODORE 64 PACKET RADIO TERMINAL NODE CONTROLLER (TNC)

refer AEM July 1987

- at last! A modem for the airwaves!

This handy project connects between your C-64 and your amateur transceiver. It enables you to send data from your C-64 to another Ham (who has the same equipment at the other end) by radio!

The Jaycar kit includes all board components, die cast box etc. A 12V plug pack is required to power the device. Cat. MP-3012 \$18.95
Cat. KM-3058

\$59.95

8 CHANNEL I.R. REMOTE CONTROL

Ref: EA June 1987

This project enables you to control up to 8 separate circuits or functions - DC or 240V AC. With the optional add on kit the full receiver will perform such functions as up-down, volume, muting, etc. The transmitter kit is enclosed in an all ABS case with neat Scotch label. The standard receiver kit is supplied with 4 relays. Extra 12V relays (up to 8 total can be fitted) are available at \$4.25 ea (Cat. SY-4061).

TRANSMITTER KIT

Cat. KA-1684 **\$45.00**

STANDARD RECEIVER KIT (4 relays)

Cat. KA-1685 **\$127.95**

ADD ON KIT FOR UP/DOWN, VOL ETC

Cat. KA-1686 **\$82.95**



RTTY ENCODER

Companion for
"Listening Post"

Ref: AEM May/June 1987

This encoder teams up with the ever popular AEM 3500 Listening Post Kit (Cat. KM-3015 - \$39.95) to make a complete transmit/receive tone decoder-/encoder. Complete kit.

Cat. KM-3016

\$29.95

TURN YOUR SURPLUS STOCK INTO CASH!

Jaycar will purchase your surplus stocks of components and equipment. We are continually on the lookout for sources of prime quality merchandise.

**CALL GARY JOHNSTON OR BRUCE
ROUTLEY NOW ON (02) 747 2022**

UNIVERSAL SPEED/LIGHT/HEAT CONTROLLER KIT

We have once again made a scoop purchase of a partially assembled fan speed controller that was part of a well known Australian made product.


The controller consists of a PCB measuring 45 x 60mm with most of the components professionally soldered in. Two other components, a set of 3 brass connection terminals and the control switch/potentiometer must be soldered in place by the user. That's the only assembly work required.

You can connect the controller to many 240V mains powered devices such as: incandescent lighting, electric motors (both series wound and shaded pole) or heating elements, etc. It will control up to 3 amps (i.e. 750VA). A small heatsink may be required on the TRIAC over 2 amps.

The kit is complete and includes all assembly/connection instructions. You only need a suitable knob for the nylon insulated pot shaft.

Cat. KJ-6522

ASTONISHING LOW PRICE! \$9.95

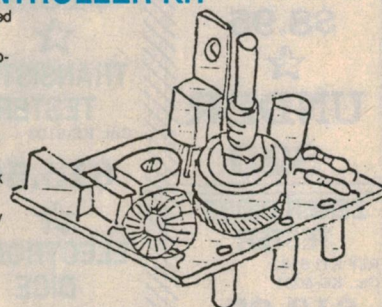

PLAYMASTER 60/60 AMPLIFIER KIT NOW YOU HAVE A CHOICE!

We believe the 'Blueprint' represents a significant improvement in the development of this project.

* Dual diagonally wound C-Core power transformer. Endorsed in writing (with each kit) by EA.

* Slightly higher power rating than toroid power transformer (which is in the standard kit).

* For lower noise, metal film 1% 50ppm resistors are now supplied

* Power supply filter capacitors - doubled! This significantly improves power supply performance.

* Special extruded heatsink.

* Special high quality pre-tinned PCB * Special front panel treatment - graphics emphasise Blueprint treatment.

STANDARD VERSION \$299 Cat. KA-1650

BLUEPRINT VERSION \$349 Cat. KA-1652



JAYCAR

BUILD A KIT

No. 1 FOR KITS

UNDER \$10

CD ATTENUATOR

REF: EA 1/86
Cat. KA-1624

\$9.95



12V FLASHER

REF: ETI 12/79
Cat. KE-4012

\$9.95



ELECTRONIC SIREN

Cat. KE-4002

\$8.90



FM MINI TRANSMITTER

REF: ETI 12/85
Cat. KE-4711

\$9.95



UNIVERSAL SPEED CONTROLLER

Cat. KJ-6522

\$9.95



SIMPLE SIREN

Cat. KS-8127

\$8.95



UNDER \$20

ZENER DIODE TESTER

REF: ETI 5/83
Cat. KE-4031

\$13.95



SIMPLE AM TUNER

Cat. KS-8104

\$12.95



UNDER \$20

LIGHT SAVER

REF: EA 6/86
Cat. KA-1670

\$15.99



MICROWAVE LEAK DETECTOR

REF: ETI 7/79
Cat. KE-4013

\$17.95



12 VOLT LAMP FLASHER

REF: EA 2/86
Cat. KA-1630

\$12.95



NiCad BATTERY CHARGER

REF: ETI 3/83
Cat. KE-4029

\$16.95



RS232 TO COMMODORE ADAPTOR

Cat. KE-4722

\$16.95



TRANSISTOR TESTER

Cat. KS-8103

\$15.50



ELECTRONIC DICE

Cat. KS-8107

\$10.95



SIMPLE TIMER

Cat. KS-8129

\$11.95



UNDER \$20

BASIC AMP

Cat. KS-8105

\$16.95



NiCad CHARGER

Cat. KS-8126

\$17.95



WIRELESS FM MIC

Cat. KS-8106

\$10.95

UNDER \$30



VOCAL CANCELLER

REF: EA 4/82
Cat. KA-1430

\$24.95



TOUCH LAMP DIMMER

REF: EA 4/83
Cat. KA-1508

\$29.95



CAR IGNITION KILLER

REF: EA 2/84
Cat. KA-1535

\$23.50



ELECTRIC FENCE

REF: EA 9/82
Cat. KA-1109

\$21.50



TRANSISTOR TESTER

REF: EA 8/83
Cat. KA-1119

\$21.50



UNDER \$30

AM STEREO DECODER

REF: EA 10/84
Cat. KA-1555

\$26.50



SPEED CONTROLLER

REF: EA 11/84
Cat. KA-1558

\$28.50



20W AMP MODULE

REF: EA 11/84
Cat. KA-1567

\$24.50



VIDEO FADER

REF: EA 1/86
Cat. KA-1626

\$24.95



TURBO (POWER OFF) TIMER

REF: EA 9/86
Cat. KA-1679

\$29.95



TEMP. PROBE for DVM

REF: ETI 7/83
Cat. KE-4033

\$27.95



DIGITAL COUNTER

Cat. KS-8114

\$23.95



SIGNAL TRACER

REF: EA 8/85
Cat. KA-1220

\$24.50



UNDER \$30

50W MODULE

REF: ETI 480
Cat. KE-4050

\$26.50



POWER SUPPLY SUIT

ETI480
Cat. KE-4048

\$29.50



HOUSE ALARM

REF: ETI 4/84
Cat. KE-4698

\$29.95



PARAMETRIC EQUALISER MODULE

REF: ETI 7/86
Cat. KE-4724

\$23.50



TRANSISTOR & FET TESTER

REF: EA 6/78
Cat. KA-1225

\$26.50



SIGNAL SPEAKER PROTECTOR

REF: ETI 10/82
Cat. KE-4023

\$22.50



RED LIGHT ALARM FLASHER

Cat. KJ-7000

\$24.50



DON'T JUST SIT THERE BUILD A KIT

UNDER \$50

BREAKERLESS TRANSISTOR ASSISTED IGNITION

REF: EA 12/83
Cat. KA-1505

\$44.95



TRANSISTOR ASSISTED IGNITION

REF: EA 1/83
Cat. KA-1506

\$42.50



MOTORCYCLE INTERCOM

REF: EA 2/84
Cat. KA-1533

\$43.50



"PEST OFF" INSECT PEST REPELLER

REF: EA 11/85
Cat. KA-1620

\$48.50



CAR CD ADAPTOR

REF: EA 4/86
Cat. KA-1645

\$32.00



LISTENING POST

REF: AEM 6/85
Cat. KM-3015

\$39.95



CIRCUIT PROTECTOR

REF: AEM 6504
Cat. KM-3045

\$49.00



Computer controlled electronic strobe

for the Apple and Microbee

The cheapest electronic stroboscope still costs over \$300 and even a project version adds up to \$100. By converting an old electronic flash from a camera and triggering it by computer, an accurate strobe can be built for a fraction of the price.


by **RICHARD WALDING**
and **PAUL PAVLUK**

The original purpose of developing this strobe was to produce an accurate and cheap electronic strobe for use in high school physics classes, to analyse standing waves on strings and wave motion in ripple tanks. Mechanical shutter strobes, common to many schools, were uncalibrated and electronic units were far too expensive. The unit described here is cheap, accurate and simple to build. It has far wider applications than originally planned.

The three parts of this project are: converting the flash; building the trigger interface and installing the software driver.

Overview

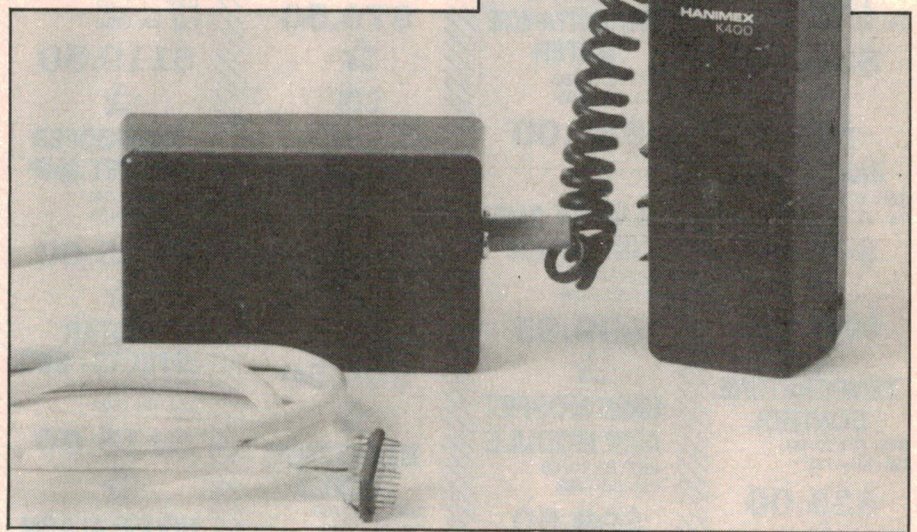Non-automatic electronic flashguns can be bought new for as little as \$20, and secondhand even as cheap as a few dollars. The flash needs to be modified, so that the recycling time can be kept low enough for stroboscopic purposes,



The authors' prototype strobe interface, with a typical low-cost electronic flash. How to modify the flash is explained.

and also to reduce intensity so as to not drain the batteries excessively.

This is done by replacing the main storage capacitor, which could have a capacitance in the order of 500 microfa-

rad, with one of about $0.5\mu\text{F}$ — depending on the frequency range required. The charging resistor in the trigger circuit has also to be replaced with one of smaller value.

The typical flash firing circuit works on the capacitor discharge principle — a capacitor is charged via a resistor from the main high tension supply (Fig.1). This capacitor is in series with the primary of the ignition or trigger transformer, and when the flash lead contacts are shorted, the discharge current passes through the transformer. This produces a high voltage spike (typically 5-10kV) across the secondary of the transformer, which is connected to the

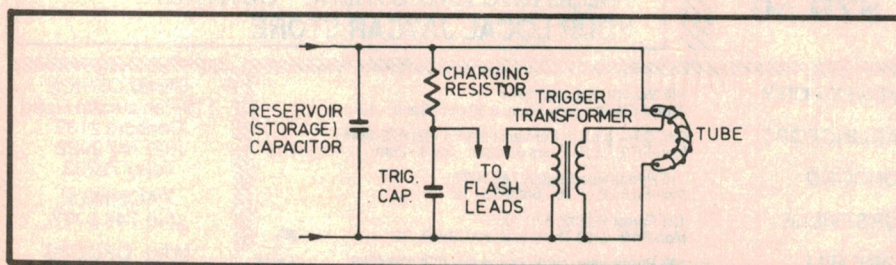


Fig.1: The basic circuit of a typical electronic flash. The main storage capacitor and trigger charging resistor must be reduced in value.

flashtube.

If the camera (or computer) contacts are used to short the capacitor directly, quite an appreciable peak current flows even if the capacitor is made quite small. And so, the camera contacts suffer due to arcing and in turn burn out. The usual output port of a computer would be devastated.

In our interface circuit (Fig.2), a thyristor device (actually a triac) and an opto-coupler are used to provide current amplification and isolation, to protect the computer from damage.

How it works

When the computer makes the terminal "IN" go from 0 to 5 volts, a pulse passes through the 10k Ω resistor and the 0.01 μ F capacitor into the base of the transistor, causing it to be biased on. A 5mA current then passes through the 1k Ω resistor and the light emitting diode within the optocoupler. The purpose of the optocoupler is to isolate the high voltage in the flash from the low voltage circuits of the computer.

The triac in the opto-coupler is then triggered by the light from the LED, thereby discharging the 0.001 μ F capacitor C2 through the main triac. This triggers and causes the strobe to flash once.

The use of a triac, rather than an SCR, for triggering the flash makes it possible to connect the interface to flash units with camera contacts in either side of the circuit (positive or negative). This is also the reason for using the MOC3021 opto-coupler, with a triac output element rather than the usual transistor.

The software

Whenever an output pulse is sent by the computer to the interface, the flash fires. The frequency of these pulses is under software control, and with the software we have developed it can be altered in realtime by the user pressing the arrow keys.

The time between pulses and hence the frequency of the pulses is determined by a machine code counter routine — the longer the program is in the counter loop, the longer the duration between flashes. This machine code routine is loaded by poke statements in the BASIC control program. It has an eight bit and a sixteen bit counter, whose count values are set and transferred across from the control program during use.

The sixteen-bit counter is made up of two nested eight-bit counters. One pass through the inside loop (255 counts) decrements the outer counter by one



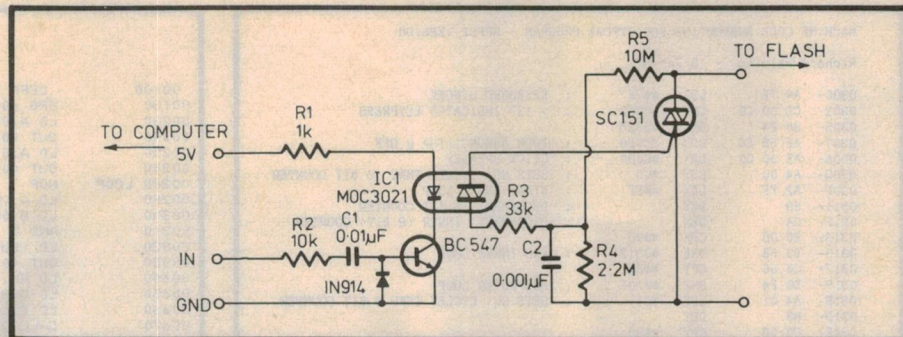


Fig.2: The circuit diagram for the triggering interface. An opto-coupler isolates the computer from dangerous voltages.

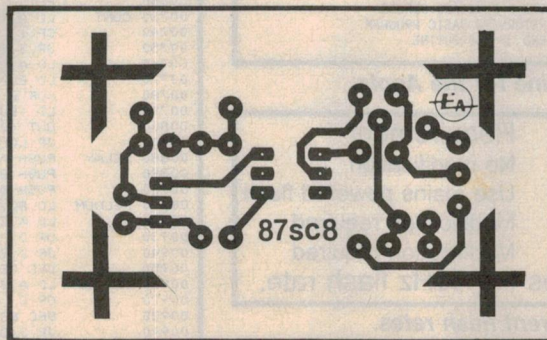

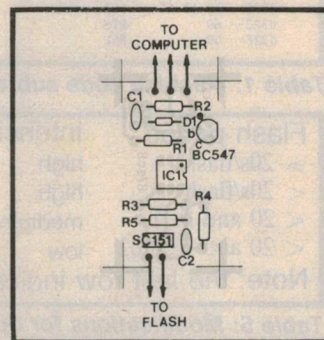
The PC board pattern, reproduced actual size (49 x 25mm).



The component overlay. Be careful with orientation of the diode!

count. Thus a maximum of $255 \times 255 = 65025$ counts is possible for this counter. Finer control is achieved by using the eight-bit counter, where up to another 255 counts can be added. The initial values of both counters are set in the BASIC control program and are altered by pressing the up or down-arrow keys.

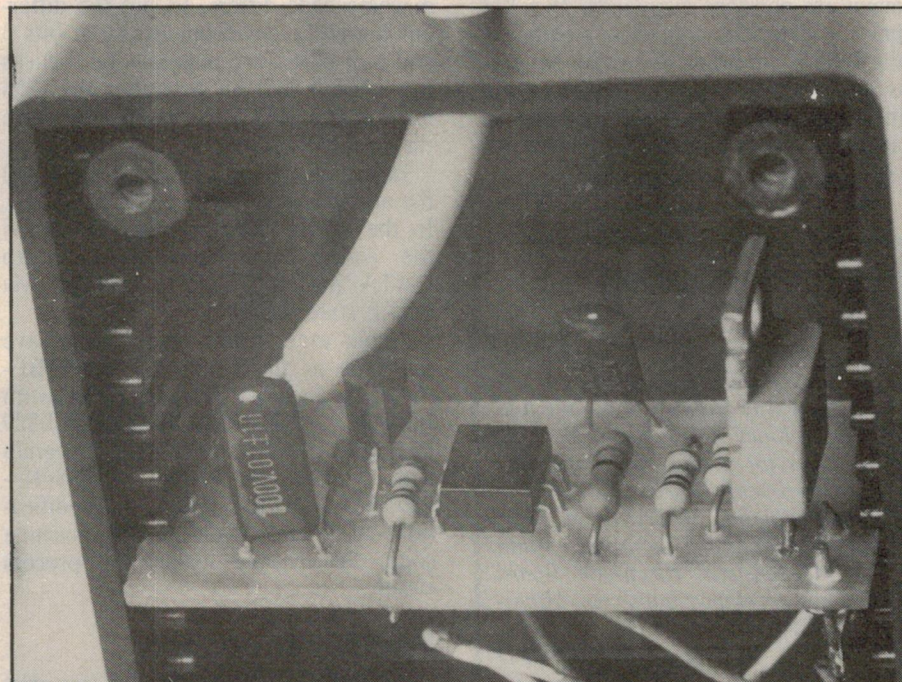After finishing counting, the annunciator (output) memory location is accessed (\$C040 for the Apple) to trigger the flash and then the speaker is "clicked" (Apple \$C030) to produce an audible signal with each flash. The machine code routine then checks for a keypress, and if none is detected an-



Inside the box, showing the components mounted on the PCB. The triac does not need a heatsink.

MACHINE CODE SUBROUTINE FOR STROBE PROGRAM - APPLE VERSION

Richard Walding - 3 Jan 87

```

0300- A9 7F LDA #97F : KEYBOARD STROBE
0302- CD 00 C0 CMP #C000 : > 127 INDICATES KEYPRESS
0305- 30 24 BMI #032B
0307- AE 58 C0 LDX #C058 : TURN ANNUNCIATOR 0 OFF
030A- AE 30 C0 LDX #C030 : CLICK SPEAKER
030D- A4 00 LDY #00 : SETS NO. CYCLES THRU 16 BIT COUNTER
030F- A2 FF LDX #5FF : START INNER LOOP
0311- 88 DEY : DECREMENT 16 BIT COUNTER
0312- CA DEX : DECREMENT INNER (8 BIT) COUNTER
0313- E0 00 CPX #000
0315- D0 FB BNE #0312 : END INNER LOOP
0317- C0 00 CPY #000
0319- D0 F4 BNE #030F : END OUTER LOOP
031B- A4 01 LDY #01 : SETS NO. CYCLES THRU 8 BIT COUNTER
031D- 88 DEY
031E- C0 00 CPY #000
0320- D0 FB BNE #031D : END 8 BIT COUNTER
0322- AE 59 C0 LDX #C059 : ANNUNCIATOR 0 ON
0325- AE 30 C0 LDX #C030 : SPEAKER CLICK
0328- 4C 02 03 JMP #0302 : RETURN TO START
032B- AD 10 C0 LDA #C010 : CLEAR KEYBOARD STROBE
032E- 60 RTS : RETURN TO BASIC PROGRAM
032F- 00 BRK : END OF SUBROUTINE
    
```

Table 1: Machine code subroutine for the Apple.

Flash period	Intensity	Requirement
> 20s/flash	high	No modification
< 20s/flash	high	Use mains powered flash
< 20 and > 1	medium	Modification required
< 20 and > 0.02	low	Modification required

Note: the last row indicates the 50Hz flash rate.

Table 5: Modifications for different flash rates.

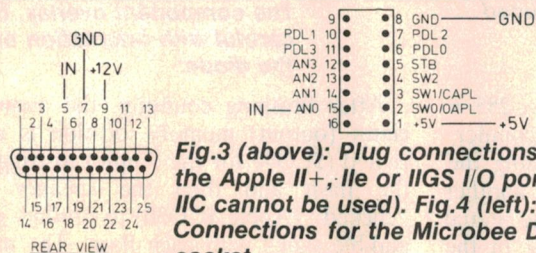


Fig.3 (above): Plug connections for the Apple II+, IIe or IIGS I/O port (the IIC cannot be used). Fig.4 (left): Connections for the Microbee DB25 socket.

other counting sequence is begun which maintains constant frequency. If a keypress is detected, control is returned to the BASIC program where the keypress is decoded into one of several options including: coarse, fine or extra-fine adjustment, sound on/off, increase/decrease frequency, stop or quit.

The Microbee BASIC control pro-

gram is similar but the operation of the machine code differs, to suit the different hardware environment. Here bits 3 and 6 of port 2 are pulses — bit 3 clicks the speaker and bit 6 strobes the CTS line on the RS232 port, used to drive the strobe interface.

In Tables 1 (Apple) and 2 (Microbee) the annotated assembly codes are listed. In the BASIC listings (Table 3 and 4) the codes have been converted to DATA that is placed in memory via POKE statements.

Apple users could alternatively save the code as the binary file STROBE.OBJ, at memory location \$0300 with BSAVE STROBE.OBJ,A\$300,L\$29 and load it from the BASIC program with a line 10 PRINT CHR\$(4)“BLOAD STROBE.OBJ”. If modifications are being made to the machine code, this change makes the process easier.

Modifying the flash

CAUTION! High voltages can exist inside a flash. Make sure the main storage capacitor is fully discharged and

```

00100 DEFR 16
00180 ORG 6000H
00230 LD A,0FFH ;INITIALIZE PORT
00240 OUT (03),A
00250 LD A,0
00260 OUT (03),A
00280 LOOP NOP
00290 LD A,(BUFF)
00300 LD B,0B3H
00310 AND B
00320 LD (BUFF),A
00330 OUT (02),A
00640 LD HL,(HOWLON) ; DELAY SOME
00650 LD D,H
00660 LD E,L
00670 CALL DELAY
00672 CALL KEYWAT
00674 JR Z,CONT ; IF NO KEY THEN PROCEED
00676 LD B,0
00678 LD C,A ; LOAD A INTO C TO RETURN IT TO BASIC
00680 RET
00730 CONT LD A,(PAUSE)
00740 CP 1
00750 JR Z,LOOP
00760 LD A,(BUFF) ; CLICK THE SPEAKER
00770 LD B,04CH
00780 XOR B
00790 LD (BUFF),A
00800 OUT (02),A
00810 JP LOOP
00880 DELAY PUSH AF
00890 PUSH BC
00900 PUSH DE
00910 DELNUM LD BC,5H
00920 LD A,E
00930 OR D
00940 JR Z,EXIT
00950 DEC DE
00960 DELOOP LD A,B
00970 OR C
00980 DEC BC
00990 JR Z,DELOOP
01000 JR DELOOP
01010 EXIT POP DE
01020 POP BC
01030 POP AF
01040 RET
02780 BUFF EQU 514D
02782 PAUSE EQU 516D
02790 HOWLON EQU 512D
02800 KEYWAT EQU 8009
03080 END
    
```

Table 2: Assembly language subroutine for the Microbee.

PARTS LIST

- 1 PCB, 87sc8, 49 x 23mm
- 1 plastic utility case, 2.5 x 8cm
- 1 1 metre length of 4 core phone cable or similar
- 1 plug — J15 (16 pin dip-header) for Apple or DB25 plug for Microbee
- 1 DC power plug (5mm) and socket
- 1 non-automatic electronic flashgun
- Resistors**(0.25W, 5%)
 - 1 x 33Ω, 1 x 1kΩ, 1 x 10kΩ, 1 x 2.2MΩ, 1 x 10MΩ
- Capacitors**
 - 1 x 0.01μF, 1 x 0.001μF
- Semiconductors**
 - 1 x 1N914 diode
 - 1 x BC547 or DS547 transistor
 - 1 x MOC3021 opto coupled triac driver
 - 1 x SC151D triac
- An additional capacitor and resistor will be required (see text for values).
- Total estimated cost (excluding flashgun): \$12 — \$14

About the Authors

Richard Walding, B.App.Sc, Grad, Dip.Tch, M.Sc., M.Phil. is the physics and chemistry teacher at Moreton Bay College, Brisbane and has developed a number of teaching packages for simple Apple interfacing experiments in science.

Paul Puvluk, B.Sc., is a computer programmer with the South East Queensland Electricity Board and has developed numerous Microbee utilities.

See EA, July '86 "Low Cost A-D Converter" for a previous computer project from these authors.


```

1
JLIST
2 REM :PROGRAM "STROBE": APPLE //E, //GS
3 REM : R.WALDING 17/4/87
4 HTAB 7: PRINT "
20 POKE -16368,0: REM CLEAR
30 POKE 34,0
40 HOME
50 POKE 34,13: REM SET WINDOW
60 X = 0
70 Y = 10
80 VTAB 2: HTAB 10: PRINT "<C> = COARSE"
90 HTAB 10: PRINT "<F> = FINE"
100 HTAB 10: PRINT "<X> = EXTRA FINE"
110 HTAB 5: PRINT "UP ARROW = INCREASE FREQUENCY"
120 HTAB 3: PRINT "DOWN ARROW = DECREASE FREQUENCY"
130 HTAB 10: PRINT "<S> = STOP/START FLASH"
135 HTAB 10: PRINT "<Q> = QUIT"
140 POKE 1160,106
150 HB = 200: REM 16 BIT COUNTER
160 LB = 100: REM 8 BIT COUNTER
170 REM :TEST FOR OUT OF RANGE
180 IF HB < 1 THEN HB = 1: GOSUB 12000
185 IF HB > 255 THEN HB = 255: GOSUB 12000
190 IF LB < 1 THEN LB = 255: HB = HB - 1
195 IF LB > 255 THEN LB = 1: HB = HB + 1
198 VTAB 13: PRINT "
200 POKE 0,HB: POKE 1,LB
205 VTAB 11
206 PRINT "COUNTER 0: "; PRINT PEEK (0)
208 VTAB 12
209 PRINT "COUNTER 1: "; PRINT PEEK (1)
210 VTAB 14: PRINT "KEEP COUNTER 0 BETWEEN 1 AND 255"
218 P = PEEK (1) + 256 * PEEK (0)
220 VTAB 16: HTAB 7: PRINT "
230 VTAB 16: PRINT "COUNT = "P
240 A = .000052:B = .00000956
250 FR = 1 / (A + B * P)
262 VTAB 18: HTAB 12: PRINT "
263 VTAB 18: PRINT "FREQUENCY = " INT (FR * 1392) / 1000 " Hz "
330 CALL 768
340 K = PEEK (-16384): REM VALUE OF KEY PRESSED
360 IF K = 11 THEN LB = LB - X:HB = HB - Y: GOTO 180
380 IF K = 10 THEN LB = LB + X:HB = HB + Y: GOTO 180
384 REM : QUIT
385 IF K = 81 THEN POKE 34,0: HOME : END
390 REM : COARSE
400 IF K = 67 THEN GOSUB 520: POKE 1160,106:X = 0:Y = 10
410 REM : FINE
420 IF K = 70 THEN GOSUB 520: POKE 1288,106:X = 0:Y = 1
430 REM : EXTRA FINE
440 IF K = 88 THEN GOSUB 520: POKE 1416,106:X = 10:Y = 0
450 REM : STOP/START
460 IF K < > 83 THEN GOTO 490
470 IF PEEK (777) = 192 THEN POKE 777,0: VTAB 7: HTAB 16: FLASH : PRINT "STOP": NORMAL : PRINT "/START": GOTO 490
480 POKE 777,192: VTAB 7: HTAB 16: PRINT "STOP/": FLASH : PRINT "START": NORMAL : GOTO 490
490 VTAB 17: GOTO 180
510 RETURN
520 POKE 1160,160: POKE 1288,160: POKE 1416,160: RETURN
800 REM : BASIC LOADER PROGRAM
820 FOR Z = 0 TO 48: READ C: POKE 768 + Z,C: NEXT
830 DATA 169,127,205,0,192,48,36
840 DATA 174,88,192,174,48,192,164,0
850 DATA 162,255,136,202,224,0,208,251
860 DATA 192,0,208,244,164,1,136,192,0
870 DATA 208,251,174,89,192,174,48,192,76,2
880 DATA 3,173,16,192,96,0,0
900 RETURN
12000 REM : OUT OF RANGE ROUTINE
12010 PRINT CHR$ (7): PRINT CHR$ (7)
12020 VTAB 13: FLASH : PRINT "OUT OF RANGE ERROR"
12030 NORMAL
12035 FOR T = 1 TO 3000: NEXT
12040 RETURN

```

Table 3: BASIC listing for the Apple.

batteries removed before modifications are attempted.

The higher the frequency required from the flash as a strobe, the lower the intensity that can be accommodated. If used unmodified, the flash can only be triggered every 20 seconds or so, but at full intensity. If full intensity is required at a higher frequency, a mains powered unit is needed. At low intensity, but still suitable for stroboscopic use, frequencies up to 50Hz can be maintained for long periods with the modified flash. Table 5 sets out these details.

There are two components which will generally need replacing inside a flash in order to achieve high flash rates. The following only applies to the inexpensive non-automatic type of flash.

```

00100 REM program Strobe
00110 REM date 17/8/86
00120 REM monitor program for flashing routine
00121 DIM M(4): GOSUB 12000: REM load machine code
00122 F=2: C=40: N1=15202: N2=2596
00124 POKE 516,0: REM RESET PAUSE
00130 GOSUB 5000: REM init the screen
00135 A=C: CURS 40,8: PRINT "COARSE": REM SET COARSE
00136 GOSUB [32,2] 6000
00138 K=USR(6*16*256)
00140 IF K>96 THEN LET K=(K AND 95)
00142 A1$=CHR$(K)
00150 IF A1$="F" THEN LET A=F: CURS 40,8: PRINT "FINE ": GOTO 1000
00160 IF A1$="C" THEN LET A=C: CURS 40,8: PRINT "COARSE": GOTO 1000
00165 IF A1$="D" THEN LET K=USR(7*256*16+3)
00170 IF A1$=")" OR A1$="." THEN GOSUB 9500: GOTO 1000
00180 IF A1$="(" OR A1$="," THEN GOSUB 9000: GOTO 1000
00185 IF A1$"<"5" AND A1$">"0" THEN LET Z=INT(VAL(A1$))+3: M(Z-3)=B: GOSUB [32,2] 6000: GOTO 1000
00190 IF A1$="S" THEN STOP
00200 IF A1$="P" THEN GOSUB 7000: GOTO 1000
00210 IF A1$=" " AND A1$"<"%" THEN GOSUB 10000: GOTO 1000
01000 GOTO 138
05000 REM clear screen and set up help
05005 Z=INT(50/N1-N2): GOSUB 9030
05010 CLS: LORES: OUTLW1
05020 FOR I=1 TO 5
05030 CURS 12,3+I: PRINT "Memory # ";[12 I];" -----";
05040 NEXT I
05050 CURS 12,2: PRINT "Current Frequency:"
05060 PLOT 0,0 TO 0,24 TO 127,24 TO 127,0 TO 0,0
05065 PLOT 18,46 TO 18,40 TO 90,40 TO 90,46 TO 18,46
05070 CURS 10,10: PRINT "S - Stop P - Pause "
05080 CURS 10,11: PRINT "F - Fine Adjustment C - Coarse Adjustment"
05090 CURS 10,12: PRINT "< - Decrease Frequency > - Increase Frequency"
05100 CURS 10,15: PRINT "1, 2, 3, 4 - Store in Memories"
05102 CURS 10,14: PRINT "Shift 1, 2, 3, 4 - Recall Memories"
05110 RETURN
06000 VAR (X,Y)
06020 CURS X,Y
06030 F1 = N1/(N2 + FLT(PEEK(513)*256 + PEEK(512)))
06040 PRINT [F8.1 F1];" Hz"
06100 RETURN
07000 REM PAUSE
07010 Z = PEEK(516)
07020 IF Z=0 THEN POKE 516,1: CURS 7,8: PRINT "PAUSE"
07030 IF Z<0 THEN POKE 516,0: CURS 7,8: PRINT "
07040 RETURN
08000 REM DISPLAY NUMBER
08010 Z = VAL(A1$)
08040 GOSUB [32,3+Z] 6000
08050 RETURN
09000 REM ADJUST deCREMENT
09010 Z=PEEK(512) + PEEK(513)*256
09020 Z=Z-A
09030 IF Z>32000 THEN LET Z=32000
09031 IF A=C THEN LET A=1 ELSE LET A=0
09035 B=Z: C = B/10: IF C=0 THEN LET C=1
09036 F=C/30: IF F=0 THEN LET F=1
09037 IF A=1 THEN LET A=C ELSE LET A=F
09040 Y=Z/256
09050 X=Z-Y*256
09060 POKE 512,X: POKE 513,Y
09065 GOSUB [32,2] 6000
09070 RETURN
09500 REM ADJUST INCREMENT
09510 Z=PEEK(512) + PEEK(513)*256
09520 Z=Z+A
09530 IF Z<0 THEN LET Z=0
09531 IF A=C THEN LET A=1 ELSE LET A=0
09535 B=Z: C = B/10: IF C=0 THEN LET C=1
09536 F=C/30: IF F=0 THEN LET F=1
09537 IF A=1 THEN LET A=C ELSE LET A=F
09540 Y=Z/256
09550 X=Z-Y*256
09560 POKE 512,X: POKE 513,Y
09565 GOSUB [32,2] 6000
09570 RETURN
10000 REM RECALL MEMORY
10025 B=M(ASC(A1$)-32)
10030 X=B/256
10040 Y=B-X*256
10050 POKE 512,Y: POKE 513,X
10060 GOSUB [32,2] 6000
10070 RETURN
12000 REM a basic loader program
12010 RESTORE 12000
12030 READ A,B
12040 FOR Z=1 TO B: READ C: POKE A+Z-1,C: NEXT Z
12050 DATA 24576,80
12060 DATA 62,255,211,3,62,0,211,3,0,58
12070 DATA 2,2,6,179,160,50,2,2,211,2
12080 DATA 42,0,2,84,93,205,58,96,205,9
12090 DATA 128,40,4,6,0,79,201,58,4,2
12100 DATA 254,1,40,220,58,2,2,6,76,168
12110 DATA 50,2,2,211,2,195,8,96,245,197
12120 DATA 213,1,5,0,123,178,40,8,27,120
12130 DATA 177,11,40,243,24,249,209,193,241,201
12140 RESTORE: RETURN
32767 END

```

Table 4: BASIC listing for the Microbee.

Firstly the main storage capacitor (the large one with a capacitance around 300-500 microfarad at 300 or so volts) will need to be replaced with one of smaller capacitance, and the charging resistor in the trigger circuit will also need to be reduced in value.

The new values required for these are given by:

New trigger resistance
 $= 300,000 / (\text{Rate} \times \text{Cap}) \text{ ohms}$
 New storage capacitance
 $= (10 / \text{Rate}) \text{ microfarad}$
 where "Rate" equals the maximum

MICROPROCESSOR DEVELOPMENT SOFTWARE

Cross compilers and assemblers
for PC/XT/AT and VAX hosts.

★ Single Chip "C" compilers by IAR for:

8051 68HC11
6301/6801/6803 64180

★ "C" Compilers by HI-Tech for:
8086/88 Z80 68000


★ Assemblers for all popular
microprocessors by HI-Tech
and 2500AD.

RTCS software for PC/XT/AT:

★ RTX real-time multitasking operating
system
★ UDI universal development interface
★ ISIM85 ISIS II simulator

MACRO DYNAMICS PTY LTD
The Development System Specialists

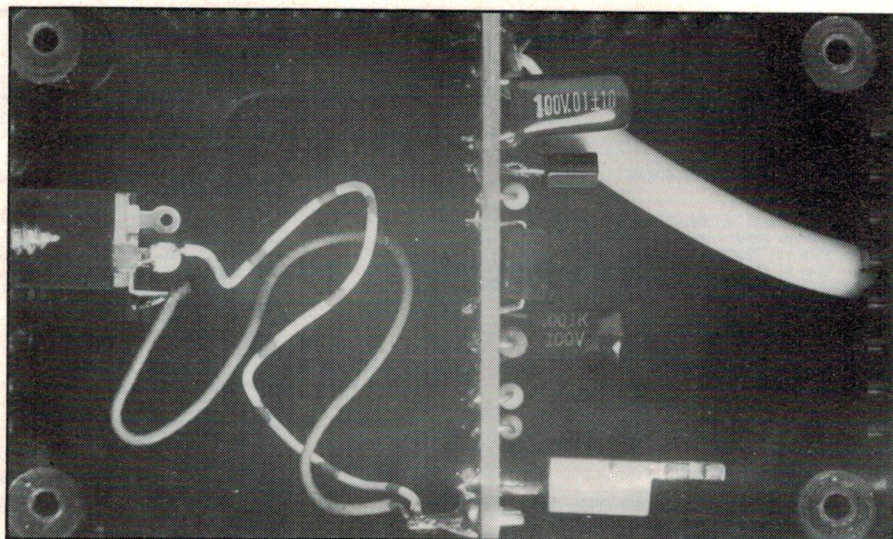80 Lewis Rd., Wantirna South 3153.
Tel: (03) 220 7260 Fax: (03) 220 7263



A general look inside the trigger interface box, showing the lead connections and the socket connecting to the modified flash.

number of flashes per second required, and "Cap" equals the value of the trigger (not storage) capacitor in microfarads (usually about 0.01 to 1 μ F).

The main storage capacitor's new value should be around 0.5 μ F. The new resistor should be about 0.5M Ω , rated at 400V DC.

Construction

The authors' interface was built on a very small PCB, measuring 49 x 23mm. The PCB pattern and component overlay are shown in the illustration. Note that the layout of their PCB should be followed fairly closely to ensure that the circuits of your computer are protected from damage. Veroboard should not be used for this project.

In mounting the components on the PCB, fit the resistors and capacitors first. Then fit the 1N914 diode and the BC547 transistor, watching the lead orientation carefully.

Finally, add the opto-coupler and the triac, again making sure of their orientation. All that is necessary now is to add the external connections.

We mounted the PCB assembly in one of the very small plastic utility boxes, Dick Smith Electronics type H-2855 or similar. This has internal slots, to allow the PCB to be mounted vertically across the centre as shown in the pictures.

The cable from the computer is brought in through a hole at one end of the case, and connected directly to the PCB. The lead from the flash unit is terminated in a small concentric-type DC power plug (5mm OD), and a matching socket mounted on the "other end" of the interface box.

This system allows the flash unit to be

disconnected from the interface for storage. The interface itself can be left permanently connected to the computer.

Conclusion

Without any modification to the software, the computer interface can be used as an external trigger for a commercially manufactured electronic stroboscope.


For externally triggered stroboscopes which require a 5V pulse, the strobe could be connected directly to pins 1 and 15 on the Apple, thus bypassing the interface.

By connecting appropriate light sensors or other transducers to the computer plug, the strobe can be started when a pre-programmed set of conditions are met. Experiments could include the stroboscopic photography of collisions in two dimensions, such as the trajectory of projectiles, or droplet formation in water streams.

As stated in the introduction, the unit described in this article can be used to examine waves in elastic media such as strings, springs and water. Like all stroboscopes, it can be used to measure the speeds of rotating shafts and even to calibrate mechanical shutter-type stroboscopes.

With modification to the software, the unit can be programmed to alter frequency at some preselected time or condition, such as in a stage presentation. To do this, time delay loops can be written into the BASIC control program before transferring counter settings and control to the machine code routine for some specified time. The program then returns to BASIC for further instructions. The possibilities seem endless.

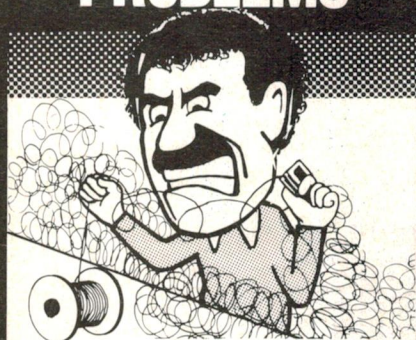DON'T GET WOUND UP OVER YOUR WINDING PROBLEMS




We custom design and manufacture
in volume, transformers and coils
for any application.



**Selectronic
Components**
PTY. LTD.

25 Holloway Drive, Bayswater,
Vic., 3153. Telephone: (03) 762 4822.

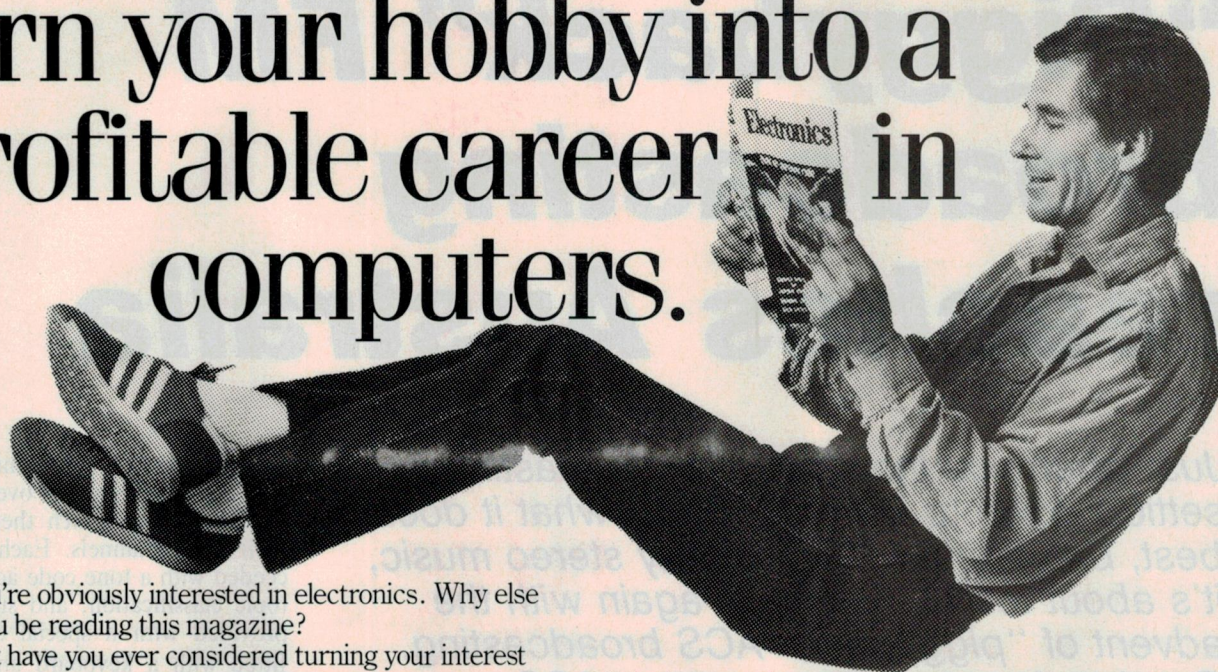Turn your hobby into a profitable career in computers.



You're obviously interested in electronics. Why else would you be reading this magazine?

But have you ever considered turning your interest into a rewarding career as a computer maintenance engineer?

The Control Data Institute can help you fulfil your goal in the shortest possible time by teaching you such subjects as basic electronics, microprocessors, data communication, disk drives and machine language programming.

We then help you further by helping more than

90% of our graduates get their first jobs in this exciting, expanding industry.

Don't delay, contact Control Data now.

Sydney 438 1300, Melbourne 268 9666.

CD CONTROL DATA INSTITUTE
A computer career starts here.

Sanford, Vick 2003.



VARTA

Positively the Battery Experts

VARTA NICAD RE-CHARGEABLE

The professional quality battery for the frequent user, resulting from exhaustive research, sophisticated product development and high-tech production. Recharges up to 1000 times. This is the economical alternative for constant long lasting trouble free operation.



Distributed by **ADEAL PTY. LTD.**

VIC: 150 Buckhurst St. Sth Melbourne 3205. (03) 690-4911. Telex: Adeal AA 37011.
NSW: 405 Sussex St. Sydney 2000. (02) 211-0422
QLD: (07) 299-6992. S.A. (08) 258-5865.
WA: (09) 279-8811.

"Piggyback" FM broadcasting reaches Australia

Just when you thought FM broadcasting had settled down to concentrate on what it does best, bringing you high quality stereo music, it's about to be shaken up again with the advent of "piggyback" ACS broadcasting. But there's no need to panic — ACS shouldn't upset your listening.

A few weeks ago, after extensive testing, the Federal Department of Communications announced that it was ready to authorise the use of Ancillary Communication Services (ACS) by FM broadcasters. This means that Australia will now be able to catch up to countries like the USA, which have been making use of this technique for many years.

In America, it's called SCA — short for Subsidiary Communications Authorization. The US Federal Communications Commission has allowed FM broadcasters to provide SCA services for over 15 years, and they are now very well established. In fact the use of SCA over there has boomed since 1983, when the FCC authorised broadcasters to run multiple SCA channels.

Don't be too worried if you've never even heard of ACS/SCA, though, because even in the USA most people probably aren't aware of its existence. That's because it isn't an enhancement for the basic FM program material being broadcast, like stereo or one of the newer noise reduction systems like FMX.

Even in the States you can't walk into a department store or electronic supplier and pick up an FM receiver or tuner with an SCA switch or output socket. They're certainly available, but not in the usual consumer outlets.

The reason for this is that ACS/SCA is a second and completely separate

broadcast signal, transmitted "piggyback" on the main FM stereo signal of a station using a second subcarrier. This second signal cannot be demodulated by normal FM receivers tuned to the station's signal, and doesn't interfere in any way with normal reception (at least with modern FM receivers).

What is this second "hidden" channel used for? For a multitude of things, actually.

In the US, its main use for many years has been to distribute background music services for use in restaurants, lifts, shopping centres and offices. For this purpose it is much more efficient and cost effective than using leased telephone lines, which were the previous medium of distribution. It also frees up a lot of telephone lines for their original purpose.

Another major use of ACS/SCA is for distributing specialised news and information services, to meet the needs of business, industry and the professions.

A Physicians' Radio Network has been operating in many states of the US for nearly 15 years, using SCA channels on more than 37 different FM stations. Medicos are provided with a free SCA receiver, so they can use the PRN news and information service to keep abreast of the latest developments.

The Dow Jones financial organisation also provides a national SCA business news service, based on the resources of its Wall Street Journal. Beamed from

New Jersey to a communications satellite, it is distributed all over the country to FM stations which then relay it on their SCA channels. Each item is preceded with a tone code according to its topic classification, and subscribers are provided with a special SCA receiver fitted with a keyboard and audio cassette recorder.

The receiver can identify and record on cassette just those items of interest, by punching in the appropriate codes. This lets the conscientious US executive take the cassette and catch up on the day's financial news, on the way home in the car.

SCA has also been used to provide news and other programs for visually impaired people.

All of these services are essentially using the ACS/SCA channel to carry normal audio, either music or speech. But more recently, it has been used for carrying digital data services like conventional teleprinter/terminal news services, and Videotex.

One such service has been operating for about five years, providing commodity future prices for farmers and wholesalers in rural areas.

Now that ACS has been given the DoC go-ahead, we could see many of these services start to spring up here.

On the technical side, ACS uses a 67kHz subcarrier added to the existing FM stereo multiplex signal. So the complete composite signal used to modulate the station's carrier is as shown in Figure 1. The "piggyback" ACS signals frequency modulate the 67kHz subcarrier, well above the stereo difference signal components centred on 38kHz.

So there will now be four different components: the basic mono sum signal from 0 to 15kHz, the stereo pilot tone at 19kHz, the stereo difference signals from 23 to 53kHz and the new ACS signals from 59 to 75kHz.

The ACS signals are held at an inject-

tion level of 10%, to prevent any cross-modulation or other interference with the main stereo signal. This means that the ACS subcarrier and its modulation signal cannot deviate the main station carrier by more than plus or minus 7.5kHz. The frequency response of the ACS channel is kept to around 5kHz for audio signals, or 3600 baud for data.

To allow for the additional modulation produced by the ACS signal, and ensure that the resulting composite FM signal does not exceed the overall bandwidth of 150kHz (± 75 kHz) allocated to FM channels, the FM station is required to reduce its main channel modulation by 1.0dB. In theory this gives a corresponding reduction in received signal level and degraded signal to noise ratio, but in practice the effect is negligible.

Modern FM stereo broadcast receivers with phase-lock loop demodulators and stereo decoders completely ignore the ACS subcarrier signal, providing this is kept at the correct levels. Apparently some early FM tuners and receivers with discrete component ratio detectors may produce minor background noise effects, but very few of these receivers are still in use.

Before making the decision to authorise ACS in Australia, the Department of Communications carried out very thorough tests in conjunction with FM stations 3EON in Melbourne, 6UVS in Perth and 2DAY in Sydney. The results showed that with well adjusted transmitters and antennas, ACS services caused virtually no deterioration of normal FM stereo reception.

Needless to say, many of our FM broadcasters are looking very seriously at getting the necessary equipment to add ACS capabilities to their transmitters. Typically this costs around \$15-20,000, not a huge sum compared with the cost of a complete new FM station plant.

On the licensing side, the Department of Communications is regarding ACS channels as entirely separate from the main station channels. They will require separate licences, regardless of whether the extra channel is operated by the main station licensee or a different organisation. And because ACS is regarded as a specialised communications service, rather than broadcasting to the public at large, its licences will be issued under the Radio Communications Act, rather than the Broadcasting Act.

That's the story of ACS, our latest development in FM broadcasting. For public broadcasters in particular, it looks like providing a welcome way to

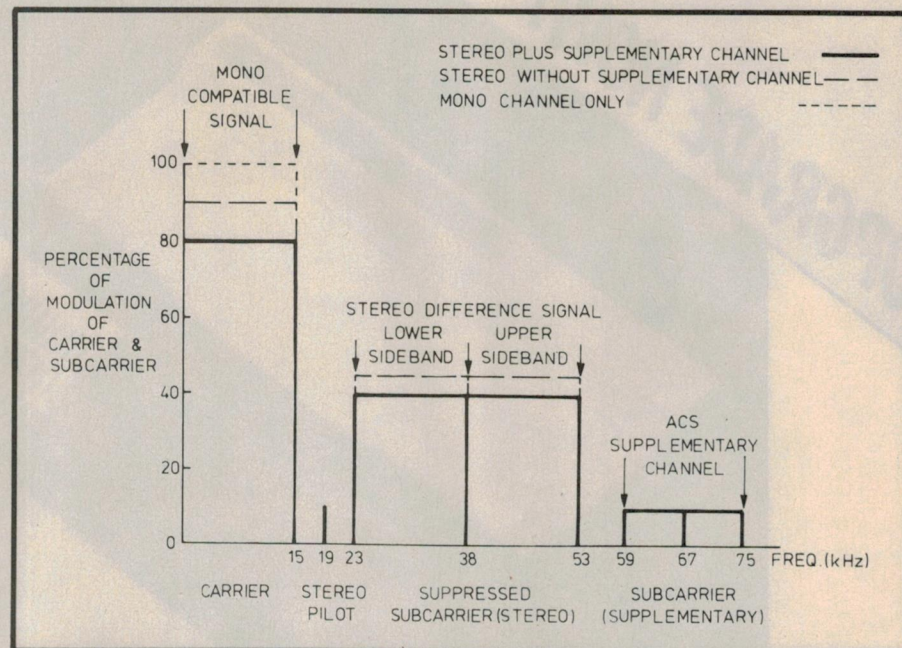


Fig.1: The complete signal spectrum for an FM stereo transmitter, showing where the ACS "piggyback" signal slots in at 67kHz.

boost their modest incomes, by leasing out their ACS channel to a background music provider or news service.

It's also likely to provide all sorts of people in our community with many more sources of helpful information, at relatively low cost. About the only people who hopefully won't even notice its arrival are normal FM stereo listeners!

Rumour has it that one large organisation is planning an Australia-wide ACS system which would call for at least 100,000 special receivers. If this goes ahead, it would almost certainly involve local manufacturing of the receivers — another boost for the local electronics industry. Hopefully we'll be able to say more about this soon.



ACS solution for FM stations

This is the Sidekick, an integrated ACS generator and processor unit made by Modulation Sciences Inc. in New York. It is very widely used by FM broadcasters in the US, to provide their transmitters with ACS/SCA music or speech capability. A matching unit, the Data Sidekick, is used to provide for ACS/SCA data capability.

Both units are crystal controlled and provide an inbuilt transmitter tuning aid and deviation monitor. As the Australian ACS standards

are essentially the same as those used in the US, they are both very suitable for use here.

The local agent for Modulation Sciences is Radio Manufacturing Engineers, of Unit A, 30-32 Skarratt Street, Auburn 2144. This company can also provide ACS receivers from Johnson Electronics, also of the USA.

Our thanks to RME for this picture, and for their help in providing information used in this article.

UPGRADE NOW!



MICROBEE 256TC

A breakthrough in Australian informatics

- 256k of Dynamic RAM
- Single or dual 3.5" 800k double density disk drives
- Ergonomic, Australian designed keyboard with numeral pad and function keys
- Optional AUTOMODEM for the complete communications package.

IT'S FOR YOU

It's a new class of very personal computer for Education and Communication the Microbee 256TC is in a class of its own.

The product of over \$1,000,000 of Australian research and development. Designed by Australians for the World market, the 256TC is a totally new concept for the Education Information Revolution. Whether you are simply seeking a better education for your family, or wishing to improve your letter writing, personal business and communication skills, the new 256TC is your kind of computer. From Homework assignments to 'Learning Can Be Fun' Educational games and even Adventure and Graphic Games of skill, the 256TC will stimulate and entertain the whole family, and what's more the education approved Microbee software will ensure your family's home learning is in tune with their day time studies.

The powerful 256 TC Executive Solution with its twin 3.5" 800k disk drives and brilliant, low cost Microbee Automodem delivers you the complete Executive Computer for your home or office. Send and receive your own Telex messages, use Viatel, do your banking at home and communicate with other systems. With this new Microbee you can do it all.

EDUCATION SOLUTION

Price \$1299.00

Package includes: Microbee 256TC single drive, M-15 High resolution monitor 15KHz, 256TC manuals and software including Simply Write, Videotext, Telcom and Learning Can Be Fun.

HOME OFFICE SOLUTION


Price \$1899.00

Package includes: Microbee 256TC dual drive, M-15 High resolution monitor 15KHz, DP-100 Near letter quality, dot matrix printer and parallel printer cable, 256TC Manuals and software including Simply Write, Videotext, Telcom, and Learning Can Be Fun.

EXECUTIVE SOLUTION

Price \$2999.00

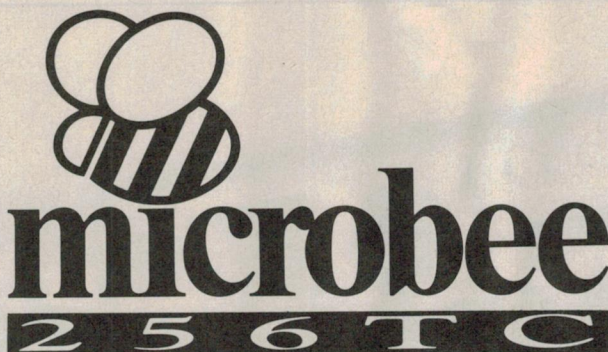Package includes: Microbee 256TC dual drives, 7030 High resolution RGB colour monitor, power supply 1.5A (for colour monitor), DP-100 Near letter quality dot matrix printer, parallel printer cable, Microbee Automodem 300+1200/75 bps RS232 serial M-M cable 256TC Manuals and software including Simply Write, Videotext, Telcom, Typing Drill, and Learning Can Be Fun.



microbee
256TC

UPGRADE

Yes. You can upgrade your old Microbee keyboard and disk unit to a brand new 256TC. Write in, phone or call in at a Microbee Computer Centre now for a free catalogue.

MICROBEE COMPUTER CENTRES AND DEALERS

GOSFORD CENTRE
Koala Crescent,
West Gosford, N.S.W. 2250
(043) 24 2711

MELBOURNE CENTRE
50 - 52 Whitehorse Road,
Deepdene, Vic. 3101
(03) 817 1371

ADELAIDE CENTRE
117 - 119 Gouger Street,
Adelaide, S.A. 5000
(08) 212 3299

PERTH CENTRE
141 Stirling Highway,
Nedlands, W.A. 6009
(09) 386 8289

WAITARA CENTRE
1a Pattison Avenue,
Waitara, N.S.W. 2077
(02) 487 2711

NEWCASTLE CENTRE
2/956 Hunter Street,
Newcastle West, N.S.W. 2302
(049) 61 1090

BRISBANE CENTRE
455 Logan Road,
Stones Corner, Qld. 4120
(07) 394 3688

NETWORK A.B. SWEDEN
Box 10 264,
43401 Kungsbacka, SWEDEN
(300) 19500

COMPU-K (066) 21 8180 • TIMBERTOWN COMPUTERS (065) 85 3311
SHORE COMPUTER SERVICES (044) 21 4522 • MICROZED COMPUTERS (067) 72 2777
SPICER'S OFFICE EQUIPMENT (080) 88 2188 • COUNTRY OFFICE SUPPLIES (069) 53 4155
COUNTRY OFFICE SUPPLIES (069) 21 1600 • CUMBERLAND COMPUTERS (02) 819 6666
THE WORDWORKS (062) 47 7739 • THE XEROX SHOP (070) 51 4341 • SOFTWARE 80 (07) 369 6888
TOWN & COUNTRY COMPUTERS (077) 75 4000 • CABBS COMPUTER SERVICE (053) 52 4326
C & G SOVEREIGN (050) 22 1777 • AUSTRALBEE MICROCOMPUTER PROMOTIONS (03) 233 9665
SIMPLY COMPUTERS (055) 62 8140 • COLAC COMPUTER SERVICE (052) 36 6290
LINCOLN COMPUTER CENTRE (086) 82 1666 • PINE STREET TRADING (091) 89 1383

Compact new 10MHz scope runs from batteries

Part of a new family of compact test instruments from OK Industries, the Model 1010 oscilloscope provides all of the features found in larger laboratory models but in a highly portable battery-powered package.

OK Industries has been around for a long time. Based in the Bronx area of New York, the company has become well known throughout the world for its wire-wrapping tools and other production equipment. More recently it formed an electronics division, which has been producing a growing range of practical and sensibly priced test instruments.

The latest addition to the company's instrument range is a family of compact models, which appear to be designed primarily for the service workshop or college/university laboratory. They are also likely to be of interest to the seri-

ous hobbyist.

Apart from the 10MHz scope, there's a 2MHz function generator, a 5MHz pulse generator, a 200MHz universal counter, a 500MHz frequency counter and three different digital multimeters. All instruments in the family are housed in matching compact low profile cases, moulded from high-impact ABS plastic. The scope, counters and multimeters are all capable of running from either internal batteries or an external AC adaptors.


To go with the new instruments there's also an attractive mini bench rack, to hold up to four of them in a

convenient assembly. OK also provides a comprehensive range of test probes and other accessories, including thermocouple probe for temperature measurement.


Perhaps the most interesting model in the new family is the model 1010 scope. There aren't too many battery operated scopes available, let alone any this compact and packed with features.

Naturally enough the screen isn't large, measuring only 32 x 26mm. But the trace itself is surprisingly bright and well focussed, providing a surprisingly good display even at high sweep speeds. As a result it actually seems bigger than its true size.

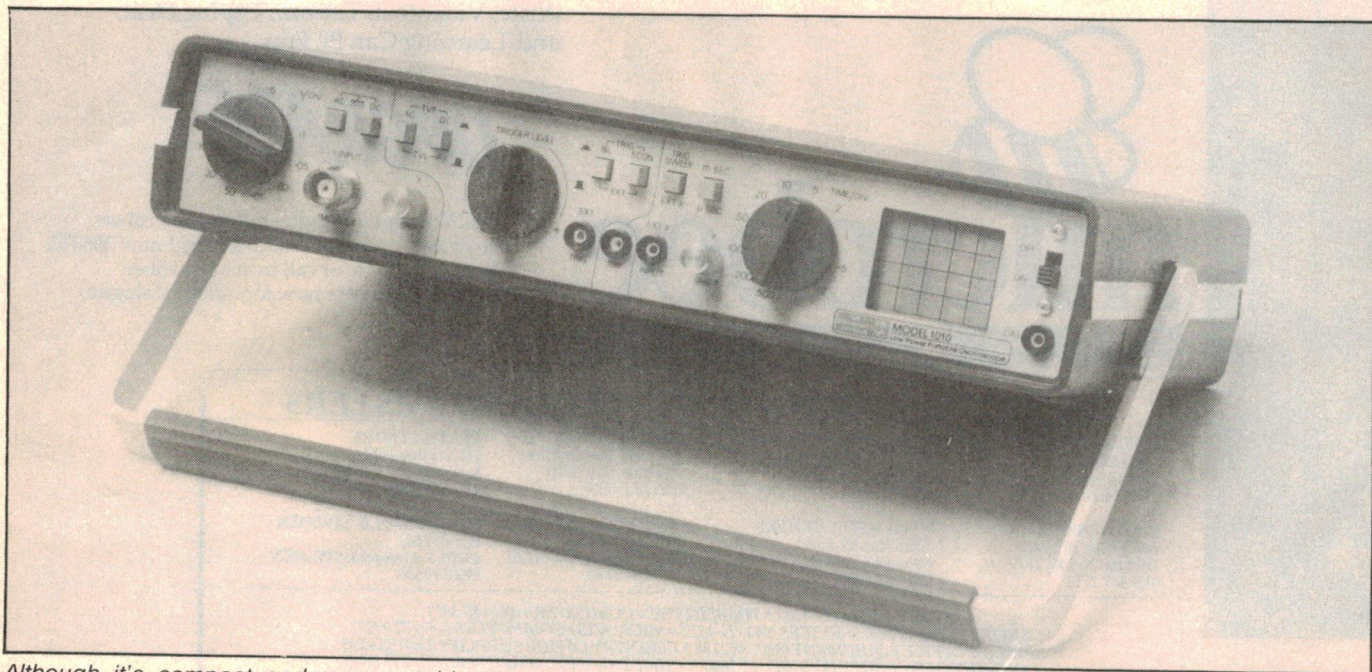For such a compact instrument it sports an impressive range of features, not the least of which is a full range of triggering modes and controls. Internal or external, AC or DC coupling, TV frame or field filtering, positive or negative slope and fully adjustable — you name it. There's even a special "econ-



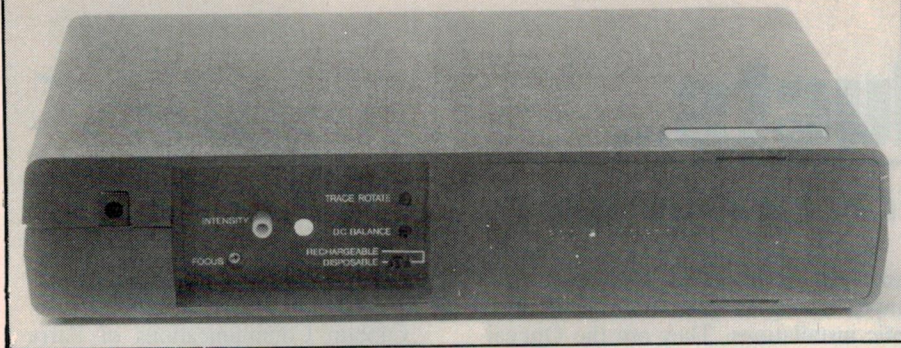Although it's compact and very portable, the model 1010 provides all of the controls and facilities found on a full-size laboratory instrument. Although small, the display is crisp and bright.



Rear view of the OK portable scope, showing the intensity focus and other presets. The batteries (four C-type cells) are housed behind the cover on the right.

omy" triggering mode, to conserve the batteries by blanking the CRT until a signal is applied and the timebase triggers. Typical average power consumption in this mode is only 350mW, roughly a third of that in normal modes.

The timebase itself provides 21 sweep speeds, from 0.5s/div to 0.1us/div in the usual 1:2:5 ratios. The timebase can also be disabled, and the X amplifier used with an external input. For this purpose it has a bandwidth of DC to 2MHz (-6dB), with a sensitivity of approximately 0.5V/div and an input impedance of 1M in parallel with 10pF.

The single vertical channel provides a bandwidth of DC to 10MHz (-3dB), for one division of deflection. Sensitivity is

10mV/div, with 12 attenuator ranges down to 50V/div again in 1:2:5 ratios. The input impedance is 1M in parallel with 47pF, compatible with most standard probes. A switchable input coupling capacitor blocks any DC component and provides AC response down to 2Hz (-3dB).

Other features of the 1010 include rear controls for trace intensity, focus and rotation (to allow alignment with the measuring graticule), and a built-in calibration source of 1kHz square waves of 1V p-p.

The power supply for the 1010 is of the switch-mode type, which can operate from any DC input between 4V and 10V. The internal battery compartment


accepts four C-type cells, and these may be either standard or alkaline dry batteries, or rechargeable ni-cad cells. Alternatively it can operate from an external plug-pack AC adaptor. In short it's a very flexible little unit.

Inside the 1010 there isn't a great deal of space to spare, as you might expect. Pretty well everything apart from the CRT is packed onto a set of compact PC boards. The CRT itself is wrapped with a magnetic shield, which appears to be of mu-metal or similar. It all looks quite snug, and should be able to take a fair degree of shock.

In use, I found the 1010 very convenient and easy to drive. It triggered reliably on a variety of signals, and gave every indication of being a dependable measuring tool. I'd say that OK Industries have produced a very nice little scope here — and it's cute, too!

If you're in the market for a compact scope, particularly one that is battery operated, it would have to be a strong contender. At the quoted retail price of \$655.00 plus tax it also seems quite good value for money.

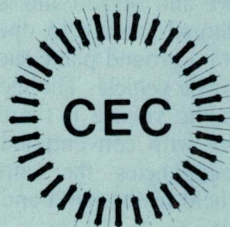The review sample came from OK's Australian distributors Electronic Development Sales, of 92 Chandos Street, St Leonards NSW 2065. (J.R.)



"MINIATURE SOLID TANTALUM CAPACITORS"

KEMET[®] ULTRADIP II

The new gold colour epoxy series with laser marking to MIL-1-46058. Conforms to Telecom spec.

CE-65050 (RJEP451 .../...)

This series has many features of the Kemet military approved types, but at prices allowing design into commercial-industrial equipment.

Available — exstock.


FREE SPECIFICATIONS AND DATA FROM:

CRUSADER ELECTRONIC COMPONENTS PTY. LTD.


81 PRINCES HWY, ST PETERS, NSW 2044 Phone 519 5030 516 3855 519 6685 Telex 23993 or 123993

APPOINTED DISTRIBUTORS:

SYDNEY GEORGE BROWN & CO PTY. LTD. PHONE 519 5855 GEOFF WOOD ELECTRONICS PTY. LTD. PHONE 810 6845
WOLLONGONG MACELEC PTY. LTD. PHONE 29 1455 CANBERRA GEORGE BROWN & CO PTY. LTD. PHONE 80 4355
NEWCASTLE NOVOCASTRIAN ELECTRONIC SUPPLIES PHONE 61 6055 MELBOURNE R.P.G. AGENCIES PTY. LTD. PHONE
439 5834 JESEC COMPONENTS PTY. LTD. PHONE 598 2333 GEORGE BROWN & CO PTY. LTD. PHONE 419 3355 BRISBANE L. E.
BOUGHEN & CO PHONE 369 1277 COLOURVIEW WHOLESALE PTY. LTD. PHONE 275 3188 ST LUCIA ELECTRONICS PHONE
52 7466 ADELAIDE PROTRONICS PTY. LTD. PHONE 212 3111 D.C. ELECTRONICS PTY. LTD. PHONE 233 6946 PERTH SIMON
HOLMAN & CO PHONE 381 4155 PROTRONICS PTY. LTD. PHONE 362 1044

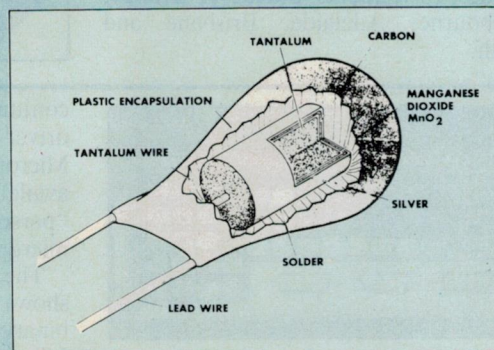

New Products...

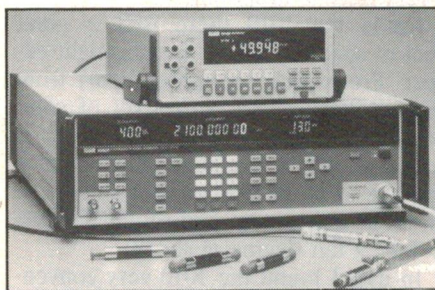

Signal generator covers to 2.1GHz

Elmeasco Instruments has introduced the Fluke 6062A Synthesized Frequency Generator, with signal generation capabilities from 0.1MHz to 2.1GHz. The instrument also incorporates a high-performance pulse modulator, which uses gallium arsenide switch technology for rise/fall times of 15ns and on/off ratios of 80dB. The 6062A is designed for L-band applications in avionics, communication and navigation.

The 6062A's output level is adjustable over the range of +16 to -137dBm (to 1050MHz), and +13 to -137dBm to 2100MHz. Absolute accuracy is +/- 1.5dB. Amplitude can be displayed in volts, dBm, dB, uV or dB mV.

Residual FM is guaranteed to be less than 6Hz (0.3 to 3kHz) in the frequency range of 245 to 512MHz, with -123dBc typical SSB phase noise 20kHz offset from a 500MHz carrier frequency.

For more information contact Elmeasco Instruments offices in Sydney, Melbourne, Adelaide, Brisbane and Perth.


Fibre optics test gear

Philips has developed two small, hand-held instruments for quick and simple testing of glass fibres and fibre optic installations. They are the Optical Power Source OPS-5 and Optical Power Meter OPM-6.

The OPS-5 is available in different versions: for single- and multi-mode operation, for the wavelengths of 850nm, 1300nm and 1550nm and with LED or laser diode. All power sources are power-controlled and provide high level stability.

The OPM-6 is used in the field to measure the absolute light level coming from a fibre. The instrument is the size of a pocket calculator and only weighs about 400g. It can be used for wavelengths of 800 to 1800nm. The calibration of the three most used wavelengths (850, 1300, 1550nm) are switched selectable, dispensing with the need for conversion with calibration factors. The measuring range of +5 dBm to -60 is well-suited for the power range of today's and future transmission systems.

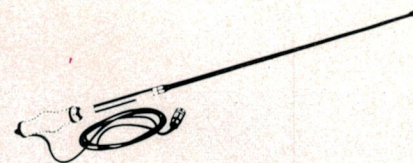For more information contact Philips Scientific and Industrial, 25-27 Paul Street North, North Ryde, 2113.




UHF mobile antenna

Captain Communications of Parramatta has just launched what they claim is Australia's (and the world's) most rugged gain antenna for UHF CB use. Named "The Safari Stick", it is a ground independent gain antenna for use on bull-bars, roof-bars, gutter mounts and on fibreglass vehicles.

The Safari Stick has a gain of 6dB over a normal 1/4-wave antenna mounted in the same position. It is mounted on a heavy duty barrel spring made from high grade stainless steel, with chrome plated brass end plates, making corrosion problems non-existent. The spring is designed to prevent the antenna from tilting more than 15 degrees from the vertical at a vehicle speed of 160km/hr, so the radiation pattern and gain remain virtually constant at high speed. At the same time, the spring acts as an effective shock absorber for off-road conditions.

The chrome plated brass round skirt is both attractive and rugged and is the key to the antenna's ability to operate independently of a ground plane such as the metal body of a vehicle. The mounting position on the vehicle is therefore less critical than with conventional antennas (in emergencies the antenna could even be held in the hand and still work efficiently).

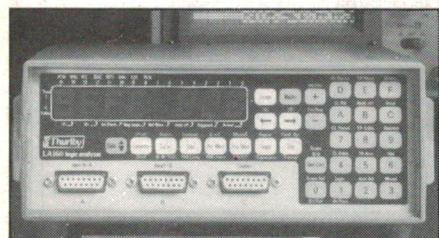Further information from Captain Communications, 28 Parkes Street, Parramatta 2150.



Low cost logic analyser

The new Thurlby LA160-PC Series Logic Analyser provides sophisticated instrument performance at low cost.

The LA160-PC has 16 data channels (expandable to 32), with a 2,000 word acquisition memory and may be used in

conjunction with an IBM PC using a driver program supplied with the unit. Microprocessor disassembly is also available via the simple connection of "personality" modules for most popular microprocessors.

The built-in state domain display shows the data in any of five formats: binary, octal, decimal, hex or mixed. A full sixteen channel timing domain display is also available by connecting to any conventional oscilloscope. The maximum clock rate is 10MHz for the LA160A-PC or 20MHz for the LA160B-PC.

The LA160-PI is microprocessor controlled via an interactive keyboard, with all the set-up information being stored in permanent memory. A non-volatile

reference memory is also included. This can be loaded from the acquisition memory or the keyboard and allows reference data to be stored for comparison purposes.

The inputs of the LA160 are fixed TTL level with optional high impedance variable threshold data pods being available. Other options include a 32 channel expander unit, an IEEE-488 bus analysis connector, and a printer interface for hard copy.

The LA160 weighs less than 1.8 kilograms and is compact enough to fit into a tool kit or briefcase. As such, it has an advantage over other logic analysers in portable applications.


Further details from Parameters, 106 Howe Street, Osborne Park 6017.

High quality electrolytics

High quality electrolytic capacitors manufactured by Lelon in Taiwan are now available from Altronic Distributors. Lelon products are manufactured under stringent conditions in a modern factory, and are used by many of the world's largest equipment manufacturers.

Types available include PCB mount (radial), axial, PCB mount low leakage, radial bipolar and chassis-mounting can types. Values range from 1uF to 100uF for bipolar types. Normal types are available in 16VW, 25VW, 50VW and 63VW sizes, low leakage types in 16VW, 25VW and 35VW, and bipolar types in 50VW.

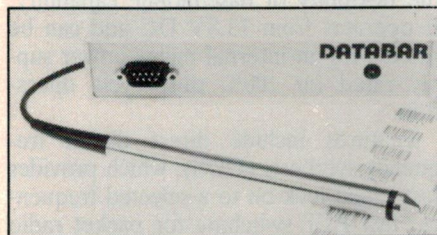Full technical specs for Lelon electrolytics are available on request, from Altronic Distributors, 174 Roe Street, Perth 6000.



Bar code reader


With the release of the Model 440, Nortronic Instruments has increased performance, reduced size and lowered the price of hand held bar code readers wands. In a package smaller than a paperback book, the new reader is available for RS-232 systems and keyboard emulation on many popular PC's and terminals.

The reader is capable of reading all common codes, including Code 39, Interleaved 2 of 5, APN, Code 128 and Codabar. The reader detects which code is being scanned and decodes it automatically. A Return, Return/Line Feed, ETX or no terminator is appended and transmitted to the computer.

Other user switch selections are parity options, baud rate and inter-character delay. A series of internal jumper pins allows initial set up of a wide variety of serial handshaking configurations.

The Databar Model 440 Reader is made in Australia and is priced at up to several hundred dollars below some imported readers. Dealer and OEM enquiries are particularly welcome.

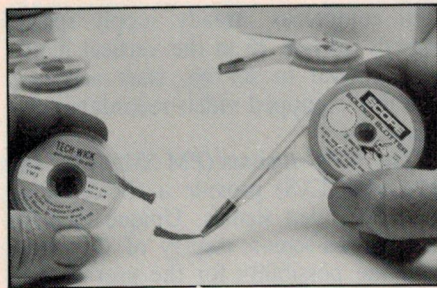Additional information is available from Nortronic Instruments, P.O. Box 300, Brookvale 2100.



Desolder braid options

There is now a choice of desoldering braids from Scope, offering either ease of use or economy.

Scope Solder Blotter is standard desolder braid which can be wound or unwound from a plastic dispenser that helps position the braid even in awkward places.

The dispenser also lets the user keep fingers well away from the hot zone and eliminates the threat of human sweat or body oil to solder joint integrity.

Scope Tech Wick has the same high absorbency fluxed braid, but offers the economy of a basic — no frills container.

Both products are available through electronic supply houses including Dick Smith Electronics in all states.

For further information contact Scope Laboratories, 3 Walton Street, Airport West, Melbourne 3042.



(E)Eprom programmer

The Bytek Writer-I is a low cost fully standalone (E)Eprom multiprogrammer. (E)Eprom programming is achieved internally within the main unit. All voltages and waveforms required are generated under software control. No personality modules or adapters are required.

The Writer-I provides serial data input and output through its RS232 port. Both down-loading and uploading to a host computer are supported.

Features include a single 28-pin ZIF socket, 30-key full travel keyboard and 6 character 0.6" 7 segment LED display.

Further information from Scientific Devices Australia, 2 Jacks Road, South Oakleigh 3167.

Knobs for instruments, appliances


A complete range of control knobs with four shaft fixing systems is available from Crusader Electronics.

The knobs are suitable for shaft diameters of 3mm, 4mm, 6mm metric and 1/2", 1/4" imperial. They can be supplied with collet, grub screw, push on with tension spring for knurled shafts, or push on with rubber friction ring for use with smooth shafts.

Supplied in a comprehensive range of colours and designs, including diamond aluminium finish, the knobs are manufactured to the highest standards. Designs to customers specifications can be supplied, subject to minimum order levels.

Included in the range is a complete assortment for gas cookers, electric cookers, washing machines, dishwashers, electric heaters, thermostats, timers and small household appliances.

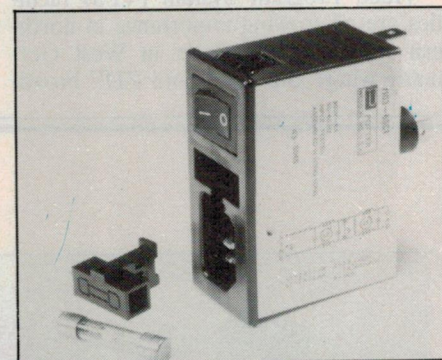For further details contact Crusader Electronic Components, 81 Princes Highway, St Peters 2044.



EMI filters

Most EMI (electro-magnetic interference) filters fitted to electronic equipment are normally an integral part of the socket, the power switch being located elsewhere. A new product recently introduced by J.A. Severn is a composite power line socket module that includes both filter and switch.

The socket is a standard 3-pin IEC connector, suitable for 250V AC and the switch is capable of switching 6 amps. Common mode insertion loss at 10MHz is claimed to be greater than 40dB and, in normal mode (line-to-line) greater than 60dB.

The module is designed for panel mounting and standard connection is by 6.3mm quick-connect terminals.

Further details of the EMI 7103 series power line socket module is available from J.A. Severn, P.O. Box 129, St Leonards 2065.

New Products...



Multistandard TV test pattern generators

Testing of VPS-equipped VCRs has been simplified by introduction of special versions of the PM 5515 and PM 5518 multistandard TV colour pattern generators, from Philips Test & Measurement. All instruments in the PM5515 family now cover Hyperband cable channels H21 to H40 (300 to 470MHz) as standard. US cable TV companies have used the Hyperband for some years and it is being adopted rapidly elsewhere in the world as cable demands grow.

Video Program System (VPS) facilities are of growing importance in northern Europe, particularly in West Germany where the ARD and ZDF broad-

cast companies already supply special signals on line 16 in the vertical blanking interval to set up, start and stop suitably equipped video recorders automatically.

The VPS versions (PM 5515-TXS and PM 5518-TXS) provide a choice of up to nine coded signals. Unique facilities include on-screen display of the codes and the possibility for the user to program the generator to set codes locally if required. Both instruments also allow verification of Teletext and PAL stereo televisions; the FM 5518-TXS offers Antiope checking as well.

Over 70 test pattern combinations are provided by the already existing versatile units, with accurate digital electronic RF frequency selection over the full 32 to 900MHz range. Coverage includes S1 to S10 and S11 to S20 and now Hyperband cable channels H21 to H40.

The microprocessor-controlled generators are particularly easy to use with pattern selection and RF setting on a multifunction front panel keyboard. Up to ten RF frequencies or television channels can be stored and recalled together with any desired pattern and sound modulation.

The PM 5515 meets both PAL and

NTSC standards, the PM 5516 works to SECAM while the PM 5518 handles all three. Instruments can operate on CCIR and RTMS TV standards to both PAL and NTSC chroma standards or to SECAM standards.

Further information from Philips Scientific and Industrial, 25-27 Paul Street, North Ryde 2113.



Two-metre mobile transceiver

The Icom IC-275A two metre transceiver offers all-mode operation, plus the flexibility of base/mobile capability. It operates from 13.8V DC and can be fitted with an internal mains power supply rated for 100% duty cycle operation.

Features include direct digital frequency synthesis (DDS), which provides fast (5ms) lock-on to a selected frequency; fast PTT switching for packet radio and AMTOR modes; 99 user programmable memory channels storing frequency, mode, duplex direction and offset; and advanced remote control functions.

Four separate scanning functions provide easy automatic monitoring of selected band segments or the entire 2m amateur band: memory scan, mode-selective memory scan, programmed scan or skip scan.

The use of a 3SK121 disk-type GaAs-FET front end provides low noise, high gain RF amplification. The receiver section also features a balanced mixer using 2SK125 junction FETs for increased sensitivity and wide dynamic range.

Transmitter power output is continuously adjustable from 2.5 to 25 watts under front panel control. For higher power applications, the IC-275H version provides continuously adjustable output up to a beefy 100 watts. Spurious output rejection is better than 60dB below peak power output, while carrier suppression and unwanted sideband suppression are better than 40dB below peak output.

The Icom IC-275A/H is on display now at authorised Icom dealers. For more information contact Icom (Australia), 7 Duke Street, Windsor 3121.


FRAKO

Electrolytic Capacitors

SEMIKRON
Innovation & service
P.O. Box 182, Springvale VIC. 3171
Telephone: (03) 561-3044

Power conditioners

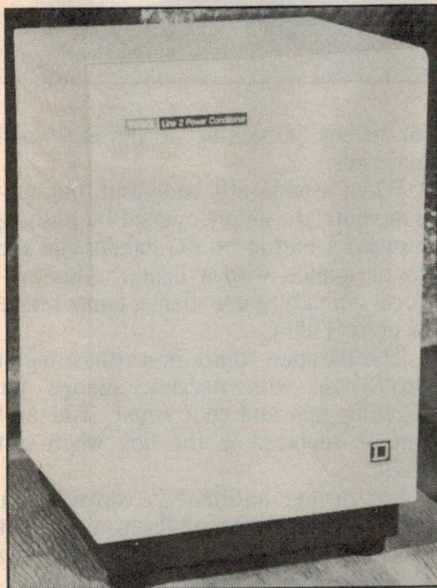The latest addition to the Topaz range of power conditioning equipment is the 3kVA Line 2 high peak current power conditioner. This model, as with the smaller 12kVA and 1kVA models, is specifically designed for personal



computers, minicomputers and other power sensitive equipment, with the added bonus of being able to offer a greater load handling capacity.

The conditioner provides voltage regulation via a high speed microcomputer controlled electronic transformer tap changer, featuring zero current switching. Very high electrical noise suppression (130dB) is achieved by an ultra isolation transformer and filter.


The one-cycle peak current rating is 14 times rated current. This allows the full steady state rating of the conditioner to be utilised with switching and series regulated DC power supplies, which typically draw a high current pulse at the peak of the voltage waveform.

The attractively styled, compact unit has the over-current circuit breaker and input-output terminals conveniently placed at the rear of the unit.

Further information is available from Online Control, Unit 2/7 Waltham Street, Artarmon 2064.

2200MHz signal generator

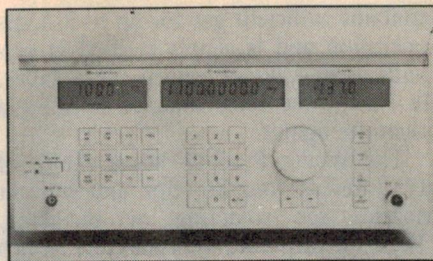The Wavetek Model 2520 is claimed to be the first 2GHz signal generator to use modern single-loop phase-lock technology and a low frequency direct digital synthesizer to provide outstanding




performance at a modest cost.

Internal and external AM and FM modulation capability are standard. Internal rates of 400Hz or 100Hz may be combined with an external source for AM on FM or FM on AM complex modulation. FM deviation of 1MHz or greater is available over most of the frequency range of the 2520. Several standard modulation options provide for phase, pulse and FSK modulation.

A broad range of output power from 137dBm to +13dBm makes the 2520 suitable for driving high level mixers, or making low level receiver sensitivity tests with a resolution of 0.1dB throughout the full range of output level.

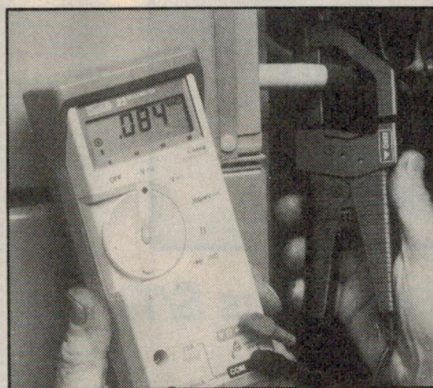For further information contact Scientific Devices Australia, 2 Jacks Road, South Oakleigh 3167.



Clamp on current probe

Elmeasco Instruments has announced the release of the Fluke model 80i-1010 clamp-on current probe. This accessory is designed for use with a digital multimeter and can accurately measure AC current to 700A and DC current to 1000A.

In use, the probe clamps around the conductor and senses the magnetic field produced by the current flow. A feature of the 80i-1010 is a thumbwheel zero control which allows the user to compensate for residual core magnetism in the clamp.

For further information contact Elmeasco Instruments Pty Ltd, 15 McDonald St, Mortlake, NSW 2137. Telephone: (02) 736 2888.

Sony's new CDP-C10 CD


Following the success of their disc jockey compact disc player for the car, Sony has now released a new unit for the home — the CDP-C10.

The CDP-C10 has a built-in changer for the 10-disc magazine. The magazines are interchangeable with the CDX-J10 disk jockey unit, allowing the user to take a compilation of discs from car to house without removing the discs from the magazine.

Features of the new player include 20 track RMS (Random Music Select) and direct access of playing selections via the 21-key pad wireless infrared remote control.

The suggested retail price of the CDP-C10 is \$1,599.

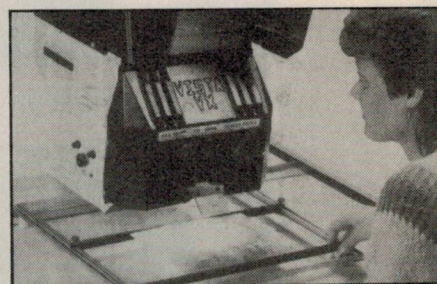For further information contact Sony (Australia) Pty Ltd, 33-39 Talavera Road, North Ryde, NSW 2113. Telephone: (02) 887 6666.



Optical inspection system

A new optical inspection system for printed circuit boards, artwork, surface mounted devices and soldering has been devised by Westinghouse Systems.

The Vista VX optical inspection systems consists of variable magnification in the range of 5 to 10 times and a low glare projection screen that can be viewed by more than one operator at a time. The usual eye strain experienced when using microscopes is eliminated.

The workpiece being inspected is quickly fitted into the special carrier which is moved manually for instant inspection along its free lateral axis. This, together with the Y axis indexing system, makes for quick and accurate inspection. Any fault can be repaired or marked for rework. The 10 times magnification enables a detailed investigation where faults are found.

For further information contact Westinghouse Systems, 80-86 Douglas Parade, Williamstown, Vic 3016. Telephone: (03) 397 1033.


New Products...

Gas powered service tool

Weller's new Pyropen is a liquid butane gas powered "cordless" service tool with adjustable temperature facility, which can be used effectively for a wide range of soldering, brazing or shrinking jobs. Comparable in size to conventional soldering irons, the tool

contains sufficient gas for up to 3 hours operation and is simply refilled in seconds using a liquid butane gas cylinder, in exactly the same manner as filling a cigarette lighter.

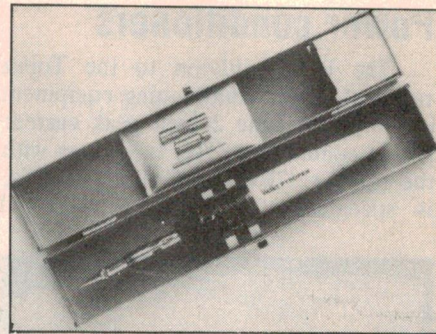The Weller Pyropen has a choice of 17 different long-life tips and hot air nozzles for soldering or shrinking. These incorporate a catalyzer, which generates infra-red and ultra infra-red radiation to provide the necessary hot-air temperature, 200-450°C for soldering and up to 700°C for shrinking tubing or



for fusing or melting acrylic and vinyl materials.


When used as a brazing tool, the ignition vents are simply opened by pushing forward a button on the handle and the gas is ignited with a lighter. This produces an adjustable flame temperature of up to 1300°C.

The Pyropen comes in a robust metal carry case with nozzles, sponge for cleaning tips and tool stand. The tool can be replaced in the box when still warm.

For further information contact your local George Brown or Protronics outlet or George Brown Group Marketing Division, 456 Spencer Street, West Melbourne. Telephone: (03) 329 7500.

OSCILLOSCOPES

DUAL TRACE 20 MHz

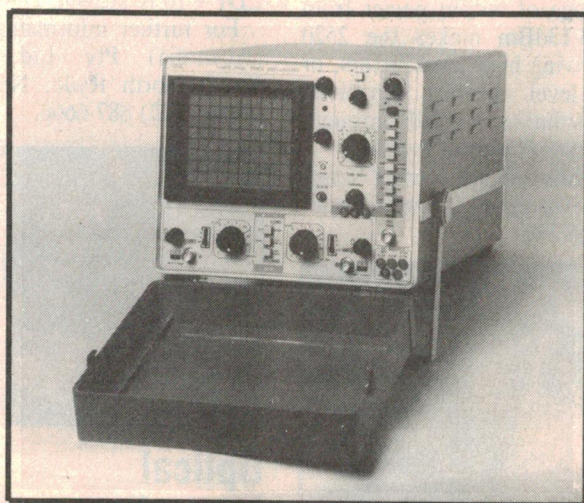

Model 3132 \$683 (Plus S/T)

(Includes Two Probes)

- * 2mV/div calibrated sensitivity on both channels
- * DC — 20 MHz Bandwidth
- * X-Y Operation
- * Algebraic Addition and Subtraction
- * 40 ns/div to 0.2s/div timebase
- * 5" CRT
- * 14 Trigger Functions
- * Triggering to 40 MHz
- * 2 Modulation
- * 10 × Div Display
- * Component Comparator
- * DC Source Triple Output



SCIENTIFIC DEVICES AUSTRALIA PTY. LTD.

MELBOURNE
SYDNEY
ADELAIDE

(03) 579 3622
(02) 95 2064
(08) 255 6575

Software education by cassettes


Until now, the only way to master software programs has been to take expensive training courses or spend perhaps weeks wading through volumes of manuals.

Two innovative and highly experienced Perth educators identified this problem and set about to design a system which would inexpensively lead to a solution. *Listen & Learn* is the fruit of their four years labour, the first audio self instruction cassette system.

The system consists of four cassette tapes plus an easy to follow, colour coded instruction manual which takes the user, step by step, through all the functions of the program. This enables one to master the most complex programs in as little as ten to twenty hours, in the user's own time and at their own pace.

The Listen & Learn library, at present, covers Lotus 1-2-3, Multimate, dBase III, Plus, MS-DOS, Wordstar and Displaywrite3 and many more titles will be available in the near future.

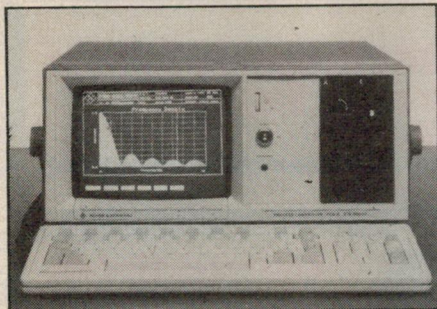Listen & Learn is distributed in Australia exclusively through Dick Smith Electronics.



Process controllers

Two new members of the Rohde & Schwarz process controller family are the PCA12 and PCA15. These are extremely powerful 16-bit desktop computers and, when used as instrumentation controllers in highly demanding measurement and test systems, afford short computing times and comprehensive mass storage for flexible and efficient data processing.

The PCA's are accommodated in a rackable, sturdy 19" cabinet, in which particular attention has been paid to active and passive immunity to RF interference. RF shielding ensures that correct measurement results are obtained even with low RF and AF signals.

The PCA12 and PCA15 incorporate a 80286 CPU as the main processor with an 80-bit arithmetic processor 80287 supporting the CPU thus speeding up calculations many times over. A parallel 80186 processor is provided for all the I/O operations, releasing the main processor from time-consuming I/O operations. The 1-Mbyte RAM with parity error detection has more storage capacity than most personal computers.

The built-in floppy disk drive stores 1.2 Mbyte and is conveniently managed by the operating system MS-DOS 3.1. A second floppy disk drive and a 21.3 Mbyte Winchester drive are optionally available for integration to enhance the memory capacity. For use in measurement engineering, the PCA12 and PCA15 feature high-resolution monochrome graphics with 640 x 480 pixels.

Further information from Rohde & Schwarz Australia, 13-15 Wentworth Avenue, Darlinghurst 2010.

24-Track audio mixing console

British manufacturer of professional mixing consoles, Soundtracs has released its CP6800.

Designed for recording studios, video post production, broadcast theatre and on-air, the CP6800 is a fully modular split analog console with microprocessor

based digital routing.

The benefits for multi-track recording include the automation of mutes and routing (FX sends) which enable 60% of mixing work to be carried out automatically.

The CP6800 is also well suited to stage and theatre production, as all routing can be programmed during rehearsals for recall at the performance. For television, the mix can be programmed "off-air" and synched to the house SMPTE clock for automatic control "on-air".

The main features of the CP6800 include SMPTE/EBU time code triggering of patches, events and muting, and automatic muting of groups and monitor. The console is controlled through an in-

tegral computer module consisting of a keyboard and monitor. "Fail Safe" and "Help" features add to ease of operation.

For further information contact Amber Technology, Unit 6, Forestview Park Estate, Frenchs Forest 2086.



Australia's Finest C Compiler

main (argc, argv) 00110101100

FROM
\$250

plus delivery

HI TECH C Compiler

- Complete production quality compiler
- Smallest, fastest code from any compiler
- High performance C Compiler for the Z80, 68000, 65816, and 8086 processors
- Runs on CP/M-80, PC-DOS, MS-DOS, CP/M-86, CONCURRENT CP/M, ATARI ST and APPLE II gs
- Now in use at thousands of sites worldwide, including Australian Government and large institutions.
- Excellent user interface
- ROM code is supported and it includes a macro assembler, linker, librarian, object code converter, cross reference utility and full library source code. The 8086 compiler supports large and small memory models and the 8087

FROM
\$300


plus delivery

Cross Compilers

- Run under MS-DOS, UNIX, and CP/M-86 and produce code for the 68000, 8086/286, 65816, 8096 and Z80 processors. Each compiler includes an assembler, linker, librarian, object code converter and cross reference utility.



The Cutting Edge

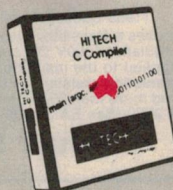

Order from: **HI -TECH SOFTWARE**

P.O. Box 103 Alderley 4051

Telephone (07) **366 6971**




Altronics Will Deliver Any Of These Quality Products To Your Door Faster Than Any Other Australian Supplier Or Your Money Back

(Within 24 Hours To Every Capital City and Suburbs - Allow Additional 24 - 48 Hours For Country Areas)

Logic Probe 20MHz Model

Max. Input Frequency 20MHz. Input Impedance 1M ohm. Operating supply Range 4 volt minimum. TTL Logic 1 Hi LED greater than 2.3 volts. Logic 0 Lo LED less than 0.8 volts. CMOS Logic 1 Hi LED greater than 70% Vcc. Logic 0 Lo LED less than 30% Vcc. Minimum Detectable pulse width 30 nano seconds. Maximum signal input 220V AC/DC (for 15 secs.) Cat Q 1272


Was \$34.95 Now \$29.95

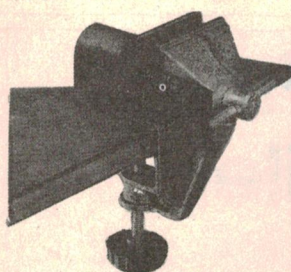

Mini Bench Vice

Direct Import Price Quality Die Cast Allow Cat. T 2365

\$8.95

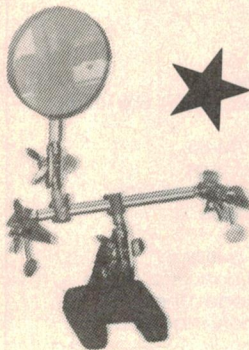

The Simply Magic Third Hand PCB Holders

We never ever used to like to hear of anything 3rd hand - until of course we tried out these fantasmagorical PCB board holders. Each unit grips the PCB by means of crocodile clips enabling you to build or service your projects with total convenience.

Two Models

(Both, we believe, a dollar or two cheaper than D.....H)

T 1450 No Magnifier \$9.50

T 1460 Inc. Magnifier \$14.95

Heavy Duty Unit Suitable For Boards Up To 400mm Long



Solder 200g Reel

\$7ea

10 or More \$6

Alarm Stickers



For Home or Office

S 5400 200mm x 75mm \$2 \$1

Rugged Ultra Quiet- Now With Metal Diecast Frame

240V High Specification Computer Fans

Durable Die Cast Aluminium Venturi PBT Plastic impeller of 94V—0 material. Shaded pole motor.

80mm x 80mm x 32mm

Air Flow 45 C.F.M. Input Power 16W Speed 2300 RPM Noise Level 31 dba. Cat. F 1020

\$24.50ea 4 or More \$22.50

120mm x 120 x 38mm

Air Flow 80C.F.M. Input Power 25W Speed 2600 RPM Noise Level 43 dbA. Cat. F 1030

\$24.50ea 4 or More \$22.50



Fan Finger Guards

F 1022 (for 80mm Fan) \$1.50

F 1032 (for 110mm Fan) \$1.50

Piezo Tweeter 150W

95.3mm Diam. Piezo Speaker Suitable for HiFi applications. Frequency Response: 3K to 40KHz Sensitivity: 104db @ 2.8V Cat. C 6100


\$16.95 4 Up \$15



150W HiFi-PA Piezo

144.8 x 54mm Rectangular Piezo Horn Speaker suitable for HiFi and Sound Reinforcement. Full 90 deg. horizontal dispersion angle • Freq. Res. 3 to 40KHz • Sens: 110db @ 2.8V Cat. C 6120

\$18.95 4 Up \$17

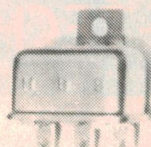

Horn Relay

12-16V coil 20 Amp Contacts S 4130

1/2 Price \$3.75



Solar Cell Module

.4V at 450mA

Great experimenters Solar Module. Connect in parallel or series as you wish. Terminal strap enables easy interconnection to other cells

A 0210 Value \$4.98

10 cells or more \$4.75

Solar Charger

Charges up to 4AA Nicads by simply placing in sun light. (we recommend placing on the inside window ledge in the extreme heat of summer). Will charge from dead flat to fully charged in 8-10 hours average sunlight.

Take Care if charging inside car e.g. on dash board etc. — ensure car inside is well ventilated — remember midsummer inside car temperatures can be extreme.

A 0230 \$14.95




Engineers Multimeter

\$10 Off This Month

Includes Continuity Buzzer

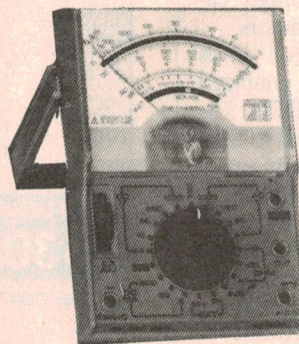20,000 Ohms/Volt DC • 8,000 Ohms/Volts AC. Mirror back- ed scale • Overload protected. 10 amp DC current range. Unique carry handle doubles as a bench stand.



RANGES
DC Voltage
2.5, 10, 50, 250, 1000V

AC Voltage
10, 50, 250, 1000V

Decibels
—8db to +62db

DC Current
5, 50, 500mA

Ohm meter 0-6 meg.

Ohms in 3 ranges, 50

Ohms centre scale.

Size 135 x 91 x 39 mm

Includes Battery Tester

Q 1018

Normally \$39.95

Now \$29.95

Check Appliances And Electrical Wiring Build This 1000V Megohm Meter

(1985 Successor to the "Megger") It uses a transistor inverter to produce a regulated 1000V DC supply which is applied to the insulation under test. Insulation resistances between 2M Ohm and more than 2000 Ohm can be measured. K 2550 (See EA July/85)

Just \$55



Manufacturers, Contractors, Resellers Visit Our Wholesale Booth At The Sydney IREECON Exhibition September 15th — 18th at Sydney Show Grounds

Get a System for Mum and the Kids Full Security System



Fantastic system for this price. Frankly we were amazed at the performance of this very compact system.

Very simple to connect and operate - New Technology has enabled very compact overall dimensions (master unit only 180 x 100 x 65) hence ideal for concealing among book shelves etc.

S 5310 ~~\$99~~ \$75

Look At The Features

EXIT DELAY 30-35 secs. ENTRY DELAY 10 secs. DC SOURCE AC adaptor 240/9V DC Supplied BATTERY BACKUP 9V Nicad rechargeable - additional cost \$50.24 \$14.50. AUTO RESET 3 minute operate cycle and auto reset RANGE Reliable to 30ft.(9M) LOW BATTERY INDICATOR included.

Accessories Included for the One Low Price 4 Sets Reed Switches for Window/Doors. 1 Roll fig. "8" cable. 1 External Type Horn Speaker. 1 AC/DC plug pack adaptor. Now there is now excuse for not Protecting yourself, your family and all your hard earned possessions!

Strobe Signal Lamp

Uses Xenon Strobe tube for High energy strobe flash output at a rate approx. 1 per second. Fantastic light energy output for the DC power used. DC input 12V 320mA Dimensions 97 dia.90H




S 5455 Blue \$19
Were \$24.50

Fantastic Multipurpose Nicad Battery Charger

Charges every conceivable size nicad from AAA through to 9V.

M 8010 \$27.50

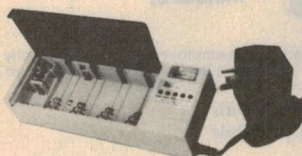

Magazine Binders for Your EA's and ETI's

Holds 12 magazines, each on a spring out wire rod. Just the shot for each years set of EA's ETI's or any of your favourite magazines. Cat. B 9999

\$8.50

Phone Double Adaptor 1/2 Price

P 0995 \$4.50



Sealed Lead Acid Batteries

These rugged high performance batteries are ideally suited for systems where uninterrupted DC power is required i.e. Security Systems, Computers, Solar Power Systems etc.



Three Models To Choose From

S 5065 12V/1.2AH \$22.95
S 5067 12V/2.7AH \$34.50
S 5069 12V/4.5AH \$45.00

Mains Transformer Bargains


Great For All Sorts of Projects

M 2851 240 — 12.6V at 150mA

Was \$5.50 Now \$4.99

M 2155 240V—6.3V,7.5V,8.5V, 12.6V, 15V at 1A

Was \$7.95 Now \$6.00

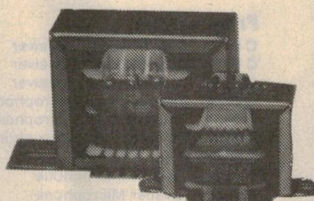

Quality Long Life Hand Tools

All stainless steel construction with insulated handles. Ideal for the hobbyist and tradesman alike.




Diagonal Cutter T 2700 \$9.95
Flat Nose Plier T 2710 \$9.95
Needle Nose Plier T 2720 \$9.95
Curved Needle Nose Plier T 2730 \$9.95

Buy the set of 4 for Only \$30 and Save

Solar Desk Calculators

Never needs batteries - works great under fluro lighting

X 1060

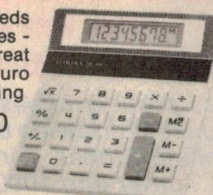

Brilliant Little Solar Credit Card Calculator With "Positive Feel" Rubber Keypads


(Allows fast error free operation)

Runs Forever Without Batteries

Operates free from the sun or fluro light. Full 8 digit 4 function calculator. Positive push button keys. Cat. X 1050

All This in Credit Card Size Incredible

\$14.95

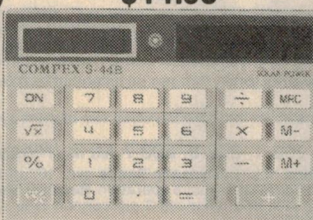

New Model IRD Has Fantastic Range

Infra Red Movement Detector

With Two Mode Lens



Features:

- Lens simply 'snaps' to either wide angle (range 40 feet) for normal use or Normal angle (range 80 feet plus) for corridor applications.
- Snazzy integral mounting bracket allows corner 90 deg. mounting as well as normal surface mount. (This is a fantastic feature as these work best in corners and are visually unobtrusive)
- 12V DC Powered
- Built-in test lamp
- Alarm output SPDT 30V 1a

S 301

Why Pay \$150 or More

Our Price ~~\$99ea~~
10 or More \$90ea

N.B. These professional detectors use state of the art circuitry to achieve ultra reliability in operation. They are currently specified by several "Name" commercial Security Companies.


Fantastic for Heatsink Cooling with Amplifiers, Power Supplies, Inverters etc.

New

DC Brushless Fan

Electronically commutated DC motor ensures low vibration and ultra long life

120mm x 120mm x 38mm

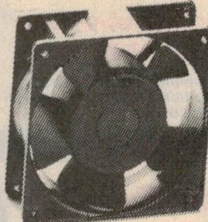

Voltage 24V DC
Current 330mA
Speed 3100 RPM
Air Flow 23 C.F.M.
Noise Level 32dbA

F 1040 \$29.98

4 or More \$28.00ea

Radar Sensation

Incorporates exclusive superheterodyne Horn Microstrip hybrid circuitry.

Was \$399


Now \$349

Accessories Included

Visor Bracket, Velcro, Lighter Plug

Features:

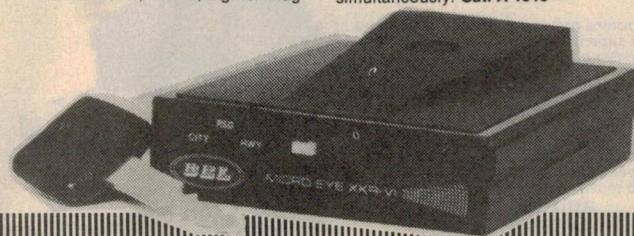- Separate audio alerts for X and K bands.
- RSD (Radar Signal Discriminator) switch eliminate extraneous signals with an LO and LR positions. The amber LED pulses to indicate LO and LR positions.
- Alarm: Red LEDs will light up in sequence as signal strength increases. When all Red LEDs are lit and signal strength continues to increase, all Red LEDs will flash simultaneously. Cat. A 1510



High Definition Computer Monitor New 2 DIN Series 4

The New 2 DIN Computer Monitor has a high performance Non Glare CRT designed to reduce eye strain and improve concentration. Coupled with the non-glare screen is a rock solid Video display and high resolution characters.

SPECIFICATIONS:

Screen Green Phosphor - Non glare 14
Front Controls Power On/Off, Contrast, Brightness
Rear Controls Vertical size, vertical hold.
Bottom Controls Horizontal position, horizontal position.
Input Impedance 75 Ohm/10K switch selectable
Bandwidth 18MHz
Resolution 900 lines at centre screen
Input/Output Connector RCA
Input Composite Video 1V P-P

D 1115 \$229 This Month \$199

Definitely Australia's Best Value in a High Resolution Monitor



Superb Eleco Wireless Microphone System uses Dual Diversity Receivers for Long Range, Noise Free Pure Fidelity Reproduction.


Now Available
In Australia For
Less Than
\$1,000

Altronics proudly release the Eleco
System - Used Worldwide by Entertainers
i.e. Rolling Stones, Dire Straites,
Tina Turner and 1000's more!

Superb
Microphone
Reproduction
Compares with
Shure, Beyer
and AKG



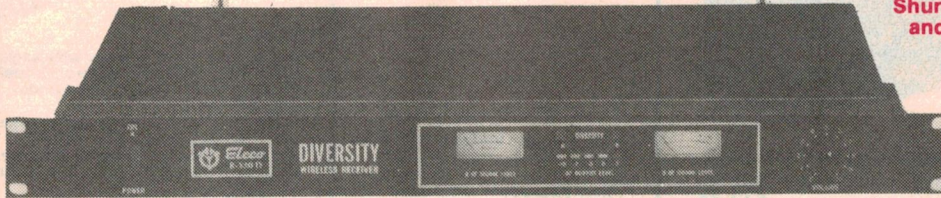Amazing
Range of Over
200 Metres in
typical
applications



Unique
Microphone
design completely
Eliminates
"Dangling"
Antenna



Breathtaking performance without signal drop-out or noise interference. The Eleco Wireless Microphone System is virtually the ultimate in an Entertainers Microphone system (or for any roving microphone application for that matter).

All the annoying wireless microphone characteristics such as "drop out", static and noise are completely eliminated by use of **auto switching dual diversity receivers**. The output of each receiver is continually monitored, with the strongest and clearest signal always selected. **Dynamic Range exceeding 100 db** is obtained by employment of a Patented special Parabola level compressor and Dynamic expander.

The operating range is a minimum of 50 metres (often this can be extended to 200 metres and more in normal circumstances).

Several Frequencies are available to alleviate cross interference when two or more systems are used in proximity.

Brief Specifications Frequency 202.1, 202.9, 203.7 MHz (Please specify if you have a preference)

Mic Carrier Power 50mW (Max) Mic Antenna built-in Dynamic Range over 100db S/N Ratio better than 90db Frequency Response 20Hz to 16KHz + or - 3db
Mic Battery 4 x AA cells Battery Life over 24 hours continuous operation. Receiver Sensitivity 12db/micro volt for 60db S/N ratio Pre emphasis/De emphasis 50us.
Receiver output unbalanced 6.3mm phone jack and balanced 3 pin cannon type. Output Level (adjustable) Unbalanced 0-2.5V Balanced 0 to + or - .3V into 600 ohms. Receiver Power Supply 200 - 260VAC.

Prices

- (A) Dual Diversity Receiver \$729.00
- (B) Entertainment Microphone (hand held type) \$349.00
- (C) Lavalier Type Microphone \$349.00

**Bonus Offer SAVE \$78 Choose Receiver and
Either Microphone For Just \$999**

Please Note 3 different operating frequencies are available (you will need to specifically nominate desired frequency only if the equipment is being used in proximity with other Eleco Systems on the 200MHz band.

Frequencies

C 0111	Dual Diversity Receiver	202.1MHz	\$729
C 0113	Dual Diversity Receiver	202.9MHz	\$729
C 0115	Dual Diversity Receiver	203.7MHz	\$729
C 0121	Entertainment Microphone	202.1MHz	\$349
C 0123	Entertainment Microphone	202.9MHz	\$349
C 0125	Entertainment Microphone	203.7MHz	\$349
C 0131	Lavalier Microphone	202.1MHz	\$349
C 0133	Lavalier Microphone	202.9MHz	\$349
C 0135	Lavalier Microphone	203.7MHz	\$349

AT LAST Design Quality Weather Proof Speakers And Sound Columns By Redford

- Rugged extruded aluminium construction • Superb powdercoat industrial paint finish • Engineered in Australia • Excellent reproduction • Superior to imports — Yet just a fraction of the price!

Altronics proudly announce the release of the superb **Redford Weatherproof Speaker and Sound Column Range**. Imagine a wide range speaker system which is highly directional and with efficiency approaching that of reflex horns!


Redford is the solution for high quality sound reproduction outdoors. The Five Models to choose from "Fill the Bill" from applications on boats to high grade paging and music entertainment installations.

RUGGED EXTRUDED CONSTRUCTION

These vibration free enclosures are constructed from die extruded heavy gauge aluminium and finished with incredibly durable industrial powdercoat enamel. The speaker ends are sealed via gaskets and tough moulded "LURAN S" UV resistant end caps. The end result is "Good Looks" together with assured rugged durability for the Australian environment.

EXCELLENT REPRODUCTION

The drivers have been chosen for wide range, low distortion, mid range "presence" (essential for high grade vocal work) and high efficiency in general. **Power Capacity** for short term use, the drivers will safely handle 150% of rated power. Acoustic wadding is used to dampen Bass resonance. **Weather Proof Construction and use of "Doped Cones"** Foam plastic and cloth is sandwiched between Baffle and Front Grill to prevent water ingress. A first for **Redford** is the use of a patented cone moisture repellent process for all models.

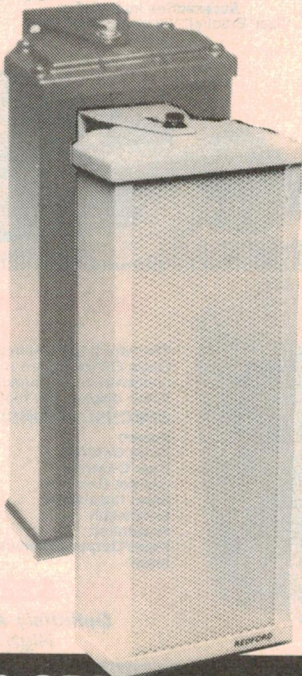

Wide Range
Weatherproof Extension
Speakers For Your Stereo
System

Great For The Back
Patio, Swimming
Pool, Games Room,
Den, Pool Room Etc.

Dimensions 260mm wide
x 170mm high x 150mm D.
(Mounting brackets are
included)

10 Watt 16 Ohm (Max 15 Watt)

Single dual doped cone driver 16 ohm impedance is employed to give a generally correct volume balance with main speakers - an added bonus is your amplifier load is kept to respectable limits!! Great for back patio, Den, Boat Deck etc.

C 0938	White	\$99ea	\$190 per Pair
C 0940	Black	\$99ea	\$190 per Pair

20 Watt 8 Ohm (Max 30 Watt)

Use 2 special dual doped cone drivers for those wanting a bit more umph!

C 0943	Black	\$139ea	\$260 per pair
C 0944	White	\$139ea	\$260 per pair

100 Volt Line Models For Use With Professional PA And Music Systems


Using a "Doped" wide range drivers and fitted with grain oriented steel line transformer Output cable allows connection to 10W/5W/2.5W with 10 watt models, 20W/10W/5W with 20 watt models and 40W/20W/10W with the 40 watt versions.

C 0941	10W/100V line Black	\$119ea	\$220 per pair
C 0942	10W/100V line White	\$119ea	\$220 per pair
C 0945	20W/100V line Black	\$169ea	\$299 per pair
C 0946	20W/100V line White	\$169ea	\$299 per pair
C 0950	40W/100V line Black	\$225ea	\$399 per pair
C 0955	40W/100V line White	\$225ea	\$399 per pair

Save Up To 50% On Top Quality
D Series Connectors!
Fantastic Value

D Series Computer Connectors. Gold Plated Professional Series

Items Marked * are 1/2 Price or Less

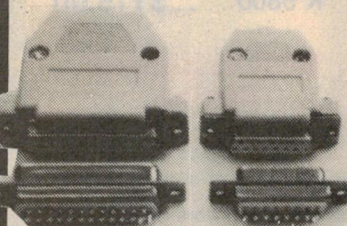

DB9

WERE NOW

P 3000 Male 9 Pin	2.95	1.95
P 3010 Female 9 Pin	3.25	1.60*
P 3020 Male PCB Rt/L	3.75	3.60
P 3030 Female PCB Rt/L	4.50	3.25
P 3040 Male PCB mnt.	2.95	2.85
P 3050 Female PCB mnt.	3.95	3.25
P 3090 Backshell cover	1.95	1.29

DB15

P 3100 Male 15 Pin	3.25	2.50
P 3110 Female 15 Pin	3.85	1.90*
P 3120 Male PCB Rt/L	4.35	2.95
P 3130 Female PCB Rt/L	5.50	2.75*
P 3140 Male PCB mnt.	3.85	1.90*
P 3150 Female PCB	4.85	2.40*
P 3190 Backshell cover	2.20	1.10*

DB25

P 3200 Male 25 Pin	4.95	2.45*
P 3210 Female 25 Pin	5.50	2.75*
P 3220 Male PCB Rt/L	4.95	3.95
P 3230 Female PCB Rt/L	6.90	3.45*
P 3240 Male PCB mnt.	4.95	2.45*
P 3250 Female PCB mnt.	6.25	3.10*
P 3290 Backshell cover	2.20	1.10*

PROFESSIONAL SERIES RACK CABINETS

Now your preamps, Amps, Control Modules Monitor Panels etc. can look every bit as good as Technics Nakamichi and other top manufacturers.



ALL ALUMINIUM CONSTRUCTION

FEATURES: These beautifully crafted rack cabinet boxes will give your equipment a real 1st class appearance with removable top and bottom cover panels • All dimensioning conforms to the International Standard • Natural or Black finish • Ventilated lid • Deluxe finish front panel • Individually cartoned • Supplied in Flat Pack Form - Easily assembled in minutes - **Side Elevations:-** D=254mm C (Internal Chassis Height) • B (mounting Bolt Centres).

SIX NATURAL AND BLACK FINISH MODELS — The Black or Natural finish cabinets are each available in 44mm, 88mm or 132mm high models. Mounting hole centres conform exactly to International Racking Specifications both vertically and horizontally.

Cat. No.	Finish	A	B	C	Were	Now
H 0401	Natural	44	34	38	\$59.95	\$50
H 0402	Natural	88	57	82	\$69.95	\$62
H 0403	Natural	132	89	126	\$85.00	\$79
H 0411	Black	44	34	38	\$59.95	\$52
H 0412	Black	88	57	82	\$79.95	\$70
H 0413	Black	132	89	126	\$89.95	\$80

High Quality — High Power Ratings Polypropylene Loudspeakers

Virtually all the famous "Name" loudspeaker makers now use Bextrene or Polypropylene Cones with their drivers. The advantages are considerable - less cone flexing or "break up", improved bottom end response and reduced enclosure sizes.

One of the problems of course, has been the high cost of P-P drivers. Fortunately, with Altronics direct import prices, you can now be the owner of any of these fine speakers for a fraction of what you'd expect.

Note: the conservative power ratings, the massive magnets employed and high order sensitivity specifications with these fine Drivers.

Brief Specifications (All 8 ohm Voice Coil Impedance)

6 1/2" Woofer/Midrange

30 Watt RMS-50 Watts Max

C 3055 \$24.50

Frequency Response fo—3000Hz Resonant Frequency 33Hz Sensitivity (M/1Watt) 90db (+ or -2db) Voice Coil 38mm Nett Weight 2200 gm. Electromagnetic Q .4 Magnet 836 gm.

10" Woofer

60 Watt RMS 100W Max.

C 3065 \$65.00

Frequency Response fo—3000Hz Resonant Frequency 30Hz Sensitivity (1M/1Watt) 92db (+ or -2db) Voice Coil 38mm Nett Weight 2650 gm Electromagnetic Q .23 Magnet 836 gm.

8" Woofer

60 Watt RMS 100W Max

C 3060 \$49.50


Frequency Response fo—3000Hz Resonant Frequency 36Hz Sensitivity (1M/1Watt) 87db (+ or -2db) Voice Coil 25mm Nett Weight 900gm Electromagnetic Q .48 Magnet 280 gm.

12" Woofer

100 Watt RMS 150W Max

C 3070 \$99.00

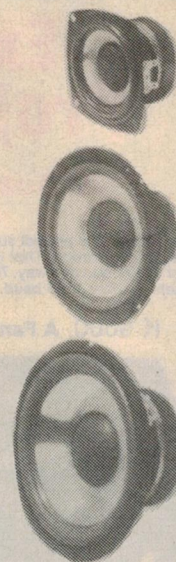Frequency Response fo—2000Hz Resonant Frequency 23Hz Sensitivity (1M/1Watt) 93db (+ or -2db) Voice Coil 38mm Nett Weight 3620 gm Electromagnet Q .22 Magnet 1410 gm.




High Energy Rack Case

The use of Super Heavy Duty Heatsinks as Rack Case sides now allows a myriad of Amplifiers, Power Supplies, Battery Chargers etc. to be built in an "Off the Shelf" rack case.

Fantastic for Stereo Amplifiers—Each Heatsink will accommodate an audio output stage of approximately 120W with normal efficiency and dissipation.

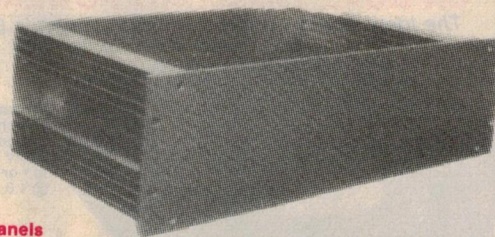A Great Chassis for Heavy Duty Power Supplies and Battery Chargers. We suggest the mounting of Rectifier Bridge or diodes on one Heatsink and the Regulator devices on the other.



Order With Either Black Or Natural Anodised Front Panels

H 0417 Natural Anodised Front Panel \$89.00 H 0415 Black Anodised Front Panel \$89.00

Specifications:

Heatsinks Altronics H 0590 **Front Panel** 3 unit Rack size 480mm x 132mm x 3mm **Base** 1.0mm steel, ventilation slots provided **Top Cover** 1.0mm steel, ventilation slots provided **Internal Dimensions** 125 x 370 x 250mm **External Dimensions** 130 x 440 x 252mm plus standard front panel **Finish** Black anodised aluminium plus powder coat black top/base.

Nifty Little Chassis Maker and Pan Brake Bender

Make Your own Chassis and Cases and Save a Fortune



Please Note: This product is a genuine Pan Brake Bender allowing you to make quite complex chassis boxes, lids, trays etc. - It is made from solid steel and is not to be confused with inferior Non Pan Brake simple benders currently sold by our competitors.


Value Plus

T 2400 \$99.95



Brilliant Solar Panel Array 18V @ 400mA

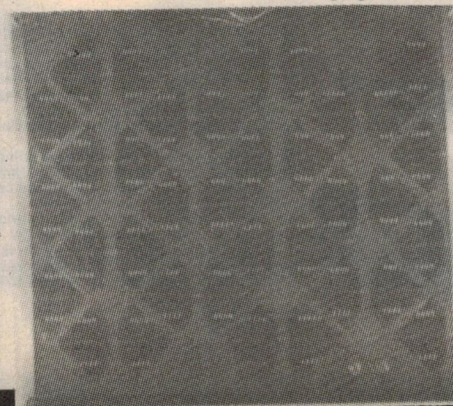Fantastic for Trickle Charging 12V Battery Systems



18V at up to 600mA under ideal sunlight conditions. Intended for charging 12 volt systems such as Car, Caravan and Boat batteries etc. Cat. A 0220


Was \$119
Now \$99

Excellent Kit Projects to Build

A 'Dual-Speed' Direct-Connect Computer Modem

Features: The project supports 300 Baud full duplex operation and 1200/75 Baud half duplex operation. That is, you can transmit and receive at 300 Baud in both directions or 1200 Baud one way, 75 Baud the other. A switch has been incorporated allowing you to select either 1200 baud.


K 9600 A Fantastic Performing Modem Only **\$169**

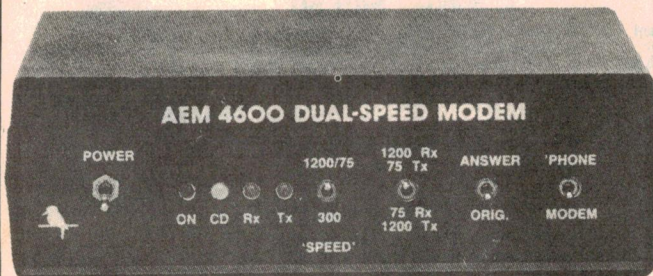

MUSICOLOUR IV

Ideal for Parties, Shop Signs, Display Windows, special lighting effects etc. Combination Colour Organ and Light Chaser. Four channel colour organ operation. Output lamp load capacity a massive 2400 watts.

K 5800 . . . **\$115.00**

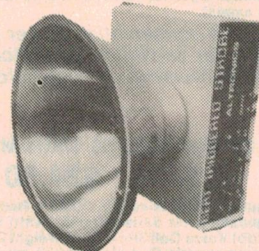

Beat Triggered Strobe

Add Some Life To Your Next Party

Designed by Australian Electronics Monthly. Flashes in time to your music. Will also work as normal strobe. Exclusively customised by Altronic into our H 0480 Instrument Case, making construction a breeze and improving stability and overall appearance. Includes silk screened panel.

K 5790 . . . **\$59.95**

Two Tube Option For Increased Power

K 5795 . . . **\$9.95**




Zener Tester

Used with your multi-meter - Reads exact zener voltage up to 60V. K 2620

\$12.50

EA DUAL TRACKING POWER SUPPLY

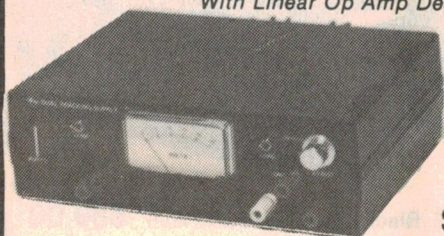The Ideal Power Supply For The Audiophile Experimenting With Linear Op Amp Designs




• Floating Ground • Meter Switchable V to A • Voltage adjustable to within 10mV • Output + or -1.3V to + or -22V at 2 Amps + 5V @ 1.0 Amps. K 3320

\$129.95

Super Low Price on Famous EA 8 Sector Alarm System Kit

(See EA Mag. Jan '85)

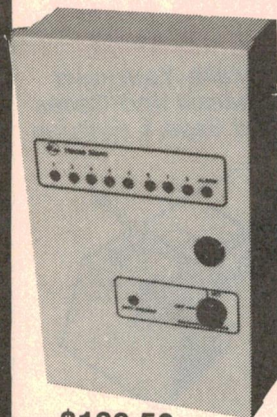


Features:

- Alarm has 8 separate input circuits - 8 sectors can be monitored independently.
- Each input circuit is provided with an indicator LED and a sector On/Off switch.
- Individual sector isolation allows the user to have some areas of the premises habited while others remain protected e.g. Inside Off/Outside On.
- Inputs accept both normally closed and normally open sensors.
- Two inputs provided with an entry delay between 10-75 seconds).
- Internal trip warning buzzer—alerts owner/occupant of pending alarm operation—great for the "forgetful" amongst us. This buzzer is pre-settable between 5 and 55 seconds prior to Alarm.
- Unique circuit detects automatically when any N/O or N/C loops are either open circuit or dead short. e.g. someone trying to bridge reed switches etc.
- Switched output can be used to send a silent alarm through an auto-dialler circuit or similar.

\$139.50

12/240V Inverter for Small Appliances

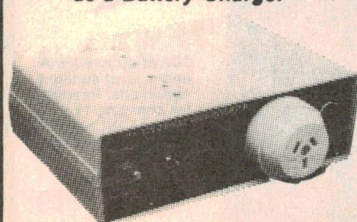Low Power Design also Works as a Battery Charger



The inverter is ideally suited to powering low wattage mains appliances from the car battery while camping. This considerably improves the comfort level of the civilised camper. Similarly, it has uses in boating. Typically, it can be used to power an electric shaver, electric blanket, electric can opener or a 40W light bulb. Alternatively, back in the home (or still on the camp site), Frequency sensitive items such as belt or idler driven turntables can be powered at a very precise crystal controlled frequency for accurate sound reproduction. If speed variation over a small range is required, then a switch is provided to change from the crystal basec 50Hz signal to a variable oscillator. K 6705

\$79.50

FANTASTIC HI TECH - HI SPEC

Audio Oscillator and Function Generator

This Ultra low distortion oscillator is comparable with the very best laboratory standard sine wave oscillators. As well as having very low distortion it has excellent envelope stability, square wave output and output metering

2 Models to choose from (metered and unmetered)

- Frequency range 10Hz - 100KHz in 4 ranges • Output level 3V RMS max adjustable
- Attenuator 0db, -10db, -20db, -30db, -40db, -50db plus fine adjustment • Output impedance — 600 ohms unbalanced • Output waveforms — sine and square.

All components mount on one single PCB making it a breeze to Construct Save \$200 and More by Building this Fine Kit Project



K 2540 Complete Kit with Front Panel Metering **\$155**

K 2545 Complete Kit Without Metering **\$139**

Stunning Design Makes Your Tape Machine Sound Like A CD Player

Dynamic Noise Reduction System

(See ETI Dec. '86)


Cut that annoying type hiss and dramatically increase dynamic range of your cassette recordings with this Dynamic Noise Reduction System It. This fantastic system improves signal to noise of your tape deck by up to an incredible 18dB without treble attenuation. It also expands dynamic range, allowing greatly improved recordings from compact disc players.

K 5575 . . . **\$99.00**



Bench Top Power Supply

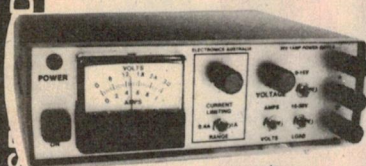3-30V to 1 amp Max. with variable current limit



\$79.00

FEATURES:


• Output 3 to 30V at 1A • Short circuit protected • Load switching • Current limiting. Dual scale meter • Housed in our Deluxe "ABS" instrument case.

SPECIFICATIONS:

• Output Voltage - 3 to 30V • Output Current - 0 to 1 amp (fully variable) • Load Regulation - Better than 0.2% from 0 to full load • Output Ripple - Less than 2mV RMS. Cat. K 3210

Transistor Tester

For In Circuit Testing

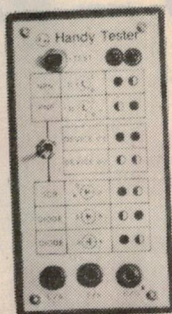

\$17.50

"NO NEED TO UNSOLDER SUSPECT TRANSISTORS"

FEATURES:


• Tests both NPN and PNP transistors in circuit at the touch of a switch • Tests Diodes and SCRS as well • No need to switch between NPN and PNP—its automatic. Two LED indicators are used to show condition of device being tested.

Altronics Kit Feature - "ABS" jiffy box and test leads supplied. Cat. K 3250


13.8V High Current Supply

Massive 10 Amps

\$119.95

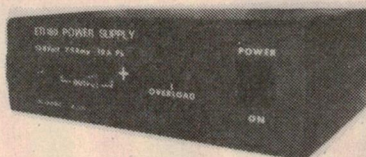

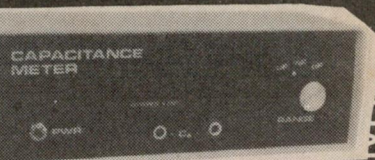• Output 13.8V DC 7.5A Continuous — 10A Intermittent • Regulation: — 0-7.5A -50mV — Now includes—Custom Designed Circuit Board as opposed to Vero Board in original article • Supplied in a quality instrument case. • Silk screened front panel—for that professional look • LED overload indicator. Cat. K 3250 (ETI July '83)



Low-Cost Unit Checks Values from 1pF to 100uF Upgraded Digital Capacitance Meter

Digital Capacitance Meter Checks capacitor value from 1pF to 99.99uF over three ranges. Features include a nulling circuit and bright 4-digit LED display. (Ea Aug. '85)

K 2522

\$79

ALTRONICS

174 ROE STREET, PERTH
FOR INSTANT SERVICE
PHONE ORDER
TOLL FREE

008 999 007

PERTH METRO
AND A/HRS

(09) 328 1599

ALL MAIL ORDERS

P.O. Box 8350, Perth Mail Exchange
Western Australia 6000

PACKING & DELIVERY CHARGE

\$3.00 DELIVERY AUSTRALIA WIDE

- We process your order the day received and despatch via. Australia Post. Allow approx. 7 days from day you post order to when you receive goods. Weight limited 1Kgs.

\$6.00 OVERNIGHT JETSERVICE - We process your order the day received and despatch via. **Overnight JetService Courier** for delivery next day Country areas please allow additional 24-48 hours. Weight limit 3Kgs.

\$6.00 HEAVY SERVICE - For deliveries exceeding 3kgs and less than 10kgs—allow 7 days for delivery
\$10.00 HEAVY HEAVY SERVICE - All orders of 10Kgs. or more must travel Express Road - Please allow 7 days for delivery.

INSURANCE - As with virtually every other Australian supplier, we send goods at consignee's risk. Should you require comprehensive insurance cover against loss or damage please add 1% to order value (minimum charge \$1). When phone ordering please request "Insurance".
TOLL FREE PHONE ORDER - Bankcard Holders can phone order toll free up to 6pm Eastern Standard Time. Remember with our **Overnight JetService** we deliver next day.

Altronics Resellers

Chances are there is an Altronics Reseller right near you - check this list or phone us for details of the nearest dealer.

Blue Ribbon Dealers are highlighted with a ■. These Dealers, generally carry a comprehensive range of Altronics products and kits or will order any required item for you.

Don't forget our Express Mail and Phone Order Service - for the cost of a local call, Bankcard, Visa or Mastercard holders can phone order for same day despatch.

Please Note: Resellers have to pay the cost of freight and insurance and therefore the prices charged by individual Dealers may vary slightly from this Catalogue - in many cases, however, Dealer prices will still represent a significant cost saving from prices charged by Altronics Competitors.

MORE ALTRONICS DEALERS WANTED

If you have a Retail Shop, you could increase your income significantly by becoming an Altronics Dealer. Phone Colin Fobister (09) 328 2199 for Details.

WA
COUNTRY
ALBANY
BP
Electronics ■ 412681
ESPERANCE
Esperance
Communications 713344
GERALDTON
K.B. Electronics
& Marine 212176
KALGOORLIE
Todays
Electronics ■ 212777
KARRATHA
Daves
Oscitronics 854836
MANDURAH
Lance Rock
Retravisson 351246
NEWMAN
Watronics 751734
WYALKATCHEM
D & J Pease 811132

NT
DARWIN
Ventronics 813491
ALICE SPRINGS
Ascom
Electronics 521713
Farmer
Electronics 522967

ACT
CITY
Bennett Commercial
Electronics 805359
Scientronics 548334

SA
CITY
Electronic
Comp & Equip. 2125999
Force
Electronic ■ 2122672
Protronics 2123111
SUBURBAN
BRIGHTON
Brighton
Electronics ■ 2963531
CHRISTIES BEACH
Force
Electronics ■ 3823366
ENFIELD
Force
Electronics ■ 3496340
PROSPECT
Jensen
Electronics ■ 2694744
COUNTRY
MT. GAMBIER
South East
Electronics 250034
PT. LINCOLN
West Coast
Elect Supplies ... 825802
WHYALLA
Eyre
Electronics ■ 454764
TASMANIA
HOBART
George Harvey ■ 342233
LAUNCESTON
Advanced
Electronics 315688
George Harvey ■ 316533
Nichols
Radio TV 316171
LEGANA
Frank Beech
Electronics 301379

VICTORIA
CITY
Active
Wholesale ■ ... 6023499
All Electronic
Components .. 6623506
Ellistronics ■ ... 6023499
MaGraths
Electronics 6631122
SUBURBAN
ASPENDALE
Giltronics 5809839
CHELTENHAM
Talking
Electronics 5502386
CROYDEN
Truscott
Electronics ■ ... 7233860
PRESTON
Preston
Electronics 4840191
COUNTRY
BENDIGO
KCJohnson ■ ... 411411
MORWELL
Morwell
Electronics 346133
SALE
Gippstech ■
Communications 447402
SHEPPARTON
GV Electronics ■ . 218866
SWAN HILL
Cornish Radio
Services 321427

NSW
CITY
David Reid
Electronics ■ ... 2671385
SUBURBAN
BLACKTOWN
Wavefront
Electronics 8311908
CARINGHAM
Hicom
Unitronics 5247878
LEWISHAM
PrePak
Electronics 5699770
SMITHFIELD
Chantronics ... 6097218
COUNTRY
ALBURY
Webb's
Electronics ■ ... 254066
COFFS HARBOUR
Coffs Harbour
Electronics 525684
GOSFORD
Tomorrows
Electronics ■ ... 247246
KURRI KURRI
Kurri Electronics . 372141
NEWCASTLE
D.G.E. Systems ... 691625
George Brown &
Company 696399
Novacastrian
Elect. Supplies ■ . 621358
NOWRA
Ewing
Electronics ■ ... 218412
EAST MAITLAND
East Maitland
Electronics 337327
ORANGE
Fyte
Electronics 626491

RAYMOND TERRACE
Alback
Electronics 873419
TENTERFIELD
Nathan Ross
Electronics 362204
TOUKLEY
TES Electronics . 964144
WINDSOR
M & E Electronics ■
Communications . 775935
WOLLONGONG
Newtek
Electronics ■ ... 271620
Madjenk
Electronics 743061
Vimcom
Electronics 284400
QUEENSLAND
CITY
Delsound P/L ... 8396155
SUBURBAN
CALOUNDRA
Hume's
Electro-Mart 914270
FORTITUDE VALLEY
F.H.S.
Electronics 8323700
Economic
Electronics 523762
PADDINGTON
Jacques
Electronics 3698594
SLACKS CREEK
David Hall
Electronics 2088808
TOOWONG
Techniparts ... 3710879

COUNTRY
CAIRNS
Thompson Instrument
Services 512404
CALOUNDRA
Electro Mart 914270
BUNDBERG
Bob Elkins
Electronics 721785
GLADSTONE
Supertronics 724321
MACKAY
Philtronics ■ ... 578855
NAMBOUR
Nambour
Electronics 411604
PALM BEACH
The Electronic
Centre 341248
ROCKHAMPTON
Electron
World 278988
Access Electronics
(East St.) 21058
Purely Electronics
(Shopping Fair) . 280100
Xanthos
Electronics 278952
TOOWOOMBA
Hunts
Electronics ■ ... 329677
TOWNSVILLE
Solex ■ 722015

Understanding colour TV — Part 7

The complete PAL colour TV receiver (1)

Now that we've looked at the basic concepts involved in PAL colour TV encoding, transmission, reception, decoding and display, we are in a position to analyse the operation of a typical PAL colour receiver in more detail.

by DAVID BOTTO

Before considering the complete circuitry contained in a PAL colour receiver, we'll first take a look at the basic schematic of a standard 625 line monochrome receiver. This will assist us as we discuss the additional circuitry needed by the PAL colour receiver.

In the block diagram shown in Fig.1 the basic arrangement of the monochrome TV is shown. The block diagram of Fig.2 shows the additional circuitry of a PAL colour receiver.

During the transmission of a television programme the energy radiated by

the TV station is in the form of an electromagnetic field. When this energy reaches the TV receiving antenna via the transmission path, an electrical signal is extracted. This signal is then fed down through the antenna cable to the TV receiver.

In the receiver the signal is taken to an RF tuner. The tuner is used to select the desired television programme broadcast from among the other received signals present at the TV antenna socket.

Fig.3 shows the total station channel bandwidth used in Australia, together

with the signal information arrangement.

The received signal is amplified by the signal frequency circuitry in the tuner. Since modern TV sets operate as superheterodyne receivers, the tuner contains a local oscillator which beats with the received amplified station frequency signal.

Two intermediate frequency signal IF are produced, one carrying the vision signal, the other the sound signal. For Australia the vision IF signal is 36MHz and the sound signal 30.5MHz. Notice that the two signals are separated by 5.5MHz. In Britain the vision IF frequency is 39.5MHz and the sound IF frequency 33.35MHz — a separation of 6MHz.

Both vision and sound IF signals pass through and are amplified in the vision IF stages.

The circuit of Fig.1 includes an automatic gain control (AGC) circuit. This is needed because when changing from one TV station to another the signal strength of the received programme


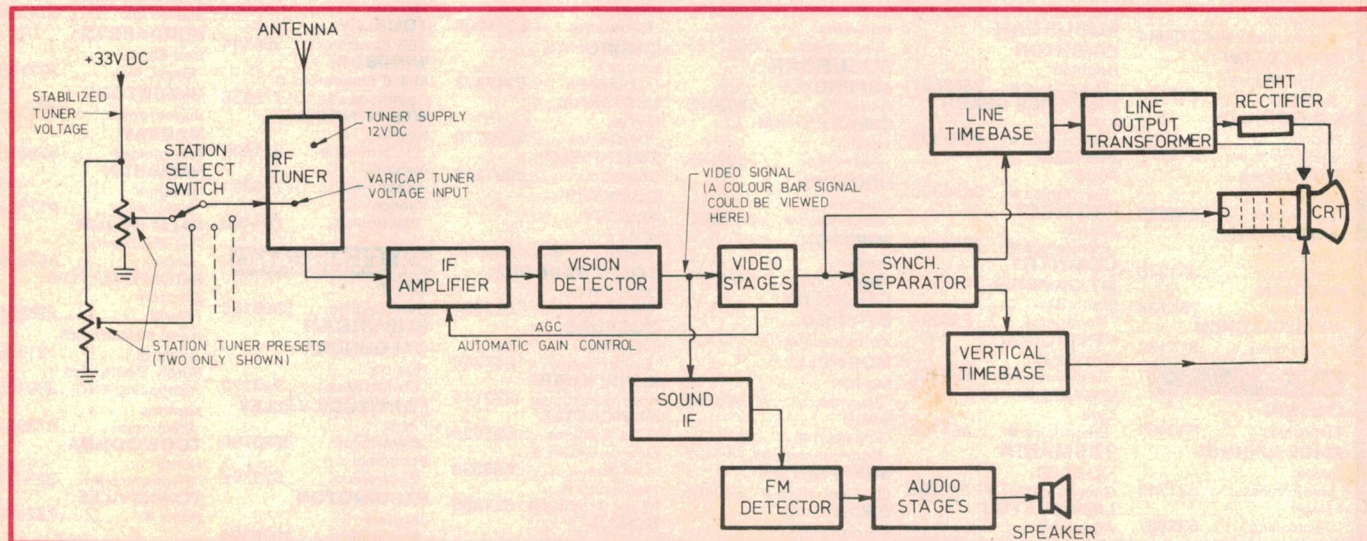


Fig.1: The block diagram of a modern monochrome TV receiver, in basic form. A colour set is virtually identical up to the output of the vision detector.

Fig.2: The additional circuitry involved in a PAL colour receiver. The main differences are in the colour decoding section.

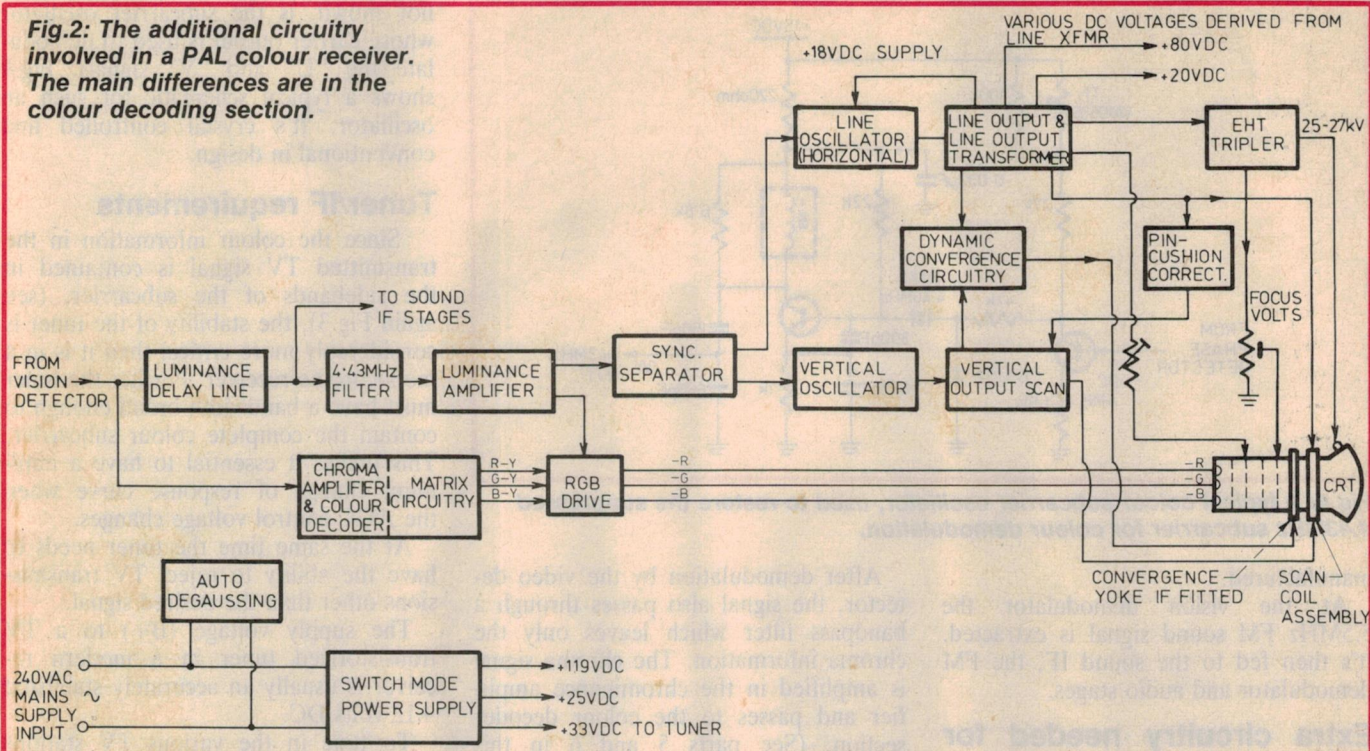

may vary. Also in weak signal areas fading may be experienced. The AGC affects the gain of all the signals passing through the vision IF amplifier, to provide a substantially constant video output level.

You will see from the block diagrams of Figs.1 and 2 that many sections of the circuitry of the monochrome and PAL colour receivers seem to be identical. However there are certain additional requirements essential for colour reception.

After IF amplification the signals are then demodulated by the vision detector. The vision signal obtained consists of the entire vision carrier modulation and is known as the video signal.

If you supply a colour bar input signal to a good quality monochrome receiver, and connect an oscilloscope to the output of the vision detector, it will display the complete colour bar signal exactly as would be viewed on the colour TV.

In the monochrome TV the demodulated video signals are directly amplified by the video stages and drive the single cathode of the monochrome picture tube.

The brightness of the picture at each point of the raster varies, as the received vision signal causes the tube beam current to increase and decrease. Provided the raster is correctly synchronized a picture will be viewed, in black and white.

Both the line timebase and the vertical timebase will run in the absence of

any signal, producing a raster on the picture tube. However it is necessary that both timebases be exactly synchronized with the horizontal and vertical scanning of the camera at the TV transmitter.

When correctly adjusted the free running speeds — with no signal input to the TV — of the receiver timebases are slightly lower than those of a synchronised picture. The sync pulses "trigger" both timebases, speeding them up so that both the scanning of the TV picture raster is exactly "in step" with the transmitted picture. These vertical scan and line scan synchronizing pulses are

extracted and separated at the output of the video amplifier.

In the PAL colour receiver similar synchronization circuitry is used to "lock" the picture raster to the transmitted signal.

The extra high tension voltage (EHT) required for the final anode of the picture tube is obtained by rectifying a portion of the energy developed by the line output transformer (Fig.1). The low-current EHT voltage produced may be between 8 to 15 kilovolts, according to the size of the picture tube. Generally at the present time only small portable monochrome TV sets are being


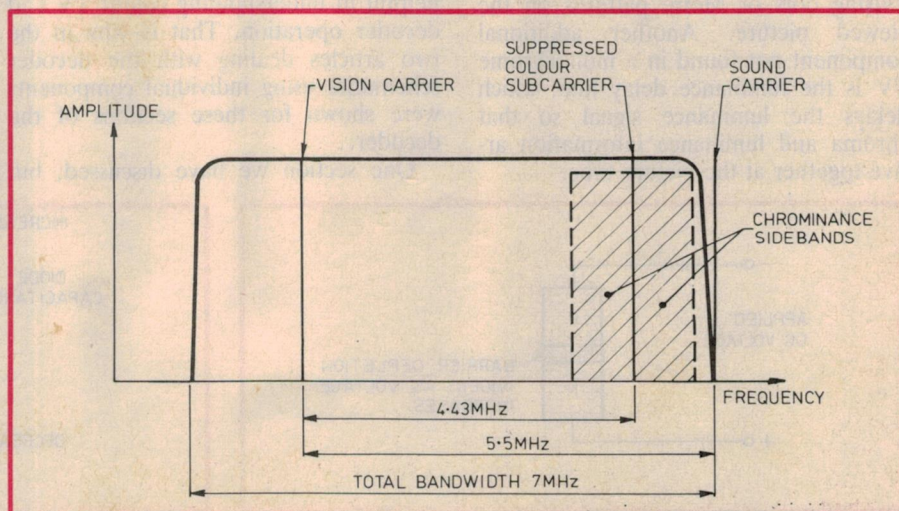


Fig.3: The total frequency bandwidth occupied by an Australian TV channel, showing the various signal components.

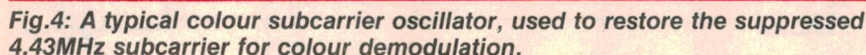

At the vision demodulator the 5.5MHz FM sound signal is extracted. It's then fed to the sound IF, the FM demodulator and audio stages.

In the block diagram of Fig.2 you'll notice some extra circuitry. The video output stage of the mono receiver is replaced by the luminance output stage of the PAL receiver. The luminance amplifier must drive the three cathodes of the colour picture tube, instead of the single cathode of a mono tube. For this reason the luminance stage has greater gain than does the monochrome TV video amplifier.

After demodulation by the video detector, the signal also passes through a bandpass filter which leaves only the chroma information. The chroma signal is amplified in the chrominance amplifier and passes to the colour decoder section. (See parts 5 and 6 in this series).

You'll recall that the decoder output consists of the (R-Y) and the (B-Y) signals and supplies these to the matrix circuitry where the (G-Y) signal is recovered. The luminance and colour difference signals are then combined in the RGB drive strages and drive the three cathodes of the colour picture tube.

In older PAL colour TV's the decoder consisted of discrete circuitry using valves or transistors.

In the latest colour receivers, practically the entire decoder is contained in a single very large scale integrated circuit (see part 6 of this series). However the study of the discrete circuitry is helpful in understanding colour TV and decoder operation. That is why in the two articles dealing with the decoder schematics using individual components were shown for these sections of the decoder.

not shown, is the subcarrier oscillator whose carrier output is used to demodulate the "U" and "V" signals. Fig.4 shows a typical schematic for such an oscillator. It's crystal controlled and conventional in design.

Since the colour information in the transmitted TV signal is contained in the sidebands of the subcarrier, (see again Fig.3), the stability of the tuner is considerably more critical than it is in a monochrome receiver. Further the tuner must have a bandwidth broad enough to contain the complete colour subcarrier. This makes it essential to have a minimum change of response curve when the AGC control voltage changes.

At the same time the tuner needs to have the ability to reject TV transmissions other than the desired signal.

The supply voltage (B+) to a TV transistorized tuner in a modern receiver is usually an accurately stabilized +12 volts DC.

To tune in the various TV stations the use of varicap diodes is now standard practice. *Electronics Australia* readers will know that varicap (or varactor) diodes are diodes that are biased in reverse at a voltage lower than their reverse breakdown voltage value. If any diode has a reverse voltage applied then its barrier depletion area widens as the voltage increases (Fig.5a).

The N and P junctions of the diode act as the plates of a small capacitor, with the barrier area as the dielectric. This means that as the applied voltage changes so does the capacitance of the diode. The varicap diode is designed to have a much larger internal capacitance than an ordinary diode. Fig.5b shows that as the voltage increases, the diode capacitance decreases.

Diagram illustrating the effect of an applied DC voltage on a PN junction. The P-region is connected to the negative terminal, and the N-region is connected to the positive terminal. The depletion region (labeled BARRIER DEPLETION) widens as the voltage increases.

RELATIONSHIP BETWEEN CAPACITY & VOLTAGE IN A VARICAP DIODE. ACTUAL CAPACITY DEPENDS ON DIODE DESIGN.

110 ELECTRONICS Australia, August 1987

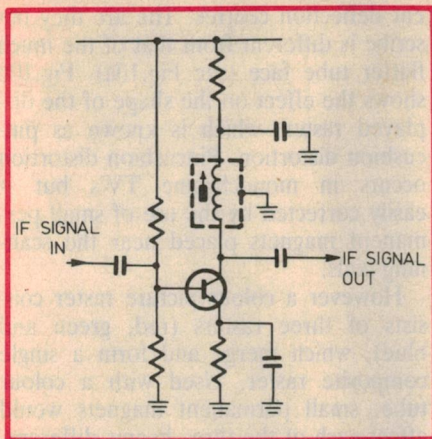


Fig. 6: A typical LC-tuned IF amplifier stage, as used in older receivers.

capacity of the tuner varicap diodes to change, and the tuned circuits to resonate at the desired frequencies. In this way the required TV station is "tuned in" — see Fig. 1. TV channel selection may be made by simple switch-type pushbuttons.

However it is now more usual to employ complex digital or infrared remote control methods. These different station selecting methods all operate in the same basic manner by changing the applied DC tuning voltage in order to select the desired programme. The result is an accurately stabilized TV tuner which does not drift away from the tuned channel frequency. Further when a different TV station broadcast is selected the tuner "locks in" to the signal at once.

Actually the tuning stability of modern colour TV receivers is made even better, by the use of automatic frequency control (AFC). This involves a voltage fed back to the RF tuner's local oscillator varicap from the FM sound detector, with such a polarity to automatically correct any drift.

The intermediate frequency amplifier (IF) section of a PAL colour receiver has basically the same requirements as that of a monochrome 625 line set.

However it is important that the chrominance signal remains undistorted, and is not attenuated by the IF amplifier. Older colour TV receivers used IF stages containing individual transistors (or valves) together with tuned IF transformers. Fig. 6 shows a section of such an IF amplifier. In the modern colour receiver some individual transistors together with integrated circuits may be found, but the trend towards the exclusive use of integrated circuitry is increasing.

Another device found in the IF circuitry of the modern PAL TV is the surface acoustic wave filter (SAWF). The SAWF may be shown in the receiver schematic either as in Fig. 7 (a) or (b). It is a piezoelectric device, about the size of a line output transistor such as a BU208.

Used in the PAL IF amplifier, the SAWF has the advantage of both better bandpass filter shape, stability of tuning and elimination of all the transformers when used with integrated circuits. Fig. 7(a) is basically a simplified schematic of a complete IF amplifier using a SAWF.

Power supplies

The mains power supply section of a modern PAL colour receiver is quite complex in design. In early PAL receivers using a valve design with perhaps just a few transistors, the stability of the power supply was not so critical. However modern PAL receivers contain transistor and integrated circuits that require accurately stabilized DC supply voltages to ensure correct and safe operating conditions. These DC voltages must remain constant even if the load current taken by the receiver varies, or when reasonable variations in the AC mains supply voltage occur. A further requirement is that in the event of any heavy overload, due to component breakdown in the TV, the power supply must switch itself off.

Practically all PAL TV receivers now

contain switch-mode power supplies. A switch-mode power supply is one where the regulator (sometimes called the "chopper") transistor is rapidly switched "on" and "off", usually in this case at about line timebase frequency (15.625kHz). The longer the "on" period lasts, the more current flows through the regulator transistor. If the "on" period shortens then less current flows.

If the current consumption of the set increases or decreases, the DC output voltage of the power supply will try to change. This is detected by the sensing circuitry, which alters the on/off ratio of the 15.625kHz pulse driving the base of the regulator transistor to compensate for this. Thus the DC output voltage is kept constant.

Fig. 8 shows a simplified block diagram of a switched mode power supply of the self-oscillating type. You'll find this basic circuit in many late model PAL receivers.

A Siemens TDA4600 integrated circuit drives the BU208 regulator transistor. This power supply can operate on a wide range of mains input AC voltages ranging from 90 to 270 volts. However the basic design shown in Fig. 8 is for an AC mains input of 240V. Tappings from transformer T1 supply various rectifier diodes and various DC voltages are produced across the electrolytic capacitors. Notice the 33 volts for the tuner varicap voltage supply. Should excessive current due to an overload be drawn from the secondary winding of transformer T1, the power supply shuts down.

Power supplies regulated by silicon controlled rectifiers (thyristors) were popular in the 1970's. Today you will encounter many different versions of switch mode supplies. Each type requires careful study in order to grasp its operating principles. In fact to properly describe all the different types of power supplies would take a series of articles on this subject alone!

Scanning circuitry

Scanning and synchronising the colour picture tube raster requires circuitry basically similar to that found in a monochrome TV. However there are again significant differences. Three electron beams must be deflected both vertically and horizontally in the colour picture tube. Also the EHT voltage is much higher on the colour CRT (24 to 27kV according to picture size). Thus increased power is necessary for the deflection circuitry.

In older receivers, discrete transistors or valves were used in the vertical oscil-

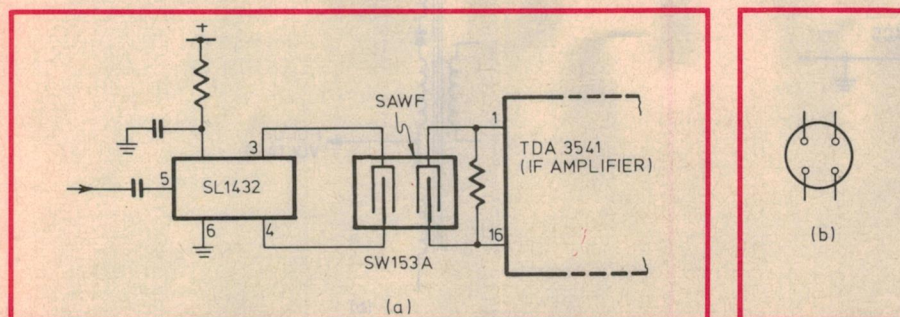


Fig. 7: In modern receivers, all IF bandpass shaping is performed by a SAW filter. An alternative symbol is shown in (b).

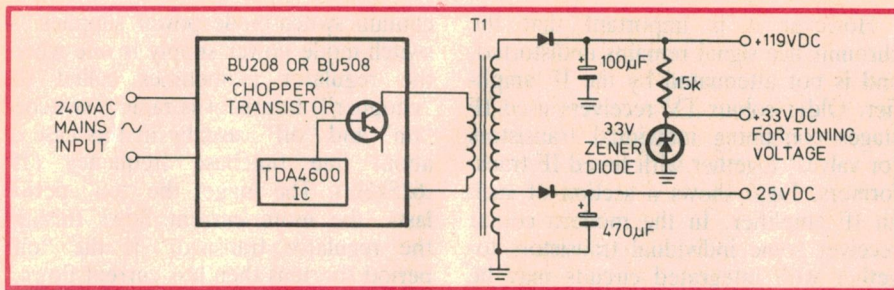


Fig.8: A simplified block diagram of the switch-mode power supply used in most modern receivers.

lator, horizontal oscillator and synchronizing stages (see again Fig.2). However nowadays a single integrated circuit, such as a type TDA 2578A contains the line oscillator and the vertical scan oscillator, together with all the necessary field and line synchronization circuitry.

In a colour TV the line output transformer (which is driven by the line output stage) fulfils several functions. Besides energising the horizontal scan coils, it also produces anything from 400 to 800 volts DC for the A1(s) grids of the picture tube.

In addition, from various windings on the line output transformer are derived AC voltages which are then rectified to produce DC voltages that supply various circuitry in the TV. Further the transformer has an EHT winding producing just over 8kV.

Since approximately 25kV is required for the final anode of the colour picture tube, the 8kV is supplied to a tripler (Fig.9a). When a line of picture is scanned at the end of the line, a positive going flyback pulse occurs as the beams return to the beginning of the scan. The capacitor C1 is then charged through diode D1 by a pulse from the EHT winding. As the input falls the charge on C1 passes via diode D2 to capacitor C2.

When the next positive going flyback

pulse arrives, C1 is again charged through diode D1. Capacitor C2 now receives an additional charge from diode D2. The original 8kV on capacitor C2 now has a further 8kV added to it, so that the charge across C2 is now 16kV and capacitor C3 charges via D3, as the flyback pulse again dies away during the next line of picture, diode D4 transfers the charge on capacitor C3 to capacitor C4. There is now 8kV at point A, and 16kV at point B.

At the junction of diodes D1 and D2 the tube focus voltage is derived and taken via the focus circuitry to the focus electrode of the colour picture tube.

When the third flyback pulse arrives, the whole process is repeated, increasing all the potentials by a further 8kV. Capacitor C5 now charges up via diode D5 to a potential of 24kV, which is taken through a safety resistor R3 to the picture tube's final anode.

The diode split line output transformer is rapidly replacing the separate tripler block. The rectifying diodes are contained within the transformer itself with the transformer windings providing the necessary capacitance (Fig.9b).

Pincushion correction

As explained in part 4 of this series, the three electron beams of the colour picture tube are deflected at the appar-

ent deflection centres. The arc they describe is different from that of the much flatter tube face (see Fig.10a). Fig.10b shows the effect on the shape of the displayed raster, which is known as pincushion distortion. Pincushion distortion occurs in monochrome TV's but is easily corrected by the use of small permanent magnets placed near the scanning coils.

However a colour picture raster consists of three rasters (red, green and blue), which merge and form a single composite raster. Used with a colour tube, small permanent magnets would affect each of the three beams differently, ruining the convergence and purity.

The solution is to use a transductor, which was developed by Mullard Ltd particularly for use with the shadow-mask picture tube (Fig.11). The pincushion correction takes place at the apparent deflection centres of the colour tube, by allowing the horizontal and vertical scanning signals to interact in a ferrite core.

The current flowing through the line deflection coils is modulated by a parabolic waveform at vertical scanning frequency. By means of this correction waveform, the sides of the composite raster are straightened. The transductor provides maximum correction at the centre of the raster, with gradually less correction falling to zero at the top and bottom of the picture.

The current flowing through the vertical deflection coils is corrected by a parabolic waveform at line frequency. At the beginning of each line of the raster this correction is zero; gradually increasing to maximum at the centre of each line and then slowly falling to zero again by the end of the line.

In later developments of colour tubes, other types of pincushion correction have been used. By careful design of

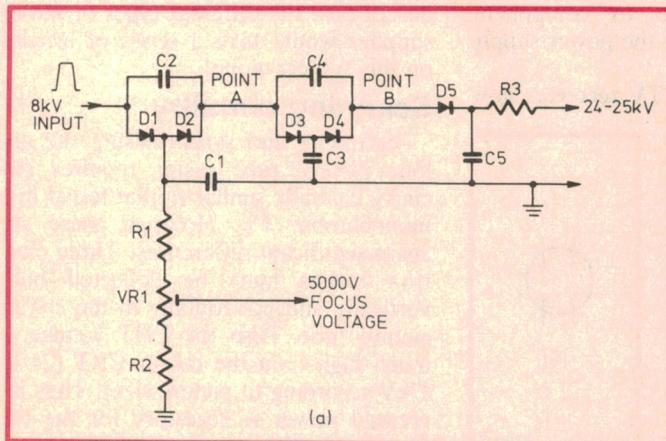


Fig.9(a): The basic voltage tripler frequently used to derive the 24-25kV EHT supply for the CRT.

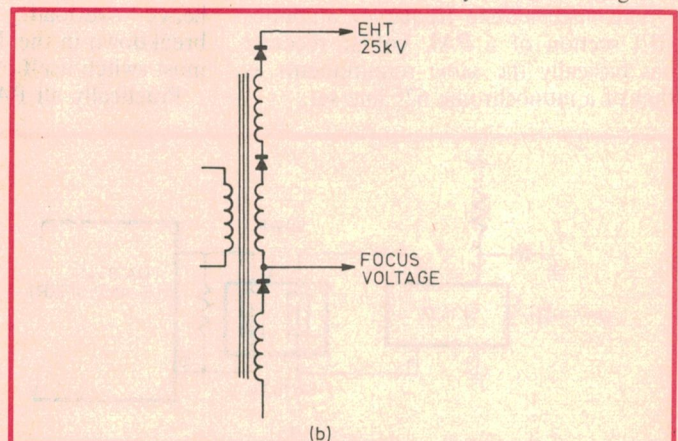


Fig.9(b): More recent designs use a split EHT winding with distributed rectifier diodes.

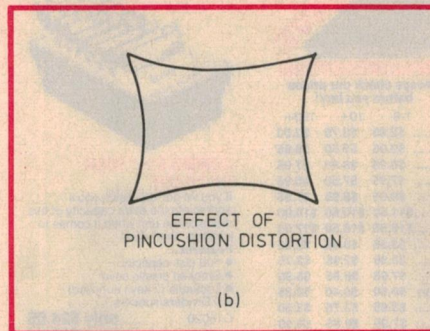
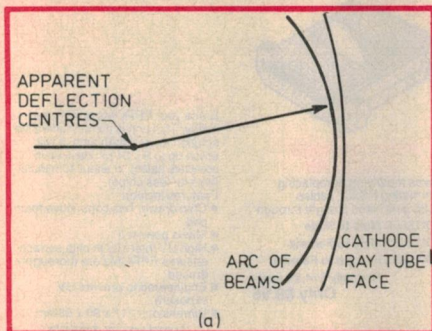


Fig.10: Because the electron beams are deflected with a radius much shorter than that of the CRT screen (a), this tends to produce a picture with "pincushion distortion" (b).

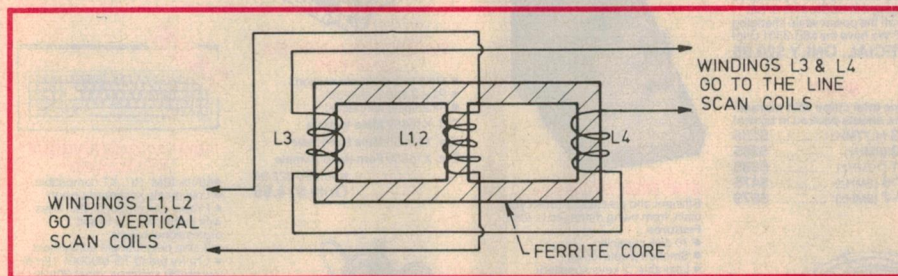


Fig.11: A transducer allows the line and field scanning circuits to interact, adding parabolic correction currents to each.

the scan coil assembly, and by using special methods of winding the coils, pincushion distortion has been largely overcome.

However, particularly with larger picture tubes, some method of pincushion correction is still necessary.

Convergence

Convergence circuitry is provided so that the three rasters properly merge to form one composite colour raster over the entire surface of the picture tube face. In part 4 of this series, the basic method of converging the three red, blue and green rasters at the centre of the screen was described. This is known as static convergence. However to obtain proper convergence at the edges and corners of the picture, *dynamic* convergence is necessary.

With the earlier shadow-mask type of picture tube coils were wound around the static convergence magnets contained in the convergence assembly. Controlled adjustable currents passed through these coils. Both line and vertical scan frequency parabolic currents were used.

The earlier colour TV receivers fitted with shadow-mask picture tubes thus contained a large number of preset convergence adjustments. A total of twenty or more (including both static and dynamic controls) were common. Each adjustment usually had to be repeated several times because of interaction in the

circuitry.

A few of these receivers are still in use. Should you encounter one, remem-

ber that it is essential to first carefully study the TV manufacturer's service instructions before attempting any convergence adjustments. They're quite complex.


A warning

If you make any adjustment or measurement on or near a colour picture tube, remember that the 24-27kV EHT voltage can be lethal. Even when the colour TV is switched off and disconnected from the supply mains, it is possible for the picture tube to hold a considerable charge of high voltage due to the tube's internal capacitance.

Fortunately you'll find that colour receivers fitted with the very latest "in line" colour tubes are practically self converging and need only minor adjustments. If the tube is a Philips 30AX none at all will be required!

In the final part of this series we'll discuss some additional sections of the circuitry found in a PAL receiver. We'll also examine the schematic of a complete line oscillator and line output stage that uses the latest technology. Finally we'll consider the interesting effects produced when faults in the chroma sections affect the colour picture. EA

SIMPLIFY YOUR POWER SUPPLY DESIGN

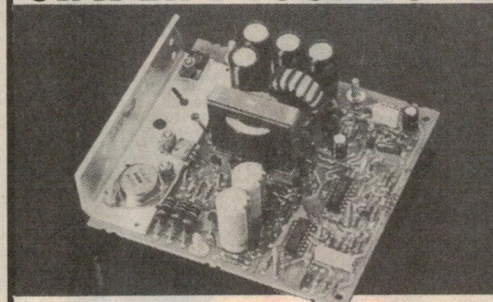

Boschert

THREE TERMINAL REGULATORS

These wide-range input three-terminal regulators are flexible, inexpensive, efficient design modules providing a single adjustable output from any raw positive DC Source. These 3T modules are complete functional blocks whose input and output flexibility easily and quickly solves unique power system requirements.

Standard features

- 25 kHz switching frequency • 75% typical efficiency • Overload and short circuit protection • Adjustable output voltage • No external components needed • Remote sensing • Parallelability • Remote On/Off

Selection guide

Model	Input voltage range (DC)	Output voltage adjustment range	Max. current
3T12AP6130	+10 to +60V	+4.5 to +30V	12A
3T20AP6115	+10 to +60V	+4.5 to +15V	20A
3T 5AN4030	+10 to +40V	-4.5 to -30V	5A
3T 5AN6030	+20 to +60V	-4.5 to -30V	5A


AVAILABLE EX STOCK

AMTEX
ELECTRONICS

36 LISBON STREET, FAIRFIELD, NSW 2165, AUSTRALIA
TELEPHONE: (02) 728 2121, 727 5444
TELEX: AA27922 ATN AMTEX
FACSIMILE: (02) 728 6908, 728 2837

A DIVISION OF METAL MANUFACTURES LIMITED
(Incorporated in Victoria)

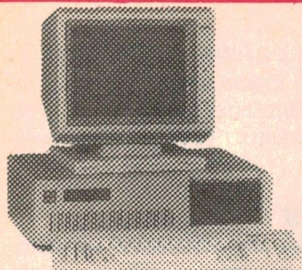MELBOURNE:
SUITE 1, 32-34 RUTLAND ROAD, BOX HILL VIC 3128
TELEPHONE: (03) 890 6999
FACSIMILE: (03) 898 6427



IBM* XT COMPATIBLE COMPUTERS from \$795*

Check these features and our prices. We're sure you'll agree they're exceptional value for money!

- Assembled in Australia!
- Tested by us for 24 hours prior to delivery!
- 150W power supply
- AT style keyboard
- Operating manual
- 8 Slot motherboard
- 6 Months warranty!

*\$795 COMPATIBLE COMPUTER

256K RAM Single Drive, Graphics and Disk Controller Card. \$795

256K RAM COMPATIBLE COMPUTER
2 x 360K Disk Drives, Multifunction Card, Colour Graphics, Disk Controller, 1 Parallel Port. (Includes Timer Disk) \$1,095

640K RAM COMPATIBLE COMPUTER
2 x 360K Disk Drives, Multifunction Card, Colour Graphics, Disk Controller, 2 Serial, 1 Parallel Port. (Includes Timer Disk). \$1,150

20 M/BYTE HARD DISK COMPATIBLE COMPUTER

20 M/Byte Hard Disk, 360K Disk Drive(s), 640K RAM, Multifunction Card, Colour Graphics, Disk Controller, 2 Serial, 1 Parallel Port. (Includes Timer Disk)
Single 360K Floppy Disk Drive only \$1,850
Dual 360K Floppy Disk Drives only \$1,995

IBM* AT COMPATIBLE

Assembled & Tested in Australia!

- 1 M/Byte Main Board
- 1.2 M/Byte Floppy Disk Drive
- Colour Graphics Display Card
- Floppy & Hard Disk Controller
- Printer Card and RS232
- 200W Power Supply
- 6 Months Warranty
- 6 MHz
- 80286 CPU
- 8 Slots
- 20 M/Byte Hard Disk
- Keyboard
- Manual

..... only \$2,975



SEMICONDUCTORS!

Always check our prices before you buy!

	1-9	10+	100+
2114	\$2.95	\$2.75	\$2.50
2716	\$9.95	\$9.50	\$8.95
2732	\$8.95	\$8.50	\$7.95
2764	\$7.95	\$7.50	\$6.95
27128	\$9.95	\$8.95	\$7.95
27256	\$11.50	\$10.50	\$10.00
27512	\$19.50	\$18.50	\$17.50
4116	\$3.95	\$3.50	\$2.95
4164	\$3.95	\$2.95	\$2.75
41256	\$7.95	\$6.95	\$5.95
5558pin	\$0.50	\$0.40	\$0.35
6116	\$3.95	\$3.75	\$3.50
6264	\$7.95	\$6.95	\$6.50
6802	\$5.00	\$4.00	\$3.75
6821	\$2.00	\$1.80	\$1.70
6845	\$5.00	\$4.00	\$3.75
7406	\$0.40	\$0.30	\$0.25
INS8250	\$29.95	\$27.95	

MEL9501


Have you blown up your Apple drive by plugging it in backwards or not turning off the power while changing boards? We have the MEL9501 chip!

SPECIAL, ONLY \$29.95

8087

Genuine Intel chips with manual and data sheets packed in boxes!


8087-3 (4.77MHz)	\$269
8087-2 (8MHz)	\$385
8087-1 (10MHz)	\$585
80287-6 (8MHz)	\$475
80287-7 (8MHz)	\$679

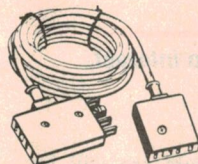

TELECOMMUNICATIONS AUSTRALIAN STYLE ADAPTOR CABLE

- Australian socket to plug/socket
- Length 10 metres

Cat. Y16015 \$14.95

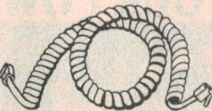

TELEPHONE CURL CORD

- U.S. plug to U.S. plug
- Replacement hand set cord
- Length 4.5 metres

Cat. Y16023 \$6.95



MAIL ORDER HOTLINE
008 335757
(TOLL FREE)
LOCAL: 543 7877



TELEPHONE ADAPTOR

- Australian plug to U.S. socket
- Length 10cm

Cat. Y16026 \$5.95




TELEPHONE EXTENSION CABLE UNIT

Allows 15 metres of telephone extension cable to be neatly wound into a portable storage container. The reel sits on a flat base and has a handle to wind cable back on to it after use. No tangles - no mess!

Ideal for the workshop, around the house, office, pool etc.

Cat. Y16013 \$22.95

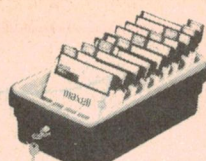

JUMBO 5 1/4" DISK STORAGE

If you've got lots of disks, you'll appreciate the extra capacity of this disk storage unit when it comes to locating "that" disk!

Features...

- 100 disk capacity
- Smoked plastic cover
- Lockable (2 keys supplied)
- 9 Dividers/spacers

C16020 only \$24.95

C16027 (Hinged Lid) \$26.95



5 1/4" DISK STORAGE

Efficient and practical. Protect your disks from being damaged or lost!

Features...

- 70 disk capacity
- Smoked plastic cover
- Lockable (2 keys supplied)
- Dividers/spacers

Cat. C16025 only \$19.95




5 1/4" DISK STORAGE

Efficient and practical. Protect your disks from being damaged or lost!

Features...

- 50 disk capacity
- Smoked plastic cover
- Lockable (2 keys supplied)
- Dividers/spacers


Cat. C16030 only \$19.95

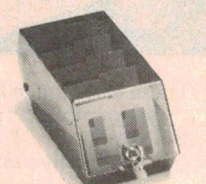

3 1/2" DISK STORAGE UNIT

- Holds up to 40 x 3 1/2" diskettes
- Lockable (2 keys supplied)
- High impact plastic lid and base
- Anti-static

Cat. C16040 only \$19.95

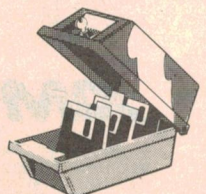

3 1/2" DISK STORAGE UNIT

- Holds up to 40 x 3 1/2" diskettes
- Lockable (2 keys supplied)
- High impact plastic lid and base

Cat. C16035 only \$19.95



RS232 GENDER CHANGERS

- Saves modifying or replacing non-mating RS232 cables.
- All 25 pins wired straight through

Cat. X15650 Male to Male

Cat. X15651 Male to Female

Cat. X15652 Female to Female

Normally \$14.95 each

Only \$9.95



RS232C NULL MODEM ADAPTOR


- Male to female connections
- Pins 2 and 3 reversed
- All 25 pins connected

Cat. X15658 Male to Male

Cat. X15659 Female to Female

Normally \$22.95

Only \$14.95

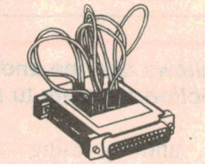

RS232 WIRING ADAPTOR BOX

- Male to female
- 25 Detachable plug on leads
- 2 mini jumpers
- Ideal for experimenting or temporary connections

Cat. X15665 Normally \$39.95

Only \$29.95



RS232 MINI JUMPER PATCH BOXES

- Interface RS232 devices
- 25 pin inputs
- 25 leads with tinned end supplied
- Complete with instructions

Cat. X15653 Male to Male

Cat. X15654 Female to Male

Cat. X15655 Female to Female

Normally \$25.95

Only \$19.95




RS232 MINI TESTER

- Male to female connections
- All pin wired straight through
- Dual colour LED indicates activity and direction on 7 lines
- No batteries or power required
- T.D. Transmit Data
- D.S.R. Data Set Ready
- R.D. Receive Data
- C.D. Carrier Detect
- R.T.S. Request to Send
- D.T.R. Data Terminal Ready
- C.T.S. Clear to Send

Cat. X15656 Normally \$39.95

Only \$29.95

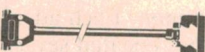

PRINTER LEAD FOR IBM*

- Suits IBM* PC XT and compatibles
- 25 pin "D" plug (computer end)
- Centronics 36 pin plug

Cat. P19029 1.8 metres \$19.95

Cat. P19030 3 metres \$29.95

UV EPROM ERASER

Erase your EPROMs quickly and safely. This unit is the cost effective solution to your problems. It will erase up to 9 x 24 pin devices in complete safety, in about 40 minutes (less for less chips).

Features include:

- Chip drawer has conductive foam pad
- Mains powered
- High UV intensity at chip surface ensures EPROMs are thoroughly erased
- Engineered to prevent UV exposure
- Dimensions 217 x 80 x 68mm

WITHOUT TIMER

Cat. X14950 Normally \$119

Special, \$89

WITH BUILT-IN TIMER

Cat. X14955 \$139

Special, \$119



"IBM" AT COMPATIBLE KEYBOARD

- 100% IBM* PC, XT compatible
- Low profile keyboard design
- Proper placement of shift keys with large key tops to suit professional typists
- 3 step height/angle adjustment
- Cherry brand TS-M00001 19mm low profile switches, meet 30mm ergonomic requirement and provides high performance and maximum reliability
- Curl lead plugs straight into PC/XT
- 3 Status displays

Just like the "Real McCoy" only at a fraction of the price!

Cat. X12020 only \$129




IBM* XT & AT COMPATIBLE EXTENDED KEYBOARD (105 KEYS)

These new keyboards are both XT and AT compatible!

- 20 Dedicated function keys
- Enlarged "Return" and "Shift" key
- Positive feel keys
- Low Profile Design, DIN standard
- Separate Numeric and Cursor control keypads
- Additional Functions:
- Key-in-lock, Audio Beep, Previous Word, Next Word, Fast Repeat, Line Feed, Pause, Clear Screen, Reset

Cat. X2022 WAS \$299

SPECIAL, ONLY \$199

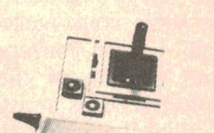

APPLE* II SERIES COMPATIBLE JOYSTICK

These joysticks have adaptor connectors to suit the Apple II, IIc, IIe and IIx computers. Features include selectable "spring centring" or "free floating". Electrical trim adjustments on both axis, 360° cursor control and dual fire buttons


Cat. C14201 only \$39.95



JOYSTICK FOR IBM

Features Selectable "Spring centring" or "free floating". Electrical trim adjustments on both axis. 360 degree cursor control

Cat. C14205 \$39.95

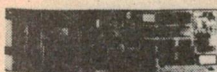

IBM® XT COMPATIBLE CARDS

NEW! NEW! NEW! NEW!

20M/BYTE HARD DISK CARD
XT compatible, simply plugs straight
in to your computer!
Cat. X18002 \$1.95

Colour Graphics Card
(Hercules compatible)
Cat. X18003 \$145

Floppy Disk Drive Controller Card
(2 Drives, 16 Bit)
Cat. X18005 \$59

Floppy Disk Drive Controller Card
(4 Drives, 16 Bit)
Cat. X18006 \$85

High Resolution Mono Card
Cat. X18007 \$199

Colour Graphics & Printer Card
Cat. X18010 \$149

768kB RAM Card (without memory)
Cat. X18012 \$89

Printer Card
Cat. X18017 \$34.95

Game I/O Card
Cat. X18019 \$37.95

XT Motherboard (without memory)
Cat. X18020 \$225

Clock Card
Cat. X18024 \$57.50

RS232 Card (without cable)
Cat. X18026 \$52.50

RS232 & Clock Card
Cat. X18028 \$95

XT Turbo Motherboard
(without memory)
Cat. X18030 \$275

Multi I/O & Disk Controller Card
Cat. X18040 \$169

I/O Plus Card
Cat. X18045 \$129

768K Multifunction I/O Card
(includes cable but not 41256 RAM)
Cat. X18050 \$199


Hard Disk Controller Card
Cat. X18060 \$195

Enhanced Graphics Adaptor Card
256K RAM on board
Cat. X18070 \$295

64K Printer Buffer Card
Cat. X18077 \$139

(AT COMPATIBLE)

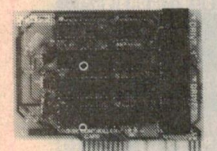Enhanced Graphics Adaptor Card
(Award Bios)
Cat. X \$495



APPLE® COMPATIBLE CARDS

PRINTER CARD
Cat. X17029 \$89

DRIVE CARD
Cat. X17019 \$79

80 COLUMN CARD
Cat. X17025 \$85

SUPER SERIAL CARD
Cat. X17035 \$119

RGB CARD
Cat. X17039 \$79

PAL COLOUR CARD
Cat. X17027 \$95

Z80 C/M CARD
Cat. X17041 \$59

APPLE® IIe COMPATIBLE CARDS


80 COLUMN/64K CARD
Cat. X \$69

64K/128K CARD
Cat. X \$69



ANTI GLARE SCREEN

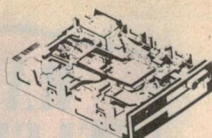Half the price of other brands!!
Relieve eye strain and headaches
and increase productivity with these
Anti Glare Screens. Suitable for 12"
monochrome and colour monitors.
Cat. X99995 \$24.95




NEC DISK DRIVES

3 1/2" DISK DRIVE
● 1 M/Byte unformatted,
(640K formatted).
● Double sided, double density.
● Access Time 3m/sec
Cat. C11906 \$265

5 1/4" SLIMLINE
● Switchable 1.6 M/Byte to 1 M/Byte
unformatted
1.2 M/Byte to 720K formatted
● Double sided, double density.
● AT compatible
Cat. C11906 \$295

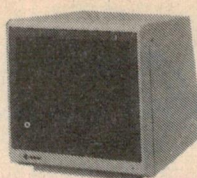8" SLIMLINE
● Double sided, double density.
● 1.6 M/Byte unformatted.
Cat. C11908 \$795



SAMSUNG TTL MONITOR

A quality 12" TTL monitor, with a
high contrast, non-glare screen at
a very reasonable price!


SPECIFICATIONS:
CRT: 12" diagonal 90° deflection,
non-glare screen.
Active Display Area:
216(H) x 160(V)mm
Display Characters: 2,000
(80 characters x 25 lines)
Scanning Frequency:
Horizontal: 18.432 ± 0.1KHz
Vertical: 50 Hz ± 0.5%
Description Cat.No. 1-9 10+
Green X14517 \$189 \$179
Amber X14518 \$189 \$179



SAKATA 13" RGB COLOUR MONITOR

High quality IBM® compatible
monitors, great with VCR's too!

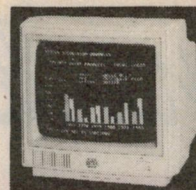SPECIFICATIONS:
CRT: 13" 90° deflection colour
Input Signal:
Video Signal: Separate video signal
Video: Positive
Sync: Positive
Input Level: TTL Level
Scanning Frequency:
Horizontal: 15.7KHz
Vertical: 60Hz
Display Size: 245(H) x 182(V)mm
Resolution:
Horizontal: 640 dots
Vertical: 200 lines
Cat. X14530 \$695




INTRA 14" RGB HIGH RESOLUTION COLOUR MONITOR

Compatible with IBM® and
compatibles, and EGA Cards.
Why pay more?

Resolution: 640 x 350 dots
Dot pitch: 31mm
Display Format: 80 x 25 characters
Cat. X14514 Normally \$1,295
Special, only \$795

INTRA 14" RGB COLOUR MONITOR

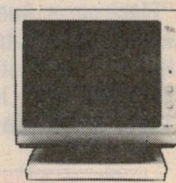Resolution: 640 x 200 dots
Display Format: 80 x 25 characters
Display Colours: 16
Dot pitch: 39mm
Sync Horiz. Scan Freq: 15.75 KHz
Sync Vert. Scan Freq: 50Hz
Band Width: 18MHz
Cat. X14520 \$695



RITRON 2 MONITORS

Stylish 20MHz, non-glare 12 inch
monitors available in green or amber
displays and featuring swivel base
that tilts forward and back and
swivels right to left!

Green Cat. X14506. Normally \$235
Amber Cat. X14508. Normally \$239
SPECIAL, ONLY \$199

SAVE!!




1 YEAR WARRANTY!

IBM® COMPATIBLE DISK DRIVES


Tired of paying out more for
Japanese Disk Drives? These
"direct import" Hong Kong disk drives
are the solution! They feature
Japanese mechanical components,
yet cost only a fraction of the price!

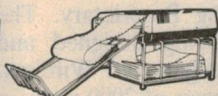Cat.No. Description Price
C11801 500K Normally \$199
SPECIAL, ONLY \$179
C11805 1.6 M/Byte \$259




PAPER TAMER

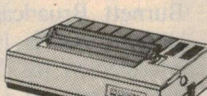● Restores order to the top of your
desk or work area
● Made of white plastic coated steel
● Stores up to 900 continuous sheets
● Allows perfect paper feed
● Allows easy examination of print out
C21050 (10") only \$49.95
C21050 (15") only \$79.95
(Printer and paper not included)




CANON A-40 PRINTER

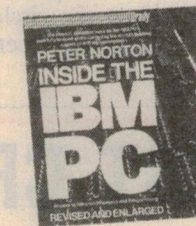● Serial Impact Dot Matrix
● 140 C.P.S.
● Near Letter Quality Mode
● 1.4K Buffer
Cat. C20040 \$595




INSIDE THE IBM PC

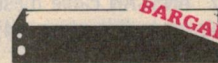(Revised and expanded edition)
-Peter Norton
The widely acclaimed guide to the
IBM PC's inner workings. The latest
edition now covers every model of
the IBM micro: PC, XT and AT, and
every version of DOS from 1.1 to 3.0
B20080 \$44.95



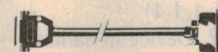PRINTER RIBBONS
CP80, BX80, DP80, BX100, MB100
ALL A CRAZY LOW \$9.95



PRINTER LEAD FOR IBM®

● Suits IBM® PC XT and compatibles
● 25 pin "D" plug (computer end)
to Centronics 36 pin plug
Cat. P19029 1.8 metres \$17.95
Cat. P19030 3 metres \$22.95



SUPER 5 EP-1201 DOT MATRIX PRINTER


● 120 C.P.S.
● Pica or Elite character set
● Print Modes: NLQ, Dot Graphics,
Proportional Font, Draft.
● Proportional Printing
● Reliable and Compact
● Proportional Printing
● Logic Seeking
● 1K Printer Buffer
Cat. C20035 only \$595



IBM PC TROUBLESHOOTING & REPAIR GUIDE

-Robert C. Brenner
Keep your IBM PC in top operating
condition with this handy reference
book. Inside you will find pages of
schematics, photos and block
diagrams to help you identify
problems. Simple instructions tell
you what's wrong and how to fix it
fast.

● Make most repairs with few or no
tools
● Quickly zero-in on a malfunctioning
component
● Reduces downtime
● Pays for itself many times over in
repair savings
● Easy to understand circuit
diagrams
The IBM PC Trouble Shooting &
Repair Guide will make even the
computer novice feel comfortable
with the complex world of electronic
trouble shooting. This fully illustrated
book is recommended for anyone
who uses an IBM PC.
Cat. B \$44.95

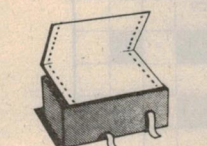


COMPUTER PAPER

Quality paper at a low price! 2,000
sheets of 60 gsm bond paper
Cat. C21003 11 x 9 1/2" \$39.95
Cat. C21005 15 x 11" \$67.95



20 M/BYTE HARD DISK DRIVE FOR IBM® AND COMPATIBLES

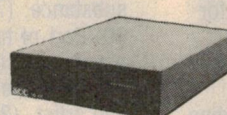NEC drive with DTC controller card.
Cat. X20010 WAS \$995
SPECIAL, ONLY \$850
*IBM is a registered trade mark.



APPLE® COMPATIBLE SLIMLINE DISK DRIVE

Japanese Chiron mechanism,
compatible with Apple 2+
Cat. X19901 Normally \$225
SPECIAL \$199
(*Apple is a registered trade mark.)

DB25 CONNECTOR SPECIALS!

We have just imported 50,000.
So you get to save a small fortune!

DB25 MALE (P10900)
1-9 \$1.50
10+ \$1.20
100+ \$1.00

DB25 FEMALE (P10901)
1-9 \$1.70
10+ \$1.40
100+ \$1.20

PASCAL PRIMER

-Mitchell Waite, David Fox
If you are learning programming or
have dabbled in the popular
language BASIC and wish to learn
the capabilities of Pascal, this book
is definitely written for you. Written
and illustrated with a touch of
humour, the informative text
describes Pascal program structure,
Pascal variables, Pascal procedures,
and many other features. There are
chapters on decision making
statements, numeric functions,
string functions, arrays and sets, and
much more. The eight appendices
present facts about the advantages
and disadvantages of Pascal,
components of a Pascal system,
interfacing assembly language
routines, and other useful
information.
Cat. B \$24.95



SENDATA DIRECT CONNECT MODEM

● CCITT V21 300 baud full duplex
● CCITT V23 1200/75
● Bell 103 300 Full duplex
● Bell 202 1200 Half duplex
● Auto answer, auto disconnect
● LED display for Power, TX, RX, CD
● AC power adaptor included
● DB25 pin connector
● Telecom Approval N° C83/37/1045
Cat. X19120 \$295
(SOFTWARE FOR VTEL \$95)

rie

Rod Irving Electronics

48 A Beckett St, MELBOURNE
Phone: (03) 863 6151

425 High St, NORTHCOLE
Phone: (03) 489 8866

Mail Order and Correspondence:
P.O. Box 620, CLAYTON 3168

Telex: AA 151938



MAIL ORDER HOTLINE
008 335757
(TOLL FREE)
(STRICTLY ORDERS ONLY)

**LOCAL ORDERS
& INQUIRIES**
(03) 543 7877

POSTAGE RATES:
\$1 - \$9.99 \$2.00
\$10 - \$24.99 \$3.00
\$25 - \$49.99 \$4.00
\$50 - \$99.99 \$5.00
\$100 - \$199 \$7.50
\$200 - \$499 \$10.00
\$500 plus \$12.50

The above postage rates are for
basic postage only. Road Freight,
bulky and fragile items will be
charged at different rates.


All sales tax exempt orders and
wholesale inquiries to:
RITRONICS WHOLESALERS,
55 Renner Rd, Clayton,
Ph. (03) 543 2166 (3 lines)

Errors and omissions excepted

*Apple and IBM are registered trade names



50 and 25 years ago...

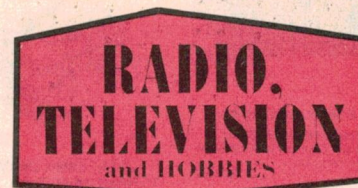

"Electronics Australia" is one of the longest running technical publications in the world. We started as "Wireless Weekly" in August 1922 and became "Radio and Hobbies in Australia" in April 1939. The title was changed to "Radio, Television and Hobbies" in February 1955 and finally, to "Electronics Australia" in April 1965. Below we feature some items from past issues.



August 1937

Calling the number: An innovation has been introduced at the Head Office of the Commonwealth Savings Bank to obviate the necessity of the paying tellers shouting the numbers of depositors. The teller now simply speaks in his ordinary tone into a small microphone. The "mike" is connected to an amplifier, which reproduces the call to the circle of clients. The new system has been found a great improvement.


Wireless telephone: A U.S.A. Government official says that even before television is properly developed "it may be possible for you, while riding in your automobile to pick up a wireless telephone and talk with your home or with any telephone connection anywhere", and he also mentions the possibility of "small radio-telephone and receiving sets of vest-pocket size".

Powerful new station: A modern broadcasting station is about to be established at Kingaroy, Queensland, for the South Burnett Broadcasting Proprietary. The station, which is being designed and constructed by Amalgamated Wireless, will operate on a power of 2000 watts in the aerial.

August 1962

Satellites — for how long? (Editorial) Much publicity has been given to the successful launching of "Telstar", the world's first active satellite repeater. Mention has been made that other similar projects are well under way, so that "Telstar" is not likely to be alone in space for very long. To date, the emphasis has been on improved communications, and the exchange of television programs, which might allow us the better to understand our neighbours.


Driverless trucks: A driverless truck with a rotating flashing beacon adds a Wellsian touch to mechanical landing.

The Robotug is fitted with an electronic guidance system and follows an energised wire buried half an inch below the surface of the ground. A flashing beacon will warn staff of the Robotug's approach and it will stop immediately if it touches any obstruction. 

AUGUST CROSSWORD

ACROSS

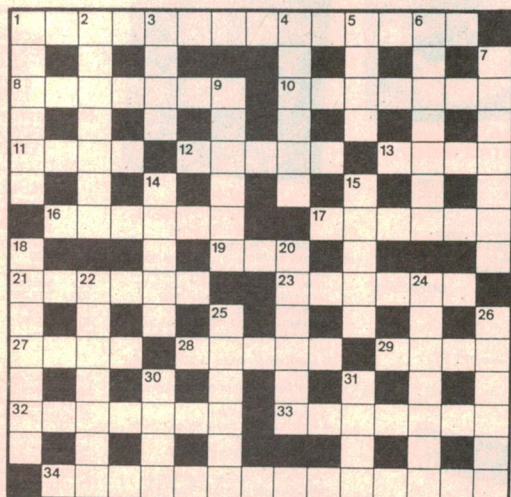1. Loss of temperature stability. (7,7)
8. Evolutionary process in electrolysis. (7)
10. Type of cartridge. (7)
11. Base SI unit. (4)
12. Sometimes it's synthesised. (5)
13. Trade jargon for crystal. (4)
16. Encapsulate. (6)
17. Feature of meter scale to lessen parallax error.
19. Type of meter used in radio applications. (1,1,1)
21. Filter or attenuator with a step-like arrangement. (6)
23. Resistor code colour. (6)




27. ANSCAN cable messages can go to this place. (4)
28. Construct. (5)
29. The standard-setting American Society of Mechanical Engineers. (1,1,1,1)
32. Device in earlier cathode-ray tubes. (3,4)
33. Metal used with platinum in thermocouples. (7)
34. Pixel. (7,7)

DOWN

1. Video pastime. (1,1,4)
2. Letter used as symbol for electric permittivity. (7)
3. Special message service, electronic ——. (4)
4. Remove wire from winding (6)
5. American Radio Relay League. (1,1,1,1)
6. Measuring instrument. (7)
7. Devices used in radiation counters. (7)
9. Wire metal sizes. (6)
14. The first name of Joule, the discoverer of magnetostriction. (5)

SOLUTION FOR JULY

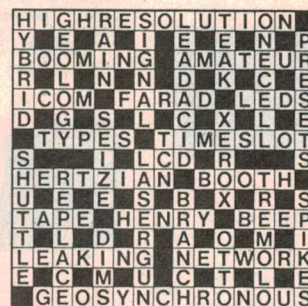

15. Kind of secondary cell. (5)
18. Typical insulating substance. (7)
20. Part of tape-deck, the pinch ——. (6)
22. Inventive genius, engineer, and artist. (2,5)
24. Heater, possibly ignited by a piezoelectric spark. (3,4)
25. Kind of connecting lead. (6)
26. Modern material made from more than metal. (6)
30. This can be removed from air by electrostatic precipitation. (4)
31. Type of laser. (2-2)

EA AUG '87

Back by Popular Dem

DATA & REFERENCE

DIGITAL IC EQUIVALENTS AND PIN CONNECTIONS

A. Michaels BP0140
Shows equivalents and pin connections of a popular user-orientated selection of European, American and Japanese digital ICs. Also includes details of packaging, families, functions, manufacturer and country of origin.

256 pages (Large Format)

\$18.00

LINEAR IC EQUIVALENTS AND PIN CONNECTIONS

A. Michaels BP0141
Shows equivalents and pin connections of a popular user-orientated selection of European, American and Japanese linear ICs. Also includes details of functions, manufacturer, and country of origin.

320 pages (Large Format)

\$18.00

INTERNATIONAL TRANSISTOR EQUIVALENTS GUIDE

A. Michaels BP0085
Helps the reader to find possible substitutes for a popular user-orientated selection of European, American and Japanese transistors. Also shows material type, polarity, manufacturer and use.

320 pages

\$12.00

CHART OF RADIO, ELECTRONIC, SEMICONDUCTOR AND LOGIC SYMBOLS

M. H. Babani, B.Sc.(Eng) BP0027
Illustrates the common, and many of the not-so-common, radio, electronic, semiconductor and logic symbols that are used in books, magazines and instruction manuals, etc., in most countries throughout the world.

Chart

\$4.00

RADIO AND ELECTRONIC COLOUR CODES AND DATA CHART

B. B. Babani BP0007
Covers many colour codes in use throughout the world, for most radio and electronic components. Includes resistors, capacitors, transformers, field coils, fuses, battery leads, speakers, etc.

Chart

\$4.00

AUDIO AND HI-FI

BUILD YOUR OWN SOLID STATE HI-FI AND AUDIO ACCESSORIES

M. H. Babani BP0220
This book covers in detail the library of any keen hi-fi and audio enthusiast. The design and construction of many useful projects are covered including: stereo decoder, three-channel stereo mixer, FET pre-amplifier for ceramic PUs, microphone pre-amp with adjustable bass response, stereo dynamic noise filter, loud-speaker protector, voice-operated relay, etc.

96 pages

\$6.00

AUDIO PROJECTS

F. G. Rayer BP0090
This book covers in detail the construction of a wide range of audio projects. The text has been divided into the following main sections: Pre-amplifiers and Mixers, Power Amplifiers, Tone Controls and Matching, Miscellaneous Projects. All the projects are fairly simple to build and have been designed around inexpensive and readily available components. Also, to assist the newcomer to the hobby, the author has included a number of board layouts and wiring diagrams.

96 pages

\$8.50

COMPONENT SPECIFIC

MODERN OP-AMP PROJECTS

R. A. Penfold BP0106
Includes a wide range of constructional projects which make use of the specialised operational amplifiers that are available today, including low noise, low distortion, ultra-high input impedance, low slew rate and high output current types. Circuits using transconductance types are also included. All of the projects are fairly easy to construct and a stripboard layout is provided for most of them so that even constructors of limited experience should be able to build any of the projects with the minimum of difficulty.

112 pages

\$9.50

MODEL RAILWAY PROJECTS

R. A. Penfold BP0095
The aim of this book is to provide a number of useful but reasonably simple projects for the model railway enthusiast to build, based on inexpensive and easily obtainable components. The projects covered include such things as controllers, signal and sound effects units, and to help simplify construction, stripboard layouts are provided for each project.

112 pages

\$8.50

AERIALS

AERIAL PROJECTS

R. A. Penfold BP0105
The subject of aerials is vast but in this book the author has considered practical aerial designs, including active, loop and ferrite aerials which give good performances and are relatively simple and inexpensive to build. The complex theory and mathematics of aerial design have been avoided. Also included are constructional details of a number of aerial accessories including a pre-selector, attenuator, filters and tuning unit.

96 pages

\$8.50

25 SIMPLE AMATEUR BAND AERIALS

E. M. Noll BP0125
This concise book describes how to build 25 amateur band aerials that are simple and inexpensive to construct and perform well. The designs start with the simple dipole and proceed to beam, triangle and even a mini-rhombic made from four TV masts and about 400 feet of wire. You will find a complete set of dimension tables that will help you spot an aerial on a particular frequency. Dimensions are given for various style aerials and other data needed for spacing and cutting phasing lengths. Also included are dimensions for the new WARC bands.

80 pages

\$6.50

25 SIMPLE SHORTWAVE BROADCAST BAND AERIALS

E. M. Noll BP0132
Fortunately good aerials can be erected at low cost, and for a small fractional part of the cost of your receiving equipment. This book tells the story. A series of 25 aerials of many different types are covered, ranging from a simple dipole through helical designs to a multi-band umbrella.

80 pages

\$6.50

25 SIMPLE INDOOR AND WINDOW AERIALS

E. M. Noll BP0136
Written for those people who live in flats or have no gardens or other space-limiting restrictions which prevent them from constructing a conventional aerial system. The 25 aerials included in this book have been especially designed, built and tested by Mr. Noll to be sure performers and give surprisingly good results considering their limited dimensions.

64 pages

\$6.00

25 SIMPLE TROPICAL AND MW BAND AERIALS

E. M. Noll BP0145
Shows you how to build 25 simple and inexpensive aerials for operation on the medium wave broadcast band and on 60, 75, 90 and 120 metre tropical bands. Designs for the 49 metre band are included as well.

64 pages

\$6.00

FAULT-FINDING

HOW TO GET YOUR ELECTRONIC PROJECTS WORKING

R. A. Penfold BP0110
The aim of this book is to help the reader overcome problems by indicating how and where to start looking for many of the common faults that can occur when building up projects. Chapter 1 deals with mechanical faults such as tracing dry joints, short-circuits, broken P.C.B. tracks, etc. The construction and use of a tristate continuity tester, to help in the above, is also covered. Chapter 2 deals with linear analogue circuits and also covers the use and construction of a signal injector/tracer which can be used to locate and isolate the faulty areas in a project. Chapter 3 considers ways of testing the more common components such as resistors, capacitors, op amps, diodes, transistors, SCRs, unijunctions, etc., with the aid of only a limited amount of test equipment. Chapter 4 deals with both TTL and CMOS logic circuits and includes the use and construction of a pulse generator to help fault-finding.

96 pages

\$8.50

TRANSISTOR RADIO FAULT-FINDING CHART

C. E. Miller BP070
Used properly, it should enable the reader to trace most common faults reasonably quickly. Across the top of the chart will be found four rectangles containing brief descriptions of these faults, viz — sound weak but undistorted, set dead, sound low or distorted and background noises. One then selects the most appropriate of these and following the arrows, carries out the suggested checks in sequence until the fault is cleared.

Chart

\$4.00

ELECTRONIC & COMPUTER MUSIC

ELECTRONIC MUSIC PROJECTS

R. A. Penfold BP0074
Provides the constructor with a number of practical circuits for the less complex items of electronic music equipment, including such things as fuzz box, waa-waa pedal, sustain unit, reverberation and phaser units, tremolo generator, etc. The text is divided into four chapters as follows:

Chapter 1, Guitar Effects Units; Chapter 2, General Effects Units; Chapter 3, Sound General Projects; Chapter 4, Accessories.

\$9.50

112 pages

ELECTRONIC SYNTHESIZER CONSTRUCTION

R. A. Penfold BP0185
Should enable a relative beginner to build, with the minimum of difficulty and at reasonably low cost a worthwhile monophonic synthesiser, and also learn a great deal about electronic music synthesis in the process. This is achieved by considering and building the various individual parts of the circuit that comprise the whole instrument as separate units, which can then be combined together to form the final synthesiser. Printed circuit designs are provided for these main modules. Later chapters deal with sequencing and some effects units.

112 pages

\$11.00

MIDI PROJECTS

R. A. Penfold BP0182
Provides practical details of how to interface many popular home computers with MIDI systems. Also covers interfacing MIDI equipment to analogue and percussion synthesisers.

112 pages

\$11.00

MORE ADVANCED ELECTRONIC MUSIC PROJECTS

R. A. Penfold BP0174
Intended to complement the first book (BP74) by carrying on where it left off and providing a range of slightly more advanced and complex projects. Included are popular effects units such as flanger, phaser, mini-chorus and ring-modulator units. Some useful percussion synthesisers are also described and together these provide a comprehensive range of effects including drum, cymbal and gong-type sounds.

96 pages

\$8.50

COMPUTER MUSIC PROJECTS

R. A. Penfold BP0173
Shows some of the ways a home computer can be used to good effect in the production of electronic music. Topics covered include sequencing and control via analogue and MIDI interfaces, computers as digital delay lines and sound generators for computer control.

112 pages

\$11.00

MISCELLANEOUS

COIL DESIGN AND CONSTRUCTION MANUAL

B. B. Babani BP0160
A complete book for the home constructor on "how to make" RF, IF, audio and power coils, chokes and transformers. Practically every possible type is discussed and calculations necessary are given and explained in detail. All mathematical data is simplified for use by everyone.

96 pages

\$9.50

AN INTRODUCTION TO Z80 MACHINE CODE

R. A. & J. W. Penfold BP0152
Takes the reader through the basics of microprocessors and machine code programming with no previous knowledge of these being assumed. The microprocessor dealt with is the Z80 which is used in many popular home computers and simple programming examples are given for Z80-based machines including the Sinclair ZX-81 and Spectrum, Memotech and the Amstrad CPC 464. Also applicable to the Amstrad CPC 664 and 6128.

144 pages

\$10.00

A Z-80 WORKSHOP MANUAL

E. A. Parr BP0112
This book is intended for people who wish to progress beyond the stage of BASIC programming to topics such as machine code and assembly language programming, or need hardware details of a Z-80 based computer.

192 pages

\$12.00

GETTING THE MOST FROM YOUR PRINTER

J. W. Penfold BP0181
Details how to use all the features provided on most dot-matrix printers from programs and popular word processor packages like Wordwise, Visawrite and Quill, etc. Shows exactly what must be typed in to achieve a given effect.

96 pages

\$11.00

CIRCUITS & CONSTRUCTIONAL PROJECTS

BEGINNERS GUIDE TO BUILDING ELECTRONIC PROJECTS

R. A. Penfold BP0227
Shows the complete beginner how to tackle the practical side of electronics, so that he or she can confidently build the electronic projects that are regularly featured in the popular magazines and books. Also includes examples in the form of simple projects that you can build.

112 pages

\$8.50

and... Babani Books!

50 PROJECTS USING RELAYS, SCRs AND TRIACS

F. G. Rayer BP0037
This book gives tried and practical working circuits which should present the minimum of difficulty for the enthusiast to construct. In most of the circuits there is a wide latitude in component values and types, allowing easy modification of circuits or ready adaption of them to individual needs.
\$8.50
112 pages

POPULAR ELECTRONIC PROJECTS

R. A. Penfold BP0049
Provides a collection of the most popular types of circuits and projects covering a very wide range of interests, including Radio, Audio, Household and Test Equipment projects.
\$9.50
144 pages

ELECTRONIC TEST EQUIPMENT CONSTRUCTION

F. G. Rayer BP0075
This book covers in detail, the construction of a wide range of test equipment for both the electronics hobbyist and radio amateur. Included are projects ranging from a FET amplified voltmeter and resistance bridge to a field-strength indicator and heterodyne frequency meter. Not only can the home constructor enjoy building the equipment but the finished product can also be usefully utilised in the furtherance of his hobby.
\$8.00
96 pages

HOW TO USE OP-AMPS

E. A. Parr BP0088
This book has been written as a designer's guide covering many operational amplifiers, serving both as a source book of circuits and a reference book for design calculations. The approach has been made as non-mathematical as possible and it is hoped, easily understandable by most readers, be they engineers or hobbyists.
\$11.00
160 pages

ELECTRONIC GAMES

R. A. Penfold BP0069
Contains a number of interesting electronic games projects using modern integrated circuits. The text is divided into two sections, the first dealing with simple games and the latter dealing with more complex circuits thus making the book ideal for both beginner and more advanced enthusiast alike.
\$8.00
96 pages

NEW RELEASES!

A TV-DXERS HANDBOOK

R. Bunney BP0176
Completely revised and updated by Roger Bunney who is probably one of the leading authorities in this country on the subject. Includes many units and devices which have been designed and used by active enthusiasts, and often, considerable ingenuity and thought have gone into the development of such units to overcome individual problems. A practical and authoritative reference to this unusual aspect of electronics. (Large Format)
\$18.00

AN INTRODUCTION TO CP/M

R. A. Penfold BP0193
CP/M is more than just a program to give a common set of standards and hence software compatibility between various computers. It includes a range of commands that help with such things as file copying and editing, the directing of data to the appropriate device etc. In order to get the best from CP/M and the programs running under it, a basic understanding of the system is highly desirable, and this book tells the story.
\$11.00
96 pages

ELECTRONIC CIRCUITS FOR THE COMPUTER CONTROL OF ROBOTS

R. A. Penfold BP0179
Provides information and circuits on computer control of electric motors (including stepper types), plus a range of useful sensors including visible light, infra-red, and ultrasonic types.
\$11.00
96 pages

USING YOUR AMSTRAD CPC DISC DRIVES

J. W. Penfold BP0189
Covers such things as tracks, sectors and formatting; AMDOS and CP/M operating systems including rules and regulations, filing from BASIC, file copying and transfer; program development including MERGE and CHAIN MERGE; CP/M turnkey discs etc.
\$11.00
96 pages

IC 555 PROJECTS

E. A. Parr BP0044
Every so often a device appears that is so useful that one wonders how life went on before without it. The 555 timer is such a device. Included in this book are basic and general circuits, motorcar and model railway circuits, alarms and note-makers as well as a section on the 556, 558 and 559 timers.
\$9.50
176 pages (Available February 1987)

HOW TO DESIGN AND MAKE YOUR OWN P.C.B.s

R. A. Penfold BP0121
Chapter 1 deals with the simple methods of copying printed circuit board designs from magazines and books and covers all aspects of simple P.C.B. construction as comprehensively as possible. Chapter 2 covers photographic methods of producing p.c.b.s and Chapter 3 deals with most aspects of designing your own printed circuit board layouts.
\$6.50
80 pages

POWER SUPPLY PROJECTS

R. A. Penfold BP0076
The purpose of this book is to give a number of power supply designs, including simple unregulated types, fixed-voltage regulated types, and variable-voltage stabilised designs, the latter being primarily intended for use as bench supplies for the electronics workshop. The designs provided are all low-voltage types for semi-conductor circuits. This book should also help the reader to design his own power supplies.
\$7.50
96 pages

HOW TO DESIGN ELECTRONIC PROJECTS

R. A. Penfold BP0127
The aim of this book is to help the reader to put together projects from standard circuit blocks with a minimum of trial and error, but without resorting to any advanced mathematics. Hints on designing circuit blocks to meet your special requirements where no "stock" design is available are also provided.
\$9.00
128 pages

ELECTRONIC SECURITY DEVICES

R. A. Penfold BP0056
Many people associate the term "security device" with only burglar alarms of various types, but in fact, any piece of equipment which helps to protect people and property against any form of danger could be termed a "security device". Therefore this book, besides including both simple and more sophisticated burglar alarm circuits using light, infra-red and ultrasonics, also includes many other types of circuits as well, such as gas and smoke detectors, flood alarms, doorphone and baby alarms, etc.
\$9.50
112 pages

FURTHER PRACTICAL ELECTRONICS CALCULATIONS AND FORMULAE

F. A. Wilson BP0144
Written in the same style as the first book (BP53) and with the same objectives in mind, this book is divided into the

COMMUNICATION

(Elements of Electronics — Book 5)
F. A. Wilson BP0089
A look at the electronic fundamentals over the whole of the communication scene. This book aims to teach the important elements of each branch of the subject. Most of the modern transmissions system techniques are examined including line, microwave, submarine, satellite and digital multiplex systems, radio and telegraphy. To assist in understanding these more thoroughly, chapters on signal processing, the electromagnetic wave, networks and transmission assessment are included, finally a short chapter on optical transmission.
\$11.00
256 pages

50 SIMPLE LED CIRCUITS

R. N. Soer BP0042
Contains 50 interesting and useful circuits and applications, covering many different branches of electronics, using one of the most inexpensive and freely available components — the light-emitting diode (LED). Also includes circuits for the 707 common anode display.
\$6.00
64 pages

IC PROJECTS FOR BEGINNERS

F. G. Rayer BP0097
Offers a range of simple projects based around a number of popular and inexpensive linear and digital integrated circuits. With most projects, complete layout and/or point-to-point wiring diagrams are included to help simplify construction.
\$8.50
112 pages

ELECTRONIC PROJECTS USING SOLAR CELLS

O. Bishop BP0082
This is a book of simple circuits which have applications in and around the home and that are designed to be powered by the energy of the sun. Although, if the reader wishes, they could alternatively be powered by the ordinary button cells or small dry batteries.
\$8.50
128 pages

following fourteen sections: Electricity, Electrostatics, Electromagnetism, Complex numbers, Amplifiers, Signal Generation and Processing, Communication, Statistics, Reliability, Audio, Radio, Transmission Lines, Digital Logic and Power Supplies.
\$16.00
512 pages

ELECTRONICS BOOKS ORDER COUPON

(If insufficient space enclose separate list)

For airmail outside Australia add \$5.00 to these charges.

BOOK TITLE	BOOK NUMBER	QTY	PRICE

Send to:
Freepost No.4
Federal Publishing
PO Box 227
Waterloo 2017 (no stamp required)

Total Price of Books\$
Plus post & handling\$ **2.75**
(flat rate up to 10 books)
TOTAL\$
Date:

Name: Telephone:
Address: Postcode:

Please tick box to indicate method of payment: ☒ **Cheque* / Money Order** ☐
*Please make payable to the Federal Publishing Company Pty. Ltd.
☒ **Mastercard** ☐ **American Express** ☐ **Bankcard** ☐ **Visa** ☐
Credit Card No:

Signature Expiry Date
(unsigned orders cannot be accepted As these books are imported, unavoidable delays may occur.)

EA AUG '87

Pt.3

The ins and outs of

Local Area Networks

So far, in our articles on the Token-Ring LAN, we have looked at the general operation of the hardware and the means of accessing that hardware via software. This article will highlight the ring functions that are performed, as well as the hardware components that perform them.

DAVID CARTWRIGHT & GREG PEAKE

Texas Instruments Australia

Major hardware components

These aspects of communicating on the Token-Ring are transparent to the user and the associated software, providing the user an "error-free pipeline" as mentioned in the previous article.

The adapter illustrated containing the Texas Instruments TMS380 chipset will

be referenced throughout this article when considering the hardware blocks needed to implement the adapter function. This chipset consists of five main chips, the basic block interconnects of which are shown in Fig.1, and the individual functions highlighted in Table 1.

Other components needed for the operation of the adapter are discrete components which interface the adapter to the network, and some logic for in-


terfacing to the host bus. Auxiliary equipment needed to complete the network are the Wiring Concentrator, the twisted pair cabling, and of course other nodes to communicate with. The auxiliary equipment is also noted in Table 1.

One of the more distinguishing features of the Token-Ring is the management and reliability control implemented on the ring. The adapter chipset performs these functions at the Medium Access Control (MAC) level, hence the implementation of network management is unknown to the users (Refer Article 1). Adapter based firmware is used by the TMS38010 (Communications Processor) to implement these functions. The firmware is stored in a 16K on-chip ROM contained in the TMS38020 (Protocol Handler), from which the TMS38010 operates and controls the rest of the adapter.

Ring management

When a DTE is to be connected to an operational ring and after diagnostics have been run, a special MAC control frame containing a proposed source address is sent on the ring. This frame is looked at by all DTE's on the ring, to make sure that the address is not duplicated. If not duplicated, the DTE is connected to the ring and an initialisation process is started. The accepted address becomes the DTE's network address at the MAC level, and is used when either sending or receiving LLC or MAC-control based frames. Fig.2 contains the descriptions of these frames.

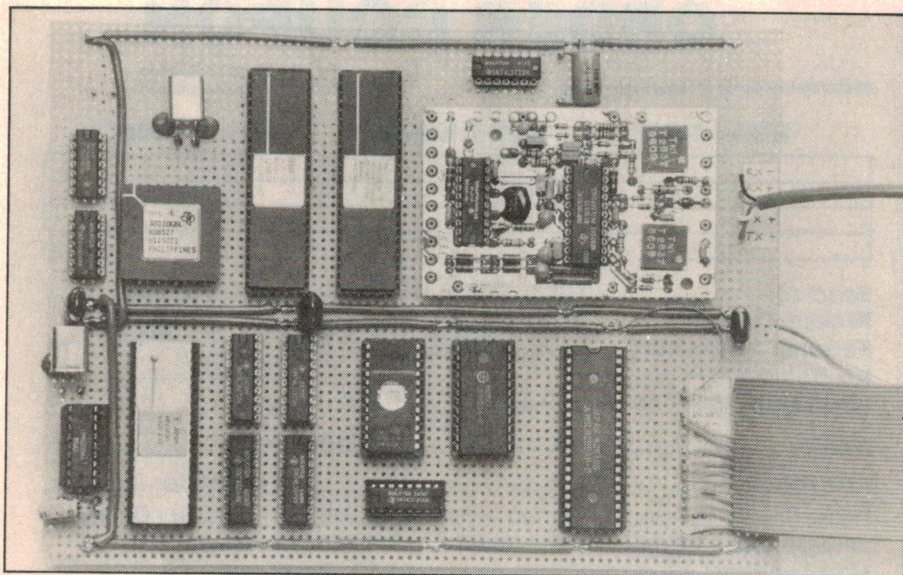For ring management at the MAC-control level, there is another type of address called "a function address", which is embedded into the MAC address field. These addresses are used to access Ring Management functions resident within particular nodes on the ring. A functional address will be recognised and the frame copied by a node, only if that node supports the function. MAC-



This intelligent printer server node using the Texas Instruments TMS380 chipset was developed in 12 weeks by a university student.

control frames can only be sent when the originating node has the token, however they are generally classed as higher priority type frames and are sent before LLC-based MAC frames.

Network manager

MAC-control frames are used for recording ring status, error recovery, and controlling the insertion and de-insertion of DTE's. For these functions to be synchronised, there is a Network Manager assigned, the function of which could be contained in any node. When any node on the ring communicates with the Network Manager, it uses a MAC-control frame and the destination address has embedded within it a functional address which always denotes the Network Manager.

The latter is responsible for keeping a list of all nodes currently on the ring and has the ability to allow additional nodes to join in. It also can de-insert a node, for time-share applications, or change the initialisation parameters within a node as required. Optimisation of Network Manager control invariably increases the efficiency of the network.

Ring parameter server and ring error monitor

These functions work under the Network Manager and are accessed by their appropriate functional addresses. The Ring Parameter server facilitates the inserting of a DTE into the ring, by providing it with parameters such as authorised priority codes and accessible functional addresses. If there is no Ring Parameter Server, the node parameters are initialised with default values.

The Ring Error Monitor acts as a col-

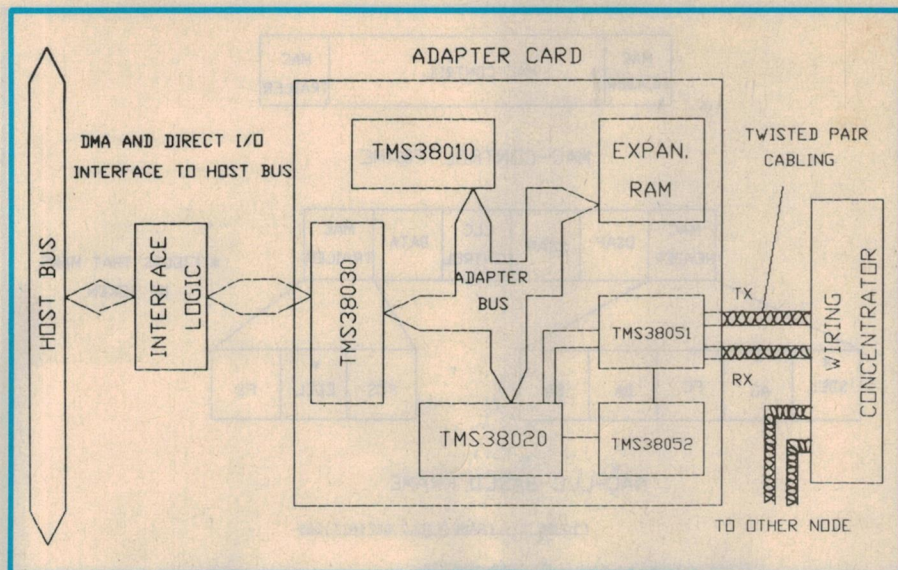


Fig.1: The block interconnect diagram for a Token-Ring node adapter using the TMS380 chipset.

lection point for errors occurring on the network. If any node detects a soft error (CRC or token errors etc.), regardless of whether there is a Ring Error Monitor, a report will be sent to that functional address. Errors detected by and about the Active Monitor are also reported to this functional address.

Active monitor and standby monitor

There is only one Active Monitor on the ring at any one time, this entity being accessed by another functional address. The remaining nodes on the ring are classed as Standby Monitors, ready to take over the Active Monitor role should it fail.

When an Active Monitor fails, the

ring moves into a monitor contention mode whereby all monitors contest for the Active Monitor role. This process involves the sending of a MAC-control frame indicating the desire to claim the Active Monitor role. The role is normally won by the node with the highest address.

So what does the Active Monitor do? Essentially it is a "labourer" to the Network Manager, that maintains the circulating token, while sending reports on token errors and new node insertion. It checks for a valid token every 10ms, which indirectly checks for any ring faults. Invalid tokens are usually caused by adapter or media faults.

On the discovery of an invalid token, the Active Monitor purges the ring.

COMPONENT	PURPOSE	FEATURES
TMS38010 COMMUNICATIONS PROCESSOR	- CONTROLS ADAPTER - BUFFERS DATA FROM HOST SYSTEM - CHECKS VALIDITY OF DATA AND ADDRESS BLOCKS FROM HOST	16 BIT CPU 2.75K ON-CHIP RAM 9 INTERRUPT LEVELS 256K ADDRESS SPACE GENERAL PURPOSE TIMER 33NS CYCLE TIME
TMS38020 PROTOCOL HANDLER 1	- CHECKS DESTINATION ADDRESS OF RING FRAME - DIFFERENTIAL MANCHESTER ENCODER - CHECKS + CREATES CRC - MANAGES PRIORITY - GENERATES FRAME DELIMITERS	4MBIT MANCHESTER ENCODER 2 PAIRS DMA CHANNELS ON-CHIP 16K ROM (CONTAINS ADAP.SOFT.) ROM BYTE PARITY PROT.
TMS38021 PROTOCOL HANDLER 2 (GENERIC VERSION OF TMS38020)	- ENABLES ROUTING INFORMATION DETECTION - ENABLES EXTERNAL ADDRESS DETECTION	EXTERNAL HARDWARE COPY INTERFACE
TMS38030 SYSTEM INTERFACE	- ADAPTER INTERFACE TO HOST BUS - USES DMA CONTROL TO EXTRACT DATA FROM HOST MEMORY - CONTROLLED BY DIRECT I/O FROM HOST - DMA -BURST TRANSFERS - CYCLE STEAL - PASSES DATA TO ADAP. BUFFER	CONNECTS ASSYNCH. BUSES DMA/HOST - 5MBITS/S DMA/ADAP. BUS - 6MBITS/S DIRECT I/O OPTION 8 OR 16 BIT SYSTEM BUSES 808X OR 680XX
TMS38051 RING INTERFACE TRANSCIEVER	- PROVIDES INTERFACE TO RING - SIGNAL RESHAPING - RETIMING OF RXED DATA	PHASE LOCK-LOOP 4MBPS ENCODED DATA RATE 2 CHANNEL - TX,RX
TMS38052 RING INTERFACE CONTROLLER	- ADAPTIVE EQUAL. - LOOPBACK FOR DIAGNOSTICS	
TWISTED PAIR CABLING (IBM SYSTEM TYPE 1/2)	- FOR CONNECTING ADAPTER TO WIRING CONCENTRATOR	MAX DATA RATE - 16MBPS MAX LENGTH TO W.C - 300M MAX LENGTH BETWEEN
WIRING CONCENTRATOR	- SHIELDED	CASCADED WIRING CONCEN. - 200M
INTERFACE LOGIC	- PROVIDES INTERFACE GLUE BETWEEN 38030 AND SYSTEM BUS - INCLUDES LATCHES, BUFFERS, DECODE LOGIC	UP TO 260 NODES/RING USING SYSTEM TYPE 1/2 CABLING. RELAY SWITCHING CONTROL BY ADAPTER INTERFACE MAX OF 2 WIRING CON. PER RING - BEING CASCADED TOGETHER

Table 1: The various components used in the Token-Ring interface adaptor shown, with a summary of their functions and features.

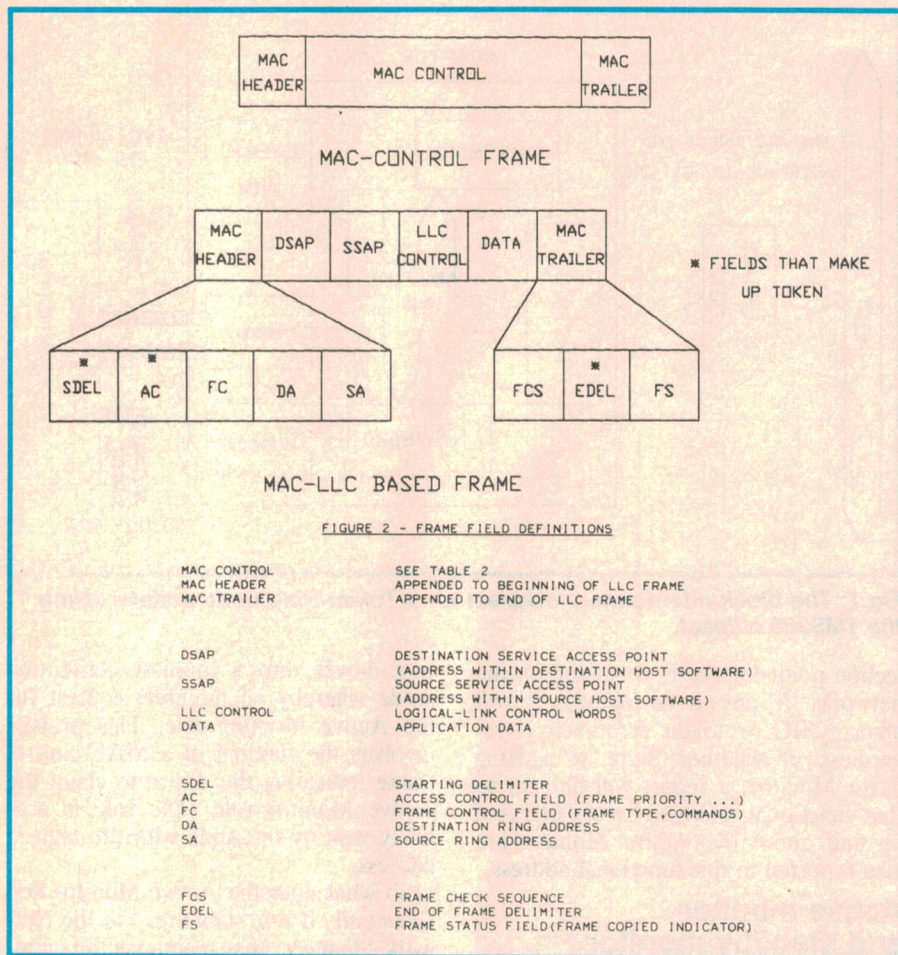


Fig.2: The two different kinds of MAC control frames.

This involves the transmitting of a MAC-control frame by the Active Monitor, which can be sent without possession of the token. The MAC-Control frame is passed around the ring and returned to the Active Monitor for error detection. If no error is detected in the frame, a new token is created and passed on for normal ring operation. If a CRC error is detected in the frame, the Active Monitor sends it again, this continuing until the faulty equipment is detected and de-inserted from the ring.

In maintaining the validity of frames on the ring, the Active Monitor also provides a master clock to compensate for frequency and phase errors (jitter) caused mainly by the filter characteristics of the ring cabling. It locks onto the incoming data via a phase-locked loop (PLL), and stores the data in an elastic buffer.

The elastic buffer allows for group delay stretching of the digital train by allowing room for the individual bits that are sampled by the PLL more than once. The buffer, which is organised as a FIFO, re-transmits the data at the adapter's crystal clock frequency.

All adapters contain this function, however it is only exercised by the Active Monitor. The Standby Monitors use the PLL for the clocking of data into and out of their respective FIFO's.

The bridge

Although there can only be 260 nodes per ring when using IBM shielded twisted pair cabling for node connection to the wiring concentrator, this does not limit the size to which a Token-Ring network can expand.

Rings can be linked together via bridges, such that a node from one ring can communicate with a node on another. The bridge function is carried out by the TMS38020 Protocol Handler, working within a dedicated ring server. Eight rings can be linked together, using seven bridges, which gives a network total of approximately 2000 nodes maximum (this is assuming only one bridge per ring).

The bridge adapter can be accessed for configuration and error checking by the network manager via a functional address. When addressing the bridge for information transfer to another ring,

routing information is included with the external destination address and local source address of the frame. This information defines the route that the frame must take to reach the desired node by using ring and bridge addressing.

When implementing the TMS38020 for the bridge function, all frames have to be copied and passed to the host — which contains the software to determine whether the frame is external or not. A generic version of the TMS38020, the TMS38021, allows more efficient bridging management. It facilitates the connection of external copy hardware, which checks the frames for routing information or dedicated external addresses, hence eliminating the need to copy all frames.

Bridges normally consist of two network adapters connected to a common host. They must remain transparent when forwarding frames across a network, and not change any frame parameters when copying. They can be used for bridging two networks of different MAC protocols (ie Token-Ring and Ethernet) with the same LLC. Hence the host must perform the function of MAC protocol conversion.

Due to the possibility of one bridge within a ring being a bottleneck, frames being transmitted to and from external rings are set at a higher priority than local frames. Two bridges working in parallel within one ring can also be used to solve bottleneck problems.

Adapter diagnostics

Prior to connection to the ring, a node undergoes hardware tests to ensure reliability of the chipset and the attached cabling. These tests are carried out under the scrutiny of the TMS38010, operating from the adapter firmware.

Fig.3(a) shows the internal loopback test, where communication between the Communications Processor and the Protocol Handler is thoroughly tested. This test checks the CRC circuitry, the RAM buffers, parity checkers, and transmission functions of the Protocol Handler which all need to be functioning for reliable adapter processing.

Fig.3(b) shows the cabling loopback test. When the node is not inserted into the ring, but the cable is physically connected, a short circuit exists between the TX and RX lines of the ring interface. This is caused by the relay in the wiring concentrator being closed, thus providing a test loop for cable fault diagnosis.

These tests ensure that a faulty adapter or cable is not inserted into the

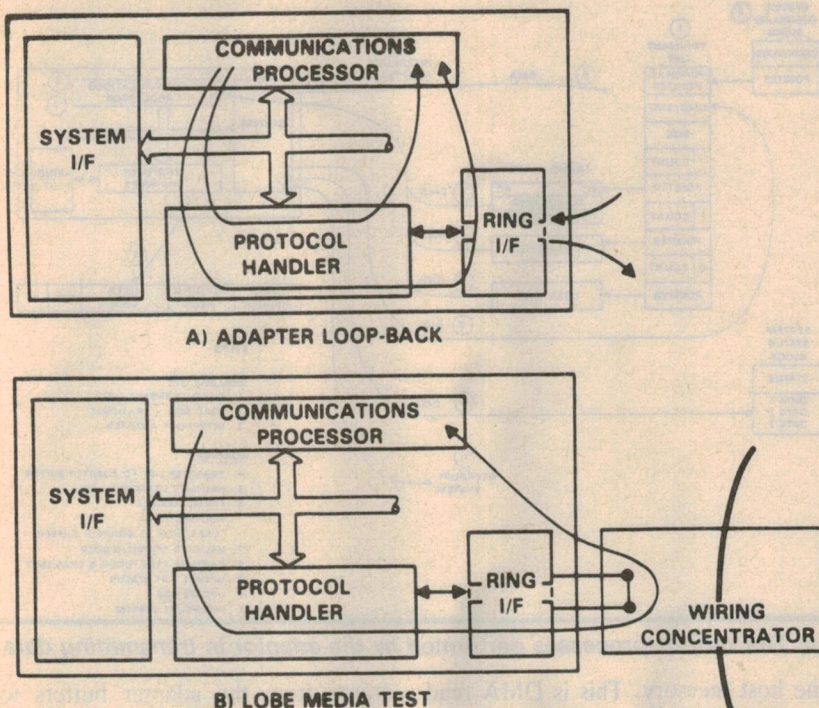


Fig.3: Before connecting a node into the ring, the adaptor controller performs both internal and cabling (b) loopback diagnostic tests.

TABLE 2 - THE MAJOR MAC-CONTROL COMMANDS

COMMAND	SENDER, DESTINATION
BEACON	NODE TO RING
LOBE MEDIA TEST	INSERTING NODE TO CABLING
CLAIM TOKEN	NODE IN MONITOR CONTENTION
REMOVE RING STATION	NETWORK MANAGER(NM) TO NODE
REPORT STATION STATE	NODE TO NM
REPORT MONITOR ERROR	NODE TO RING ERROR MONITOR
REPORT STORED UPSTREAM ADDRESS (SUA) CHANGE	NODE TO NM
REPORT NEW MONITOR	ACTIVE MONITOR (AM) TO NM
REPORT STATION ATTACHMENT	NODE TO NM
REPORT RING POLL FAILURE	AM TO RING ERROR MONITOR
REPORT ERROR	NODE TO RING ERROR MONITOR
REPORT STATION ADDRESS	NODE TO NM
REQUEST STATION STATE	NM TO NODE
REQUEST INITIALISATION	NODE TO RING PARAMETER SERV
REQUEST STATION ATTACHMENT	NM TO NODE
REQUEST STATION ADDRESS	NM TO NODE
REPORT TRANSMIT FORWARD RESPONSE	NODE TO NM
ACTIVE MONITOR PRESENT	GENERAL RESPONSE TO REQUEST
STANDBY MONITOR PRESENT	NEW AM TO DOWNSTREAM NODE
RING PURGE	STANDBY MONITOR TO AM
CHANGE PARAMETERS	AM TO RING
INITIATIVE RING STATION	NM TO NODE
TRANSMIT FORWARD	RING PARAMETER SERV TO NODE
DUPPLICATE ADDRESS TEST	NODE TO RING
	NODE TO RING

Table 2: The major MAC control commands used for controlling ring operation, and the active participants involved.

ring. If an adapter detects an error *after* insertion into the LAN, it immediately de-inserts and completes diagnostic testing to determine the fault. If the tests are successful the node re-inserts. If testing is unsuccessful, it stays de-inserted and reports the error to the host. All such errors are reported to the Ring Manager.

MAC-Control processes

Table 2 contains a list of the major

MAC-control commands used for the underlying services of the ring and the active participants in implementing the function. These commands are used for communication between adapters for error reporting, initialisation, and Active Monitor functions. Certain commands are used in addressing network management functions, while other commands are directed at all nodes on the ring. Some of the major commands will be discussed briefly here.

Hundreds of other items not listed — Send 40c postage stamp for list

L.E. CHAPMAN

122 PITT ROAD, NTH CURL CURL
MAIL ORDERS, BOX 156, DEE WHY, NSW 2099
TELEPHONE 93-1848

SUPER SPECIAL

FM STEREO KITS

All three modules supplied are fully assembled and aligned. Circuit diagram supplied.

ONLY \$22

P.P. \$1.90

SUPER SPECIAL \$15



GRAMO MOTOR AND PICK-UP

204V 16-33-45-78
4 speed includes cartridge stylus turnover. Ideal for recording old 78 records to tape recorders.

P.P. NSW \$3.80 Interstate \$4.50

RECORD PLAYER CABINET

Solid timber base, hinged perspex lid **\$20**

P.P. NSW \$5 Interstate \$7 W.A. TAS \$12

TRANSISTOR TV TUNERS 11 Volt 46300-5 \$15

POTS

1/2 Meg Switch	\$1.00	2 Meg Ganged Tapped Log	\$1.50
1/2 Meg Single	\$.50	50K Dual Concentric	\$1.80
25K Dual Ganged Switch	\$1.50	25K TAP 32K	\$1.50
1.5 Meg Single	\$.50	25K	\$.50
100K Dual Concentric	\$1.50	1/4 Meg Dual Concentric Linear	\$1.50
1/2 Meg Ganged Log	\$1.50	100K Log Switch	\$1.00
2 Meg Linear Ganged	\$1.00	50K Mini 4 for	\$1.00
10K Dual Concentric	\$1.50	10K Mini 4 for	\$1.00
Double Pole Switch	\$1.50	50 Ohm	\$.50
25K 4 Gang Linear	\$2.00	0.25 Meg Dual Concentric	\$1.00
20K Linear Single	\$.50	25K Dual Ganged Switch	\$1.50
1 Meg Log Switch	\$1.00	10K Dual Ganged Switch	\$1.00
1 Meg Dual Ganged Log	\$1.00	250K Dual Ganged Switch	\$1.00
100K Sub Mini	\$.50	1 Meg 1/2 Meg Dual Concentric	\$1.00
10K Sub Mini	\$.50	TAP 40K Double Pole Switch	\$1.50
50K Log Switch	\$1.00	300 Ohm Linear	\$.50
250K Linear	\$.50	1500 Log	\$.50
100K Log	\$.50	0.25 Linear or Log	\$.50
50K Log	\$.50		



SPECIAL DUAL VU METERS

\$3 pp \$1

TOUCH MICRO SWITCHES 4 for \$1	Shielded leads 7ft 3.5 to 3.5 \$1.00 6.5 to 3.5 \$1.00 6.5 \$0.50
MICRO SWITCHES 5A 250 volt 50c.	VALVES 6V6 \$10 EF86 \$5
IF's 455kHz For valve radios \$1 ea.	VALVE SOCKETS 7 pin 4 for \$1 9 pin 4 for \$1 OCTAL 4 for \$1
OSCILLATOR COILS 75c	5 MIXED ROTARY SWITCHES \$2.50
TAG STRIPS Mixed 10 for \$1	CHROME 1/4 PUSH ON KNOBS 10 for \$1
MIXED SWITCHES 12 for \$4.50	SLIDE POT KNOBS 10 for \$1
MIXED RESISTORS 100 for \$2 all handy values	MIXED CAPACITORS Fresh stock 100 for \$2
SHIELDED CABLE Single strand. 25 metres for \$2.50	TV COLOUR CRYSTALS 4433 — 619kHz \$2
VALVES 6DQ6 \$10.00 6K7 \$ 5.00	VALVES: 6 B05 \$5, 6 B08 \$5 6 B18 \$4
TRANSISTOR EARPIECE PLUG & LEAD 4 for \$1	THERMISTERS 4 for \$1
STICK RECTIFIERS TV 20 SC \$1 each	SPARK GAPS 10 for \$1
	CAR RADIO SUPPRESSORS 4 for \$1
	TRANSISTOR AD149 \$1 ea
SLIDE POTS	
1 1/2 Meg DUAL \$1	5K single 50c
1 Meg dual \$1	250K single 50c
2 Meg dual \$2	10K single 50c
250K dual \$1	2 Meg single 50c
1K dual \$1	25K dual ganged \$1

stamp for list — Hundreds of other items not listed — Send 40c postage

BEACON — The beaconing process is created when a hardware fault is detected, for example a discontinuity in the ring. The node closest to the break will time out, due to not having received a token or frame in a specified time. It will send a beacon MAC frame onto the ring to the address of the node preceding it on the ring, in order to isolate the error location. This process continues until a return frame is detected. In this period, other nodes will also move into beacon transmit mode, while others will just repeat the beacon. After a succession of beacon frames have been sent to the faulty node, it will de-insert from the ring and perform self-tests. Meanwhile, the ring will reconfigure.

TRANSMIT FORWARD — The transmit forward process is used to test links between nodes in the ring. When a node receives a transmit forward MAC frame, it notifies the Network Manager and uses the data contained within the frame to re-transmit the frame. The data could include addressing, frame type, or a MAC command.

RING POLL — A ring poll is a process where each node transmits its address to its downstream neighbour. If a downstream node identifies its upstream node's address as being different from that which it has stored, then a request is made to the Network Manager to report a change in that address. Ring polls are useful for letting the Network Manager know of any un-recorded nodes on the network, as well as letting each node know the address of its neighbour for easy detection of ring discontinuities.

Adapter data flow process

Let us now examine the method of transmitting and receiving data on the LAN via a TMS380 based adapter. The TMS38030 (System interface chip) has the necessary control lines to support 8 or 16 bit host buses, with the choice of 808X or 680XX memory arrangements. Extra interface glue is required for the DMA and Direct I/O modes, since the address and data lines of the TMS38030 are multiplexed. These lines need to be de-multiplexed and address-decoded to enable memory mapped I/O operations between the two buses.

Data transmission

When the host has data to send, the adapter is interrupted by a direct I/O write to its interrupt register. The host then transfers the System Command Block (see Fig.4) to the adapter, via a DMA. The command block contains the address of the Transmit List contained

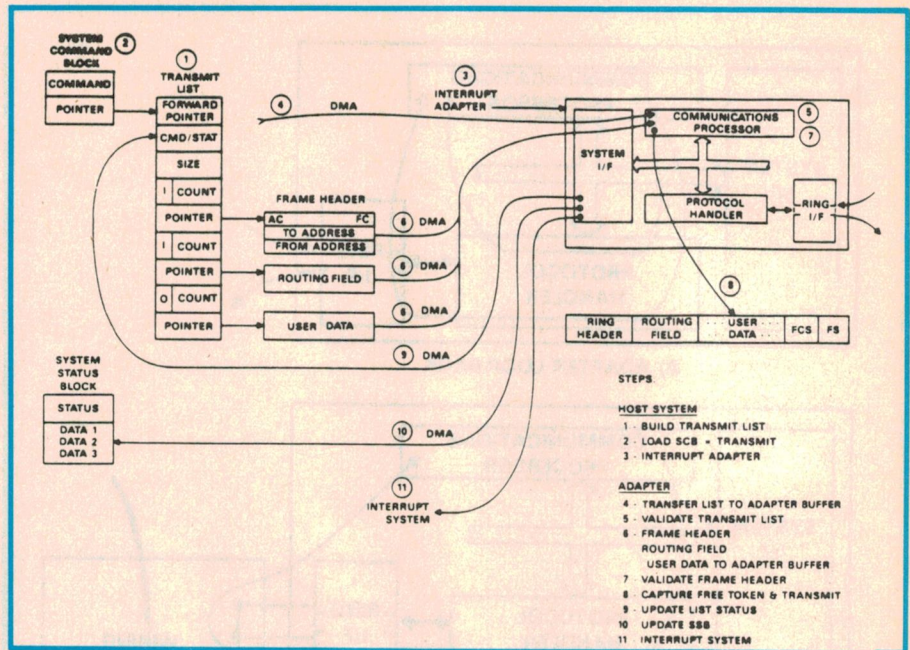


Fig.4: The various processes performed by the adaptor in transmitting data.

in the host memory. This is DMA read into the on-chip buffers of the TMS38010.

The size and number of buffers available is setup during the initialisation process with the host. The transmit list contains the "TRANSMIT" command from the host, as well as the address pointers to the host memory where the frame is being stored. The frame is broken up into segments, the total size of the frame being stored in "SIZE". The "COUNT" field contains the number of bytes contained in the following frame segment. The bits before the "COUNT" field indicate the position of the frame end, and a "0" marks that end. The adapter can now DMA read the frame into the adapter RAM for processing.

The TMS38010 firstly checks the frame headers for validity and then sets up the Protocol Handler (TMS38020) for data transmission onto the ring. The TMS38020 then starts transferring the

frame from the adapter buffers to its own registers. In the meantime it catches a free token from the ring and starts to add the frame headers and eventually the data. The beginning of the frame is transmitted on the ring while the data is still being appended. When all data has been added, the Frame Check Sequence which is simultaneously generated with the frame creation, is appended to the end and sent as the completion to the frame.

While transmission of the frame is occurring, the TMS38020 is receiving data and checking for a match with its source address. This is facilitated by separate transmit and receive channels. Thus the node can actually detect the beginning of the return frame before the end has been fully transmitted. Once the node finishes transmitting the end of the frame, receives the return frame with its own source address, and detects whether the frame has been copied properly by the destination, a new

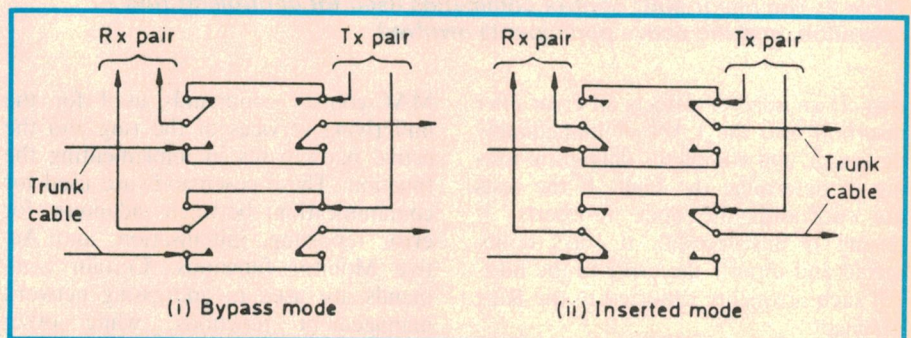


Fig.5: Inside the wiring concentrator, relays are used to either bypass (de-insert) or insert the adaptor and node concerned.

token is passed onto the ring.

Data reception

On receiving a frame, the Ring Interface (TMS38051, TMS38052) chips clock the data into the TMS38020, regardless of whether the frame is destined for that node or not. Clock recovery is performed by training a phase-locked loop (PLL) with the incoming Manchester-encoded data stream. Equalisation is also performed, so that the signal level is TTL compatible with that of the TMS38020.

A serial data stream is passed to the TMS38020, which in turn deserialises the data into 16 bit registers. Parity protection is then added for error detection in data transfer to the host, while the destination address is compared to see if the frame was destined for its node. If that test fails, the data is serialised and clocked back onto the ring using the PLL frequency (unless that node is the Active Monitor).

While the frame is being transferred to the adapter RAM, the TMS38020 calculates the CRC and compares it to that contained in the frame. If there is a match, it indicates to the TMS38010 that the message has been received error-free. However if an error is de-

tected, the TMS38020 signals the TMS38010 to ignore that frame.

Once the data has been buffered in the adapter RAM, the TMS38010 begins to DMA transfer the data to the host memory. When that process is completed the adapter interrupts the host and sends a status signal via the System Status Block.

Concentrator & cabling

Both the wiring concentrator and cabling used in a Token-Ring have to conform to the IBM Token-Ring standard. These are various types of cabling that can be used, including telephone twisted pair (system 3) for 4Mbps transmission, shielded twisted pair (system 1/2) for up to 16Mbps transmission, and fibre optics cable. These cables have varying limits and must have the correct connections for compliance to the standard.

For twisted pair cable there are two sizes of wiring concentrators currently defined: 72 nodes maximum for system 3 cabling and 260 nodes maximum for system 1/2 cabling. The format of the relays for each node connection is shown in Fig.5.

In the by-pass node the relay acts as a short circuit and the node is de-inserted from the ring. The inserted mode allows

the DTE to receive and transmit data.

Fibre Optics cable requires special adapters, such as those available from Dupont Optoelectronics, which interface between a wiring concentrator and fibre optic cable. In addition a number of US, European and Japanese manufacturers are working on fibre optic wiring concentrators that conform to the Token-Ring standards.

Conclusion

The efficiency and architecture of a LAN's hardware is crucial in the performance and speed of the network, hence benefitting the most important component of a network, the user.

The Token-Ring LAN can support the high speeds at low error rates, owing to its comprehensive ring management and the implementation of the standard in "state of the art" chipset design.

Recent industry surveys by companies such as the Yankee Group and the Gartner Group indicate that the Token-Ring LAN will be the dominant LAN architecture by the early 1990's. Users can therefore look forward to an abundance of software and hardware supporting the Token-Ring LAN, clearly making it the LAN of choice. EA

Books *Continued from page 52*

and finally complete functional systems.

The first section begins with atomic and crystal structure, leading to semiconductor physics. It then deals with diodes, bipolar transistors, JFETs and MOSFETs, UJT and the various kinds of thyristors, ending up with photoelectric devices.

Section two then deals with the various basic circuits: rectifiers and filters, amplifiers, tuned amplifiers, power amplifiers, operational amplifiers, oscillators and waveshaping circuits. Finally section three deals with two typical kinds of system: regulated power supplies and thyristor power control systems.

The treatment throughout is systematic, thorough and concise, with all basic maths given to cover device operation and circuit analysis/design. At the back there is also a very useful appendix with manufacturers' data on a range of representative devices.

In short, a very well produced text on basic semiconductor devices and their application in circuits.

The review copy came from Prentice-Hall of Australia, but copies should be available from all larger and technical bookstores. (J.R.)




(model 630L illustrated)

IQD DTMF MICROPAD

- Single contact tactile keyboard
- High stability encoder
- Automatic PTT with two second hold
- High quality dynamic microphone
- Choice of outputs
- Adjustable tone level
- Microphone muted when sending tones
- Integral tone monitoring
- Optional voltage free PTT contacts
- Hang up button for CTCSS disable

IQD These self contained DTMF keyboard encoders are designed specifically for mobile radio use and are available in a wide variety of sizes and styles. Low profile and small size make the 217 series particularly suitable for hand portable equipment. The 216 and 220 models provide larger keys for base or mobile use and are available with illuminated keyboards. Both the 217B and the 220 feature separate keyboard and electronics. All models incorporate automatic PTT with a two second hold after key release and adjustable tone level output.

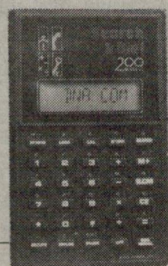

SEARCH AND DIAL

- Store 200 phone numbers
- Directory function
- Light & portable
- Last number redial
- Alpha numeric memory
- Calculator
- Stopwatch
- Security code
- Store personal no's.

DNA COMMUNICATIONS

P.O. BOX 47, ALSTONVILLE, N.S.W. AUSTRALIA 2477
TELEPHONE: (066) 28 3454 FAX: (066) 28 3841

Letters *Continued from page 7*

and for TV. Also production information and service data.

The cost of this catalogue was 3 pounds sterling, including postage to Australia. They do advertise in "The Gramophone" on occasion. It is a Mail Order and Export company only, selling direct to their customers. My relation with them was for old TV books and instruction leaflets, sent very promptly (photostats).

I hope this information is of interest.

E.F. Watts,
Newcomb, Vic.

Comment: Thanks for sharing the good news, Mr Watts!

More on metal fume fever

I write in reply to M.W.'s letter in the June 1987 issue of *Electronics Australia* Forum.

As a medical practitioner myself, I read with some amusement, M.W.'s reference to my profession and your appropriate reply. However I would like to comment on your subsequent text.

"The Merck Index" is, as its name indicates, an index of chemicals, giving brief details of around 10,000 substances. My copy cost me \$27.50 new. It is not a useful reference when considering medical or veterinary toxicology. Far more appropriate is:

E. Broiung, "Toxicity of Industrial Metals" (Appleton-Century-Crofts. New York, 2nd Ed., 1969); or

R. Baselt, "Disposition of Toxic Drugs and Chemicals in Man"

(Biomedical Publications. Davis, California, 2nd Ed., 1982).

It would appear from the latter that copper is more likely to be the aetiological agent, if indeed the diagnosis is Metal Fume Fever, rather than cadmium or cerium.

Finally, I would advise M.W. to contact the Occupational Health or Industrial Health Medical Officer of his State Health Department, for more information.

Hoping this is of interest.

Dr. C.A. Appleton,
Chemical Pathologist,
Queensland Medical Laboratory,
West End, Qld.

Starter battery care

I write to help inform both your contributors and your readers in the matter

of starter battery care, including charging and fault diagnosis.

Nearly 30% of all batteries are replaced because they are "just flat". This is the result of a combination of several factors, drive times and trip distances, for example short drives at night in cold winter conditions will cause the battery to be discharged because:

(a) Lighting, heating and ventilation loads will consume most of the alternator output and cause voltage drop in the wiring, reducing the volts applied to the battery terminals, so the battery is not charged. In fact, when idling at traffic lights, the battery is being discharged.

(b) With a cold vehicle, the alternator warms to engine temperature quite rapidly in 5 minutes or so but the battery takes up to an hour to heat. Cold batteries need higher voltages to charge them and the regulator in the alternator reduces the output voltage as its temperature rises, so there is a "no charge" situation.

All of these conditions prevail in vehicles where all of the manufacturers specifications are within tolerance. Voltage settings vary from 14.2 volts to 14.6 volts when the battery, alternator and regulator are all at 25°. In Australia, battery temperatures vary from 0°, to above 60°C and while the regulator may be cold before starting it quickly heats to 85°C or more.

Investigations of the battery/starter motor relationship have also been enlightening. The most difficult engine start was found to be when the engine is very hot but starts were certain if the battery was fully charged. This and other unexpected results were explained by reference to the battery internal resistance. Internal resistance increases rapidly as the battery is discharged, so that when it is connected to the small and nearly fixed load resistance, the current, torque and power delivered by the starter is required.

Overcharge is no longer a problem with automotive batteries due to better alloys in the grid metal, greater control of the purity of ingredients and the highly reliable solid state regulators.

Recent research has shown that some changes need to be made to both the regulation of charging and the installation of the battery in the vehicle. We must assume that batteries may be discharged by 5% during a 30-minute journey; this is about 125 ampminutes. For this to be recharged in next 30-minute trip, the charge must average 4.16 amps.

The charge acceptance diminishes with time, state of charge and tempera-

ture by around 5 times, so this calls for 21 amps initially, reducing to 1 amp at the journey end. This is only possible if the battery terminals are maintained at 14.6 volts with a temperature correction of -20 millivolts per °C away from 25°C.

This means that the EA voltmeter should indicate 14.6 volts shortly after starting during a day of 20 to 30°. On a 5°C morning, a satisfactory battery condition would be indicated by a reading of $20 \times 20 = 400$ millivolts more i.e., 15.0 volts. This is the maximum permissible and the regulator will not allow higher outputs.

The effects of high temperature encountered in summer in Australia also greatly influence battery life and performance. Batteries operated above 60°C tend to be unstable, to the extent that they enter a condition known as "thermal runaway" if overcharged at this temperature. So vehicle engineering must locate the battery where it will not reach this maximum.

Between 25 and 55°C the terminal voltage must follow the thermal coefficient above, so that at 45°C in the battery the EA instrument should read 400 millivolts less, i.e., 14.2 volts. You will see now that the addition of a temperature sensor and scalar correction would greatly add to the value of this project.

The open circuit voltage of a 12-volt lead acid battery happily coincides with the digits used to express specific gravity of the electrolyte. As a result, the so-called electric hydrometer is just another suppressed zero voltmeter, where 12.60 volts equates to an average specific gravity of 1.260. This relationship holds down to about 40% full charge.

Care must be taken that temperature is around 25°C and the surface charge has been allowed to dissipate; this takes one hour to occur. Voltages displayed during driving periods reflect several aspects of the vehicle electrical system, ranging from drive belt slip to load, regulator setting and even battery state of charge.

I write with the experience of more than 30 years in the technical, research and development of Dunlop Batteries and would be happy to assist your very good magazine, which I have received for 35 years.

J.C. Howlett,
Cheltenham, Vic.

Comment: Many thanks for your information. We'll see if it is possible to modify the voltmeter project along the lines you suggest.



TEXAS
INSTRUMENTS

THIS

LOCAL AREA NETWORK DEVELOPMENT SYSTEM

could be yours!!!

WIN
\$10,000
TOTAL VALUE

**GRAND
PRIZE!**

**TOTAL VALUE
\$10,000**



Includes: Texas Instruments Professional Computer

• TMS 380 LDK Design
-in Accelerator Kit
with complete chip set

for token ring network
• TMDS PCF LAN inter-
face card

• TND 380 TWC Test
wiring concentrator
with debug software

ENTRIES CLOSE 15th SEPTEMBER, 1987

HOW TO WIN

*Simply explain in less than 500 words why you de-
serve to win this Local Area Network Development
System.*


**Entries should include details of at least one
LAN application for which the system will be used.**

Entries will be
judged on
originality and
presentation.

**ENTER
NOW!**

Send your entry to
The Editor,
Electronics Australia,
PO Box 227,
Waterloo 2017

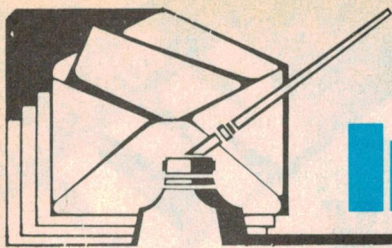The winner will be notified by mail and the result announced in the November 1987 issue of
Electronics Australia



Information centre

Connecting a CD player

I have recently purchased a Compact Disc player, and have experienced difficulties matching it to my amplifier. I have only one spare input left in the amplifier, a 2.5mV/50k ohm phono input. I am wondering how I could design an attenuator to match it to my CD, which puts out 2.0V at 10k ohms. Thank you. (P.S., Mt. Riverview, NSW).

• *It sounds as if the input concerned is for a magnetic pickup, and will have the appropriate equalisation circuitry built in. As a result, you would have to use an attenuator with "reverse equalisation", to bring the response to "flat". The results are likely to be rather disappointing and would scarcely do justice to the signals delivered by the CD player.*

Frankly, we'd suggest you organise things another way, so the 'CD signal can be fed into a higher level "flat" input like "AUX" or "Tuner". This is likely to give far better results.

Electronic rain gauge

I have just completed an electronic rain gauge to the specifications published in your issue of March 1987.

I thought the following may be of interest to you or any of your readers who may have experienced the same effect on the operation by the use of a relatively long trigger cable as I did.

I made the unit up exactly as described by Mr Clarke. I had to make the funnel out of 26ga sheet galvanised iron as a plastic one was not obtainable in these parts. The board was obtained from RCS Radio and the parts from the local Dick Smith Electronics store.

No difficulty was experienced in getting the unit to work, its operation on the bench was faultless using about 2m of twin figure 8 light duty flex for the trigger lead.

But on increasing this lead to about 15m, a "double" trigger effect was experienced doubling the count x2. Increasing the time constant to about 2 secs by increasing the 1 Meg resistor to 2.2M only slowed the second pulse. I tried various types of cable, larger, with the same results.

Reasoning that this was no doubt a spurious pulse developed by an unterminated line, a damping resistor of 330

ohms was placed in series with one leg of the line. This effected a cure and the unit now works as intended with the 15m of light flex. Unfortunately, I do not have a CRO to check this out to my complete satisfaction.

I must compliment the author of the article for a well presented and very clean description of the unit. In conclusion I take this opportunity to thank you for your recent help with the Video Fader. You may recall Jaycar supplied the wrong IC in the kit supplied to me. Changing this to the correct type as suggested by you completely fixed the problem and the fader now works well. (T.D.K., Rosewood, Qld.)

• *Thanks for writing. We didn't strike any problems of the kind you describe, but your solution seems quite in order. It's good to know that your Video Fader is now working as it should, too.*

Turbo-timer

I have constructed the turbo-timer but I have struck several problems in its operation.

Firstly a 500 ohm trimpot had been supplied by Jaycar in the kit instead of the 200 ohm trimpot specified. This caused the adjustment to be too sensitive but was solved after the trimpot was replaced with the correct value.

Secondly, I found it better to set the trigger voltage at pin 6 of IC1a to about 5.5V, rather than by experiment. This was done with the engine cold.

The problem that I have is that the unit triggers prematurely, only after a short drive. When tested on the bench this problem does not occur. After replacing IC1, IC2 and the LM334, I suspect that it is being triggered by electrical noise when installed to the vehicle.

Can you explain the problem? At present I have to ensure that S1 is pressed when turning off the ignition after a short drive. (B.C., Gunnedah, NSW).

• *We suspect that your problem is due to incorrect adjustment of VR1. It is not recommended that the Turbo-timer be calibrated by measuring the voltage at pin 2 of IC1a. While the setting of VR1 does determine the number of mV per degree C from the LM334, it is the actual high going trigger voltage for pin 6 of IC1a that determines the final*

setting of VR1. Consequently, the setting of VR1 must be made on the vehicle as suggested in the article or unreliable results will be obtained.

Tachometer on the TAI

I built the Hall Effect pointless electronic ignition from your February 1983 and September 1984 issues of *Electronics Australia*. It is fitted to a 1975 202 Holden Torana with a full GMH instrument panel.

The engine fires up and runs very well. The problem that I have is that when the ignition is switched off the tachometer jumps. Some of the time the tachometer drops to zero, but most of the time it jumps to between 2000 to 5000 RPM mark. The tachometer reads steadily and accurately when the car is being driven.

Connection of the tachometer is to the negative side of the coil. Could you please give a possible cause for tachometer movement as the ignition is switched off? (R.R., Ipswich, QLD).

• *The reason your tachometer jumps at switch off is probably due to discharge current through the coil. When the ignition is switched off, the BUX80 transistor used to switch on the coil will go open circuit and the only path for the coil current to flow is through the tachometer.*

We suggest connecting a 1k ohm 1W resistor between the negative of the coil and chassis to divert the coil current.

Screecher alarm

I am an avid student interested in the field of electronics. I intend to install the Screecher Car Burglar Alarm from August 1986 into my mother's car, together with the UHF Remote Switch from January 1987.

This will mean that the exit and entry delay timers and also the three second soft alarm feature are not necessary. Could you please tell me what is necessary to leave out of the alarm circuit and how to hook it up to the remote switch.

When adding a piezo alarm transducer, the article states that a 1k ohm resistor should be placed in parallel. Where should this be fitted?

The adjustment of the UHF remote switch transmitter requires setting to 304MHz. Since I do not have a frequency meter how can this be adjusted correctly? Also can you please tell me which output for the UHF receiver (1 to 4) should be connected to the screecher alarm. I would also like to install the external relay for the blinkers. (I.T., Greenfield Park, NSW).

• *The appropriate modifications to enable use of this project with the remote switch are as follows: Leave out diode D3 to remove the exit delay, leave out diode D6, the 10uF capacitor on pin 2 of IC2c and replace the 1M ohm resistor in parallel with D6 with a wire link to remove the entry delay.*

Removal of the soft alarm feature is not recommended since if you forget to switch off the alarm before entering the car the soft alarm feature will give a quiet reminder rather than a deafening screech. However, to disable the soft alarm feature, leave out transistor Q2.

To connect the UHF remote switch to the screecher alarm, simply delete switch S1 from the alarm and connect the +12V switched supply from the remote receiver to the supply for the screecher car alarm.

To set the UHF transmitter to 304MHz does require a frequency meter. Perhaps your local TV serviceman may be able to help you.

Further information on using the remote switch with the car burglar alarm is in our June issue.

Voltage regulator for outboard motors

I am interested in obtaining a voltage regulator circuit to incorporate in an outboard motor electrical system. The alternator installed is a single phase 6A unit feeding a bridge rectifier, to a battery.

The main problem is that during extended running periods the battery voltage can rise to over 16V. This is too high for electrical equipment such as the radio and depth sounder. Could you recommend a suitable solution to cure this problem. (K.C., Northgate, QLD).

• *Although we have not tried it, the VK Powermate described in December 1983 may form the basis of a suitable regulator. The approach would be to leave out the transformer and bridge rectifier in the existing circuit and feed the output of the alternator bridge directly to the 10A fuse.*

Playmaster amplifier

I have purchased and constructed the 60/60 amplifier and the results are very impressive indeed.

One thing concerns me however, is the loud switch off thump in the loudspeakers.

Is it normal for such switch off thumps to occur and can you offer any suggestions to a cure? (M.L., Woodville, SA).

• *You can cure the switch off thump in two ways. Firstly try increasing the 1000uF capacitor connected to pin 7 of IC2 and IC3 (located near IC3). The value of 2200uF should be suitable. Alternatively, install an 8.2V zener in series with the resistor at the base of transistor Q21 and replacing the 2.2k ohm resistor with a 1k ohm resistor.*

Notes & Errata

VZ-300 MEMORY EXPANSION (May 1987, CDI). Pins 2 and 4 of IC4 should be tied low and pins 6 and 15 tied high; not 4 and 15 low, and 2 and 6 high, as indicated. Connecting the circuit as shown may cause damage to either the static RAMS or the VZ-300.

Combination Lock

Continued from page 73

from IC3 goes high from 1 to 9 consecutively.

Allow more than 3 seconds to elapse, so that the power supply is disconnected from the ICs, and press S1 again. Wait for D6 to flash, and then press S1 the number of times equal to the first digit in the combination code. Check that after 1 second D6 flashes and T1 closes to pull pin 2 of IC5 high.

Press S1 again for the number of times equal to the second code in the combination. This time T2 should close, to bring pin 6 of IC5b high. Press S1 again for the number of times equal to the third number in the combination code. This time T3 should close to bring pin 12 of IC5c high. Press S1 again for the number of times equal to the fourth number in the combination code, and T4 should close to trigger T5 and the solenoid.

The solenoid can be held energised for as long as S1 is held closed. R21 may need to be reduced in value to suit the particular latch solenoid used for the striker.

Release S1 and wait 3 seconds for the power supply to be removed, then press

S1. Wait for a second, and then press S1 a number of times equal to the first digit of the combination code. Wait for T1 to close. Now press S1 a number of times which is not equal to the next digit in the combination code. After D6 flashes, transistor Q3 should turn off, removing power to the anodes of the SCRs. This will release SCR, T1.

If everything has happened according to the above description, your combination lock should be working properly.

Installation

The electric striker plate will require installation into the door jamb. This normally will replace the original striker plate of a key operated lock, allowing use of the original lock to gain entry to the door when the combination lock is

not activated.

Cut away sufficient material in the door jamb to accommodate the striker plate and temporarily locate the plate to check that the door will close satisfactorily. Once it is installed correctly, wiring can begin.

Wiring to the striker plate should be concealed within the door frame and run to the combination lock circuit which can be located in the ceiling or under the floor. Ideally, the latch unit part of the PCB should be located as close as possible to the striker plate, as noted earlier.

Further wiring is necessary between the combination lock PCB and the switch S1 and LED D6. These can be unobtrusively located near the door, with the wiring again run within the door frame if possible. EA

Australia's Communications Revolution

Over the last few years, there's been a revolution in communications technology. Online databases, packet-switching, fax, direct-connect modems, local area networks, satellite links, videotex and teletex have all grown up, to name just a few.

Are you fully aware of what's been going on? If not, this book can bring you up to date with its easy-to-read explanations. It's almost essential reading, in today's world . . .

only \$4.95

plus \$1.00 for postage & handling

Send your order to: Freepost No.4, Federal Publishing, Book Sales, PO Box 227, Waterloo NSW 2017. (no stamp required if posted within Australia).

EA marketplace EA marketplace

ADVERTISING RATES FOR THIS PAGE

SMALL ADS: The minimum acceptable size of 2 centimetres x one column costs only \$40. Other sizes up to a maximum of 10 centimetres are rated at \$20 a centimetre. **CLASSIFIEDS:** \$4 for 40 letters. Just count the letters divide by 40 and multiply by \$4, **ROUND UP TO NEAREST WHOLE NUMBER.** **CLOSING DATE:** Ads may be accepted up to the 18th of the month two months prior to issue date. **PAYMENT:** Please enclose payment with your advertisement. Address your letter to THE ADVERTISING MANAGER, ELECTRONICS AUSTRALIA, PO BOX 227, WATERLOO, NSW 2017.

FOR SALE

AMIDON FERROMAGNETIC CORES:

Large range for all receiver and transmitter applications. For data and price list and 105X220 SASE to: R. J. & U. S. Imports, P.O. Box 157, Mortdale, N.S.W. 2223. N.S.W.: Geoff Wood Electronics, Lane Cove. Webb Electronics, Albury. A.C.T.: Electronic Components, Fyshwick Plaza, Vic.: Truscott Electronics, Croydon. W.A.: Willis Trading Co., Perth.

DO YOU WANT TO BE A RADIO AMATEUR?

The Wireless Institute of Australia, established in 1910 to further the interests of Amateur Radio, conducts a Correspondence Course for the A.O.C.P. and L.A.O.C.P. Examinations conducted by the Department of Communications. Throughout the Course, your papers are checked and commented upon to lead you to a successful conclusion. For further information, write to:

THE COURSE SUPERVISOR W.I.A. (N.S.W. DIVISION)

P.O. Box 1066
PARRAMATTA, N.S.W. 2150.

NEW RADIO VALVES: For entertainment or industrial use. Waltham Dan, 96 Oxford St., Darlinghurst, Sydney. Phone (02) 331-3360.

EX-ABC AUDIO TAPES: 1/4" wide on 10 1/2" Standard metal spool \$6.85. Robust metal spool \$12.85 7" spool \$2.85. 5" spool \$1.25. Post extra. Also in stock 1/2", 1" and 2" tapes. Waltham Dan, 96 Oxford St., Darlinghurst, Sydney. Phone (02) 331-3360.

Build the AEM March 87: STAR PROJECT 256K printer buffer. Double sided plated through board, Eprom & inst. \$39 plus \$3 P&P. IBM type printer cables \$15 plus \$3 P&P. Other boards, connectors, and components available. For more info. Send SAE to Don McKenzie, 29 Ellesmere Cres. Tullamarine 3043.

PRINTED CIRCUIT BOARDS

Minimum postage & packaging on all EA & ETI Project PCBs.

Catalogue 1976-85 (inc components) \$1.50. PCBs made to order — 48 hr prototype service. Bankcard/Mastercard.

Acetronics PCBs
112 Robertson Rd, Bass Hill 2197
(02) 645 1241

WANTED

WANTED: Old Microphones — Pre 1960, Broadcast and P.A. Also films and Newsreels on 16 and 35 mm. Write John Henderson, 85 Parker St. Bassendean, Western Australia. 6054. Phone: (09) 279-1234.

MUSIC SOUND RECORDING STAGE LIGHTING SONICS MAGAZINE

For: Musicians, Road Crews, Recording Engineers, Lighting People, Managers, Promoters and anybody interested in what goes into today's music-making.

THE ALL AUSTRALIAN MUSIC MAKERS' MAGAZINE

A NEW CONCEPT FOR LOW VOLTAGE PROJECTS

COPPER FOIL TAPE: thin pure copper tape backed by special hi-tack adhesive. Current carrying capacity, 5 amps, FULLY TESTED at 24V 5A. Not recommended for mains voltage.

4mm...RRP \$8.03 6mm...RRP \$9.84 33 metre rolls

GIFFORD PRODUCTIONS
PO Box 62, St Kilda, Vic 3182. (03) 534 3462

GENERATE ELECTRICITY FROM THE SUN ARCO PV PANELS

M55B 53 WATTS 12V
M75B 47 WATTS 12V

Provide power for pumping, lighting and refrigeration. Now only \$8/WATT.

ELANTE PTY LTD

382 CANTERBURY RD.
SURREY HILLS, 3127
Ph: (03) 836-9966

RCS. RADIO PTY. LTD.

Established 1933
IS THE ONLY COMPANY
WHICH MANUFACTURES AND
SELLS EVERY PCB & FRONT PANEL
published in EA and ETI
651 Forest Road Bexley 2207
AUSTRALIA
RING (02) 587 3491 FOR INSTANT PRICES
24 HOUR TURNAROUND SERVICE

Do computers play any part in your life?

If they do — or if you just want to find out
about them — don't miss each month's issue of

your computer

NEWS

REVIEWS

PROGRAMS

TUTORIALS

A magazine for all computer users and enthusiasts, Your Computer has something for everyone — topical features on all aspects of the computing world, expert reviews of the latest software and hardware, up-to-the-minute information for business people and even games and advice for hobbyists.

Available at your Newsagent now!

OPEN FOR BUSINESS: Monday to Friday 8.30 am to 5.00 pm.
Saturday Morning 8.30 am to NOON.

10B/3 Kenneth Road, Manly Vale 2093

A.C.E.
RADIO

ELECTRONICS CENTRE

ESTABLISHED OVER THIRTY YEARS

Phone: (02) 949 4871

ETONE SPEAKER SPECIALS
38 cm (15 inch) WOOFERS

Model	Size	Cone Type	V/Coil	Reson Hz	Freq Hz	Watts Rms	Price Ea or	2 for
4180	38cm	Hi-Fi	8 or 15 Ohms	30	30-3500	100	\$104.50 or	\$205.00
4310	38cm	Straight surround	8 or 15 Ohms	45	40-6000	60	\$108.00 or	\$212.00
4510	38cm	Straight surround	8 or 15 Ohms	45	40-6000	100	\$150.00 or	\$294.00
4350	38cm	Hi-Fi	8 or 15 Ohms	30	30-4000	120	\$127.00 or	\$251.00

Pack and Post for 1 speaker NSW/VIC \$8.75; Q/T \$13.50; NT/WA \$17.50; SA \$11.50
Pack and Post for 2 speakers NSW/VIC \$15.00; Q/T \$23.00; NT/WA \$30.00; SA \$20.00

ETONE 50 WATT RMS
A PAIR FOR \$60.95 OR \$34.95 EACH

- RUGGED TOP QUALITY HI-FI WOOFER 30cm 8 ohms
- 90 DAYS FACTORY WARRANTY • FOAM POLY SURROUND
- STURDY SUSPENSION FOR RICH REPRODUCTION • 3.5cm VOICE COIL • FERRITE MAGNET • FREQ. RESPONSE . . . 35-4500Hz
- RESONANCE 35Hz

P & P for 1 Speaker NSW \$4.80 VIC \$5.20 TAS \$6.25 WA/NT \$7.95 QLD/SA \$5.80
P & P for 2 Speaker NSW \$5.50 VIC \$7.20 TAS \$9.95 WA/NT \$11.45 QLD/SA \$8.20

POLYPROPYLENE CONE TOP QUALITY HI-FI WOOFERS

80hm Voice Coil — Foam Poly Surround —
Sturdy Suspension — Fitted Moulded Gasket —
Ferrite Magnet — 90 days factory warranty

Model	Size	Reson Hz	Watts R.M.S.	Price Ea or 2 For
12 POL 12"	25	30-4000	80	\$47.50 \$89.00
10 POL 10"	30	35-4000	60	\$42.95 \$79.95
8 POL 8"	35	40-5000	50	\$36.95 \$68.95

P & P for 1 Speaker NSW \$4.80 VIC \$5.20 TAS \$6.25 WA/NT \$7.95 QLD/SA \$5.80
P & P for 2 Speaker NSW \$5.50 VIC \$7.20 TAS \$9.95 WA/NT \$11.45 QLD/SA \$8.20
5" Polypropylene Mid-Range Speaker to suit above Woofers P.O.A.

NEW FOR '87 CONVENIENT DISKETTE FILES

Includes Lock + 2 keys

Features

- Capacity: 50 pcs 3-1/2" diskette
- High impact plastic lid and base
- Easy access handle for opening and carrying

\$28.95 ea.

Features

- Double row display filing systems
- Protective racks for diskette separation
- Smoked PS plastic cover with lock
- High impact plastic lid and base
- Easy access handle for opening and carrying
- One hundred disk capacity 5-1/4" disk

\$26.95 ea.

★ ★ **PROFESSIONAL VIDEO UNITS** ★ ★

BRAND NEW IN CARTONS

14inch GREEN SCREEN MONITOR
COMPOSITE VIDEO INPUT

Cabinet & Fully Adjustable Swivel Tilt Base.
All metal construction, fully shielded.

PRICE \$180.00 EA
LIMITED STOCK

FREIGHT P.O.A.

Internal regulated power supply 12V/5VDC output with sufficient capacity to supply up to 2 disk drives & also power your computer.

BRIDGE RECTIFIERS

1.5 A 200 PIV is for \$3.95
10 A 150 PIV 5 for \$10.00
* **HEAVY DUTY** *
10 A 400 PIV \$3.75 ea.
15 A 400 PIV \$4.15 ea.
35 A 400 PIV \$4.99 ea.
10 A 1000 PIV \$5.95 ea.
15 A 1000 PIV \$6.50 ea.
35 A 1000 PIV \$7.50 ea.

3 WAY CROSSOVERS

200 Watts RMS
Crossover Freq. 1KC and 5 KC
12db/Octave
\$34.95 ea. or \$65.90 a pair
P & P \$2.50 ea. P & P \$5.00 pair



COMPONENTS

Computer Keyboard Switches
1" for \$2.00 P & P \$1.50

New PC Boards (no components)
New PC Boards (components mounted)
AS PER JULY ADVERT.

★ **KONICA SPECIAL** ★

Floppy Disks Single Sided/Double Density
3 1/2 MF/1DD \$52.50/Pk of 10
P and P \$2.00

TOP QUALITY JAPANESE 5.25" MINI FLOPPY DISKS

"DUE TO PRICE WE CAN'T MENTION BRAND"
SUPER VALUE PACK OF 10 DISKS
\$18.00/PK
P & P \$2.00

I.C.'s

LM555	10 for \$4.95
LM3301	10 for \$6.00
74S287	5 for \$5.00
74LS151	5 for \$5.00
7406	5 for \$5.00
7417	5 for \$5.00
7441	5 for \$6.00
MC1488	5 for \$7.50

ABOVE P & P \$2.00

TRANSISTORS

BC337	.20 ea. OR 10 for \$1.70
BC 548	10 for \$1.00
BC 549	10 for \$1.00
BD139	.70ea. OR 10 for \$6.50
BD140	.70 ea. OR 10 for \$6.50
TIP31C	\$1.20 ea. 10 for \$11.00
TIP32C	\$1.20 ea. 10 for \$11.00
2N3055	10 for \$15.00
2N6027	.80 ea. OR 10 for \$7.50
2N646	\$1.30 ea. 10 for \$12.00
GES2646	\$1.00 ea. 10 for \$9.00
4N25	\$1.50 ea. 10 for \$14.00
MJE350	\$1.00 ea. 10 for \$7.50
MJE3055	\$1.80 ea. 10 for \$15.00

P & P \$2.00

NEW FOR '87

YES WE NOW STOCK
COMPUTER PRINTER PAPER

STANDARD FAN-FOLD

ACE871 (279x241)2500/ctn SINGLE PART
PLAIN 70 GSM BOND
PRICE \$48.59/ctn OR 5 + \$44.85/ctn
P&P SYD. METRO \$3.50 NSW \$4.80
QLD/SA \$11.30 TAS \$13.25
WA/NT \$19.75 VIC \$8.70

ACE872 (279x381)2500/ctn 1Part Blue
H/S 60 GSM B.O.M.
PRICE \$41.47/ctn OR 5 + \$39.74/ctn
ACE873 (279x381)2500/ctn 1Part Blue
H/S 60 GSM Bond.
PRICE \$51.41/ctn OR 5 + \$49.27/ctn
ACE874 (279x381)2000/ctn Plain
70 GSM Bond.
PRICE \$49.08/ctn OR 5 + \$47.03/ctn
ACE875 (279x241)2500/ctn 1Part EXACT
A4 Tear out clean edge perf.
70 GSM Bond.
PRICE \$58.75/ctn OR 5 + \$56.30/ctn
ACE876 (279x381)1000/ctn 2Part Blue
Half Shadow CARBONLESS.
PRICE \$67.24/ctn OR 5 + \$64.43/ctn
ACE877 (279x381)750/ctn 3Part Blue
Half Shadow CARBONLESS
PRICE \$81.01/ctn OR 5 + \$77.65/ctn
ACE878 (279x381)500/ctn 4Part Blue
Half Shadow CARBONLESS.
PRICE \$73.16/ctn OR 5 + \$70.12/ctn
REGULAR POSTAL RATES APPLY

★ **KONICA FLOPPY DISK** ★


3 1/2 MF/2DD \$72.03/Pk
5 1/4 MD/2DD \$42.68/Pk
P and P \$2.00

LOOKING FOR A PRELOVED MONITOR

PRICE \$97.50 EA
FREIGHT P.O.A.

LIMITED STOCK

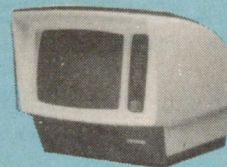What about this,
ITT 14inch GREEN SCREEN MONITOR fibreglass
case. Illuminated on/off push button, brightness
& contrast controls at front, composite video signal input.



Credit card facilities now available after first registering following details with Ace Radio.
THIS IS FOR YOUR PROTECTION.

EXPIRY DATE:

YOUR NAME: CARD NO:

RESIDENTIAL ADDRESS:
P.O. Box numbers unacceptable

SIGNATURE: MIN ORDER \$20.00

★ ★ ★ **THIS MONTH'S SPECIALS** ★ ★ ★

FOR POSTAL INSURANCE ADD: \$2.00 for parcel up to \$200.00 value plus
\$1.00 for each additional \$100.00 value

Next month in

Electronics Australia

All about thermocouples

Ever wonder how thermocouples are used to measure high temperatures? One of our features next month looks at the various kinds of thermocouples, how they work and how they're used. There's even news of a recent breakthrough in thermocouple technology — made right here in Australia!

Switch-tuned shirt pocket radio

Tuning a compact shirt-pocket type radio can be tricky — and if you bump it accidentally, the setting is usually lost. One of our projects next month is a low cost radio that solves this problem by using switch tuning. It's built in a novel case, too!

Experimenters' power supply

Looking for a good low cost power supply for experimenting with new circuits? Then don't miss next month's issue, when we'll be describing just the thing. It has adjustable current limiting, and runs off a standard low cost plug-pack.

**Note: although these articles have been prepared for publication, circumstances may change the final content.*

Electronics Australia Reader Service

"Electronics Australia" provides the following services:

BACK ISSUES: available only until stocks are exhausted. Price: \$4.00.

PHOTOSTAT COPIES: when back issues are exhausted, photocopies of articles can be supplied. Price: \$4 per project or \$8 where a project spreads over several issues.

PCB PATTERNS: high contrast, actual size transparencies for printed circuit boards and front panels are available. Price: \$5 for boards up to 100 square centimetres; \$10 for larger boards. Please specify positive or negative.

PROJECT QUERIES: advice on projects is limited to postal correspondence only, and to projects less than five years old. Price: \$5. Please note that we cannot undertake special research or advise on project modifications. Members of our technical staff are not available to discuss technical

problems by telephone.

OTHER QUERIES: technical queries outside the scope of "Replies by Post", or submitted without fee, may be answered in the "Information Centre" pages at the discretion of the Editor.

PAYMENT: must be negotiable in Australia and made payable to "Electronics Australia". Send cheque, money order or credit card number (American Express, Bankcard, or Mastercard), name and address (see form). All prices include postage within Australia and to New Zealand.

ADDRESS: send all correspondence to The Secretary, "Electronics Australia", PO Box 227, Waterloo, NSW 2017. Please note that we are unable to supply back issues, photocopies or PCB artwork material over the counter.

Back Issues

Photostat copies

Total price of magazines/photocopies, including postage and handling.

No off issues reg x \$4 = \$.....

Cheque/Money Order ☐ Please tick box to indicate method of payment.

*Please make payable to the Federal Publishing Company Pty Ltd.

Mastercard ☐ American Express ☐ Visa ☐ Bankcard ☐ Tick ☒

Card Expiry Date

Credit Card No.

Signature
(Unsigned Orders cannot be accepted)

NAME:

ADDRESS:


POSTCODE

ADVERTISING INDEX

Ace Radio	131
Acetronics	130
Adeal	89
Altronics	102-107
Amtext	65,113
Bose	15
Chapman L E	123
Control Data	89
Cooper Tools	33
Crusader	95
David Reid	49
DNA Communication	125
Dick Smith Electronics	53-60
Elante	130
Elmeasco	4
Emtronics	33
Federal Publishing	15,65,77,117,118,134,135
Geoff Wood	23
Gifford Production	130
Hi Tech	101
Jaycar	78-83
Kalextronics	63
Kenelec	19
Macro Dynamics	88
Marantz	41
Microbee	92,93
Micro Education	50
Microgram	45
Oatley Electronics	73
Odyl	10
Philips	47
RCS Radio	130
Resurrection Radio	32
Ritronics	24,34,35,114,115
Scan Audio	51
Scientific Devices	39,100
Selectronic Components	88
Semikron	98
Teac	136
Texas Instruments	2,3
Stotts	11
VSI	133
WES Components	62
WIA	130

This index is provided as an additional service. The publisher does not assume any liability for errors and omissions.

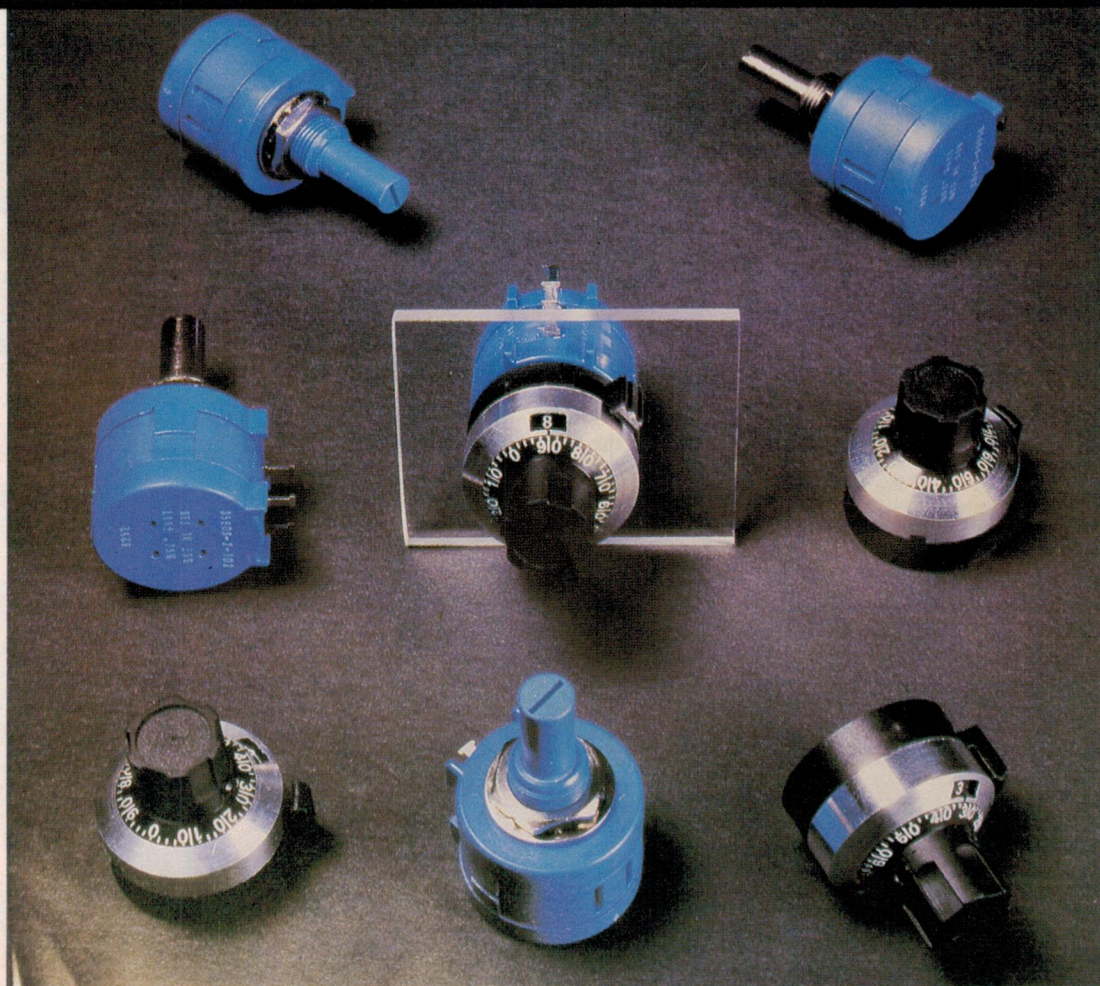THE MOST COMPETITIVE POT/DIAL COMBINATION IN THE INDUSTRY



Bourns® 3590/H506 Precision Control Devices

3590 SERIES 7/8 Inch Dia. 10-Turn Bushing Mount Potentiometers Wirewound Element

- Space saving size: extends less than 3/4" behind panel
- Unique, rugged mechanical construction
- Available with "O" ring seals for boardwashing
- Choice of metal or plastic shaft/bushing combinations
- Available with PC pins (for board mounting) or solder lugs
- Performance guaranteed by the Bourns Reliability Program
- Available in metric shaft and bushing configurations.

H-506 SERIES 7/8 Inch Dia. 15-Turn, Turns - Counting Dial

- For use with precision potentiometers or other rotating devices up to 15 turns
- Excellent legibility - white marking on black background
- High quality, rugged construction
- Two set screws
- No backlash
- Primary dial will not rotate when brake is applied
- Compact - Requires only 23mm (7/8") diameter panel space
- Standard models available for 6mm and 1/4" diameter shaft

VSI
THE SOURCE OF

COMPONENTS

VSI Electronics (Aust) Pty. Ltd.,
16 Dickson Ave., ARTARMON
NSW 2064, AUSTRALIA
Telephone (02) 439 8622
Telex AA 22846 Fax (02) 439 6435

NEXUS 11/024

• QUEENSLAND (07) 262 5200 • VICTORIA (03) 543 6445 • SOUTH AUSTRALIA (08) 267 4848 • WESTERN AUSTRALIA (09) 328 8499

SUBSCRIBE NOW!

to **ELECTRONICS AUSTRALIA** Magazine

for one year and not only do you receive a free Travel Alarm Clock, but you also have a chance to WIN a trip for two to Thailand's exotic Bangkok and Pattaya Beach.

ELECTRONICS AUSTRALIA gives you quality articles on the latest technology. Provides you with popular electronics constructional projects.

THE PRIZE: A return trip for two people flying Thai International to Thailand, visiting Bangkok and Pattaya. A total of 8 days and 6 nights accommodation, breakfast and a set of transfers are all included in this exotic trip.

THE FREE GIFT: A stylish Travel Alarm Clock in Burgundy Leatherette. (See Free Gift panel for details.)

IF SUBSCRIPTION COUPON IS MISSING

Enclose cheque for \$42.00

Name.....

Address

..... Phone.....

Send to: **FREEPOST No 4, THE FEDERAL PUBLISHING COMPANY**
PO Box 227, Waterloo, NSW 2017. (No stamp required)



Thai Airways International 747

Siam Bayshore Resort Hotel is on the farthest tip of South Pattaya's beachfront, close to Pattaya village. Tennis lessons are available, as well as many watersports. With three restaurants, two bars and a nightclub, the Siam Bayshore Resort Hotel has all the charm and hospitality you could wish for.

Mandarin Hotel is a first class hotel conveniently located in the city centre, with beautifully appointed rooms decorated in Thai silk and cottons. There are three bars and night-spots to suit your mood. An excellent restaurant, 24 hour coffee shop, pool with sundeck and 24 hour room service.

The Grand Palace, Bangkok. Former Royal residence unequalled in the world for its ornate architecture. "... One of the most beautiful places on earth and home of the most revered Emerald Buddha — carved from a solid piece of jade."

Thai food — a spicy tale. You must try Thai food. It will be on the menu in at least one of the restaurants in your hotel. Enormous amounts of time, patience and talent go into the preparation of traditional Thai dishes.

Shopping — a pleasant surprise. The shopping is really great, and excellent value. You can have clothes made to measure, or pick up sophisticated fashions in some of the ultra-modern department stores, boutiques and shopping squares.

There's a promise of marvellous food inflight, including some taste-tingling Thai delicacies, free drinks, free stereo headsets, first run movies and individual attention to your comfort and enjoyment. The Thai people consider friendliness, good manners, courtesy and hospitality essential to their daily lives. And nowhere are the unique characteristics of a country more evident than on Thai, the National Airline of Thailand.

The Chao Phya River is Thailand's lifeline. It's worth an hour or so just to watch the endless procession of water traffic — heavily laden barges, the ubiquitous long-tail boats, commuter boats and pleasure craft. Across the river is the Temple of Dawn, with its intricate mosaics of antique Chinese porcelain. And one of the most enjoyable features of a visit to Thailand is the genuine friendliness of the Thai people. No wonder they call it the Land of Smiles.


Transfers on your trip will be courtesy of World Travel Service



Siam Bayshore Resort Hotel, Pattaya



The Grand Palace, Bangkok.

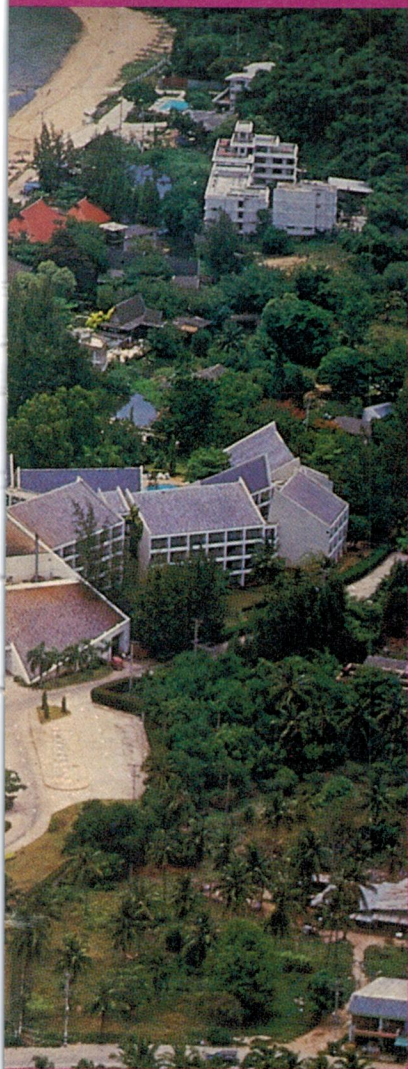

The Grill Room, Mandarin Hotel, Bangkok.


SEE SUBSCRIPTION COUPON

If subscription card is missing, phone (02) 693-0000 and ask for subscriptions.

The Federal Publishing Company Pty Ltd, PO Box 227, Waterloo, NSW 2017.



Thai Airways International Ltd

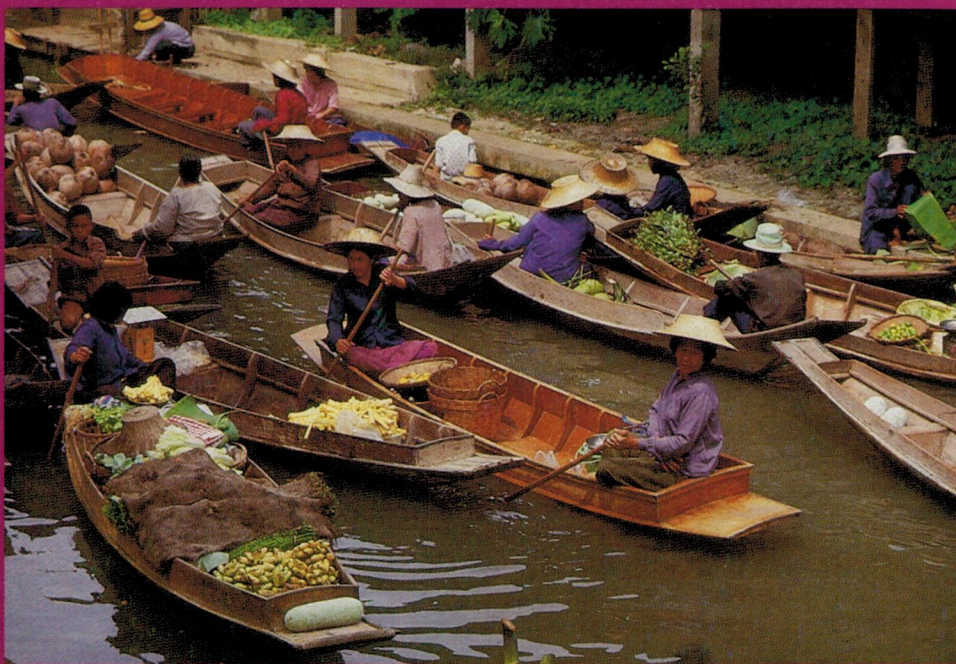

The Floating Markets



CONDITIONS OF ENTRY

1. The competition is open only to Australian Residents authorising a new/renewal subscription before last mail September 30, 1987. Entries received after closing date will not be included. Employees of The Federal Publishing Company, Thai Airways International Limited and their families are not eligible to enter. To be valid for drawing, subscription must be signed against a nominated valid credit card, or, if paid by cheque, cleared for payment.

2. South Australian residents need not purchase a subscription to enter, but may enter once only by submitting their name, address and hand-drawn facsimile of the subscription coupon to The Federal Publishing Company, PO Box 227, Waterloo, NSW 2017.

3. Prizes are not transferable or exchangeable and may not be converted into cash.

4. The judges decision is final and no correspondence will be entered into.

5. Description of the competition and instructions on how to enter, form a part of the competition conditions.

6. The Competition commences on July 1, 1987, and closes on August 31, 1987. The draw will take place in Sydney on September 3, 1987 and the winner will be notified by telephone and letter. The winner will also be announced in The Australian on September 7, 1987, and a later issue of this magazine.

7. The prize is: A return trip for two people flying Thai Airlines economy class Bangkok with 8 days and 6 nights accommodation. Breakfast, one set of transfers to and from the International Airport in Bangkok and your hotel are included.

8. Passports, visas, insurance, departure taxes, transportation between any other destination, immigration formalities, transfers to the nearest Thai Airlines International departure Airport, are the responsibility of the winner. The promoter accepts no responsibility for any delay, cancellation, accident, personal or property damage arising from and/or in connection with the travel prize.

9. Entrants under the age of 18 years will be required to nominate a guardian to accompany them on the journey should they win.

10. The winner and their companion agree to abide by the booking conditions as laid out in the Royal Orchid Holiday Brochure. All travel must be completed by September 3, 1988.

11. The promoter is The Federal Publishing Company, 180 Bourke Road, Alexandria, NSW, 2015. Permit No. TC 87/1119 issued under the Lotteries and Art Unions Act 1901; Raffles and Bingo Permits Board Permit No. 87/635 issued on 28/4/87; ACT Permit No. TP87/317 issued under the Lotteries Ordinance 1964.

FREE BONUS GIFT!



This leatherette TRAVEL ALARM CLOCK is the ideal companion for any traveller. The LCD readout gives the time and date, along with an effective alarm. Lightweight and compact, the alarm folds away for use in a briefcase or handbag. The gold-colour corner trim and face give a stylish finish.

(Free gift is forwarded under separate cover.)

Another ace in the deck.



At a time when most cassette manufacturers are trying to figure out how to catch up with the new digital phenomenon, DENON already knows. DENON'S new high density cassette tapes are dramatic proof. DENON knows because in 1969 it developed the world's first digital audio tape recorder.

As a record company DENON'S expertise in professional digital recording is unsurpassed, and as one of the handful of manufacturers in the world that actually produce their own tape, DENON'S experience in the art and science of high fidelity recording cassettes is equally unsurpassed. It's an experience that has its roots back in 30 years of tape production.

Today's DENON HD Cassettes and DENON Compact Disc Titles carry this proud tradition forward into the age of digital audio.



DENON  **TEAC**
Where Art and Technology Meet.

VIC: TEAC: 115 Whiteman Street, South Melbourne 3205. (03) 699 6000.
NORD: Unit 11, Dunne Crescent Estate, Dunne Crescent, Dandenong 3175. (03) 794 8433.
NSW: TEAC: 814 Elizabeth Street, Waterloo 2017. (02) 319 2744.
AUDIOACCESS: 17 Memorial Avenue, Ingleburn 2065. (02) 605 6196.
QLD: TEAC: 4 Sneyd Street, Bowen Hills 4006. (07) 854 1465.
SOUNDJAYS: 147 Robertsons Street, Fortitude Valley 4106 (07) 854 1441.

TAS: GEORGE HARVEY ELECTRICS: 76 York Street, Launceston 7250. (003) 316 533.
GEORGE HARVEY ELECTRICS: 162-164 Argyle Street, Hobart 7000. (002) 342 233.
WA: DAWSON WHEATLEY: 4 Braceby Close, Willetton 6155. (09) 457 9350.
SAMPSON AGENCIES: Suite 1, 60 Coghlan Road, Subiaco 6008. (09) 382 3370.
SA: NEIL MULLER PTY LTD: 74 Mary Street, Unley 5061. (08) 272 8011.